

Agilent EEsof EDA

Presentation on Power Amplifier Design using ADS

This document is owned by Agilent Technologies, but is no longer kept current and may contain obsolete or inaccurate references. We regret any inconvenience this may cause. For the latest information on Agilent's line of EEsof electronic design automation (EDA) products and services, please go to:

www.agilent.com/find/eesof



Agilent Technologies

Power Amplifier Design using ADS

PA Workshop

Wilfredo Rivas-Torres
Technical Support Application Engineer
October 12, 2004



Agilent Technologies


Outline

- **Introduction**
- **DC and Loadline analysis**
- **Bias and Stability**
- **LoadPull**
- **Matching using Smith Chart Utility**
- **SourcePull**
- **PA Characterization – Did we meet the specification?**
- **Optimize/Fine Tune the design**
- **Test Design with real world modulated signals**
- **Layout**

Why do we need a Power Amplifier?

Power Amplifiers (PA) are in the transmitting chain of a wireless system. They are the final amplification stage before the signal is transmitted, and therefore must produce enough output power to overcome channel losses between the transmitter and the receiver.

Basic Transmitter

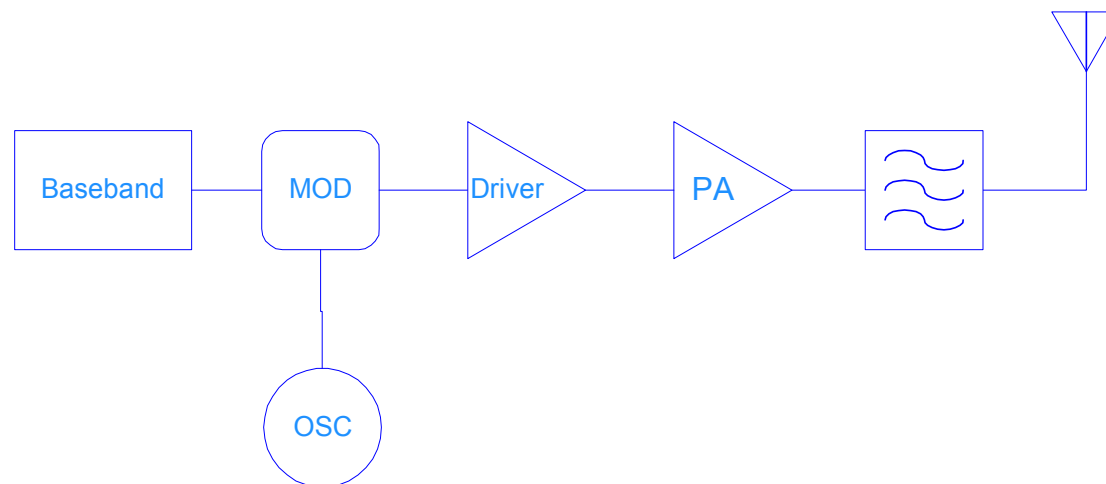

PA requirements


- The PA is typically the primary consumer of power in a transmitter. A major design requirement is how efficiently the PA can convert DC power to RF output power.
- The design engineer has to often concern himself with the Efficiency of the Power Amplifier. Notice that efficiency translates into either lower operation cost (e.g. cellular basestation) or longer battery life (e.g. wireless handheld).
- PA linearity is another important requirement, the input/ output relationship must be linear to preserve the signal integrity.
- The design of PAs often involves the tradeoff of efficiency and linearity.




PA Design Requirement

- RF Output Power: 50 W PEP
- Input Drive Level : 1 W
- Output Load (RL): 50 Ω
- Efficiency (η) > 50%
- Bias Voltage: 28 V
- Device: MRF9045M

DC Curves

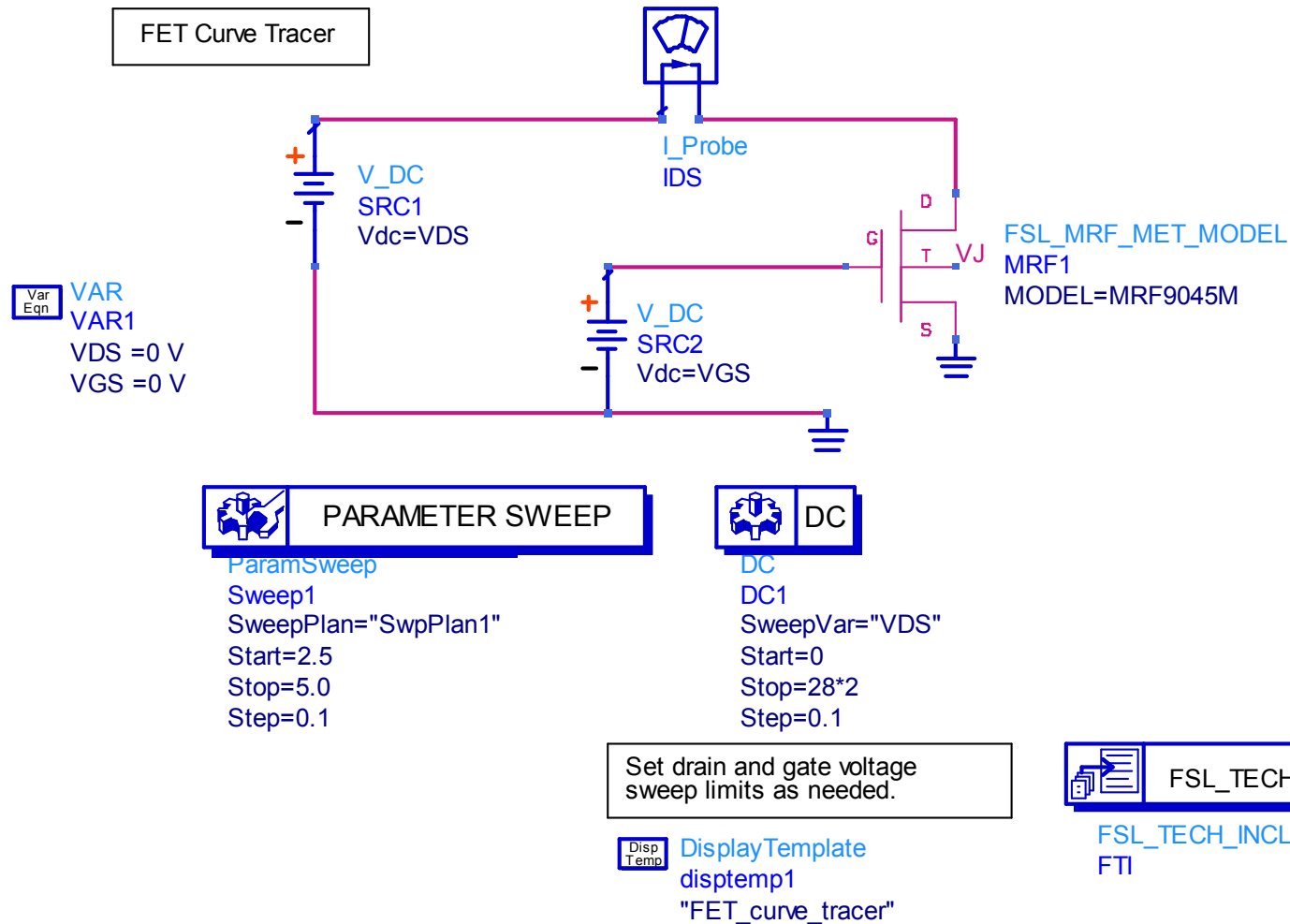

DC Curves

 

V_{Dsats}
$V_{DS}=0.600$
$I_{DS.i}=0.562$
$V_{GS}=3.800000$


I_Q
$V_{DS}=28.000$
$I_{DS.i}=0.717$
$V_{GS}=3.800000$

$m3$
$V_{DS}=33.400$
$I_{DS.i}=0.004$
$V_{GS}=2.500000$




Agilent Technologies


Bias and Stability

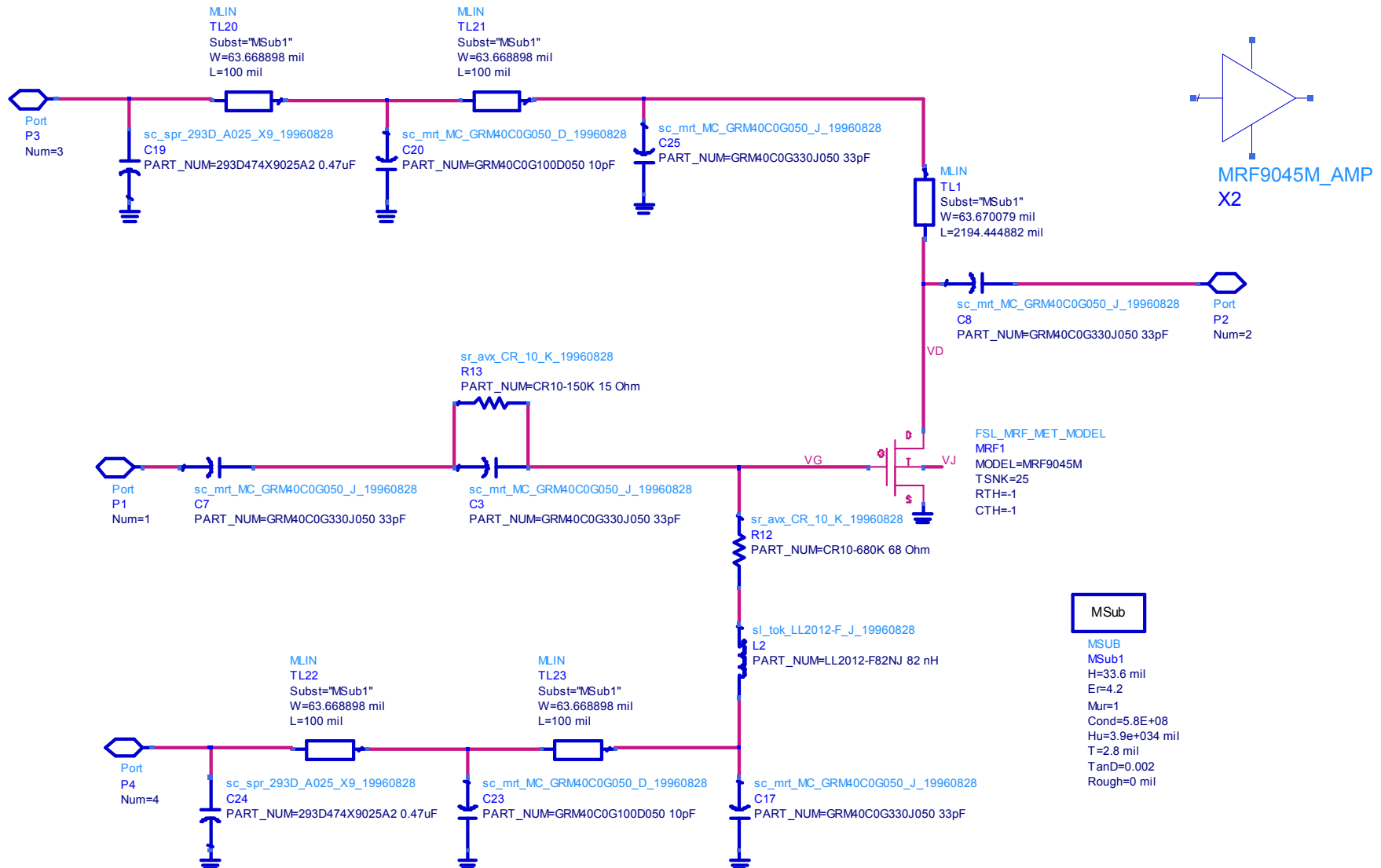

Stability Analysis

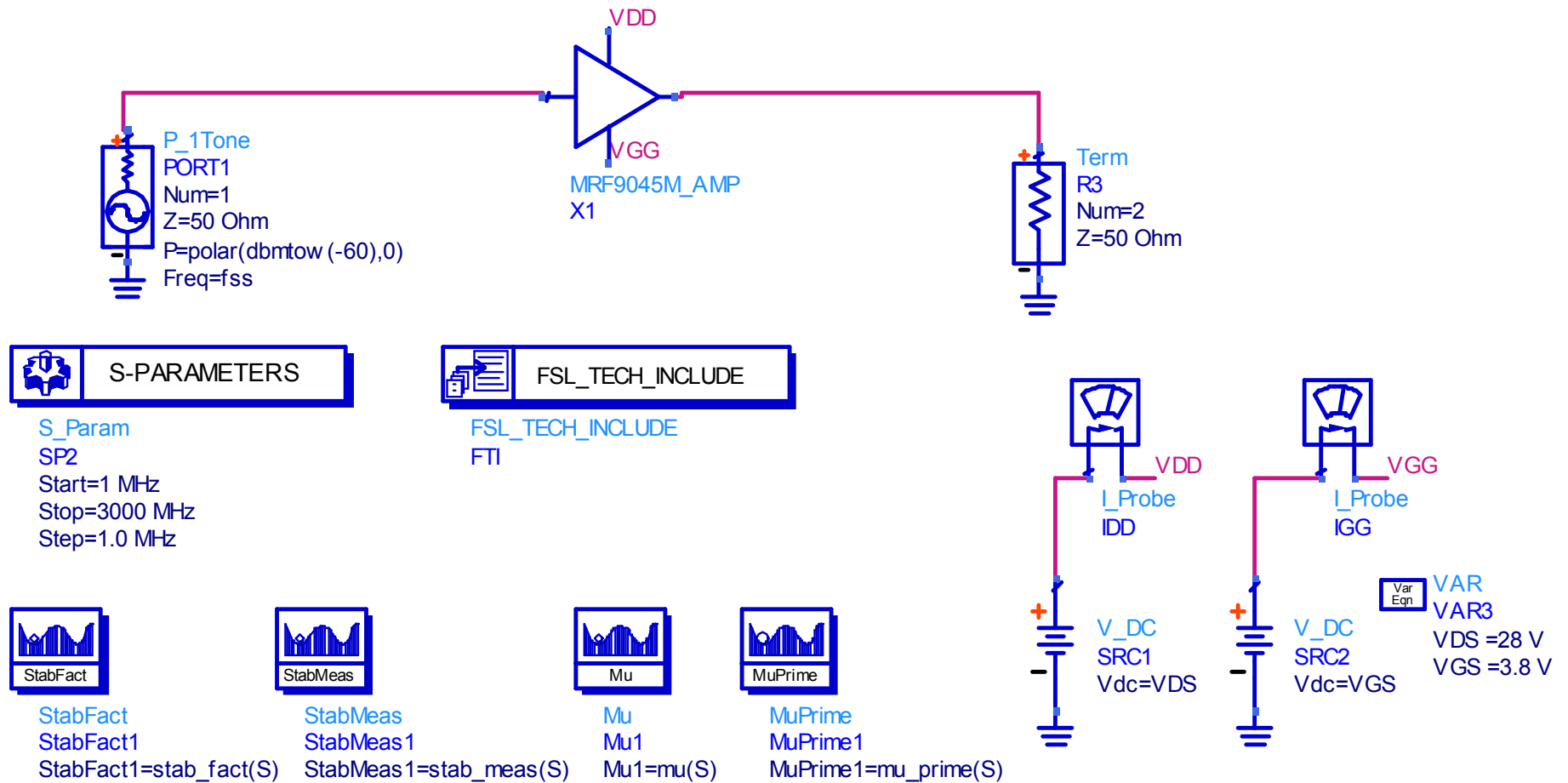

Stability Analysis

 

Impedance Matching

- The need for matching circuits is because amplifiers, in order to perform in a certain way (e.g. maximize output power), must be presented with a certain impedance at both the load and the source ports.
- For example in order to deliver maximum power to the load R_L the transistor must have termination Z_s and Z_L .
- The input matching network is designed to transform the generator impedance R_s to the optimum source impedance Z_s .
- The output matching network transform the load termination R_L (50 Ω) to the optimum load impedance Z_L .
- A LoadPull measurement will help the designer determine the optimum load impedance Z_L .



LoadPull Setup

PARAMETER SWEEP
 ParamSweep
 Sweep2


HARMONIC BALANCE
 HarmonicBalance
 HB1
 Freq[1]=RFfreq
 Order[1]=15

Set Load and Source impedances at harmonic frequencies

VAR
VAR2
 $Z_{l_2} = Z_0 + j*0$
 $Z_{l_3} = Z_0 + j*0$
 $Z_{l_4} = Z_0 + j*0$
 $Z_{l_5} = Z_0 + j*0$
 $Z_{s_fund} = 1.0 + j*0$
 $Z_{s_2} = Z_0 + j*0$
 $Z_{s_3} = Z_0 + j*0$
 $Z_{s_4} = Z_0 + j*0$
 $Z_{s_5} = Z_0 + j*0$

Set these values:

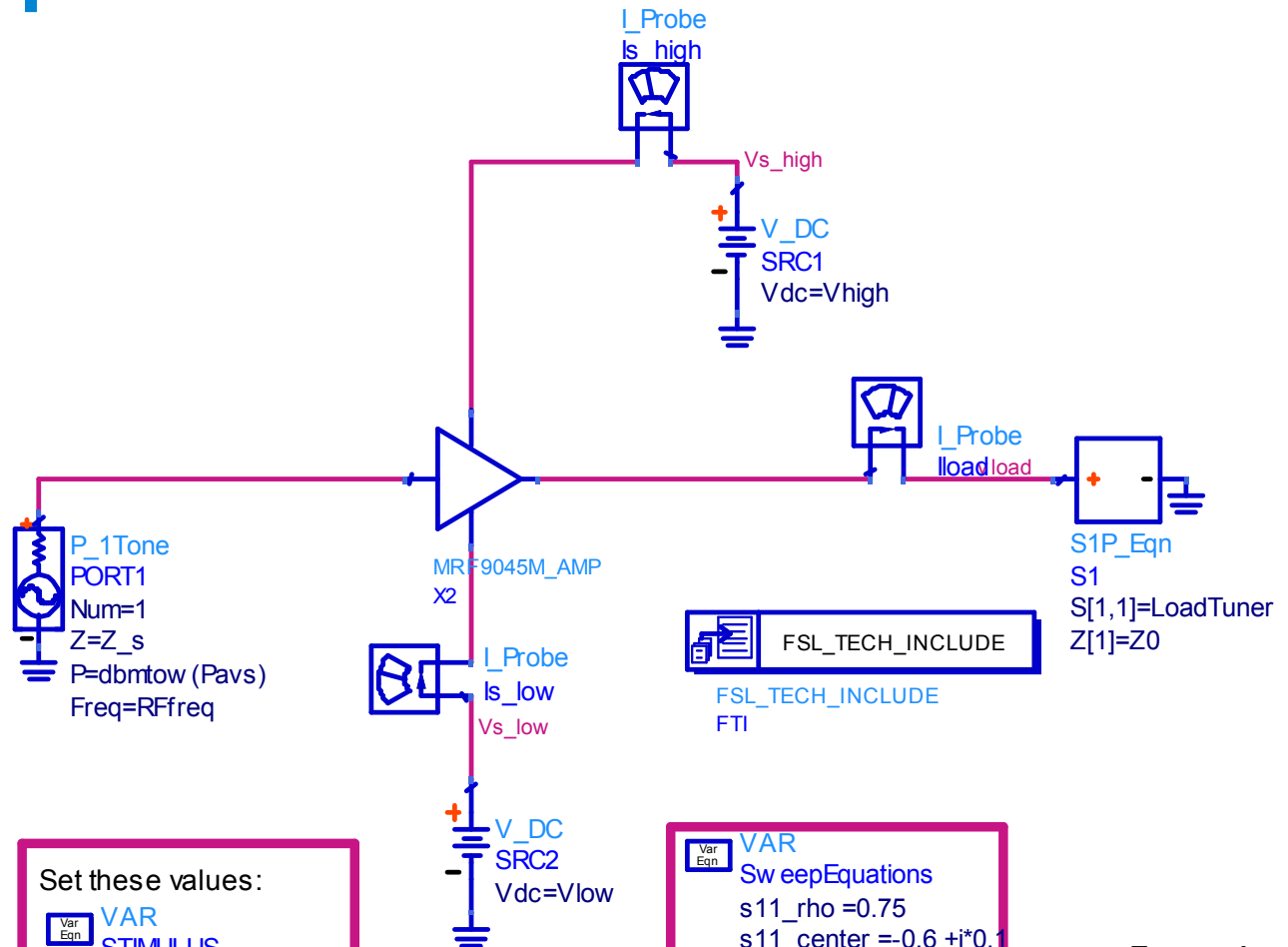VAR
STIMULUS
 Pavs=30_dBm
 RFfreq=760 MHz
 Vhigh=28.0
 Vlow=3.8




FSL_Tech_Include
 FSL_Tech_Include
 FTI

VAR
SweepEquations
 $s_{11_rho} = 0.75$
 $s_{11_center} = -0.6 + j*0.1$
 pts=100
 $Z_0 = 50$

Examples
 Search



LoadPull Contours

 

PAE_contours_p
Pdel_contours_p


indep(Pdel_contours_p) (0.000 to 46.000)
indep(PAE_contours_p) (0.000 to 18.000)

m2
indep(m2)=6
Pdel_contours_p=0.914 / 171.170
level=44.195857, number=1
impedance = 2.265 + j3.852


m1
indep(m1)=6
PAE_contours_p=0.914 / 171.180
level=47.552308, number=1
impedance = 2.265 + j3.848





Matching using Smith Chart Utility

 

Matching using Smith Chart Utility

 

Output Match

 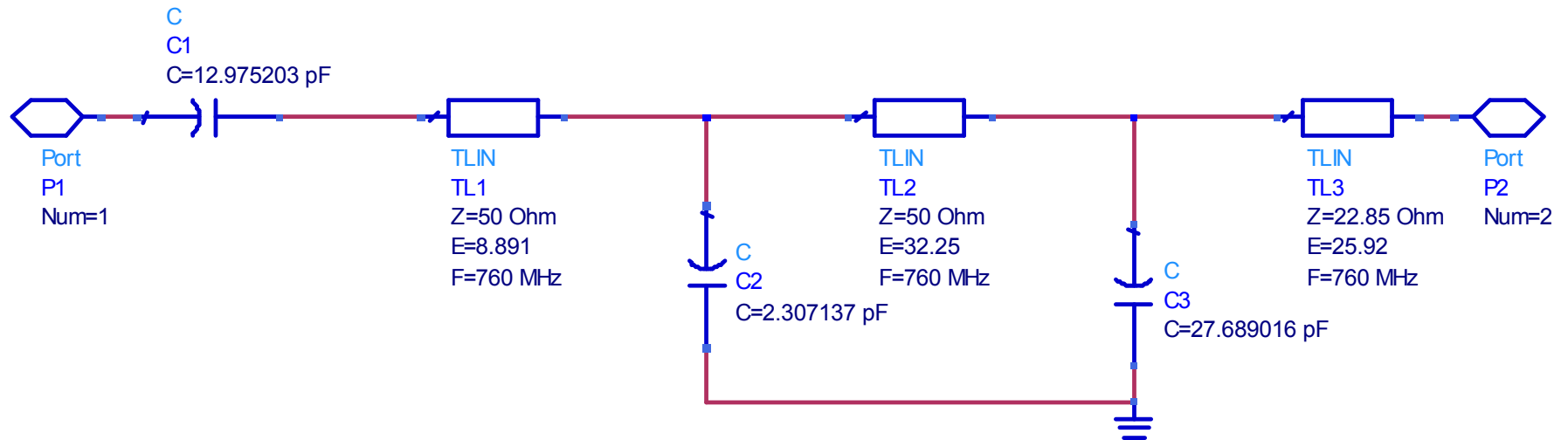

DA_SmithChartMatch1_output_match_design

DA_SmithChartMatch1

F=760 MHz

Zs=50 Ohm


Zl=(2.300-j*3.800) Ohm

Z0=50 Ohm



Agilent Technologies

SourcePull Contours

 

Pdel_contours_p
PAE_contours_p

indep(PAE_contours_p) (0.000 to 77.000)
indep(Pdel_contours_p) (0.000 to 66.000)


m2
indep(m2)=4
Pdel_contours_p=0.960 / 174.023
level=46.038749, number=1
impedance = 1.016 + j2.609

m1
indep(m1)=4
PAE_contours_p=-0.952 + j0.100
level=58.130703, number=1
impedance = 1.096 + j2.618




Matching Circuits


Output Match

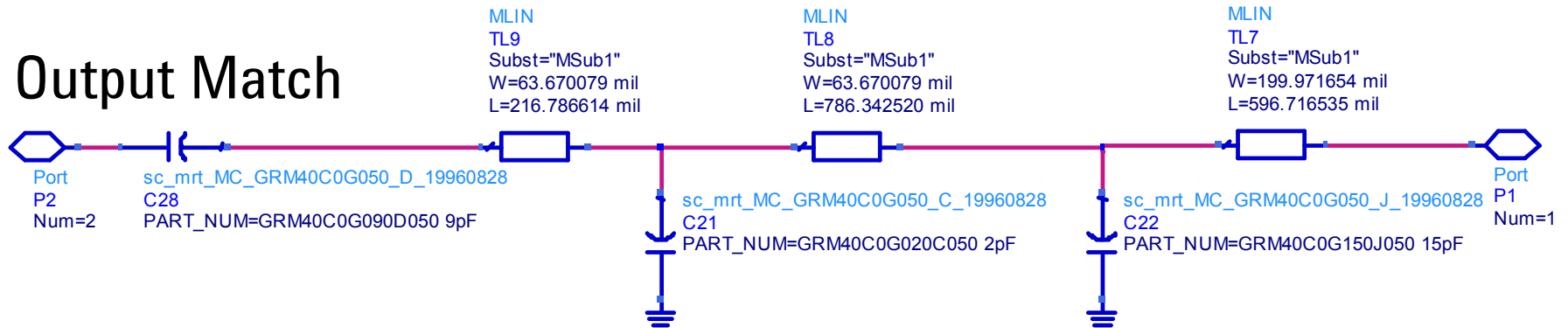


Input Match

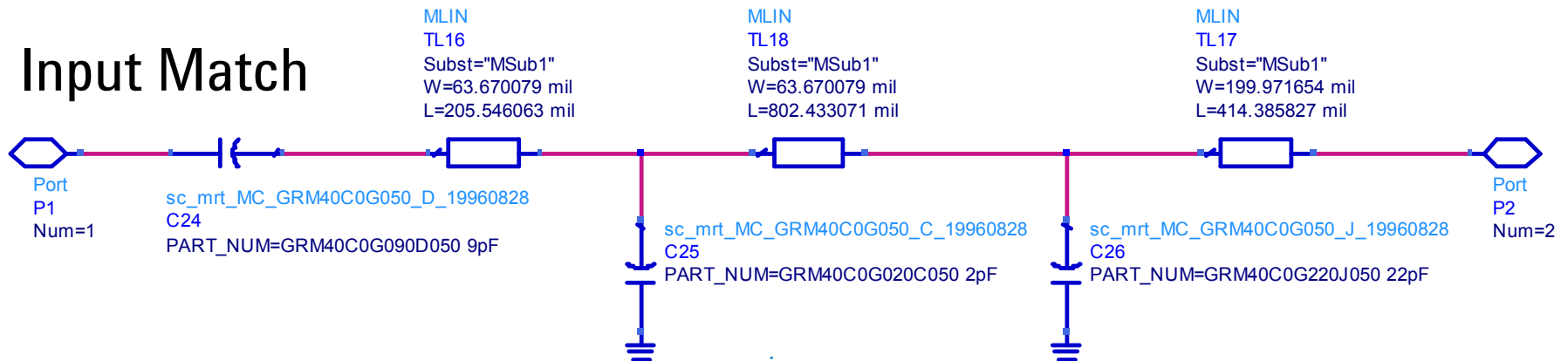


Complete Design Power Sweep

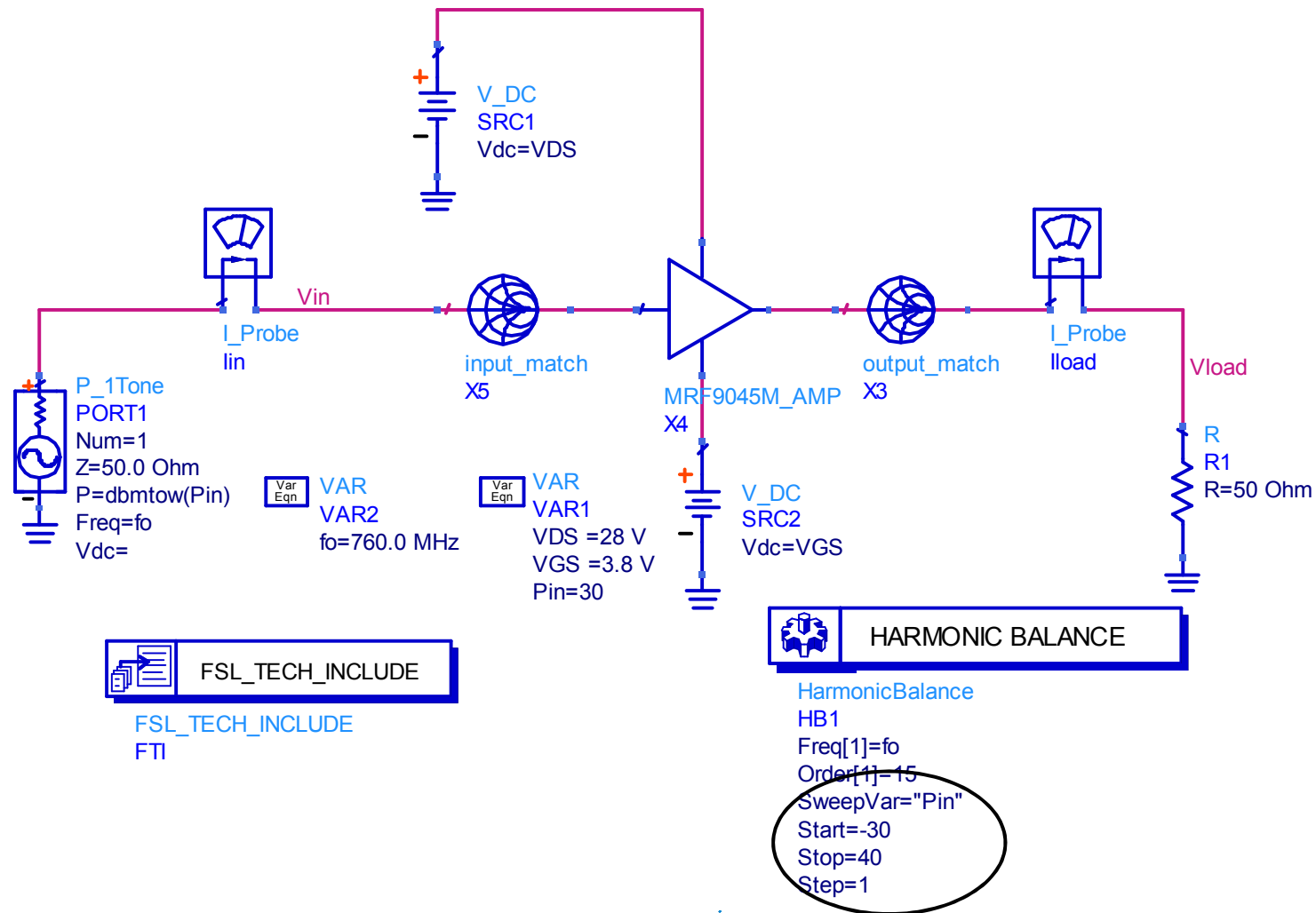


Power Compression Curve

 

Gain Compression Curve

 


Power Added Efficiency

 

Getting ready to Optimize the PA

- The next step is to optimize the design to meet the requirements.
- The Designer can take the opportunity to see if other requirements, such as layout will require any changes before proceeding to optimize.
- Example: we notice that the transistor pads are rather wide and the Tlines leading up to it are not the same width.
- Since the Tlines are much narrower, we could add a taper so we have a nice transition.
- We included a MTAPER at the input and output side

 MTAPER
Taper2
Subst="MSub1"
W1=199.971654 mil
W2=63.670079 mil
L=100.0 mil



dBm(Vload[1])
41.549



Agilent Technologies

Optimization Setup



OPTIM

Optim

Optim1

OptimType=Gradient

MaxIters=25

DesiredError=0.0

FinalAnalysis="None"

NormalizeGoals=no

SetBestValues=yes

SaveSolns=yes

SaveGoals=yes

SaveOptimVars=no

UpdateDataset=yes

SaveNominal=no

SaveAllIterations=no

UseAllOptVars=yes

UseAllGoals=yes

SaveCurrentEF=no

GOAL

Goal

Goal1

Expr="dBm(Vload[1])"

SimInstanceName="HB1"

Min=47.0

Max=

Weight=

RangeVar[1]=

RangeMin[1]=

RangeMax[1]=

GOAL

Goal

Goal2

Expr="dBm(Vload[2])-dBm(Vload[1])"

SimInstanceName="HB1"

Min=

Max=-40

Weight=

RangeVar[1]=

RangeMin[1]=


RangeMax[1]=




Optimization Results

InitialEF	FinalEF
67.187	0.000

optIter	Goal1	Goal2
10	47.003	-40.017

 **MLIN** Before
TL39
Subst="MSub1"
W=63.670079 mil
L=2194.444882 mil opt{ 250 mil to 3500 mil }

 **MLIN** After
TL39
Subst="MSub1"
W =63.670079 mil
L=551.591 mil opt{ 250 mil to 3500 mil }

Optimization Values

TL39.L*1e5/2.54
551.591

TL15.L*1e5/2.54
247.144

TL7.L*1e5/2.54
320.449

TL30.L*1e5/2.54
814.900

TL8.L*1e5/2.54
622.341


TL31.L*1e5/2.54
202.643

TL9.L*1e5/2.54
248.635


TL32.L*1e5/2.54
184.709

TL10.L*1e5/2.54
244.711


PA Results

 


Power Added Efficiency

 


Gain Compression Curve

 

Complex Modulated Signal

 

16 QAM Modulated Source

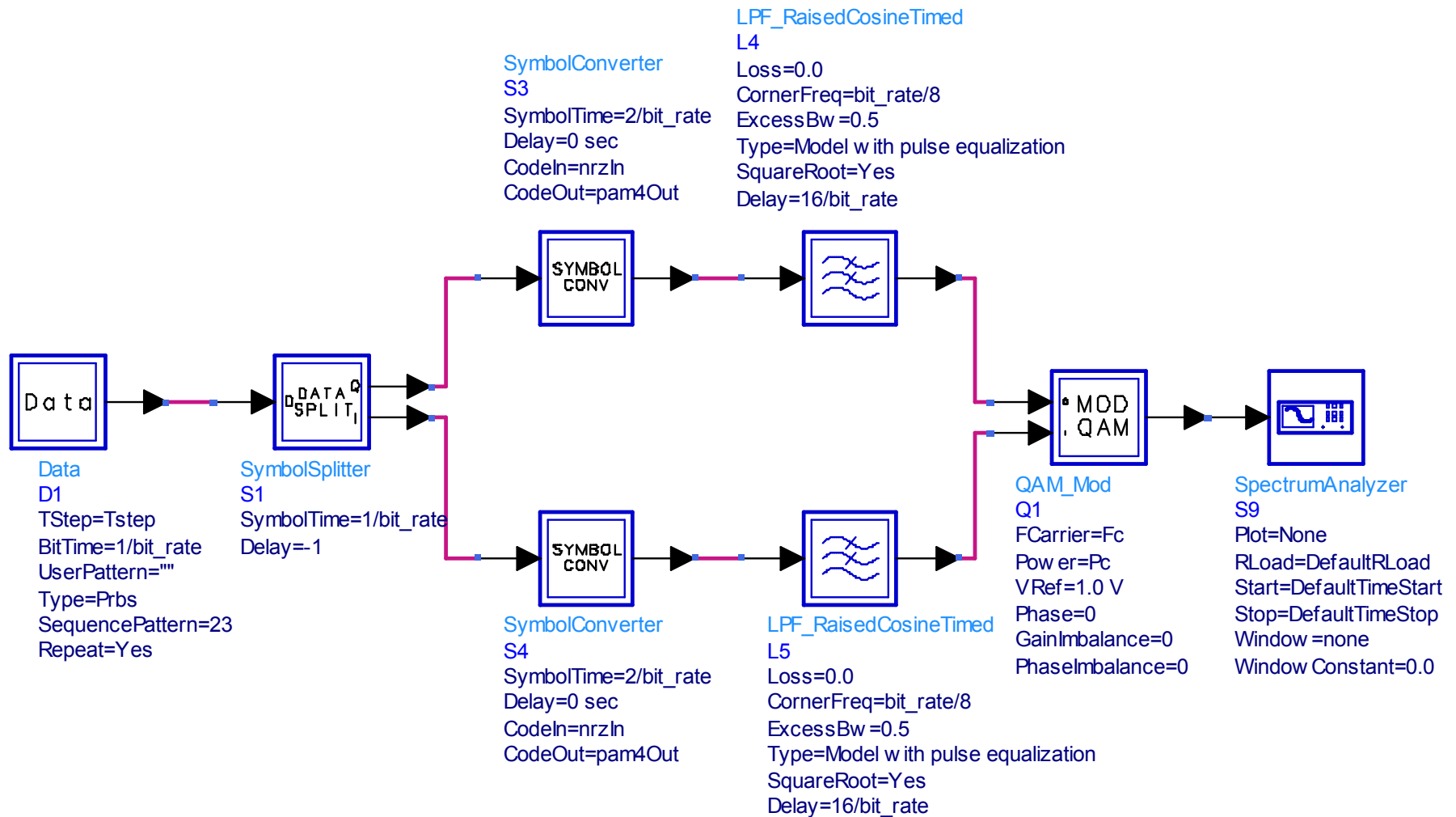


DSP and Analog Circuits Setup


- **Create a subcircuit with your analog design.**
- **You need to add either Circuit Envelope or Transient controller to the analog circuit.**
- **We use Circuit Envelope specifically with our PA since we have a Modulated Carrier.**
- **Circuit Envelope will also allow the use of Fast Cosim (Automatic Verification Modeling – AVM). This will dramatically increase the simulation speed.**
- **In the DSP schematic we will create the Modulated Carrier, feed it to the PA and collect the signal samples and spectrum.**
- **The DSP schematic contains a Envelope Output Selector component used for interfacing between circuit subnetwork output and the signal processing components.**



Ptolemy Cosim Schematic

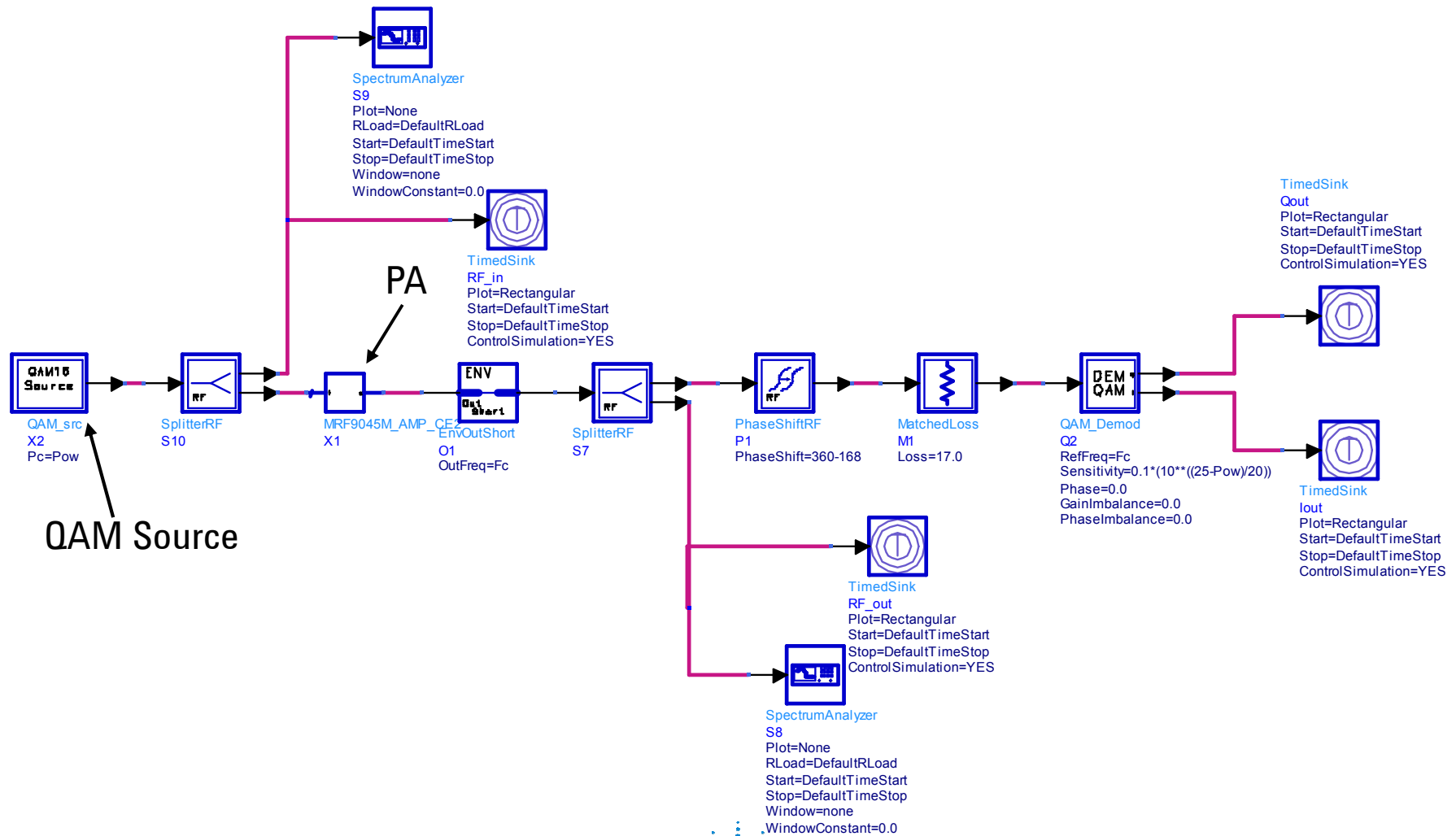

Fast Cosim Improvements

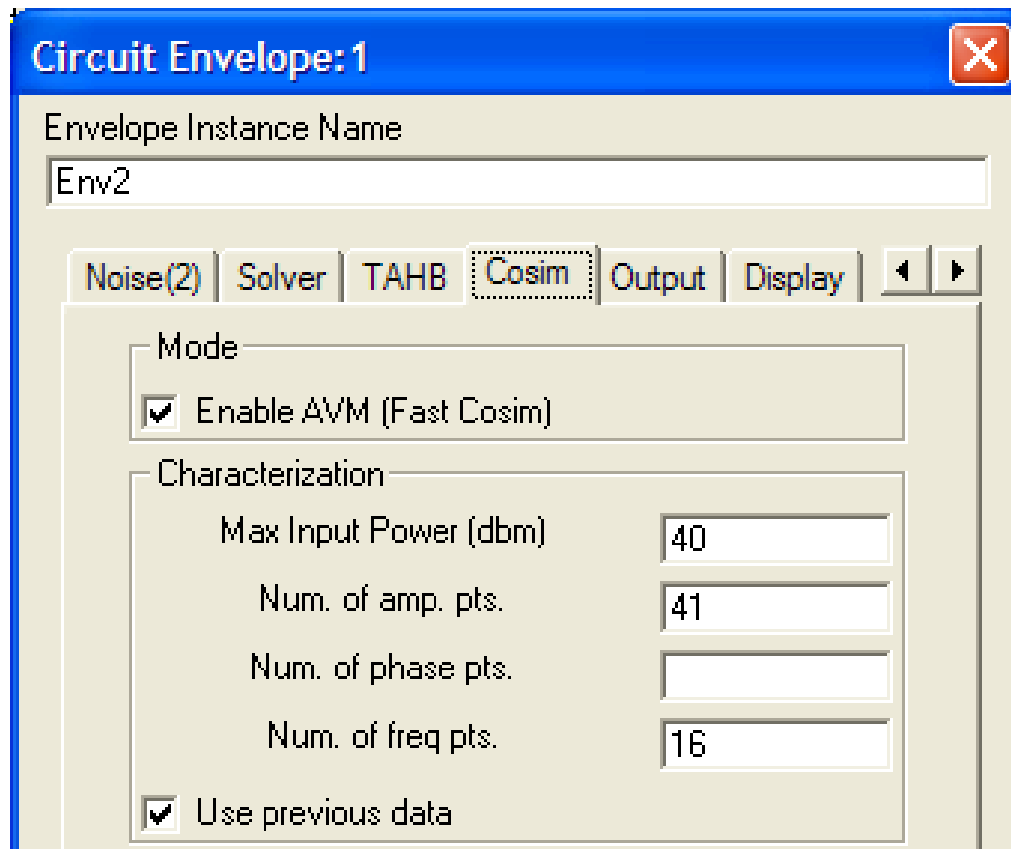

Simulation Time Benchmark:

Total bits: 1024 bits

AVM disabled : 410 sec

AVM enabled: 13 sec


AVM data reuse: 5.5 sec

AVM data reuse (16 Kbits): 17.5 sec




Cosimulation Results - Spectrum


Carrier Power
25 dBm

 

Carrier Power
30 dBm

 

Cosimulation Results - Constellation

 

Cosimulation Results

Carrier Power
30 dBm

peakP_in	peak_avg_in	avgPin
32.163	4.951	27.212

peakP_out	peak_avg_out	avgPout
47.969	3.516	44.453


Carrier Power
25 dBm

peakP_in	peak_avg_in	avgPin
30.000	7.788	22.212


peakP_out	peak_avg_out	avgPout
44.715	4.832	39.883

Cosimulation Results – CCDF


Carrier Power
25 dBm

 


Carrier Power
30 dBm

 


EVM vs. Power Measurement

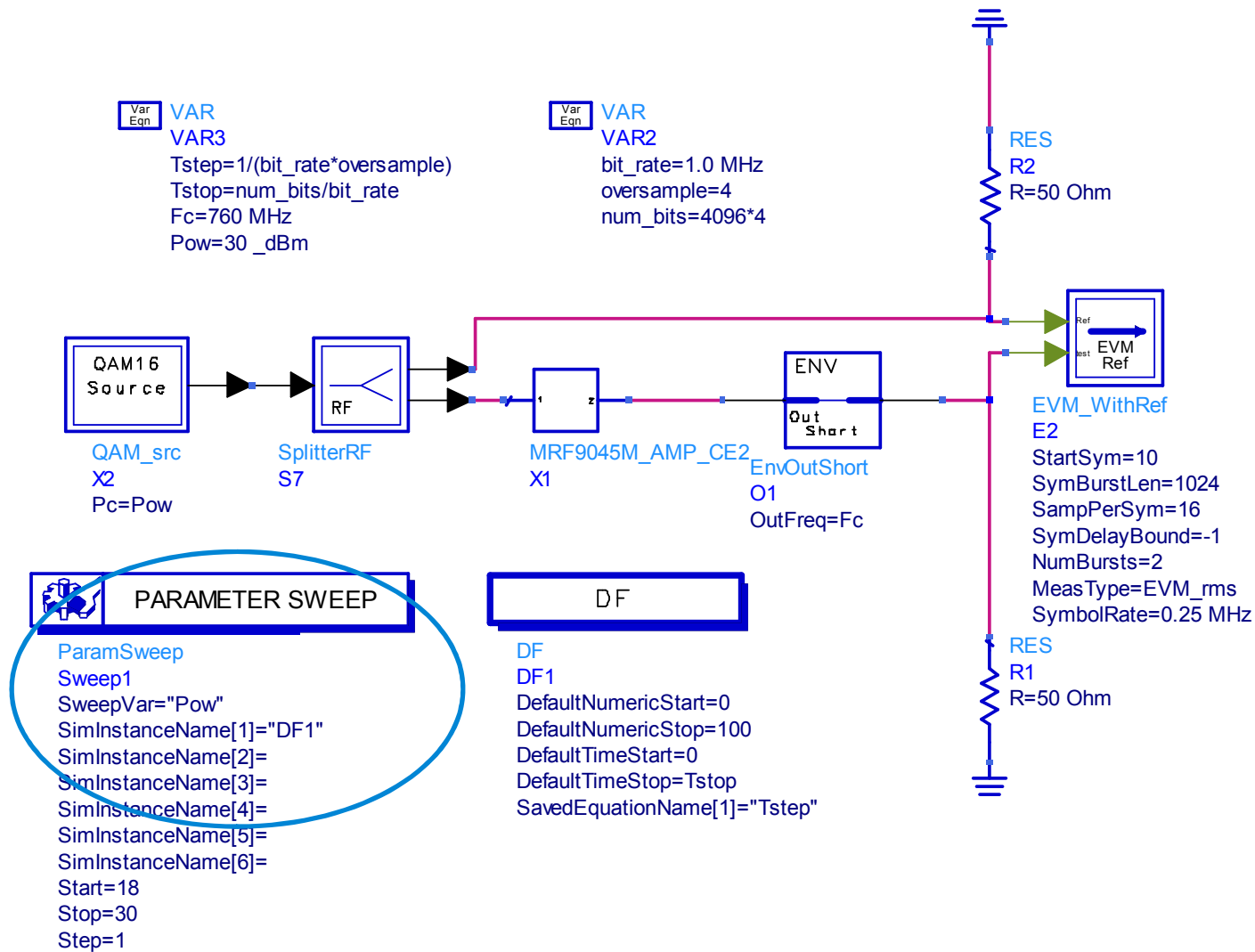


EVM vs. Power Results

 


ADS to VSA link

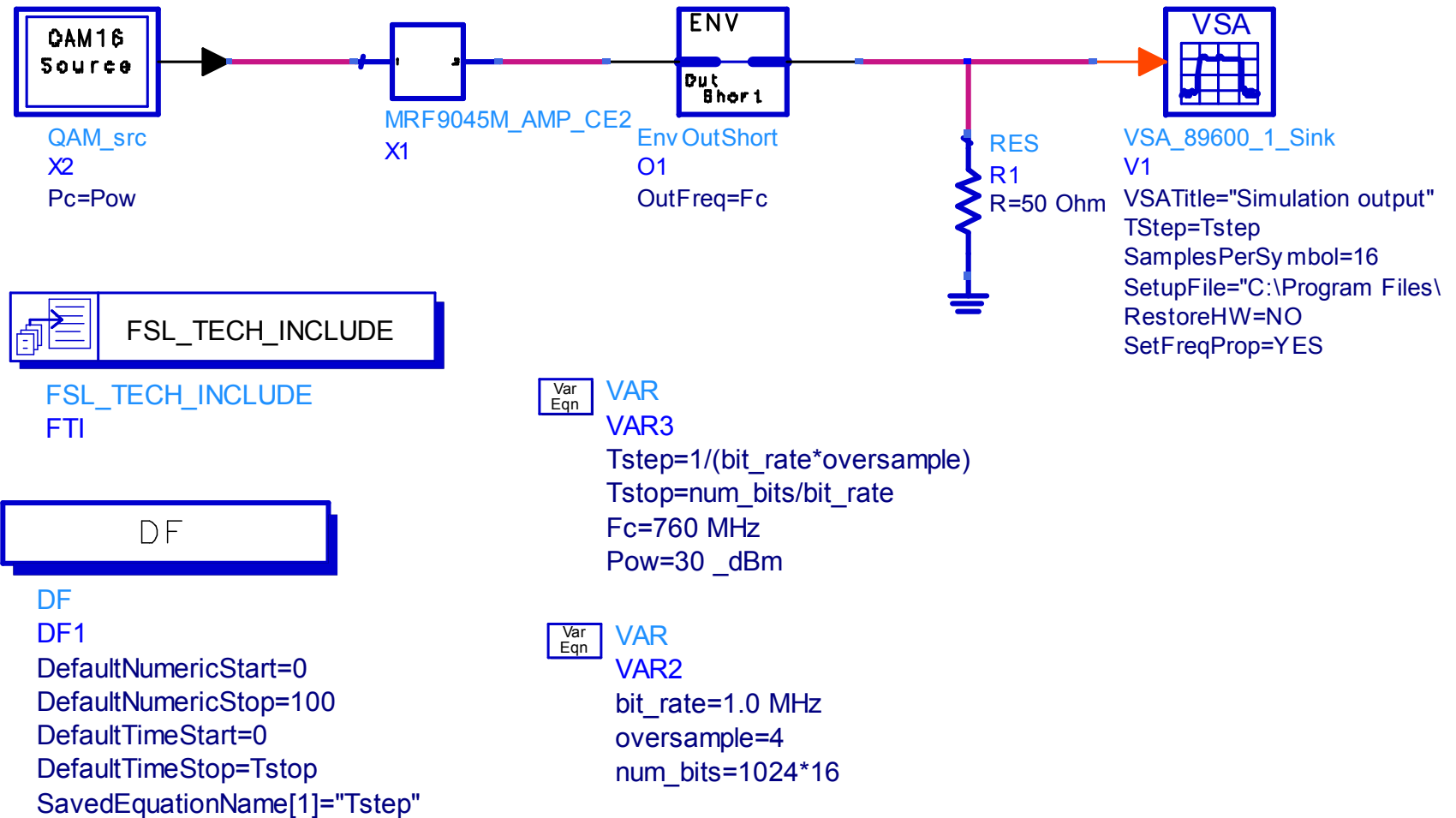


VSA Spectrum from ADS Cosim

 

VSA Constellation from ADS Cosim

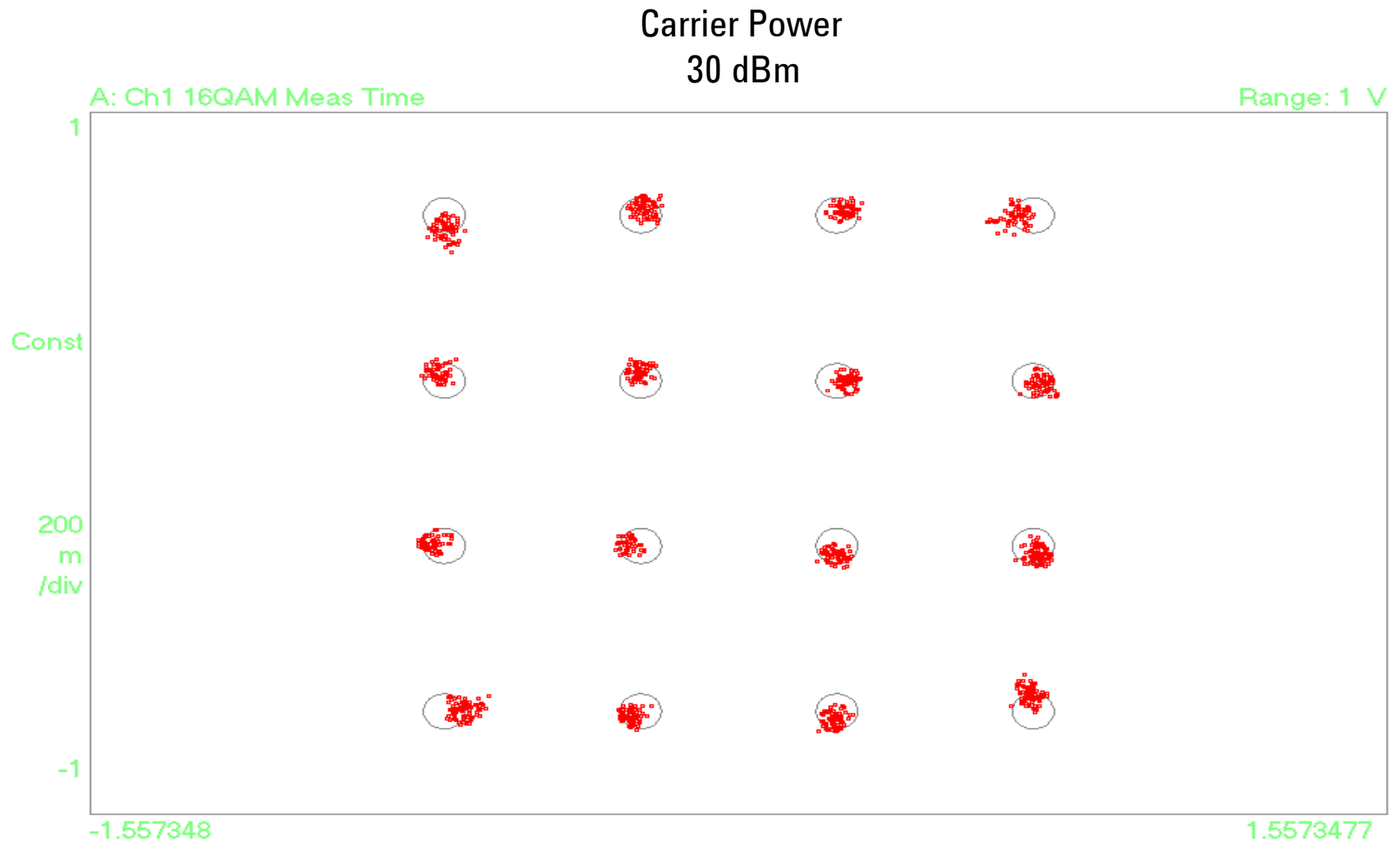

VSA Constellation from ADS Cosim

 

VSA EVM from ADS Cosim


Carrier Power
30 dBm

D: Ch1 16QAM Syms/Errs


Time:27

EVM	= 4.1676	%rms	12.719	% pk at sym	1468
MagErr	= 3.1291	%rms	-11.221	% pk at sym	2507
Phase Err	= 2.6647	deg	-11.881	deg pk at sym	3471
Freq Err	= 5.1206	mHz			
IQ Offset	= -65.85	dB	SNR(MER) = 25.051		dB
QuadErr	= 94.065	mdeg	Gain lmb = 0.01		dB


PA Layout

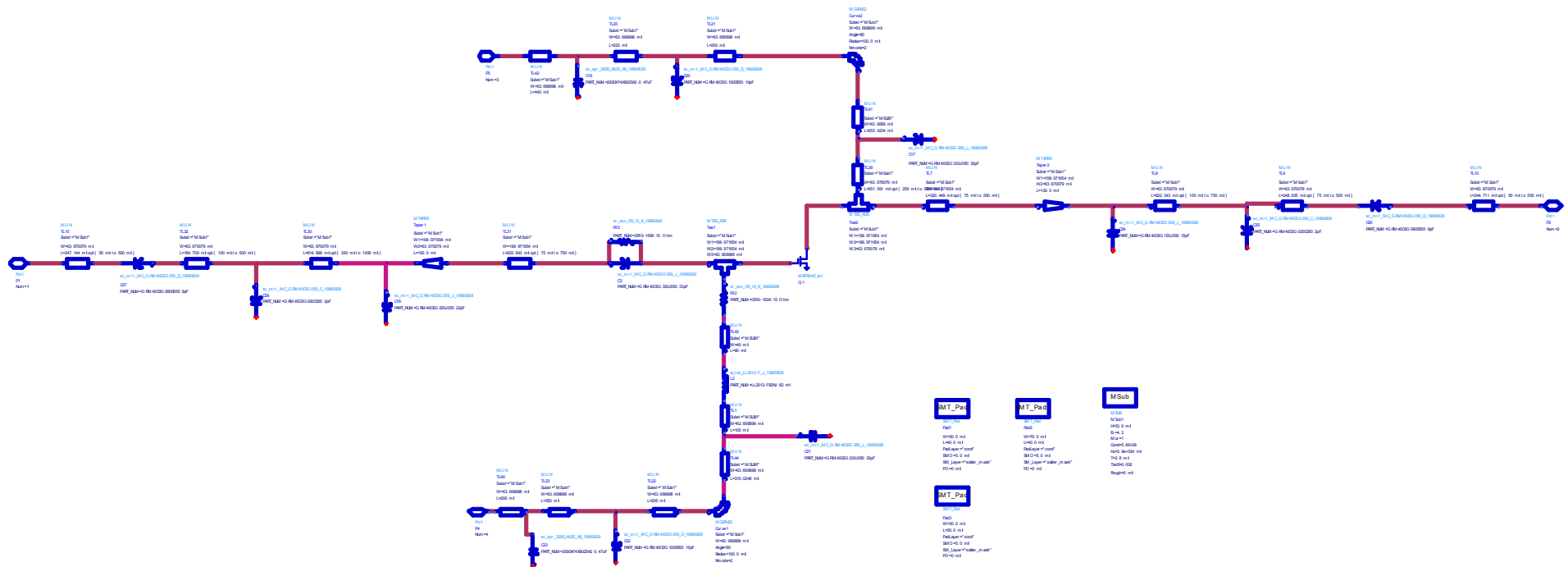

PA Layout – Generated from Schematic

 

PA Layout – Ground Fill

 

Other Possibilities

- **Run an EM Cosimulation – include layout effects in the simulation. Optimize design if necessary.**
- **Run Loadpull for IP3 or ACPR. The optimum load would then be a compromise between all the requirements.**
- **Use Connection Manager and real PA to validate design and compare vs. simulated results.**
- **Create a behavioral data model that can be used to protect you IP yet give access to your design results.**

If there is any topic about PA Design and ADS you wish to discuss email me: wilfredo_rivas-torres@agilent.com

For more information about
Agilent EEsof EDA, visit:

www.agilent.com/find/eesof



Agilent Email Updates

www.agilent.com/find/emailupdates
Get the latest information on the
products and applications you select.



Agilent Direct

www.agilent.com/find/agilentdirect
Quickly choose and use your test
equipment solutions with confidence.

www.agilent.com

For more information on Agilent Technologies'
products, applications or services, please
contact your local Agilent office. The
complete list is available at:

www.agilent.com/find/contactus

Americas

Canada	(877) 894-4414
Latin America	305 269 7500
United States	(800) 829-4444

Asia Pacific

Australia	1 800 629 485
China	800 810 0189
Hong Kong	800 938 693
India	1 800 112 929
Japan	0120 (421) 345
Korea	080 769 0800
Malaysia	1 800 888 848
Singapore	1 800 375 8100
Taiwan	0800 047 866
Thailand	1 800 226 008

Europe & Middle East

Austria	0820 87 44 11
Belgium	32 (0) 2 404 93 40
Denmark	45 70 13 15 15
Finland	358 (0) 10 855 2100
France	0825 010 700*
	*0.125 €/minute
Germany	01805 24 6333**
	**0.14 €/minute
Ireland	1890 924 204
Israel	972-3-9288-504/544
Italy	39 02 92 60 8484
Netherlands	31 (0) 20 547 2111
Spain	34 (91) 631 3300
Sweden	0200-88 22 55
Switzerland	0800 80 53 53
United Kingdom	44 (0) 118 9276201

Other European Countries:

www.agilent.com/find/contactus

Revised: March 27, 2008

Product specifications and descriptions
in this document subject to change
without notice.

© Agilent Technologies, Inc. 2008

Printed in USA, October 12, 2004

5989-9594EN



Agilent Technologies