

Chapter 9 Sample-and-Hold Circuits


馮武雄 教授
長庚大學 電子系

1

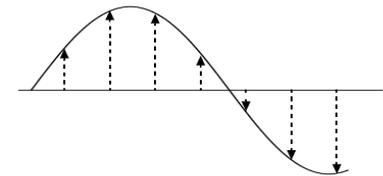3. Sample-and-Hold Circuits

Sampling


Ideal uniform *sampling* of a continuous-time, band-limited signal, $x(t)$, corresponds to a multiplication of that signal by an ideal impulse train.



2

Testing S/Hs

Test setup

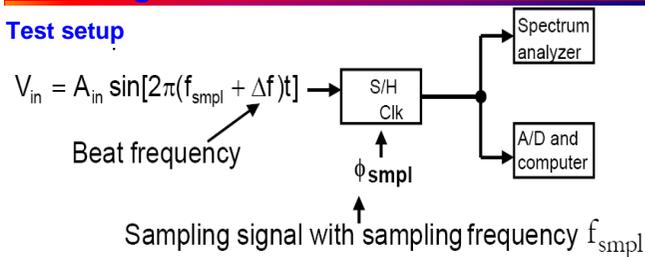


where the S/H is operating at its maximum sampling frequency f_{smpl} .

3

Testing S/Hs(Cont.)

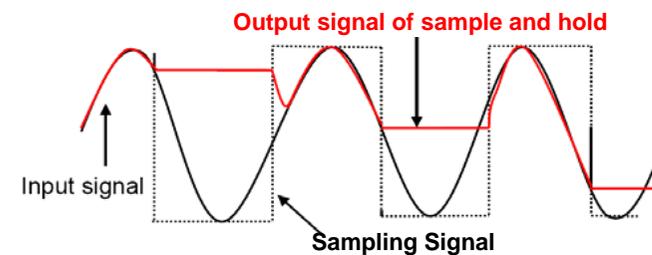
• Example waveforms for the above test setup •



• The ideal sinusoidal wave at the beat frequency is subtracted from the measured signal. The error signal is then analyzed for RMS content and spectral components using FFT (fast Fourier Transform).


4

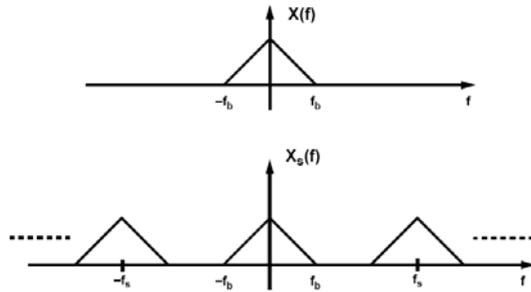- In the frequency domain this is equivalent to convolving the input spectrum with a train of impulses and results in images of the input spectrum centered at integer multiples of the sampling frequency.




5

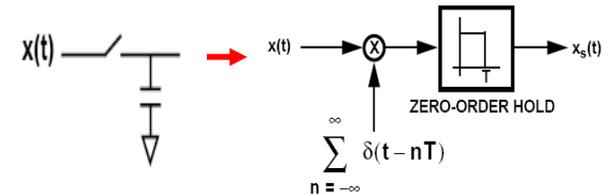- Generally, it is necessary to “hold” the sampled signal for some period of time. A simple SAMPLE & HOLD circuit is formed by sampling switch followed by a hold capacitor. Ideally, this is equivalent to impulse sampling followed by a zero-order hold.




6

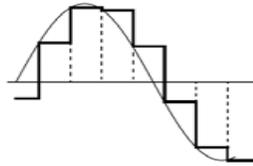which results in a continuous time output waveform that steps between the sampled signal values




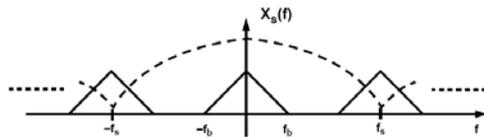In the frequency domain, the continuous-time output of this sample & hold circuit consists of repeated images of band-limited input spectrum shaped by a sinc envelope.



7

- In practice, it is not feasible to implement an impulse sampler in which the sampling switch is close and then opened in virtually “zero” time relative to the rate of change of the signal. Instead, the sampling switch and hold capacitor are operated as a TRACK & HOLD circuit. The switch is closed for some fraction of the sampling period, during which time the output “tracks” the input, and then is quickly opened at the sampling instant.

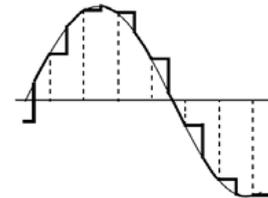


- In the frequency domain, the zeros of the sinc envelope are altered corresponding to the length of the hold time. For example, if the hold time is $T_s/2 = 1/2f_s$, then the zeros of the sinc occur at integer multiples of $2f_s$.

8

Classes of Sampling

NYQUIST-RATE SAMPLING

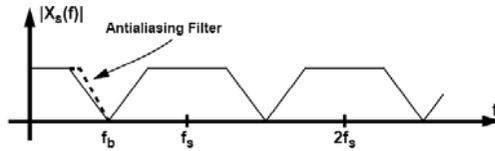
If signal has a bandwidth of f_b , then $f_s = 2f_b$.



9

OVERSAMPLING

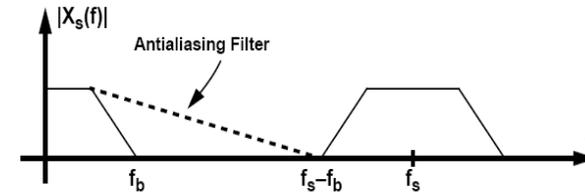
- If signal has a bandwidth of f_b , then $f_s \gg 2f_b$
- Relaxes requirements on the preceding antialias filter.
- Reduces inband quantization noise when the sampler is followed by a quantizer.



10

UNDERSAMPLING (also called SUBSAMPLING)



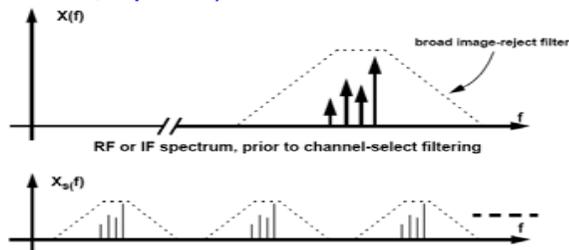
- Sampling at a rate less than the Nyquist rate results in aliasing.
- But, if the signal is centered at an intermediate frequency and band-limited, it is not necessarily destructive.
- Undersampling can be exploited to mix a narrowband RF or IF signal down to a lower frequency. (P. Chan, et al., ESSCIRC, Sept. 1993)




11

Sample & Hold Circuits

Ideal Track & Hold

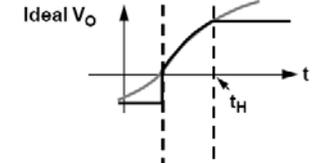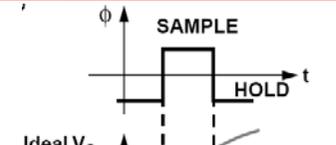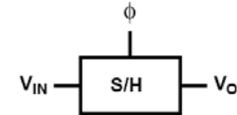


REAL TRACK & HOLD

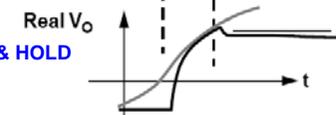

12

MOS Sample & Hold

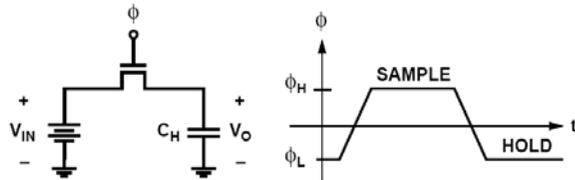

Imperfections

- Non-zero acquisition time / Finite bandwidth in sample (track) mode
- Acquisition time = τ

$$\tau = R_{on}C_H \quad R_{on} = \frac{1}{\mu C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_T)}$$

- Bandwidth in sample mode = $1/\tau$

13

• EXAMPLE

$$\begin{aligned} W/L &= 10 \mu\text{m} / 1 \mu\text{m} & V_T &= 0.7 \text{ V} \\ C_H &= 1 \text{ pF} & \mu C_{ox} &= 155.2 \mu\text{A/V}^2 \\ V_{IN} &= 0 \text{ V} & \mu &= 450 \text{ cm}^2/\text{V-sec} \\ \phi_H &= 3.3 \text{ V} \end{aligned}$$



$$R_{on} = \frac{1}{\mu C_{ox} \left(\frac{W}{L}\right) (\phi_H - V_{IN} - V_T)} = \frac{1}{(155.2)(10/0.8)(2.6)} = 198 \Omega$$

$$BW \cong \frac{1}{\tau} = \frac{1}{R_{on}C_H} = 5.05 \times 10^9 \text{ rad/s} = 804 \text{ MHz}$$

14

MOS S/H Basics

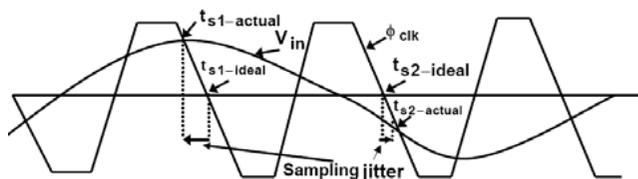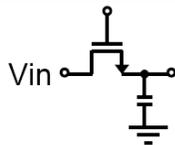- Two error sources due to switch
 - a. channel charge injection
 - b. Clock feedthrough
 where b is usually smaller than a
- Time jitter
 - caused by clock waveforms having finite slopes




- When V_{in} is above 0V, the true sampling time is earlier than the ideal sampling time.
- When V_{in} is less than 0V, the true sampling time is late.

• S&H Pedestal Error

臺座


- error introduced at the S&H output during transition from sample to hold
- caused by charge injection
- depends on clock transition time (waveform of ϕ)

Quasi-Static (slow) Gating

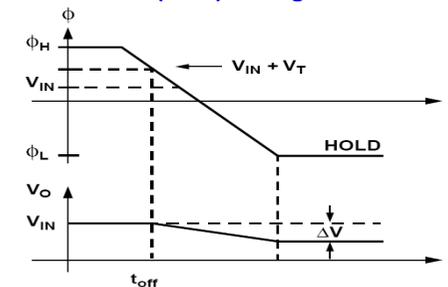

16

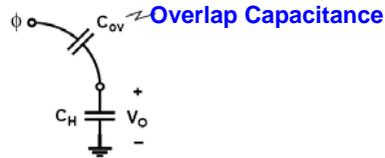- Channel charge has disappeared by t_{off} w/o introducing offset (all channel chg $\rightarrow V_{IN}$)
- For $t > t_{off}$ ($\phi < V_{IN} + V_T$)




At $\phi = \phi_L$
$$\Delta V = \left(\frac{C_{ov}}{C_{ov} + C_H} \right) (V_{IN} + V_T - \phi_L)$$

Thus, in the hold mode

$$V_O = V_{IN} - \Delta V = V_{IN} - \left(\frac{C_{ov}}{C_{ov} + C_H} \right) (V_{IN} + V_T - \phi_L)$$

17

Fast Gating

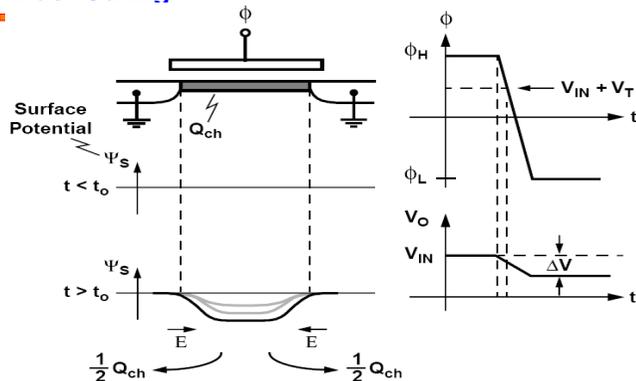


- Channel pinches off at source and drain
- Q_{ch} divides between source and drain depending on impedances loading these nodes

19

$$\therefore V_O = (1 + \varepsilon)V_{IN} + V_{os}$$

where
$$\varepsilon = -\frac{C_{ov}}{C_{ov} + C_H} \quad V_{os} = -(V_T - \phi_L) \left(\frac{C_{ov}}{C_{ov} + C_H} \right)$$

EXAMPLE

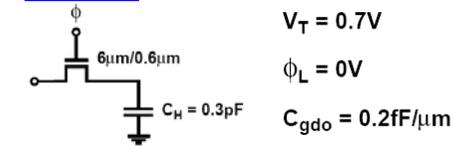


$$\varepsilon = -\frac{(6\mu\text{m})(0.2\text{fF}/\mu\text{m})}{(6\mu\text{m})(0.2\text{fF}/\mu\text{m}) + 0.3\text{pF}} = -\left(\frac{1.2\text{fF}}{0.3\text{pF}} \right) = -0.4\%$$

$$V_{os} = -(0.7\text{V} - 0\text{V}) \left(\frac{1.2\text{fF}}{0.3\text{pF}} \right) = -2.8\text{mV}$$


18

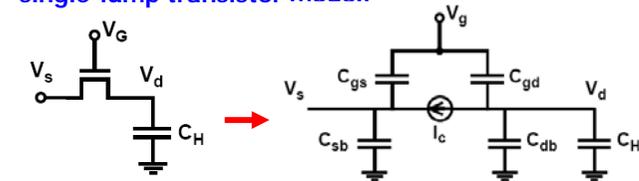In the "fast gating" case, charge trapped in the channel is removed by diffusion to the source and drain. The isolation of charge in the channel and its subsequent diffusion cannot be modeled with a single-lump transistor model.



20

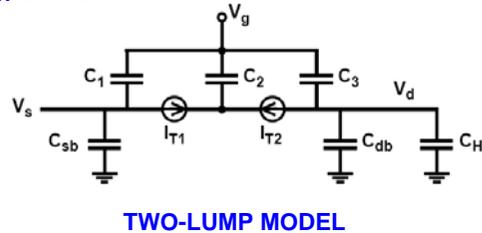•To model the isolation of channel charge in the fast-gating case, a distributed model (i.e. multiple lumps) must be used. The simplest of these is a two-lump model.



21

Limiting Fast Case

•Assume that Qch divides equally between the input and output, which is true if CH is large and RS (source resistance) is small.

$$\Delta V = \left(\frac{C_{ov}}{C_{ov} + C_H} \right) (\phi_H - \phi_L) + \frac{1}{2} Q_{ch} \left(\frac{1}{C_H} \right)$$

$$Q_{ch} = C_{ch} [\phi_H - (V_{IN} + V_T)]$$

where

$$C_{ch} = C_{ox} \cdot W \cdot L_{ELEC} = C_{ox} (L - 2L_D) W$$

$$\Delta V = \left(\frac{C_{ov}}{C_{ov} + C_H} \right) (\phi_H - \phi_L) + \frac{1}{2} \left(\frac{C_{ch}}{C_H} \right) (\phi_H - \phi_L - V_T)$$

Therefore, in the HOLD condition

$$V_O = V_{IN} - \Delta V = (1 + \varepsilon) V_{IN} + V_{os}$$

where

22

$$\varepsilon = \frac{1}{2} \left(\frac{C_{ch}}{C_H} \right) = \frac{1}{2} \left(\frac{C_{ox} W L_{ELEC}}{C_H} \right)$$

$$V_{os} = - \left(\frac{C_{ov}}{C_{ov} + C_H} \right) (\phi_H - \phi_L) - \frac{1}{2} \left(\frac{C_{ch}}{C_H} \right) (\phi_H - V_T)$$

EXAMPLE $W/L = 10 \mu m / 1 \mu m$ $V_T = 0.7 V$
 $C_H = 1 pF$ $C_{ox} = 3.54 fF / \mu m^2$
 $\phi_H = 3.3 V$ $C_{ov} = 0.3 fF / \mu m^2$
 $\phi_L = 0 V$ $L_D = 0.1 \mu m$

$$C_{ch} = W(L - 2L_D) C_{ox} = (10)(0.8)(3.54) = 28.3 fF$$


$$\varepsilon = \frac{1}{2} \left(\frac{28.3 fF}{1 pF} \right) = 1.4 \%$$

$$V_{os} = - \left(\frac{0.3 fF}{0.3 fF + 1 pF} \right) (3.3 V - 0 V) - \frac{1}{2} \left(\frac{28.3 fF}{1 pF} \right) (3.3 V - 0.7 V)$$

$$\cong - 9.9 mV - 36.8 mV = - 46.7 mV$$

23

•In practice, $|\varepsilon|$ and $|V_{os}|$ decrease as the fall time of ϕ increases

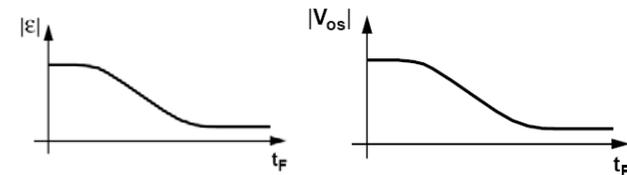

24

S&H SPEED/ACCURACY TRADEOFF

- To first order, the worst case pedestal error is approximately

$$\Delta V_{\text{error}} = \frac{1}{2} \left(\frac{Q_{\text{ch}}}{C_H} \right)$$

while

$$BW \cong \frac{1}{\tau} = \frac{1}{R_{\text{on}} C_H}$$

where

$$R_{\text{on}} = \frac{1}{\mu C_{\text{ox}} \left(\frac{W}{L} \right) (V_{\text{gs}} - V_T)} = \frac{L^2}{\mu C_{\text{ox}} W L (V_{\text{gs}} - V_T)} = \frac{L^2}{\mu Q_{\text{ch}}}$$

Thus

$$\begin{aligned} \frac{\Delta V_{\text{error}}}{BW} &= \tau \cdot \Delta V_{\text{error}} \\ &= \left(\frac{L^2 C_H}{\mu Q_{\text{ch}}} \right) \left(\frac{Q_{\text{ch}}}{2 C_H} \right) = \frac{L^2}{2\mu} \end{aligned}$$

25

EXAMPLE

$$\begin{aligned} W/L &= 10 \mu\text{m} / 1 \mu\text{m} & V_T &= 0.7 \text{ V} \\ C_H &= 1 \text{ pF} & \mu C_{\text{ox}} &= 155.2 \mu\text{ A/V}^2 \\ V_{\text{IN}} &= 0 \text{ V} & \mu &= 450 \text{ cm}^2/\text{V-sec} \\ \phi_H &= 3.3 \text{ V} \end{aligned}$$

$$BW \cong \frac{1}{\tau} = \frac{1}{R_{\text{on}} C_H} = 5.05 \times 10^9 \text{ rad/s} = 804 \text{ MHz}$$

$$\tau \cdot \Delta V_{\text{error}} \cong \frac{(1 \mu\text{m})^2}{1450 \text{ cm}^2/\text{V-sec}} = 0.71 \times 10^{-12} \text{ sec-V}$$

Drop in Hold Mode

- discharge of capacitor during hold mode
- depends on leakage currents drawn by parasitic DC paths


26

- Feedthrough
 - percentage of input signal that appears at output during hold mode
 - due to parasitic capacitive path between switch input and output terminals
- Dynamic Tracking Nonlinearity
 - input-dependent switch on-resistance introduces distortion
 - primarily a concern in high-speed sampling circuits
- Signal-Dependent Sampling Instant
 - due to finite clock transition time
 - primarily a concern when clock transition time is comparable with input signal slew rate


27

kT/C Noise

For a simple MOS sample & hold circuit

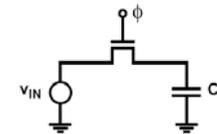

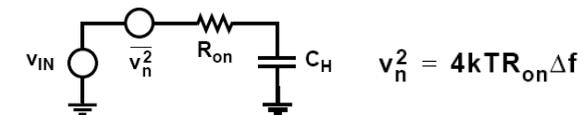the equivalent circuit in the sample (track) mode is:



$$v_n^2 = 4kTR_{\text{on}}\Delta f$$

The total noise appearing across C_H is then

$$v_{\text{OT}}^2 = \int_0^{\infty} v_n^2 |H(f)|^2 df$$

28

where $H(f) = \frac{1}{1+j2\pi f\tau} = \frac{1}{1+j2\pi R_{on}C_H f}$

Thus, $\overline{v_{oT}^2} = 4ktR_{on} \int_0^\infty \frac{1}{1+(2\pi R_{on}C_H f)^2} df$


$$= 4ktR_{on} \left(\frac{1}{2\pi R_{on}C_H} \right) \int_0^\infty \left(\frac{1}{1+x^2} \right) dx = \frac{2kT}{\pi C_H} \left(\frac{\pi}{2} \right) = \frac{kT}{C_H}$$

29

Reduction of S&H Nonidealities

S&H Offset Cancellation

- Dummy Switch

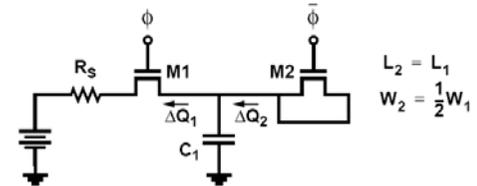

$$\Delta Q_2 = \Delta Q_{ov1} + \frac{1}{2} \Delta Q_{CH1}$$


but

$$\Delta Q_1 = \Delta Q_{ov1} + \alpha \left(\frac{\Delta Q_{CH1}}{2} \right)$$

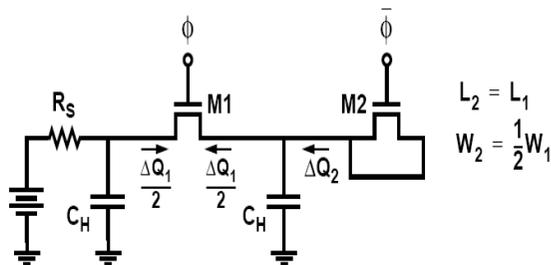Problem: α not exactly = 1, especially if R_s is small

30


- Dummy Switch w/ Equalizing Capacitor (*Bienstman & De Man, JSSC 12/80*)



- Better cancellation
- Limits bandwidth in sample mode

31

CMOS Sampling Switch

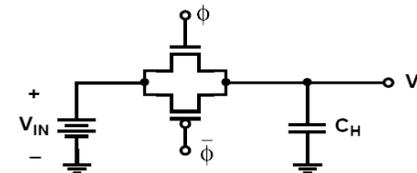

In the limiting "fast gating" case:

$$\frac{1}{2} |Q_{chN}| = \frac{1}{2} (\phi_H - V_{IN} - V_{TN}) W_N L_N C_{ox}$$


$$\frac{1}{2} |Q_{chP}| = \frac{1}{2} (V_{IN} - \phi_L - |V_{TP}|) W_P L_P C_{ox}$$

$$\Delta V_o = -\frac{1}{2} \frac{|Q_{chN}|}{C_H} + \frac{1}{2} \frac{|Q_{chP}|}{C_H}$$

• Partial cancellation of the channel charge is achieved, but the cancellation is signal dependent.

32

Fully Differential Sampling

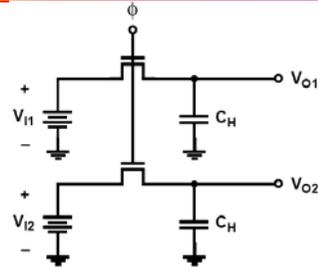

$$V_{O1} - V_{O2} = [V_{I1}(1 + \varepsilon_1) + V_{os1}] - [V_{I2}(1 + \varepsilon_2) + V_{os2}]$$

$$= (V_{I1} - V_{I2}) \left[1 + \left(\frac{\varepsilon_1 + \varepsilon_2}{2} \right) \right] + V_{os1} - V_{os2} + (V_{I1} + V_{I2}) \left(\frac{\varepsilon_1 - \varepsilon_2}{2} \right)$$

Thus

33

$$V_{O1} - V_{O2} = (V_{I1} - V_{I2})(1 + \varepsilon_D) + V_{os} + (V_{I1} + V_{I2})\varepsilon_C$$

$$\varepsilon_D = \frac{\varepsilon_1 + \varepsilon_2}{2} = \text{Differential-Mode Gain Error}$$

$$\varepsilon_C = \frac{\varepsilon_1 - \varepsilon_2}{2} = \text{Common-Mode Gain Error}$$


$$V_{os} = V_{os1} - V_{os2} = \text{Offset}$$

- V_{os} and common-mode gain error determined by mismatch
- Good CMRR and PSRR
- Insensitive to clock waveform
- Even with no mismatch, $V_{O1} - V_{O2} = (1 + \varepsilon_D)(V_{I1} - V_{I2})$

34

Bottom Plate Sampling

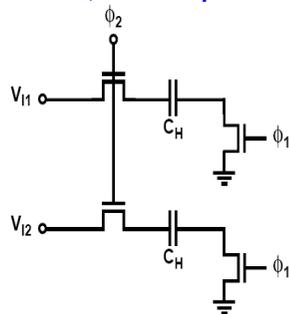- Used to eliminate input-dependent charge injection error, which is present in differential S&H circuits.




- with ϕ_1 and ϕ_2 HIGH, V_{I1} and V_{I2} are tracked (sampled)
- first $\phi_1 \rightarrow$ LOW
 - V_{I1} and V_{I2} are held on CH's
 - charge injection is independent of V_{I1} and V_{I2}
- next $\phi_2 \rightarrow$ LOW
 - no charge injection since CH's are floating

35

Bootstrapping (Abo & Gray, JSSC 05/99)

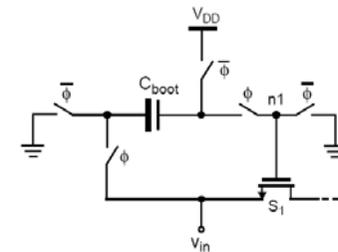- Used to eliminate dynamic tracking nonlinearities by reducing signal dependency of switch on-resistance.



- when ϕ LOW:
 - C_{boot} is precharged to V_{DD}
 - sampling switch is off
- when ϕ HIGH:
 - constant voltage, equal to V_{DD} is established between gate and source terminal of sampling switch

36


- ideally: switch on-resistance is independent of input signal
- in practice: parasitic capacitance at node n_1 , C_{n1} , and dependence of V_T on input voltage limit linearity that can be achieved

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W_1}{L_1} \left(\frac{C_{boot}}{C_{boot} + C_{n1}} V_{DD} - \frac{C_{n1}}{C_{boot} + C_{n1}} v_{in} - V_T \right)}$$

37

TRACK (SAMPLE) MODE (ϕ high)

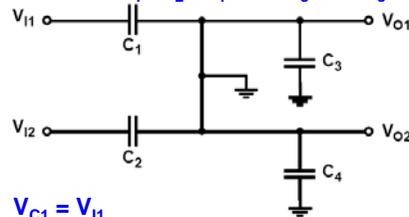- Switches M_1 , M_2 , M_4 and M_5 on, M_3 off



$$\begin{aligned} V_{C1} &= V_{I1} \\ V_{C2} &= V_{I2} \\ V_{O1} &= V_{O2} = 0 \end{aligned}$$

HOLD MODE (ϕ low)


- First $\phi 1 \rightarrow$ LOW, turning off M_1 , M_2 , M_4 and M_5
- Then $\phi 2 \rightarrow$ HIGH, turning on M_3

39


Switched-Capacitor Circuit

Common-Mode Cancellation

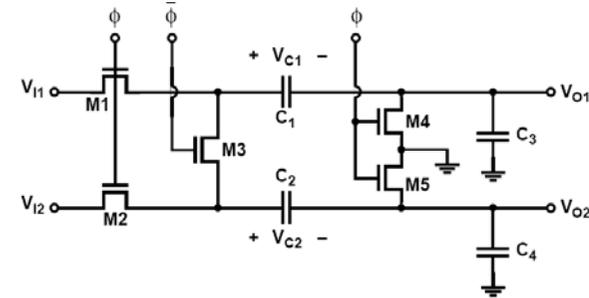- In a fully differential sample & hold circuit, the common-mode input level can be removed with the following circuit (Yen & Gray, JSSC 12/82)



38

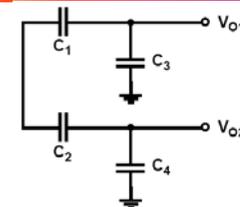

- If $C_1 = C_2$ and $C_3 = C_4$, while transistor pairs M_1 - M_2 and M_4 - M_5 match, then


$$V_{O1} - V_{O2} = -(V_{I1} - V_{I2}) \left(\frac{C_1}{C_1 + C_3} \right)$$

and

$$V_{O1} + V_{O2} = 0$$


40

Charge Redistribution Amplifiers

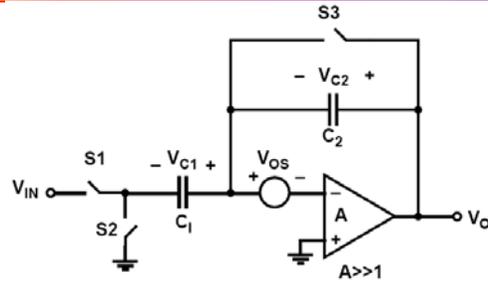

SAMPLE $S_1 = S_2 = 1$ (on)
 $S_2 = 0$ (off)
 $V_{C1} = V_{os} - V_{IN}$
 $V_{C2} = 0$
 $V_O = V_{os}$

41

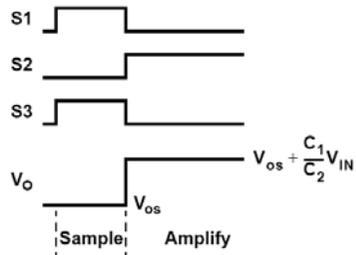


- Offset is not cancelled, but it is NOT AMPLIFIED
- Input-referred offset = $(C_1/C_2)V_{os}$, where usually $C_2 < C_1$

43

AMPLIFY

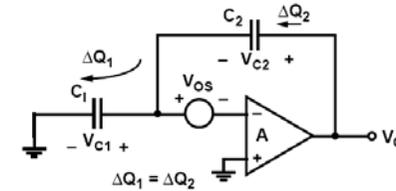
$S_1, S_3 \rightarrow 0$
 $S_2 \rightarrow 1$



$V_{C1} \rightarrow V_{os}$
 $\Delta V_{C1} = V_{os} - (V_{os} - V_{IN}) = V_{IN}$
 $\Delta Q_1 = C_1 \Delta V_{C1} = C_1 V_{IN}$
 $\Delta Q_2 = C_2 \Delta V_{C1} = \Delta Q_1$
 $\Delta V_{C2} = \left(\frac{C_1}{C_2}\right) V_{C2} = V_{C2}$
 $V_O = V_{C2} + V_{os} = \left(\frac{C_1}{C_2}\right) V_{IN} + V_{os}$

42

INPUT DIFFERENCE AMPLIFIER

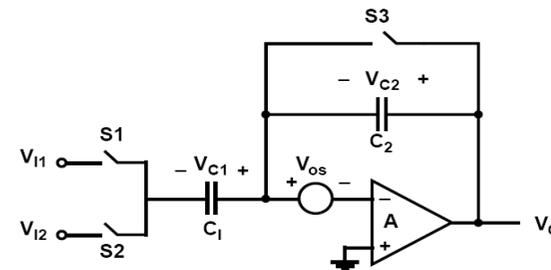

SAMPLE $S_1 = S_3 = 1, S_2 = 0$
 $V_{C1} = V_{os} - V_{I1}$
 $V_{C2} = 0$
 $V_O = V_{os}$

44

SUBTRACT & AMPLIFY

$$S_1 = S_3 = 0, \quad S_2 = 1$$

$$V_{C1} = V_{os} - V_{I2}$$

$$\Delta V_{C1} = (V_{os2} - V_{I2}) - (V_{os} - V_{I1}) = V_{I1} - V_{I2}$$

$$\Delta V_{C2} = \left(\frac{C_1}{C_2}\right)\Delta V_{C1} = \left(\frac{C_1}{C_2}\right)(V_{I1} - V_{I2})$$

$$V_O = \left(\frac{C_1}{C_2}\right)(V_{I1} - V_{I2}) + V_{os}$$

45

AMPLIFY

$$S_1 = S_3 = S_5 = 0, \quad S_2 = S_4 = 1$$

$$V_{C1} = V_{os} - V_{I2} \Rightarrow \Delta V_{C1} = V_{I1} - V_{I2}$$

$$V_{C2} = V_{os} - V_{I4} \Rightarrow \Delta V_{C2} = V_{I3} - V_{I4}$$


$$\Delta Q_1 = \Delta Q_1 + \Delta Q_2 = C_1 \Delta V_{C1} + C_2 \Delta V_{C2}$$

$$\Delta V_{C3} = \frac{\Delta Q_3}{C_3} = \left(\frac{C_1}{C_3}\right)(V_{I1} - V_{I2}) + \left(\frac{C_2}{C_3}\right)(V_{I3} - V_{I4})$$

$$V_O = \left(\frac{C_1}{C_3}\right)(V_{I1} - V_{I2}) + \left(\frac{C_2}{C_3}\right)(V_{I3} - V_{I4}) + V_{os}$$

47

SUMMING AMPLIFIER

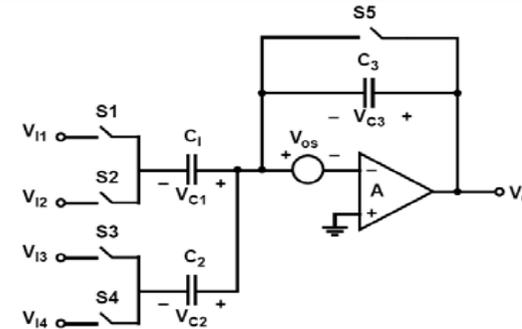

SAMPLE $S_1 = S_3 = S_5 = 1, S_2 = S_4 = 0$
 $V_{C1} = V_{os} - V_{I1}, V_{C2} = V_{os} - V_{I3}, V_{C3} = 0$
 $V_O = V_{os}$

46

System Considerations

- Introduction
- Spectra of Sampled Signals
- Prefiltering
- Postfiltering
- Oversampling Approach
- Conventional Switched-Capacitor Approach
- Examples

48


Filters

- Continuous-time filter
 - RLC passive
 - Active RC
- Sampled-Data filter
 - Switched-Capacitor filter
- Digital filter

49

Switched-Capacitor Filter

- Basic concept

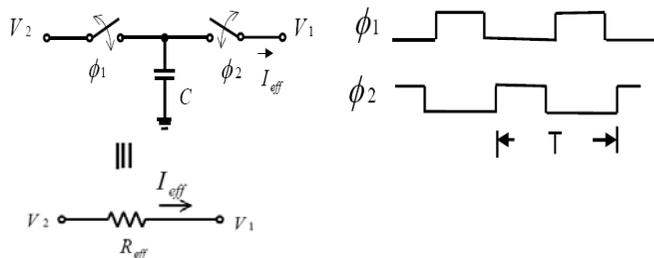


$$\Delta Q = C(V_2 - V_1) \Rightarrow I_{eff} = \frac{\Delta Q}{T} = \frac{V_2 - V_1}{R_{eff}} \Rightarrow R_{eff} = T/C$$

51


Continuous-Time Filters

Example: 1 pole low pass filter

- passive

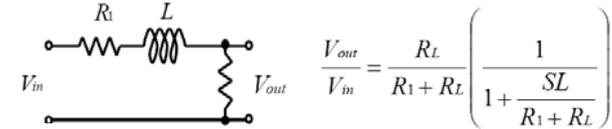

- active

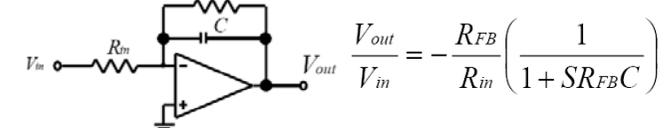

- Equivalence conditions:

$$R_m = R_1, \quad R_{FB} = \frac{R_1 R_L}{R_1 + R_L}, \quad C = \frac{L}{R_1 R_L} \quad 50$$

SCF (Cont.)


- Example: SC integrator

$$V_{out}(n) - V_{out}(n-1) = -\frac{C_S}{C_I} V_{in}(n-1)$$

$$\Rightarrow V_{out}(n) = V_{out}(n-1) - \frac{C_S}{C_I} V_{in}(n-1)$$

$$\Rightarrow V_{out}(z) = z^{-1} V_{out}(z) - \frac{C_S}{C_I} z^{-1} V_{in}(z)$$
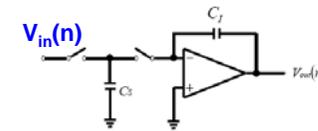
$$\Rightarrow H(z) = \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C_S}{C_I} \frac{z^{-1}}{1 - z^{-1}} \quad \text{where } z = e^{j\omega T}$$





- If $\omega T \ll 1$

$$\lim_{\omega T \ll 1} [e^{j\omega T}] = -\frac{C_S}{C_I} \frac{e^{-j\omega T}}{1 - e^{-j\omega T}} = -\frac{C_S}{C_I} \frac{1 - ST + \frac{(ST)^2}{2} - \dots}{ST - \frac{(ST)^2}{2} + \dots}$$

$$\approx -\frac{C_S}{C_I} \frac{1}{ST} = -\frac{1}{S \left(\frac{T}{C_S} \right) C_I} = -\frac{1}{SR_{eff} C_I}$$


52

Digital Filter

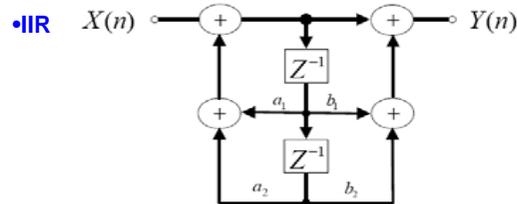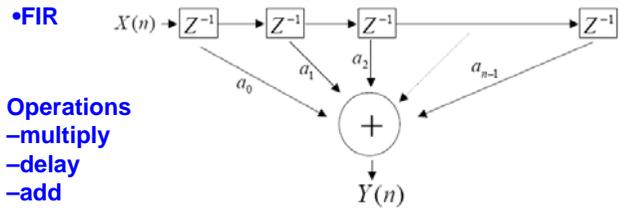

53

Analog Sampling Circuit

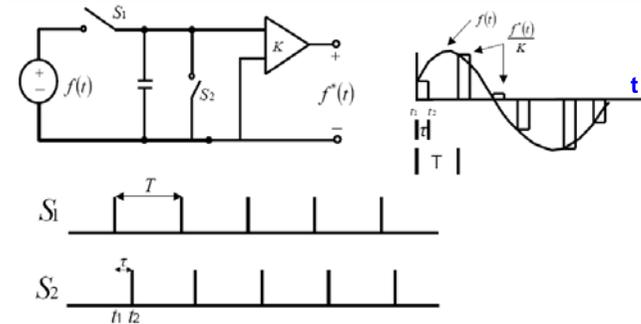

- Original continuous-time signal $f(t)$
- Sampled/Held Signal $f^*(t)$


54

Signal Spectra of Zero-Width Samples

- For $\tau \rightarrow 0$ (zero-width sampling)
 $f(t) \rightarrow F(j\omega)$ original signal
 $f^*(t) \rightarrow F^*(j\omega)$ sampled-data signal

• Spectrum of Sampled Signal
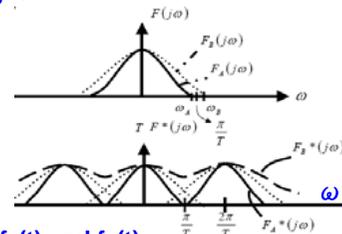
$$F^*(j\omega) = \frac{1}{T} \sum_{k=-\infty}^{\infty} F\left(j\omega - jk\frac{2\pi}{T}\right)$$



- Continuous-time signals $f_A(t)$ and $f_B(t)$
- Sampled-Data signals $f_A^*(t)$ and $f_B^*(t)$

55

Nyquist Theorem

- There is a one-to-one relation between values

$$F_{\frac{A}{B}}(j\omega) \text{ and } F_{\frac{A}{B}}^*(j\omega)$$

- Replicas forming $F_B(j\omega)$ overlap (This phenomenon is called aliasing or folding. It is a nonlinear distortion.)

- Low-pass Filter

$$F_A^*(j\omega)H(j\omega) = F_A(j\omega) \quad \text{where } H(j\omega) = \begin{cases} 1 & ; \left| \omega \leq \frac{\pi}{T} \right| \\ 0 & ; \left| \omega > \frac{\pi}{T} \right| \end{cases}$$

- ⇒ The continuous-time signal $f_A(t)$ is recovered.
 But no such operation can regain $F_B(j\omega)$ from $F_B^*(j\omega)$
- Nyquist first observed this phenomenon
 ⇒ Nyquist Theorem

56

Signal Spectra of S/H Samples


- Assume $\tau = T$ (Nonzero-width sampling)

$$F_{SH}(j\omega) = H_{SH}(j\omega)F^*(j\omega)$$

Where $F^*(j\omega)$ is the spectra of zero-width sample (refer to the second previous page)

$$H_{SH}(j\omega) = \frac{1 - e^{-j\omega T}}{j\omega} = T e^{-\frac{j\omega T}{2}} \left(\frac{\sin \frac{\omega T}{2}}{\frac{\omega T}{2}} \right)$$

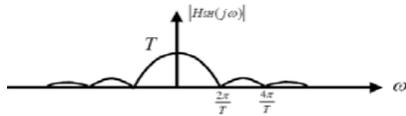$\Rightarrow H_{SH}(j\omega)$ has a linear phase. Its amplitude has SinX/X response which is characteristic of S/H signal spectra




57

S/H Effect

$$F_{SH}(j\omega) = H_{SH}(j\omega)F^*(j\omega)$$

$F^*(j\omega)$ is formed by replicas of $F(j\omega)$

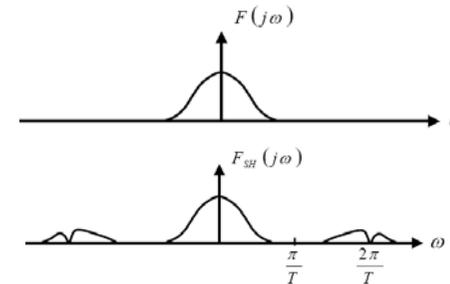$F(j\omega)$ is replicated and multiplied by the SinX/X response.



58

S/H Effect (Cont.)

- We look at the frequency response that occurs when we change a discrete-time signal back into an analog signal with the use of a sample-and-hold circuit. Note that here we plot a frequency response for all frequencies (as opposed to only up to $f_s/2$) since the output signal is continuous-time signal rather than a discrete-time one.
- A sample-and-hold signal, $x_{sh}(t)$, is related to its sampled signal by the mathematical relationship.

$$x_{sh}(t) = \sum_{n=-\infty}^{\infty} x_c(nT) [\mathcal{G}(t - nT) - \mathcal{G}(t - nT - T)] \quad (9.37)$$


Note that, once again, $X_{SH}(s)$ is well defined for all time, and thus the Laplace transform can be found to be equal to

$$X_{sh}(s) = \frac{1 - e^{-sT}}{s} \sum_{n=-\infty}^{\infty} x_c(nT) e^{-snT} = \frac{1 - e^{-sT}}{s} X_s(s) \quad (9.38) \quad 59$$

S/H Effect (Cont.)

- This result implies that the hold transfer function, $H_{sh}(s)$, is equal to

$$H_{sh}(s) = \frac{1 - e^{-sT}}{s}$$

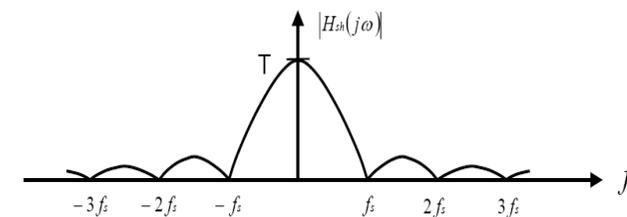

Sample-and-hold response (also called the sinc response).

60

S/H Effect (Cont.)

- It should be mentioned here that this transfer function usually referred to as the sample-and-hold response although, in fact it only accounts for the hold portion.
- The spectrum for $H_{sh}(s)$ is found by substituting, $s = j\omega$ into (9.39) resulting in

$$H_{sh}(j\omega) = \frac{1 - e^{-j\omega T}}{j\omega} = T \times e^{-j\omega T/2} \times \frac{\sin(\omega T/2)}{\omega T/2} \quad (9.40)$$

61

Sampled-Data System with Continuous-time Input & Output Signals

- The distortion due to $H_{SH}(j\omega)$ is linear as opposed to the nonlinear distortion which aliasing introduces.
- $F(j\omega)$ can be recovered from $F_{SH}(j\omega)$ by two steps
 1. Low-pass filter
 2. Amplitude equalizer with a transfer function

$$H_{EQ}(j\omega) = \frac{1}{H_{SH}(j\omega)}$$

63

S/H Effect (Cont.)

- The magnitude of this response is given by

$$|H_{sh}(j\omega)| = T \frac{|\sin(\omega T/2)|}{|\omega T/2|}$$


or

$$|H_{sh}(f)| = T \frac{|\sin(\pi f/f_s)|}{|(\pi f)/f_s|}$$

and is often referred to as the $(\sin x)/x$ or sinc response. This magnitude response is illustrated in Fig . 11-13 .

62

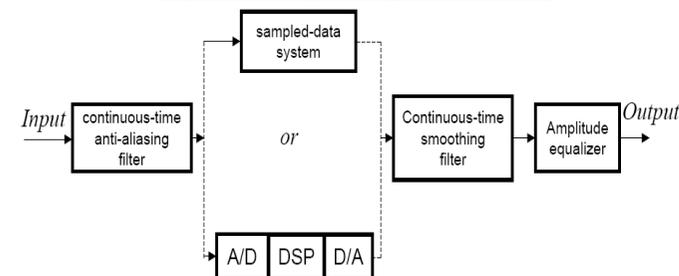Sampled-Data System with Continuous-time Input & Output Signals (Cont.)



- The anti-aliasing and smoothing filters can be identical lowpass filters, and should ideally have sharp cutoff frequency (except oversampling rate signal processing where Decimation and interpolation are used) .

64

Prefiltering

- Nyquist rate
 - prefilter = anti-alias filter (AAF)
 - Brick wall AAF
- Oversampling rate
 - prefilter = anti-alias filter + Decimation filter
 - (AAF) (DF)

AAF : continuous-time filter


DF : SCF or Digital filter

- usually < 60 dB or 10 bit
- small size
- usually used for resolution > 60 dB or 10 bit
- large size


65

Prefiltering (Cont.)

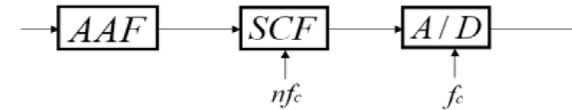- Examples: (For Data Acquisition)
 - conventional Nyquist-rate A/D converter




- oversampling A/D converter

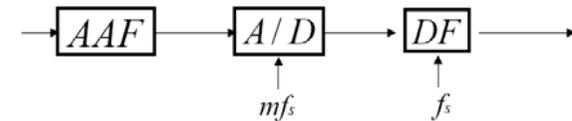

66

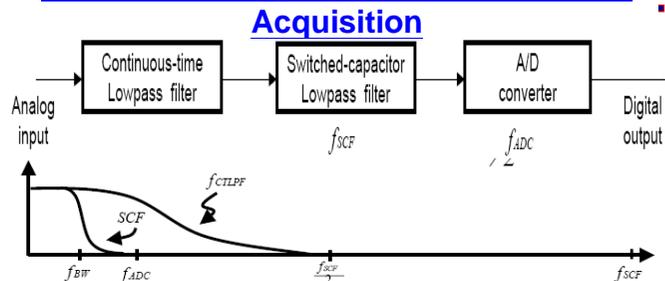
Prefilter Strategy for Conventional Data Acquisition



- Since $f_{SCF} \gg f_{ADC} \Rightarrow$ decimation occurs without aliasing effect since SCF performs decimation and A/D conversion.
- Hence, ADC performs decimation and A/D conversion.
- Sometimes, SCF instead of ADC performs filtering and decimation. For either way, control clocks had better be synchronized.


67

Conventional Postfiltering

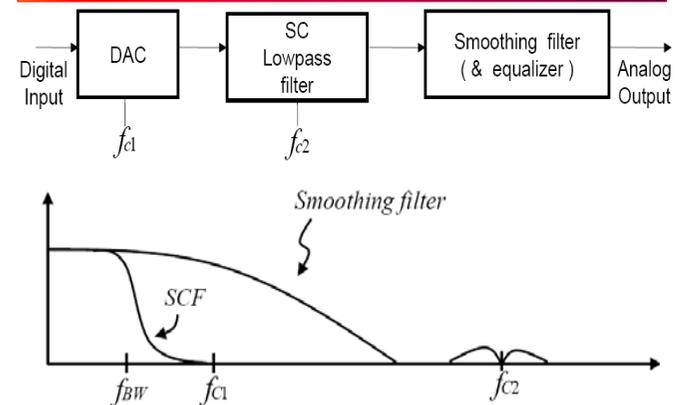


68

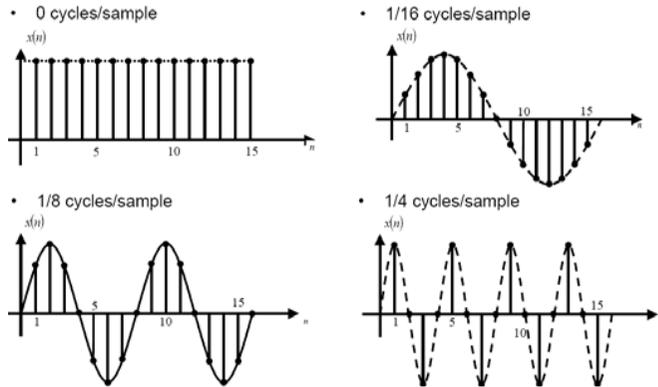Some discrete-time sinusoidal signals with different sampling rates



69

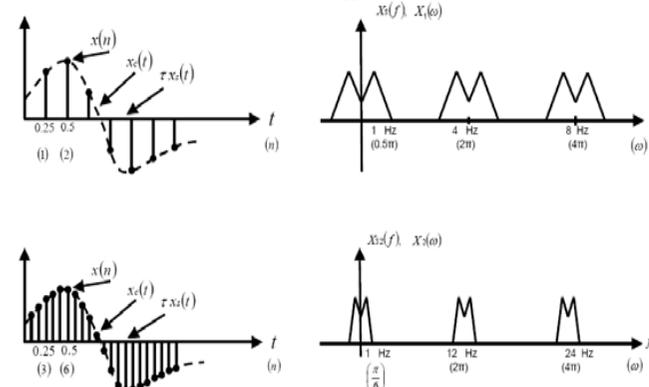Comparison time and frequency of two sampling rates



70


Use of Oversampling Approach to Relax Requirements of Prefilter and Postfilter

- **Front End**
 - Use oversampling A/D converter
 - Use decimation after A/D conversion
- **Back End**
 - Use interpolation before D/A conversion
 - Use oversampling D/A converter

71


Use of Oversampling Approach to Relax Requirements of Prefilter and Postfilter (Cont.)

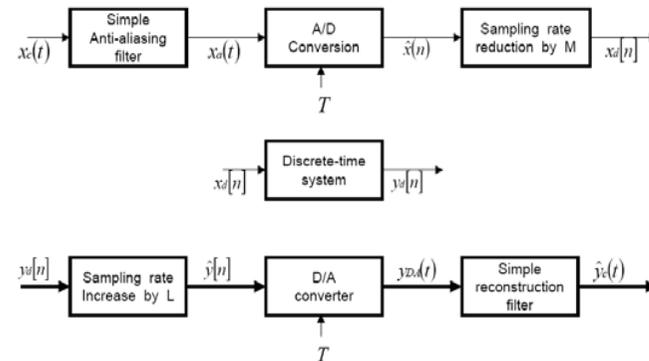• Example: Block diagram of a signal processing system




72

Use of Decimation in A/D Conversion

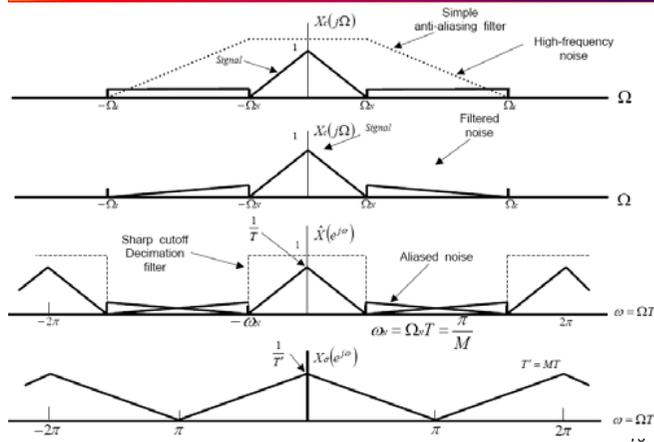


Use of Interpolation in D/A conversion

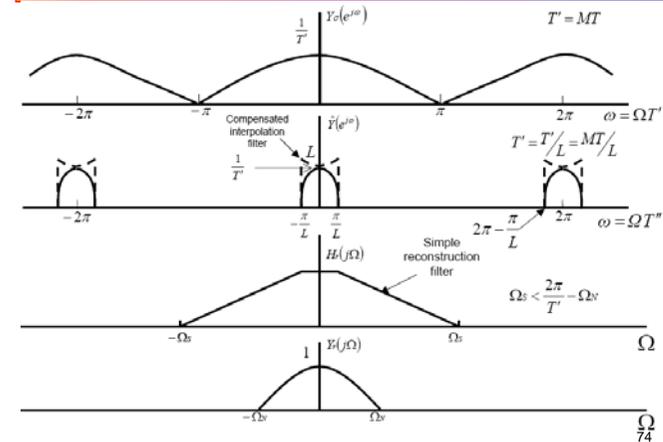


Decimation

• Lowpass filtering + downsampling

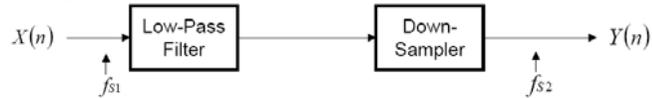

• Downsampling (by 4)

– time-domain

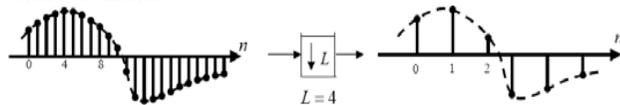


– frequency domain



Decimation (Cont.)

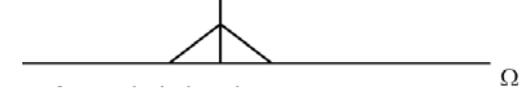
(a) spectrum of original continuous-time signal



(b) spectrum of sampled signal




(c) spectrum after decimation

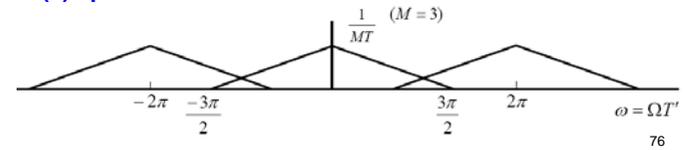


Decimation (Cont.)


(d) Low-pass filtering

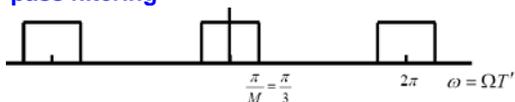

(e) Spectrum after filtering

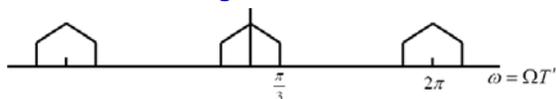

(f) Spectrum after decimation

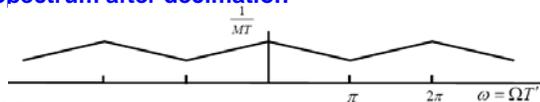


-(a)-(c) Downsampling with aliasing.

-(d)-(f) Downsampling with prefiltering to avoid aliasing.

Interpolation


• Upsampling + lowpass filtering

-time-domain

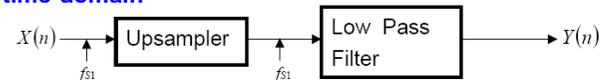


• Upsampling (by 4)

- time-domain

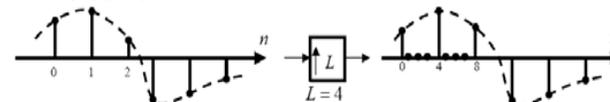

- Frequency-domain

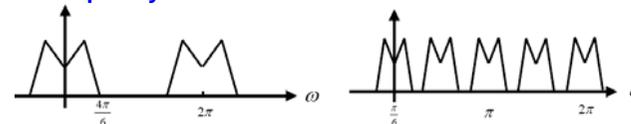


Interpolation (Cont.)


• Baseband signal (Analog)



• Original signal (Digital)

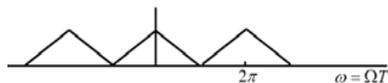


• upsampling

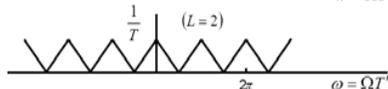

• Low-pass filtering



• Spectrum after filtering

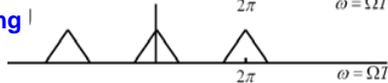

79

Decimate-By-N Filter

• Example: with sincfunction



Input rate f_c

Output rate $f_c/N = f_d$

$$Y(n) = 1/N [x(Nn) + x(Nn-1) + x(Nn-2) + \dots + x(Nn-N+1)]$$

$$Y(z) = \frac{x(z)}{N} \sum_{i=0}^{N-1} z^{-i} = \frac{x(z)}{N} \left[\frac{1-z^{-N}}{1-z^{-1}} \right]$$

80


Decimate-By-N Filter (Cont.)

•Gain of sinc filter

$$\frac{1}{N} \left| \frac{1-z^{-N}}{1-z^{-1}} \right| = \frac{1}{N} \left| \frac{\sin \frac{N\omega\tau}{2}}{\sin \frac{\omega\tau}{2}} \right| ; z = e^{j\omega\tau} \text{ and } \tau = \frac{1}{f_c}$$


$$= \left| \frac{\text{sinc} \frac{N\omega\tau}{2}}{\text{sinc} \frac{\omega\tau}{2}} \right| ; \text{sinc} X = \frac{\sin X}{X}$$

•Example: N=6

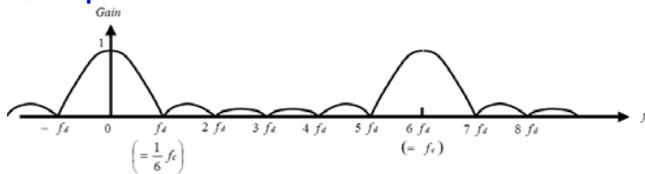

81


Digital Decimator with Sinc Filtering

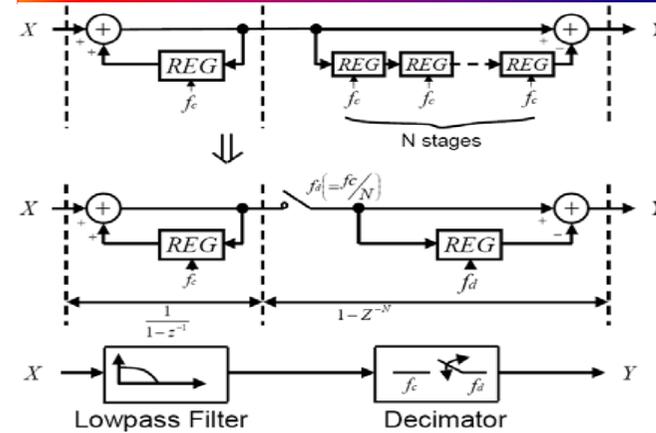

82

SC Sampling Stage Without Decimation

•Example: Integrator

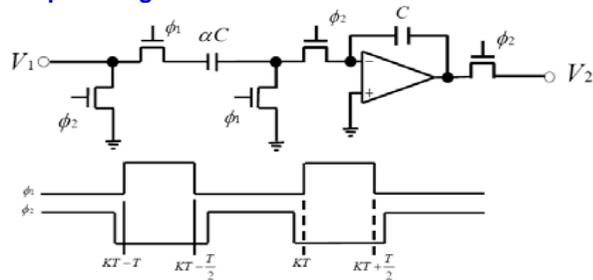


$$V_2(kT) - V_2(kT - T) = \alpha V_1 \left(kT - \frac{T}{2} \right)$$

$$H(z) = \frac{V_2(z)}{V_1(z)} = \frac{\alpha z^{\frac{1}{2}}}{1 - z^{-1}}$$

83

SC Sampling Stage With Decimation

•Example: Modified Integrator

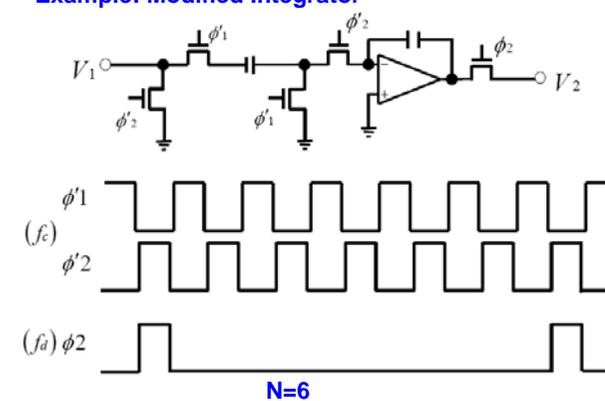

84


SC Sampling Stage With Decimation (Cont.)

$$H(z) = H_I(z)H_D(z)$$

where $H_D(z)$ is a sinc transfer function

$$|H_D(e^{j\omega\tau})| = \left| \frac{\sin \frac{N\omega\tau}{2}}{\frac{\omega\tau}{2}} \right| ; \tau = \frac{1}{f_c} = T$$



•Example : N=6

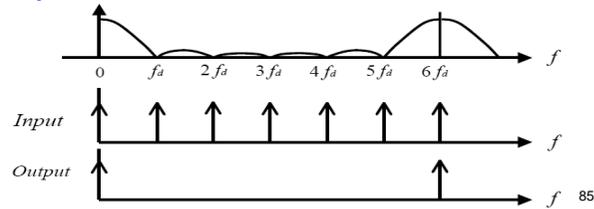

85

Interpolation Filter

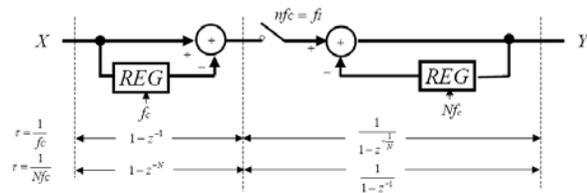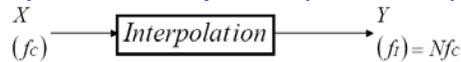•Example: Linear Interpolation (sincfunction)




$$H(z) = \frac{1-z^{-N}}{1-z^{-1}} ; H(z) = \frac{1}{N} \frac{\sin \frac{N\omega\tau}{2}}{\sin \frac{\omega\tau}{2}} ; \tau = \frac{1}{f_i}$$

87

Cosine Filter


N = 2

$$|H_I(e^{j\omega\tau})| = \left| \frac{\sin \omega\tau}{\sin \frac{\omega\tau}{2}} \right| ; \tau = \frac{1}{f_c}$$

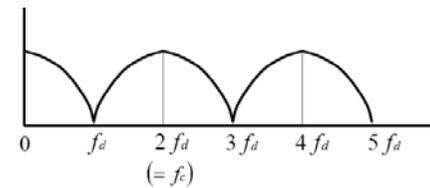

86

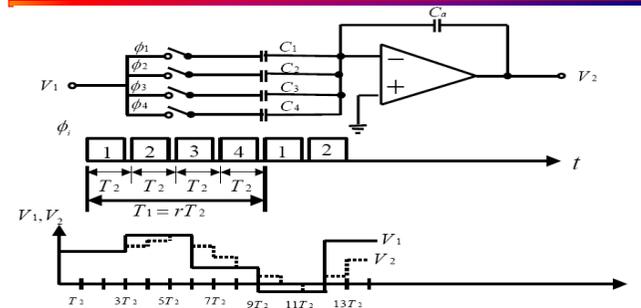SC Sampling Stage With Linear Interpolation




$$V_2(nT_2) - V_2(nT_2 - T_2) = \frac{1}{N} [V_2(nT_2) - V_2(nT_2 - NT_2)] \quad H(z) = \frac{V_2(z)}{V_1(z)} = \frac{1}{N} \frac{1-z^{-N}}{1-z^{-1}} = \frac{1}{N} \sum_{k=0}^{N-1} z^{-k}$$

$$|H_I(e^{j\omega\tau})| = \frac{1}{N} \left| \frac{\sin \frac{N\omega\tau}{2}}{\sin \frac{\omega\tau}{2}} \right| ; \tau = \frac{1}{f} = T_2$$

88

Sinc Filtering Function


- Not ideal lowpass
- FIR

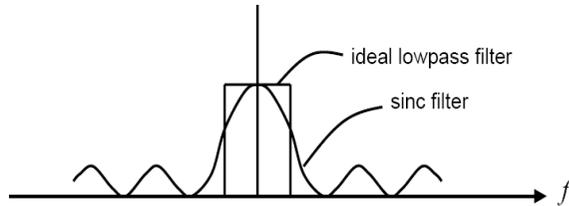

- To implement ideal lowpass function, other approaches can be used.

89

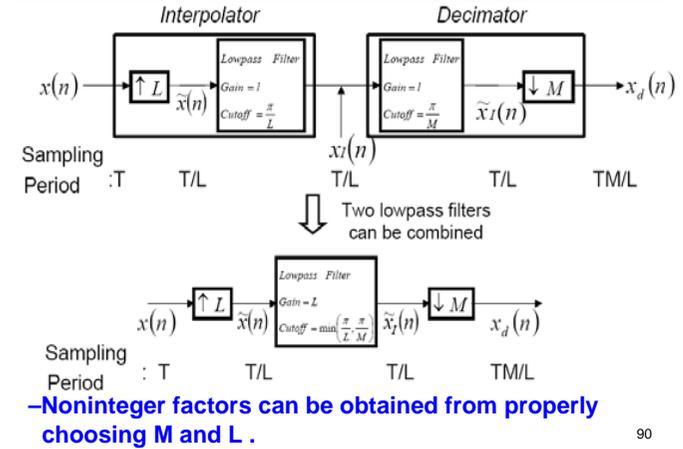Changing The Sampling Rate By A Noninteger Factor




- Noninteger factors can be obtained from properly choosing M and L .


90

Examples

- Talking Back

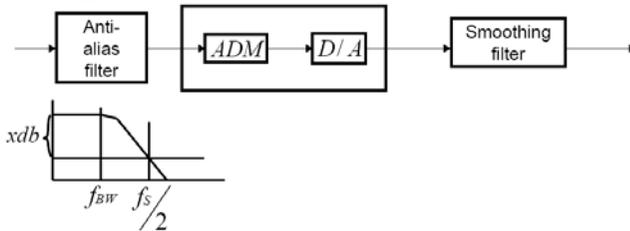

- Speech Reconstruction

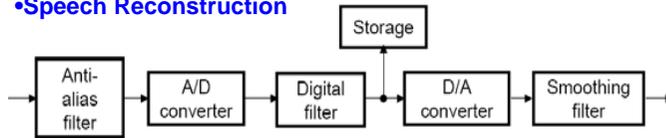

91

Examples (Cont.)

- Approach 1: better LPF can be used other than sinc one

continuous-time + oversampling + digital + DAC + SMF
 AAF ADC Decimator and LPF

- oversampling ADC and digital decimator may be combined

- Approach 2:

continuous-time + SCF + conventional + digital + DAC + SMF
 AAF ADC (Nyquist rate) Decimator and LPF

No cost factor is considered.

92

Ex14_SamplingandHold

1. A basic track and hold circuit is shown in the following figure. It consists of an NMOS switch S1 and a hold capacitance, C_H . Assume $V_{DD}=3.3V$ and that the substrate is tied to $V_{SS}=0V$. Also assume the input signal V_i has a full scale range from 0 to 2V. You are to model the transistors using the Level 1 model and assume that $T = 25^\circ C$. Ignore any parasitic capacitances in your calculation unless otherwise mentioned.


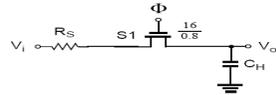


Fig. 1

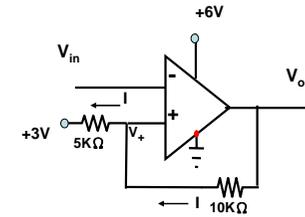- (a) Consider the case when the voltage clock signal goes high to initiate the tracking phase. The holding capacitor C_H starts charging through R_S and the NMOS switch. What is the minimum value of the sampling capacitor so that the rms noise contribution of the MOS switch becomes less than $1/4LSB$ after sampling, if this circuit is used in a 14-bit A/D converter?
- (b) The finite bandwidth of the track and hold circuit introduces a minimum acquisition time for the voltage at the output to track the voltage at the input to within a given accuracy ($1/2$ LSB of the resolution envisioned). If the clock has a 50% duty cycle, calculate the maximum frequency at which a steady input can be sampled to within 14 bits of resolution at the end of the tracking phase. In your calculations, use the worst-case value of the MOS switch "on" resistance, i.e., the value that would result in the slowest response. Assume $C_H=5pF$ and $R_s=50\Omega$.



2. For the op-amp in the circuit, $A_v=200000$, assume $V_{out} = 6V$ if $V_+ > V_-$, $V_{out} = 0V$, if $V_+ < V_-$, and the currents into the + and - inputs are negligible.
- (a) When $V_{in} = 0V$, $V_{out} = 6V$, find $V_+ = ?$
- (b) Find the values of V_{in} for which the output high-to-low (V_d) and low-to-high (V_u) transitions occur.
- (c) Make a graph of V_{out} vs. V_{in} for $0 \leq V_{in} \leq 6V$ indicating the transition voltage V_d and V_u . How would you classify this circuit (i.e. does it have a name) ?



94