

**EDN MOMENT**  
Mother of  
COBOL Grace  
Murray Hopper  
is born.



Solve the unique challenges of your smart end-products  
with Infineon's innovative offerings.

FIND OUT MORE >



DESIGN CENTERS

TOOLS & LEARNING

COMMUNITY

EDN VAULT

About Us

Sign In | Sign Up

Home > Analog Design Center > Design Idea

## Cancel PWM DAC ripple with analog subtraction

Stephen Woodward -November 28, 2017

19 Comments

Share

11

G+

Tweet

Like 13

Every PWM DAC design needs analog filtering to separate the desired PWM duty-cycle-proportional DC component from unwanted AC ripple. The simplest of these is the basic RC low-pass filter, which gives a peak-to-peak ripple amplitude (for the worst case of 50% PWM duty cycle, where  $T_{PWM}$  = PWM cycle time, and assuming  $RC > T_{PWM}$ ) of:


$$V_{ripple} / V_{fullscale} = T_{PWM} / 4 \cdot RC$$

The obvious design tradeoff is that while any desired degree of ripple attenuation can be achieved by choosing a large enough RC product, settling time will correspondingly suffer. For example, if we (fairly logically) choose a definition for the settling band as equal to ripple amplitude, then...

$$T_{settle} = RC \cdot \ln(V_{fullscale} / V_{ripple})$$

$$= T_{PWM} \cdot V_{fullscale} \cdot \ln(V_{fullscale} / V_{ripple}) / (4 \cdot V_{ripple})$$

ADVERTISING

 


The consequences of this relationship can be illustrated by the 8-bit case:

$$\text{Given: } V_{ripple} / V_{fullscale} = 1/256; RC = 64 \cdot T_{PWM}$$



$$T_{\text{settle}} = 64 \cdot \ln(256) \cdot T_{\text{PWM}} = 355 \cdot T_{\text{PWM}}$$

which, even for a fairly speedy 32 kHz ( $31\mu\text{s } T_{\text{PWM}}$ ), predicts a positively *glacial* 11ms settling time.

 Clearly, if settling time is a critical design parameter, we'll need to do better and find a less simplistic filtering scheme. The extreme possibilities that lie in this direction are illustrated by my previous DI, [Fast-settling synchronous-PWM-DAC filter has almost no ripple](#).



But not every application that can't tolerate molasses-in-January  $355 \cdot T_{\text{PWM}}$  settling times need or can justify such a complex filtering solution. The **Design Idea** presented here addresses these middle-of-the-road applications. As shown in **Figure 1**, it augments the basic R1/C1 low-pass with an inverter, R2, and C2, which combine to negate and subtract (most of) the undesired AC component from the wanted DC signal, leaving a relatively clean analog output with settling time much less than a simple RC filter.

  

**Figure 1** Waveforms & schematic of PWM DAC ripple canceller

But how pure is “relatively clean”, and how fast is “much less”? Setting  $R2=R1$  and  $C2=C1$ , the ripple and settling time figures for the new circuit are:

$$V_{\text{ripple}} / V_{\text{fullscale}} = (T_{\text{PWM}} / 4 \cdot RC)^2$$

$$T_{\text{settle}} = T_{\text{PWM}} \cdot \ln(V_{\text{fullscale}} / V_{\text{ripple}}) \cdot (V_{\text{fullscale}} / 16 \cdot V_{\text{ripple}})^{1/2}$$

Referring again to the 8-bit case (illustrated graphically in Figure 1):

$$\text{Given: } RC = 4 \cdot T_{\text{PWM}}$$

$$T_{\text{settle}} = 22 \cdot T_{\text{PWM}} = 0.69 \text{ ms}$$

READ MORE  
designideas

with a 32 kHz cycle, it's 16 times faster, with a squared ripple-amplitude ratio!

For many applications, this represents a very worthwhile tradeoff between a modest increase in circuit complexity and a significant increase in PWM DAC performance.

—*W. Stephen Woodward* is one of EDN's most prolific and innovative Design Ideas authors, with dozens of contributions to his credit.

#### Related articles:

- [Fast-settling synchronous-PWM-DAC filter has almost no ripple](#)
- [A faster PWM-based DAC](#)
- [Hybrid PWM/R2R DAC improves on both](#)
- [Double  \$\mu\$ C's PWM frequency & resolution](#)
- [Circuit maximizes pulse-width-modulated DAC throughput](#)
- [Three paths to a free DAC](#)
- [Ternary DAC: Greater resolution, less bits](#)

---

11

13

---

#### SPONSORED CONTENT

**Fast-track JESD204B-Based Designs for High-Speed Data Acquisition**

Date: Dec., 14th @ 8am PST/11am EST

Sign up for this free webinar to learn:

- The specifics of the Arrow development kit, including the two major components — the Arria 10 GX FPGA development board and AD-FMCDQAQ2-EVK data converter evaluation board
- How to set up the boards that come with the kit, install the firmware, and run the built-in demo
- How to develop high-speed solutions using the kit, including where to go for documentation, firmware downloads, reference designs, and more

Register Now!

Sponsored By Arrow / Analog Devices

#### 19 Comments

Write a Comment

To comment  
please [Log In](#)



ReAIAI

Very interesting, especially for microcontroller with complementary outputs on PWM.

Thanks!

Dec 8, 2017 5:53 AM EST

👍0 | 🗑️0

Reply



Al Grasso

I think the circuit proposed, within the boundary conditions stated in the narrative by the author, is perfect. I would like to add a small suggestion and that is to replace the single term negative integrator with a two-terms op-amp that adds a degree of differentiation to speed-up the time response. In that way it may be possible to match the original rise-time of the ripple and reduce even more the residual.

I am retired now and have no access to a lab else I would love to test it out.

Dec 7, 2017 4:13 PM EST

👍0 | 🗑️0

Reply



rydel0

But well, its a simple solution without opamp's, that's why it will be interesting. But I'm maybe wrong ? We have to Spice it.

Dec 5, 2017 6:33 PM EST

👍0 | 🗑️0

Reply



rydel0

A double T or a Wien bridge will do the same think I guess, eliminating the fondamental...

Dec 5, 2017 6:10 PM EST

👍0 | 🗑️0

Reply



WStephenWoodward

Wien bridge? With or without the traditional lightbulb?

Sorry. Couldn't resist.

Dec 5, 2017 6:37 PM EST

👍0 | 🗑️0

Reply



WStephenWoodward

I agree with both Brian and Dave that there's more than one way to defrock this particular feline. Thanks for your contributions.

However, please note that both your suggestions are not only compatible with each other, but can also be combined with my analog subtraction DI to get the ripple-reducing benefits of any two or all three.

Dec 5, 2017 4:38 PM EST

👍0 | 🗑️0

Reply



Brian park

There is a simpler way! (following explanation is for 8-bit PWM). The secret is to manipulate the order of the (PWM period x  $2^8$ ) so the power output of the "PWM" is pushed higher in frequency. You do this by writing the PWM generator in software (routine in assembly requires 9-10 instructions per iteration and 256 byte table). This requires a 256 byte bit-reverse table. In software, you have 8-bit counter running at PWM frequency x  $2^8$ ). This value is put in index to read from table. This result is bitwise ANDed with 8-bit amplitude. If result is zero, you write zero to port, else write 1. This goes to conventional RC filter, but highest power is at PWM period x 128. (Each bit lower has frequency half, but also power 1/4th the previous). In comment below, some do this in FPGA. Why not put the "rate multiplier" circuit in FPGA?

Dec 5, 2017 3:29 PM EST

👍0 | 🗑️0

Reply



undertalk

But what are the contents of the indexed table? Do you have additional information on this technique? Thanks

Dec 7, 2017 6:27 AM EST

👍0 | 🗑️0

Reply



ReAIAI

Just bit-reversing (one assembly instruction for cortex-M3, no tables).

See "Synchronous 6-Bit Binary Rate Multiplier" internals

<http://www.ti.com/lit/ds/symlink/sn7497.pdf>

Dec 8, 2017 5:48 AM EST

0 | 0

Reply



DaveR1234

You can get the same or better response with a two or three stage RC filter.

Dec 5, 2017 2:13 PM EST

0 | 0

Reply



Mohan.Gurunathan

Hi, you state that the settling time is much less with the ripple cancellation circuit; however in the figure the black curve appears to take longer to settle to the final value, as compared to the curve with the higher ripple. Can you explain? Thanks.

Dec 5, 2017 12:05 PM EST

0 | 0

Reply



WStephenWoodward

The 355T pwm settling time of the case of a single-pole RC filter with 1lsb of ripple isn't graphed. It wouldn't fit!

Dec 5, 2017 12:31 PM EST

0 | 0

Reply



Guillermo Jaquenod

Good solution, even better if PWM is generated by an FPGA, because the inverter can be synthesized into the FPGA and the cost/benefit is increased (only one R and one C to add). Thanks!

Dec 5, 2017 10:02 AM EST

0 | 0

Reply



StuMichaels

So, where's Figure 1? Tried with both Firefox and IE; just a caption. By the comments, there used to be a Figure 1 so where did it go?

Dec 4, 2017 3:50 PM EST

0 | 0

Reply



WStephenWoodward

Good question, Stu! Looks like the EDN web elves decided you could just rely on my oh-so "picturesque" text and your imagination.

Meanwhile, see if this works:  
<http://i68.tinypic.com/2gt9s82.jpg>  
Dec 4, 2017 5:00 PM EST  
0 | 0 Reply

 WStephenWoodward  
Trying again: <https://imgur.com/a/YWvwb>  
Dec 4, 2017 6:07 PM EST  
0 | 0 Reply

 fast3931  
This is one of those, I wish I would have thought of that years ago circuits. I think the more you appreciate this circuit the more years you have spent hours mining for simple elegant solutions to problems you have faced with over your own career, trying to find simple elegant solutions such as this one.  
Dec 3, 2017 2:57 AM EST  
0 | 0 Reply

 Pesky Varmint  
I'm very fond of simple, clever methods like this. Especially since I've had to use analog PWM so often.  
Nov 30, 2017 12:59 PM EST  
0 | 0 Reply

 relaxe  
Thanks! That's a good one.  
Nov 28, 2017 3:00 PM EST  
0 | 0 Reply



Searching for holiday gift ideas for the engineer in your family?  
Arrow.com [SHOP NOW >](#)

**Most Popular** | **Most Commented**

Understanding the basics of setup and hold time

Control an LM317T with a PWM signal

Remembering Jim Williams, 5 years later

Addressing core loss in coupled inductors

AM detector more sensitive than simple diode

Vintage electrical measuring instruments from the 1950s

Simple reverse-polarity-protection circuit has no voltage drop

Air pressure sensors in smartphones: Transforming navigation and fitness tracking

Autonomous cars on various terrains

Sensor conditioning amidst a sea of focus on MEMS and sensors



#### FEATURED RESOURCES

>> **Wide VIN Range Buck-Boost Charge Pump with Watchdog Timer**

>> **ENTER OUR GIVEAWAY - *For a chance to win the Art of Electronics by Paul Horowitz!***

>> **Chip Fuse Protects Against Excessive Temperature & Overcurrent**

>> **Know the Difference Between an Inverter, Converter, Transformer and Rectifier**

>> **Advancing the Art of Parasitic Extraction**

Subscribe to RSS: or

DESIGN CENTERS

MORE EDN

- 5G
- Analog
- Automotive
- Components & Packaging
- Consumer
- DIY
- IC Design
- LEDs
- Medical
- PCB
- Power Management
- Sensors
- Systems Design
- Test & Measurement
- Blogs
- Design Ideas
- Tech Papers
- Courses
- Webinars
- EDN TV
- Events
- About Us

ASPENCORE NETWORK

- EBN
- EDN
- EE Times
- EEWeb
- Electronic Products
- Electronics-Tutorials
- Embedded
- Planet Analog
- ElectroSchematics
- Power Electronics News
- TechOnline
- Datasheets.com
- Embedded Control Europe
- Embedded Know How
- Embedded News
- IOT Design Zone
- Motor Control Design
- Electronics Know How

GLOBAL NETWORK

- EE Times Asia
- EE Times China
- EE Times India
- EE Times Japan
- EE Times Taiwan
- EDN Asia
- EDN China
- EDN Taiwan
- EDN Japan
- ESM China

[Working With Us: About](#) | [Contact Us](#) | [Media Kits](#)

[Terms of Service](#) | [Privacy Statement](#) | Copyright ©2017 AspenCore All Rights Reserved