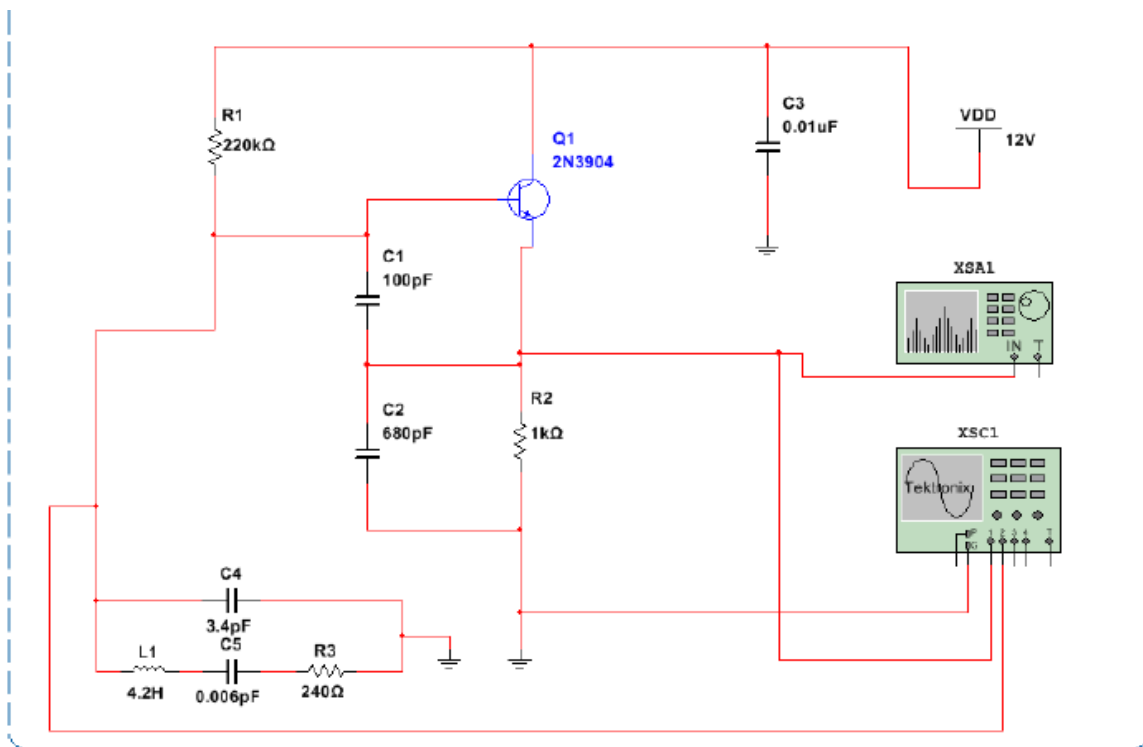



CIRCUIT1 – Crystal Oscillator



XSA1 is spectrum analyser

XSC1 is oscilloscope

CIRCUIT2 – Clapp Oscillator

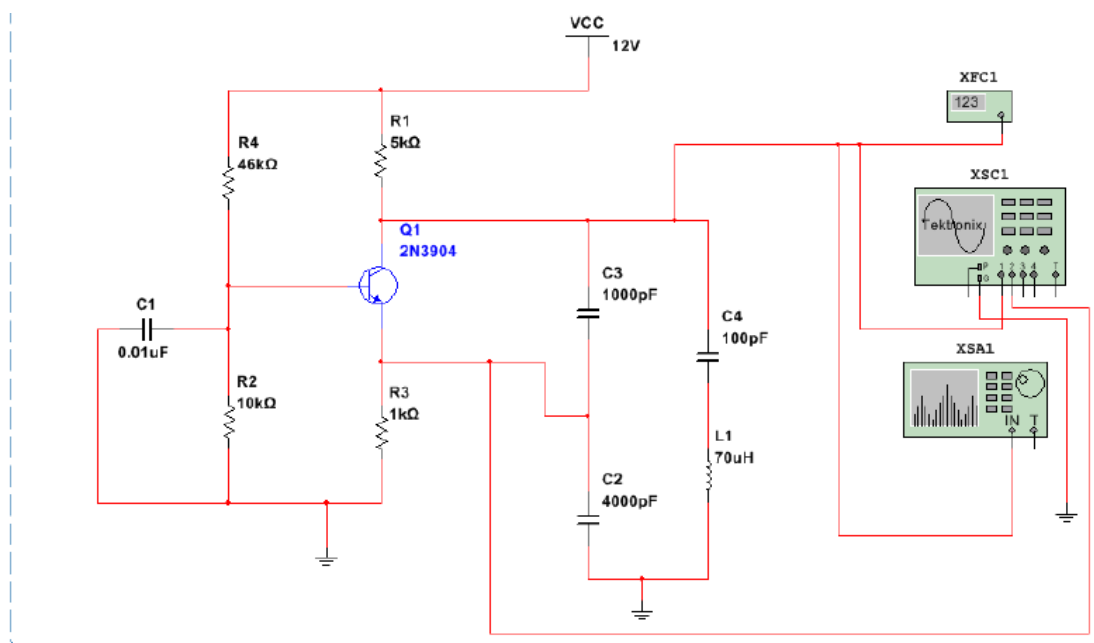

XFC1 is frequency counter

XSA1 is spectrum analyser

XSC1 is oscilloscope

Circuit3 - Phase Detector

