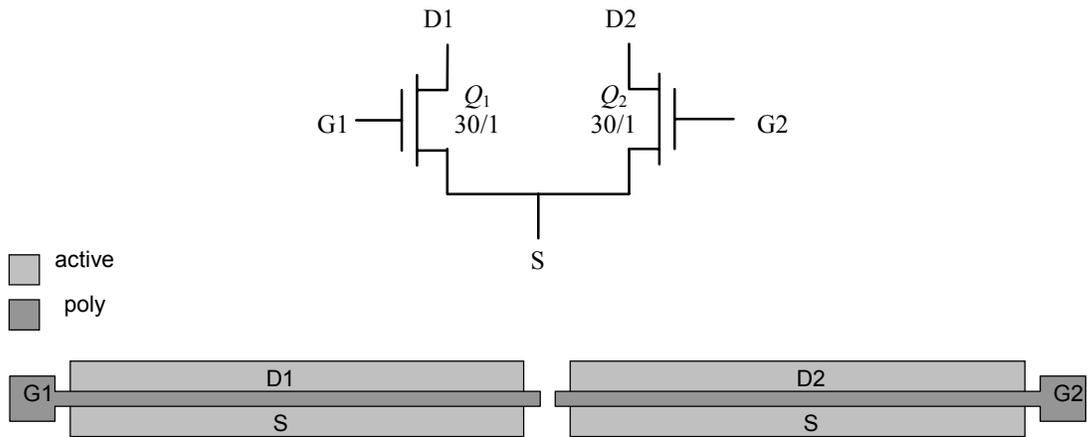



### Basic Differential Pair Layout



Good matching in the absence of cross-chip gradients; both drain currents flow in same direction.


---

### Alternative Differential Pair Layout

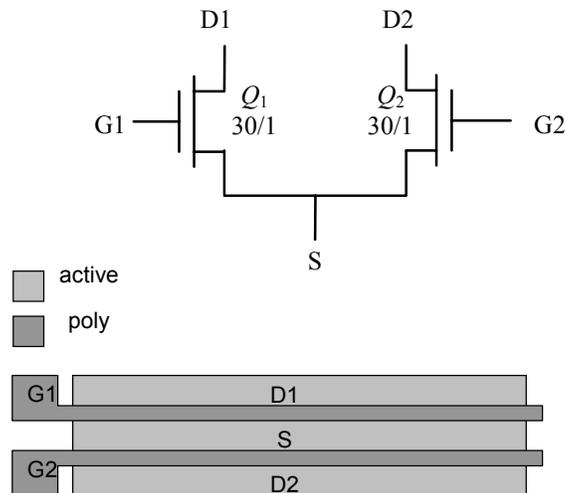


More compact, but worse matching than previous case; drain currents flow in opposite directions.

## Common Centroid Layout

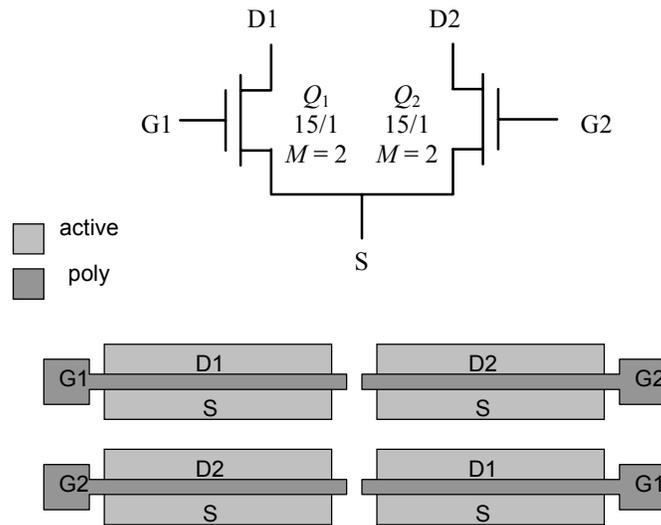


$Q_1$  and  $Q_2$  have a “common centroid”, which makes them immune from cross-chip gradients. Best matching performance possible.

## Alternative Common-Centroid Layout

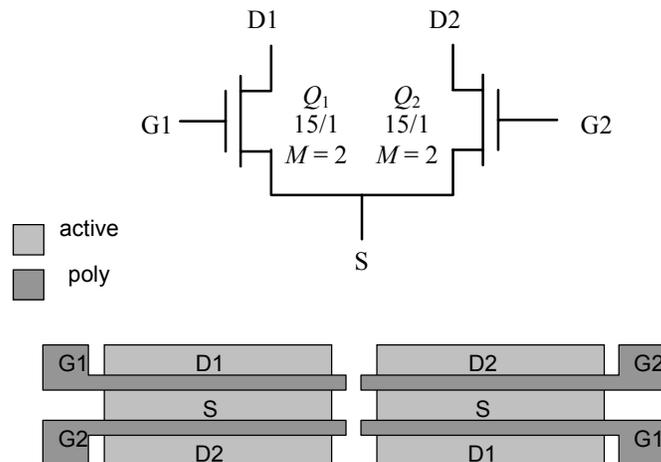

Immune from cross-chip gradients like previous case, but area is saved by sharing sources.

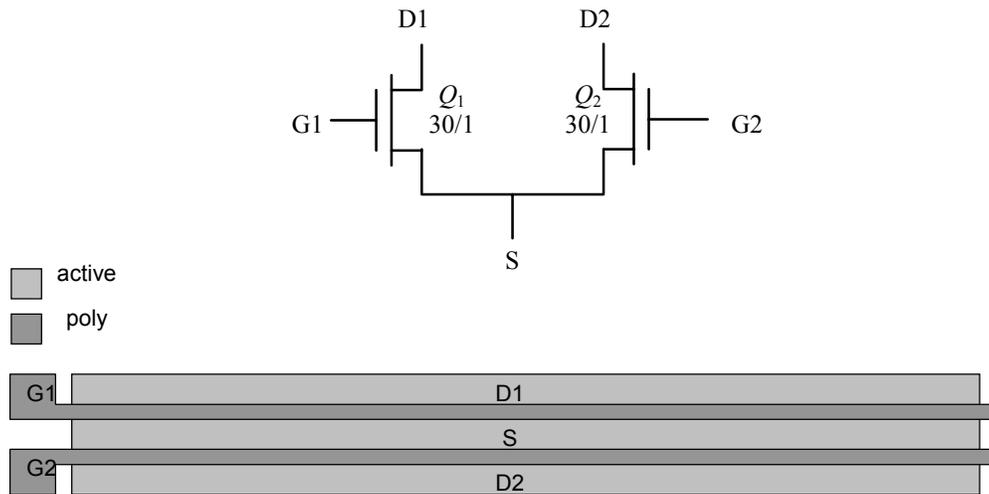
## Differential Pair with Very Wide Transistors



Very wide transistors can lead to awkward layout and significant series gate resistance.


---

## Multi-Finger Transistors

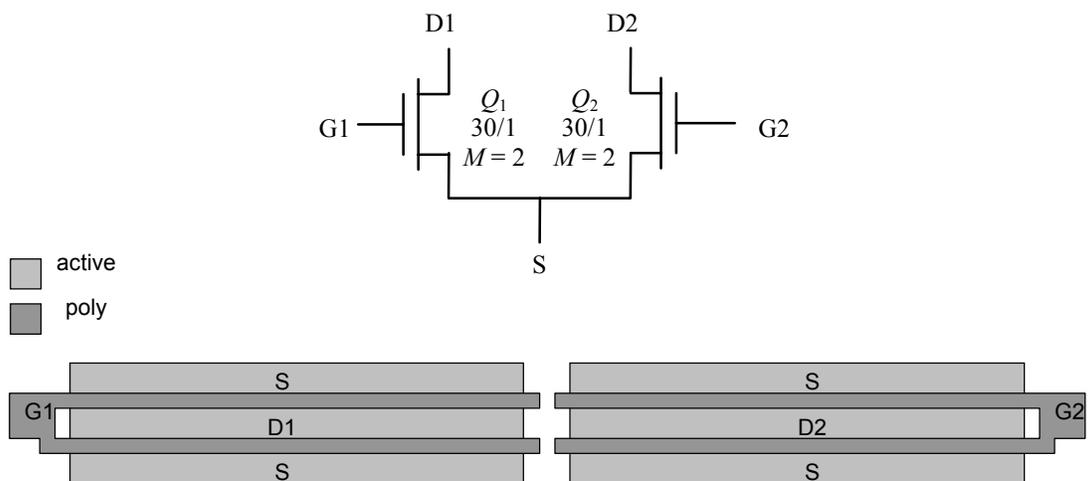


Multi-fingered gates save space and reduce series resistance in gate. Notice that drains are selected to minimize parasitic capacitance to bulk.
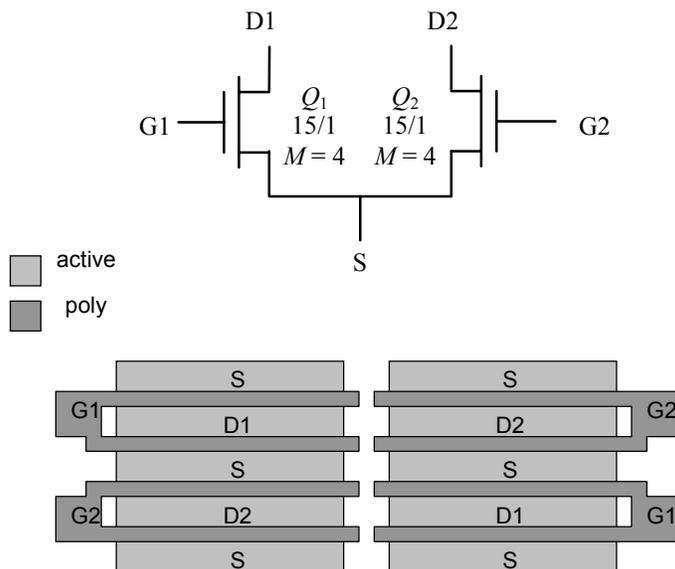
## Common Centroid Layout with Multi-Fingered Gates



Drain-to-bulk parasitic capacitance is minimized; sources are partially shared to save area.

## “Doughnut” Transistors

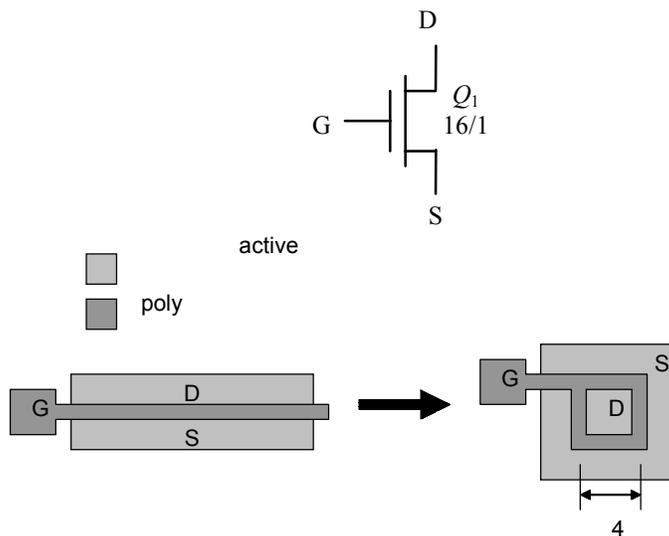

Gives the minimum  $C_{gd}$  (gate-to-drain overlap) and  $C_{db}$  (drain-to-bulk) parasitic capacitances for a given  $W/L$  ratio. May be used to minimize Miller effect when high speed is desired and a dominant pole is created elsewhere.