

Operational Amplifier Stability

Part 4 of 15: Loop-Stability Key Tricks and Rules-of-Thumb

by Tim Green

Strategic Development Engineer, Burr-Brown Products from Texas Instruments

Part 4 of this series focuses on loop-stability key tricks and rules-of-thumb. First we discuss the 45° phase, loop-gain bandwidth rule. The translation between poles and zeros in the A_{ol} plot and $1/\beta$ plots to the loop-gain plot, $A_{ol}\beta$, are reviewed. Frequency “decade rules” are discussed for loop-gain stability and are used for poles and zeros in $1/\beta$, A_{ol} , and $A_{ol}\beta$ plots. We present the magnitude “decade rule” for the op amp input network, Z_I , and the feedback network, Z_F . A technique is developed for plotting dual feedback paths on a $1/\beta$ plot. A special case, the “BIG NOT,” to avoid when using dual-feedback paths is explained and, finally, an easy-to-use real-world stability test is presented. A combination of these key tools allow us, in Part 5 of this series, to methodically and easily stabilize a useful real-world op amp application, with a complex feedback circuit.

Loop-Gain Bandwidth Rule

The established loop stability criterion is less than a 180° phase shift at f_{cl} , the frequency at which loop-gain is zero. How close the phase shift is to a full 180° at f_{cl} is defined as phase margin. The rule-of-thumb recommended (Fig. 4.0) for real-world circuits is to design for 135° phase shift (45° phase margin) throughout the loop-gain bandwidth ($f \leq f_{cl}$) allowing for the real-world cases of power-up, -down and -transient conditions: where the op amp can have changes in its A_{ol} curve which may result in transient oscillations, especially undesirable in power op amp circuits.

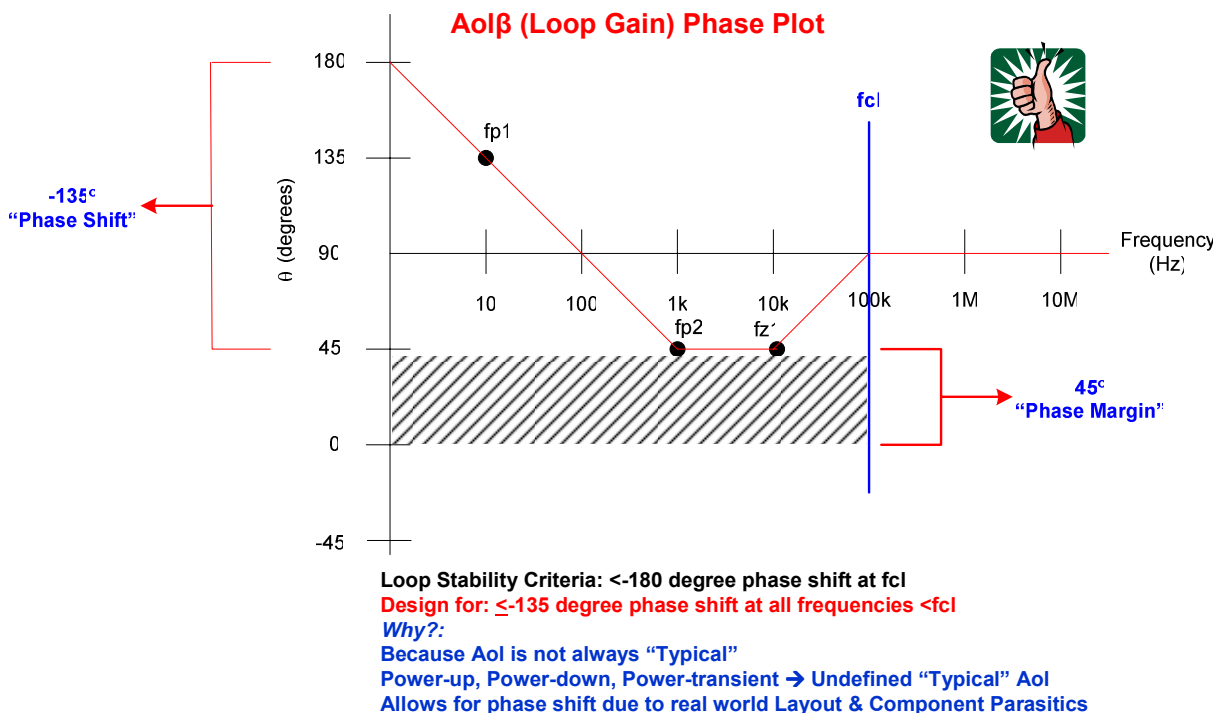


Fig. 4.0: Loop-Gain Bandwidth Rule

This rule-of-thumb also allows for extra phase margin in the loop-gain bandwidth to account for additional real-world phase shifts due to parasitic capacitances and PCB layout parasitics. Also, phase margins less than 45° within the loop-gain bandwidth can result in undesired peaking in the closed-loop transfer function. The lower the phase margin dip, and the closer it is to f_{cl} , the more pronounced the closed-loop peaking will be.

Poles and Zeros Transfer Technique

Fig. 4.1 reminds us of the relationship between the loop-gain plot and the Aol plot, with a $1/\beta$ plot included on it. This relationship allows us to use the manufacturer's Aol curve from an op amp data sheet and plot our feedback curve, $1/\beta$, on it. From these two plots it is easy to infer what is going on in the loop-gain plot and therefore easy to synthesize what we need to modify in our feedback for good stability. Think of the loop-gain plot as a "open-loop" plot. The Aol plot is already an open-loop plot and therefore poles in the Aol plot are poles in the loop-gain plot, and zeros in the Aol are zeros in the loop-gain plot. The $1/\beta$ plot is a plot of small-signal ac closed-loop-gain. If we want to open the loop and look at the effects of the feedback network we will see an inverse relationship as we analyze the network. A simpler way to remember the translation between the $1/\beta$ plot and loop-gain plot is that the loop-gain plot is $Aol\beta$ and the closed-loop feedback plot is $1/\beta$. Therefore, since β is the reciprocal of $1/\beta$ poles in the $1/\beta$ plot will become zeros in the loop-gain ($Aol\beta$) plot and zeros in the $1/\beta$ plot will become poles in the loop-gain plot ($Aol\beta$).

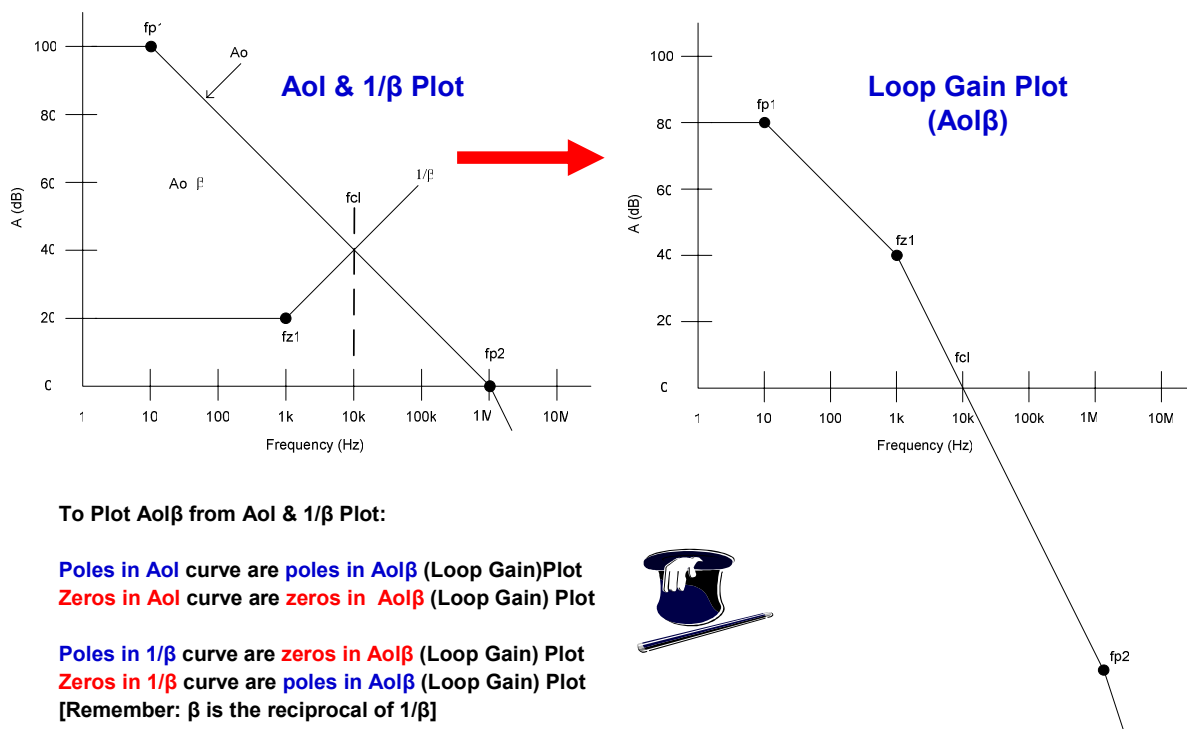


Fig. 4.1: Poles and Zeros Transfer Technique

Frequency Decade Rule

The “decade rules” for frequency in the loop-gain plot are detailed in Fig. 4.2. These frequency-decade rules will be used for $1/\beta$ plots and A_{ol} plots as well as predicting directly the $A_{ol}\beta$, loop-gain plots. For this circuit the A_{ol} curve contains a second pole, $fp2$, around 100 kHz due to the capacitive load, CL , and the op amp’s R_O , the details of which will be presented in Part 6 of this series. We will create a feedback network that will meet our loop-gain bandwidth rule of 45° margin for $f \leq f_{cl}$. We will analyze and synthesize the feedback network using the $1/\beta$ plot and A_{ol} plot with the knowledge of what we are doing to the loop-gain plot, $A_{ol}\beta$. $fp1$ gives us a first pole at 10 Hz in the loop-gain plot which implies -45° phase shift at 10 Hz and -90° at 100 Hz. At 1 kHz, $fz1$, (zero in the $1/\beta$ plot) we add a pole in the loop-gain plot and another -45° phase shift at 1 kHz. Our total phase shift is now -135° at 1 kHz. But if we continue on with just $fz1$ we will reach -180° phase shift at 10 kHz!! So we add $fp3$ (pole in the $1/\beta$ plot) which is a zero in the loop-gain plot at 10 kHz ($+45^\circ$ phase shift at 10 kHz, with a $+45^\circ/\text{decade}$ slope above and below 10 kHz). This keeps the phase shift at 1 kHz to -135° and flattens the phase plot to -135° phase shift from 1 kHz to 10 kHz (remember: poles and zeros have an effect a decade above and below their actual frequency location). $fp2$ adds another pole in the loop-gain plot at 100 kHz since $fp2$ is from the A_{ol} plot. Between 10 kHz, where $fp3$ is, and 100 kHz, where $fp2$ is, we expect no change in phase shift since $fp3$ is a loop-gain plot zero and $fp2$ is a loop-gain plot pole.

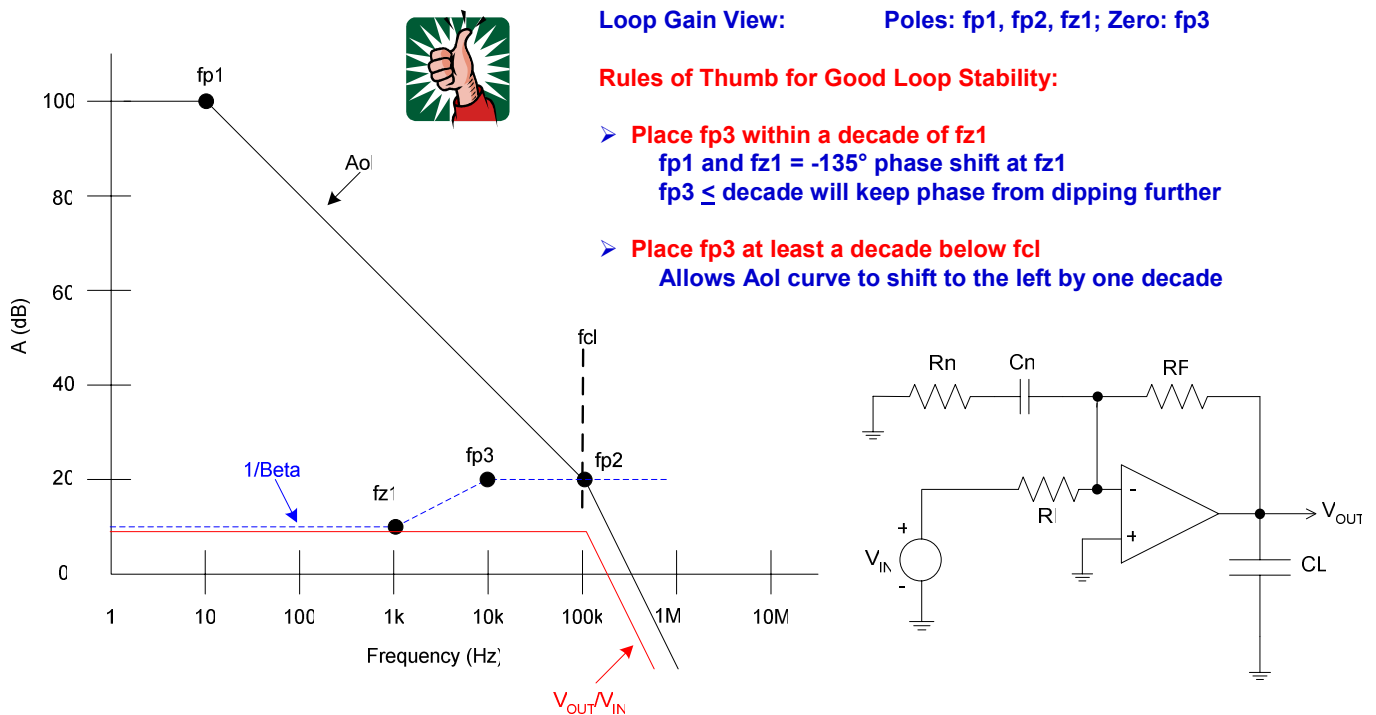


Fig. 4.2: Poles and Zeros Transfer Technique

So if we keep poles and zeros spaced a decade away from each other they will keep the phase shift from dipping between them because of the effect on one another a decade above and below their location. The final key part of the frequency decade rules for loop-gain is to place $fp3$ no closer than a decade away from f_{cl} , allowing for a decade shift in A_{ol} towards the lower frequency range before we would have marginal stability. When pressed for a worst case A_{ol} shift over process and temperature many IC designers will cite a number of 2 to 1 (ie a 1 MHz unity gain bandwidth op amp may have that frequency shift from 500 kHz to 2 MHz). We prefer our decade rule because it is easy to

remember and readily seen on a Bode plot. Extra phase margin design never got anyone in trouble. However, if one is pushed for bandwidth, stability, and performance the 2 to 1 rule is a good fallback.

The V_{OUT}/V_{IN} for this circuit is predicted to be flat until loop-gain goes away at 100kHz, at which point it will then follow the A_{ol} curve downward. Fig. 4.3 shows the first-order hand analysis prediction for the loop-gain phase plot of the circuit described in Fig. 4.2. We add another pole, fp_4 , to our analysis at 1 MHz to simulate a typical real-world two pole op amp.

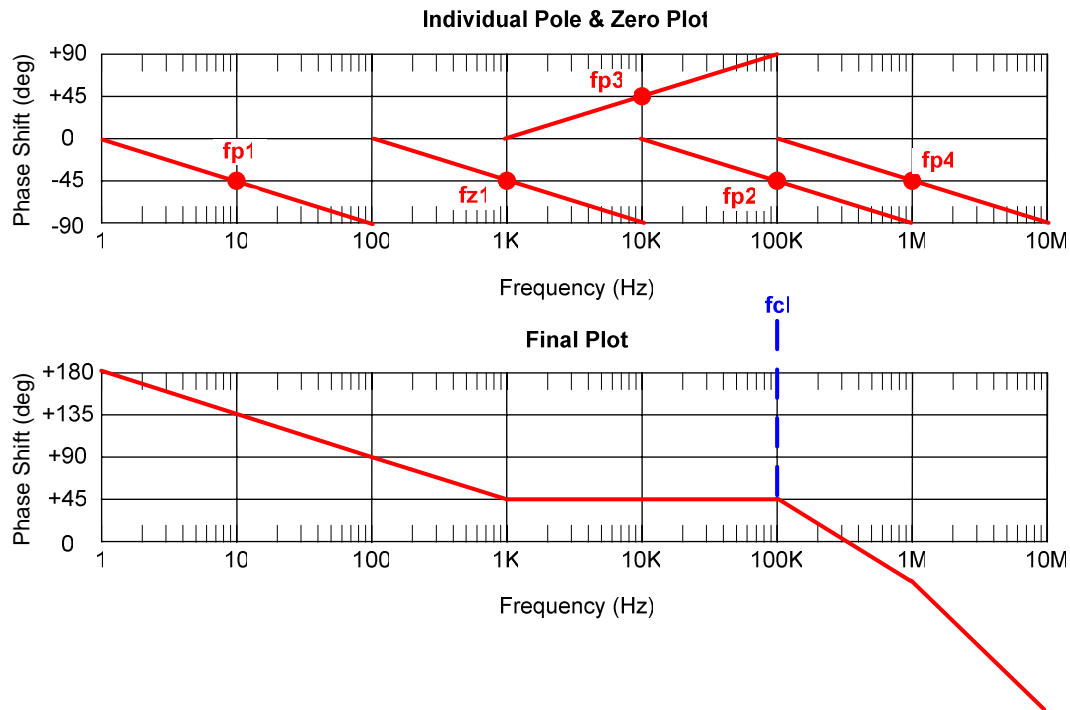


Fig. 4.3: First-Order Loop Phase Analysis

To check our first order loop phase analysis we build our op amp circuit in Tina SPICE (Fig. 4.4) and use the SPICE loop-gain test to measure the A_{ol} plot and $1/\beta$ plot.

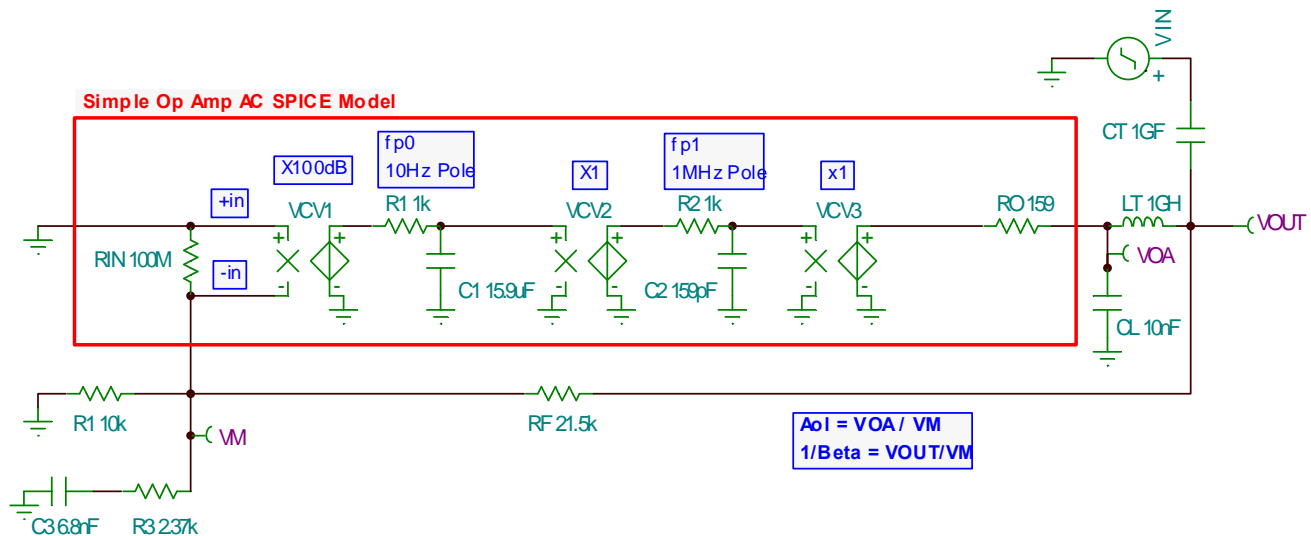


Fig. 4.4: Tina SPICE Circuit: SPICE Loop-Gain Test

The Tina SPICE results for A_{ol} and $1/\beta$ (Fig 4.5) correlate closely to our first-order hand analysis.

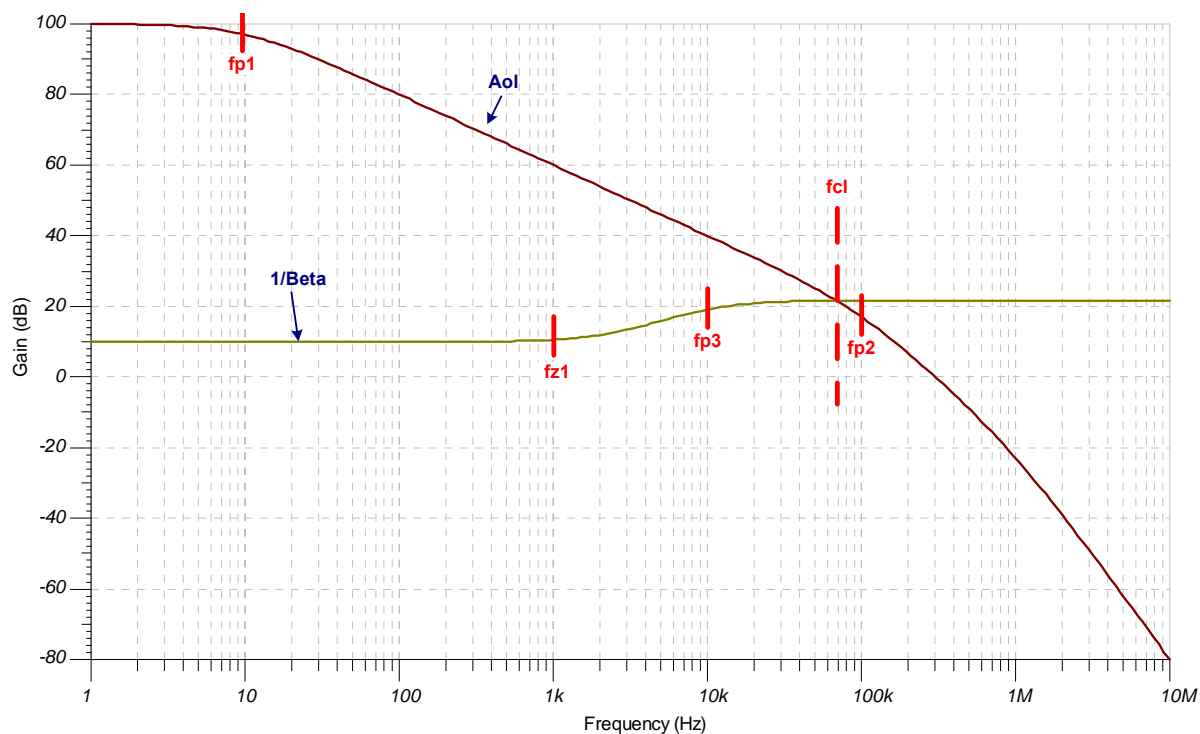


Fig. 4.5: Tina SPICE Circuit: $A_{ol}\beta$ and $1/\beta$

Our Tina SPICE simulation was also used to plot loop-gain and loop phase (Fig. 4.6) and is what we expected, based on our first-order hand analysis.

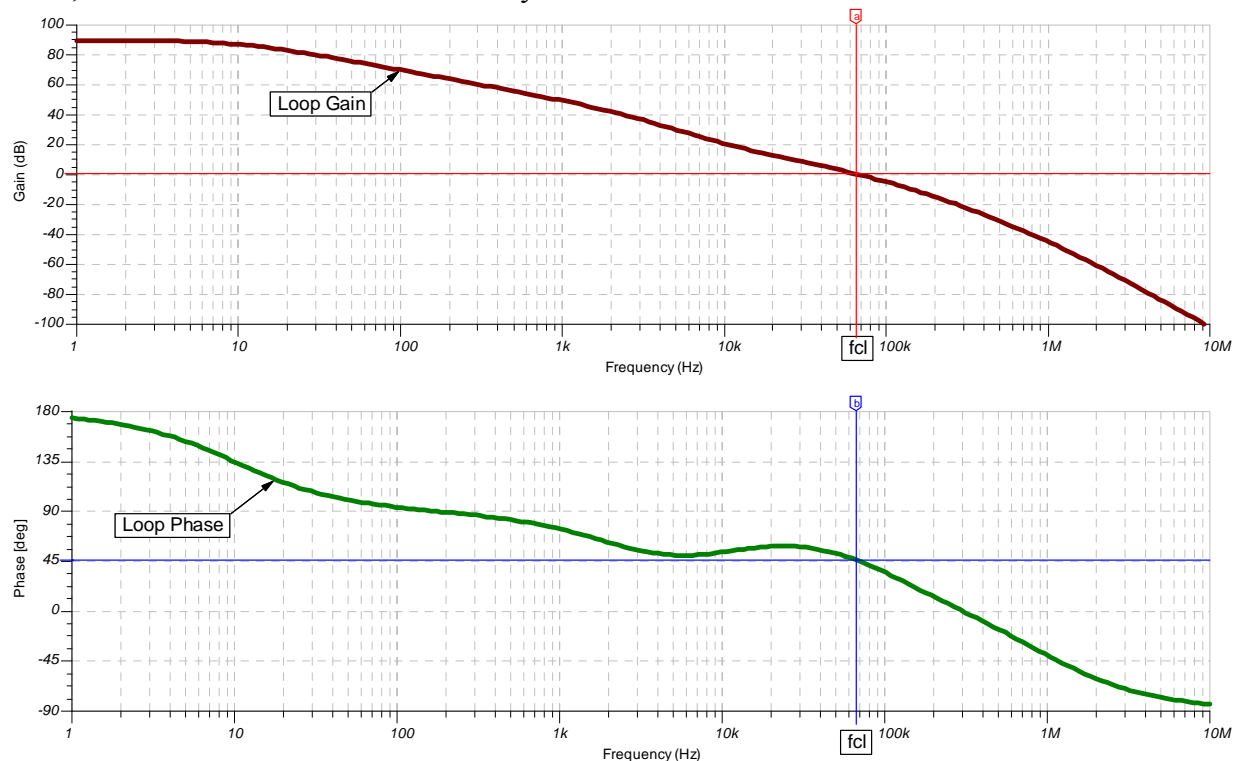


Fig. 4.6: Tina SPICE Circuit: Loop-Gain and Loop Phase

To check if our V_{OUT}/V_{IN} predictions were correct we modify our Tina SPICE circuit (Fig. 4.7) and simulate.

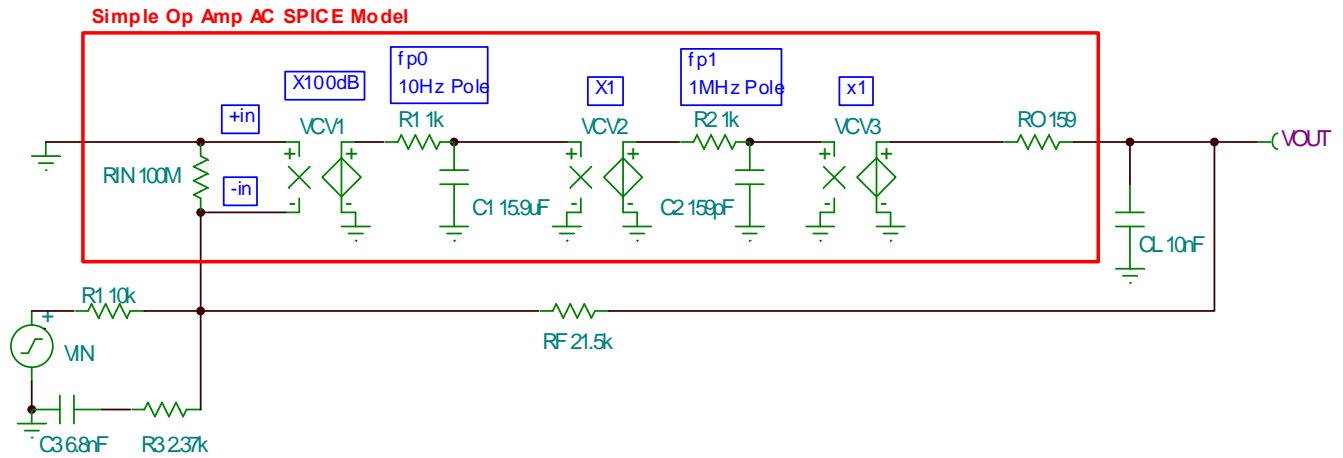


Fig. 4.7: Tina SPICE Circuit: V_{OUT}/V_{IN}

The Tina SPICE simulation results for V_{OUT}/V_{IN} (Fig. 4.8) show a slight rise in the V_{OUT}/V_{IN} transfer function starting at about 10 kHz. This is due to the fact that the loop-gain is beginning to be significantly reduced due to the Rn-Cn network. However, we are not far off from our first-order, hand analysis prediction. A key point to note again is that V_{OUT}/V_{IN} is not always the same as $1/\beta$.

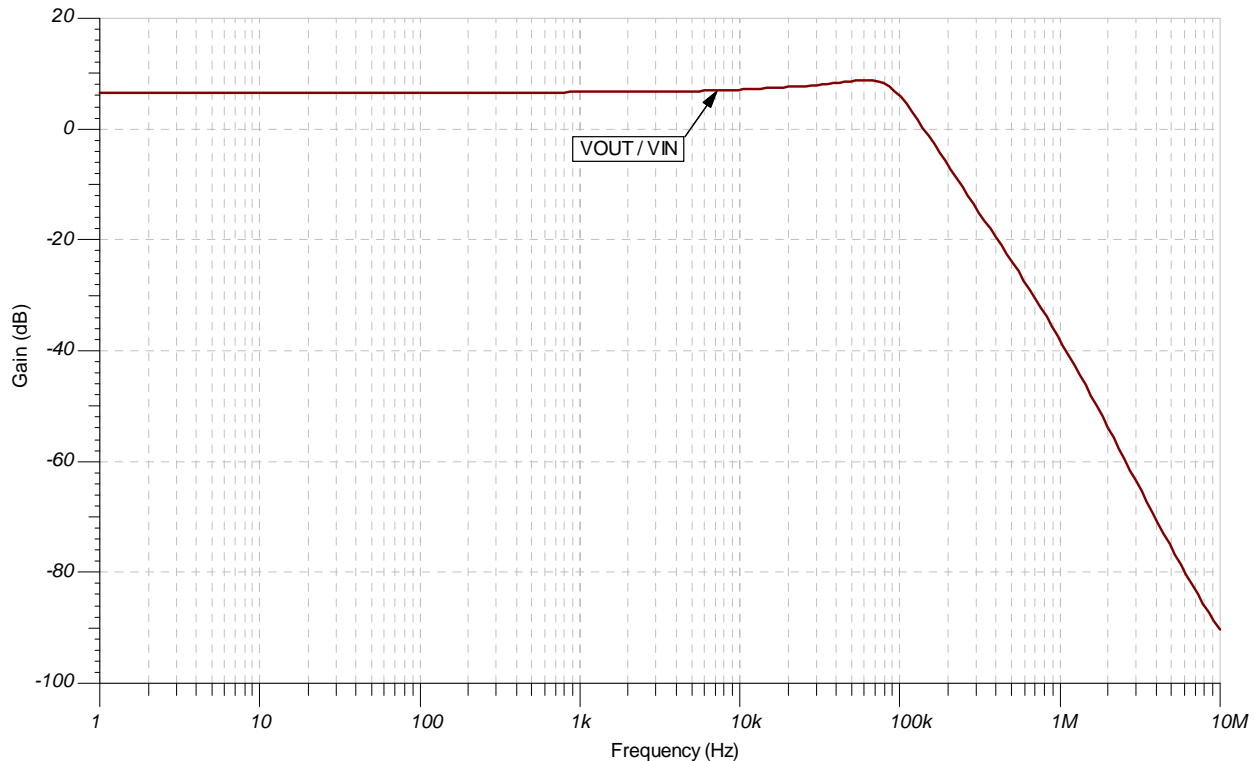


Fig. 4.8: Tina SPICE Circuit: V_{OUT}/V_{IN} Transfer Function

ZI and ZF Magnitude Decade Rule

We discussed ZI and ZF networks in Part 2 of this series. The “decade rule” for magnitudes in the ZI input network (Fig. 4.9) is if we scale $R_n = R_I/10$ (a “decade” in value less than R_I) we can be assured that at high frequencies, when the impedance of C_n is a short, R_n will set the high frequency as R_F/R_n . Scaling this way allows us to easily plot the dominant first-order results for a $1/\beta$ plot. The other advantage to our decade rule for magnitudes is that it forces the pole/zero pair, f_p and f_z , we are adding to be within one decade of each other and therefore between f_p and f_z the phase shift will remain flat.

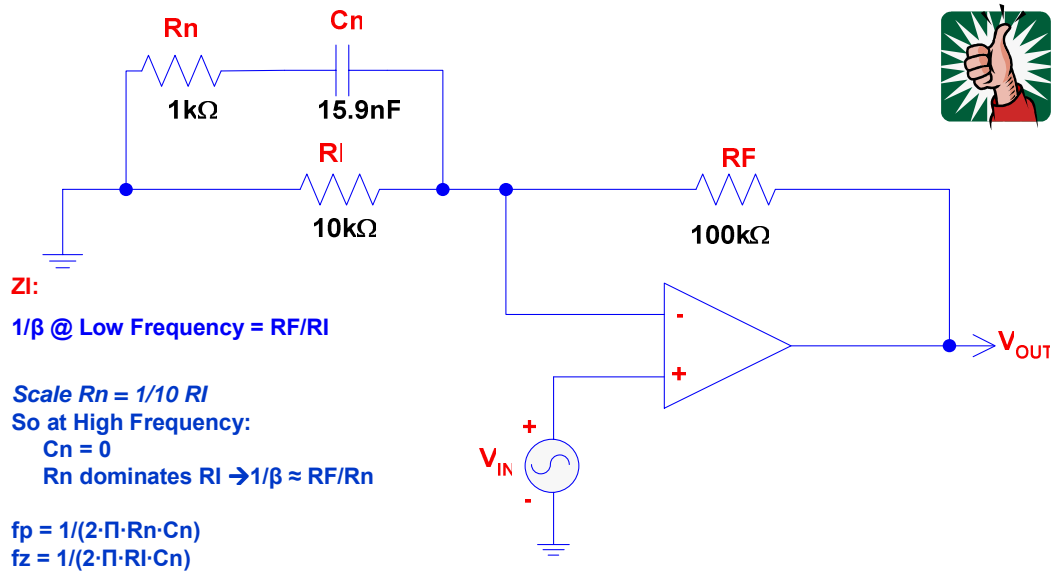


Fig. 4.9: ZI Magnitude Decade Rule

The “decade rule” for magnitudes in the ZF feedback network (Fig. 4.10) is if we scale $R_p = R_F/10$ (a “decade” in value less than R_F) we can be assured that at high frequencies, when the impedance of C_p is a short, R_p will set the high frequency as R_p/R_I . Scaling this way allows us to easily plot the dominant first-order results for a $1/\beta$ plot. As with the input network, ZI, the other advantage to our decade rule for magnitudes in ZF is that it forces the pole/zero pair, f_p and f_z , we are adding to be within one decade of each other and therefore between f_p and f_z the phase shift will remain flat.

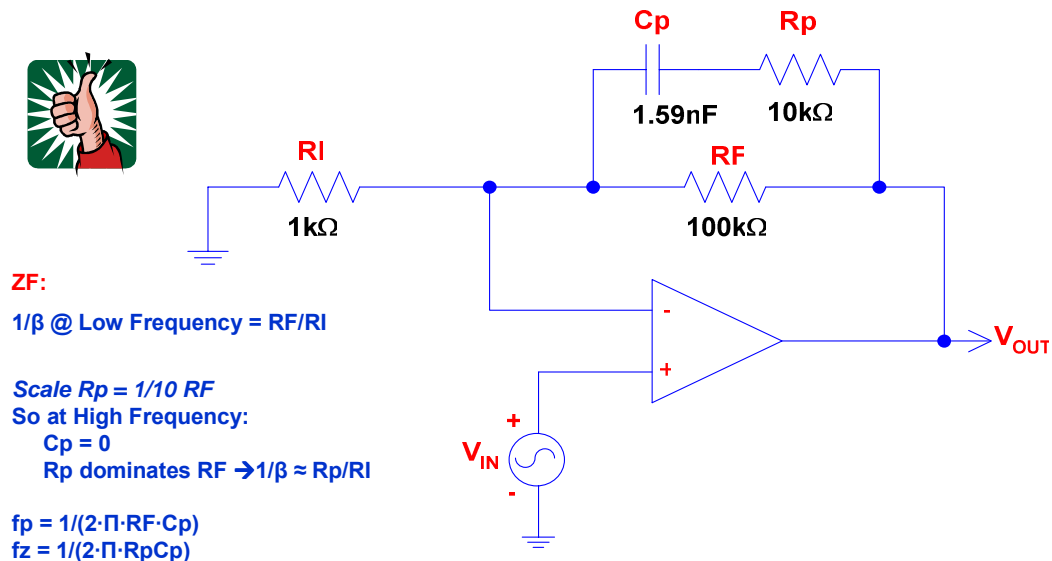


Fig. 4.10: ZF Magnitude Decade Rule

Dual-Feedback Paths

We will see later in this series that oftentimes the feedback circuits around op amps to guarantee good stability will require the use of more than one feedback path. To easily analyze and synthesize these types of multiple feedbacks we will call upon the superposition rule (Fig. 4.11). In our case we will analyze each effect independently and then use the dominant effect as the final one for our feedback.

Superposition:

If cause & effect are linearly related, the total effect of several causes acting simultaneously is equal to the sum of the effects of the individual causes acting one at a time.

From: Smith, Ralph J. Circuits, Devices, And Systems. John Wiley & Sons, Inc. New York. Third Edition, 1973.

Fig. 4.11: The Superposition Principle

In Fig. 4.12 we see an op amp circuit which uses two feedback paths. The first, FB#1, is out of the op amp, through R_{iso} and CL back through R_F and R_I to the $-$ input of the op amp. The second feedback, FB#2, is out of the op amp, through C_F and back to the $-$ input of the op amp. The equivalent $1/\beta$ plots for each of these feedbacks are plotted separately. The details of this derivation will be seen later in this series. When more than one feedback path is used around an op amp the one which feeds back the largest voltage to the input will become the dominant one. This implies that if $1/\beta$ is plotted for each feedback the one with the lowest $1/\beta$ at a given frequency will dominate at that point. Remember that the smallest $1/\beta$ implies the largest β and since $\beta = V_{FB}/V_{OUT}$, the largest β implies the largest fed-back voltage. An analogy to remember is that if two people are talking to you in one ear the person you hear the easiest is the one talking the loudest! So the op amp will “listen” to the feedback with the largest β or smallest $1/\beta$. The net $1/\beta$ plot the op amp sees is the lower one at any frequency of FB#1 or FB#2.


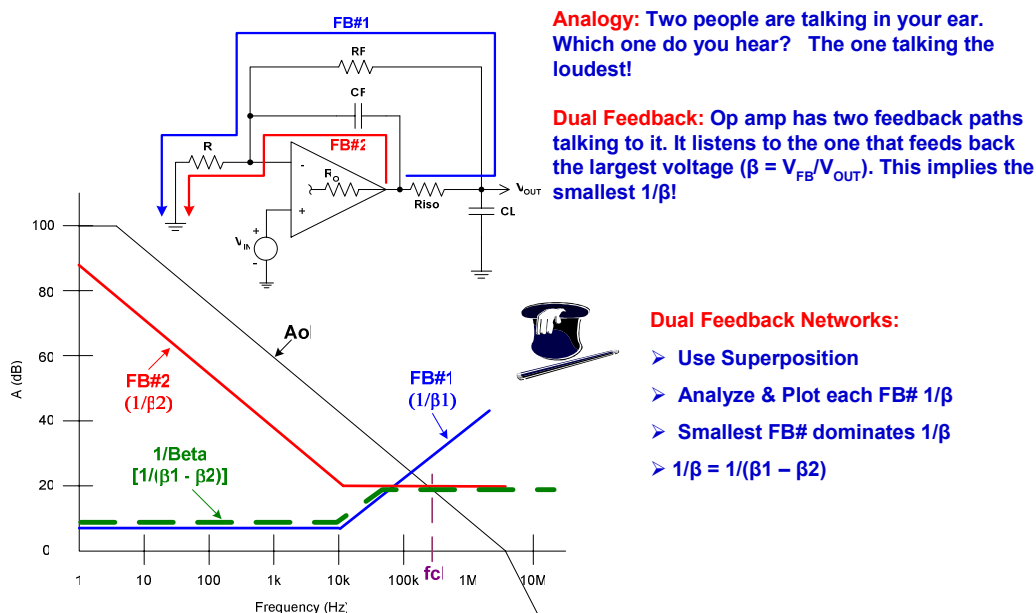
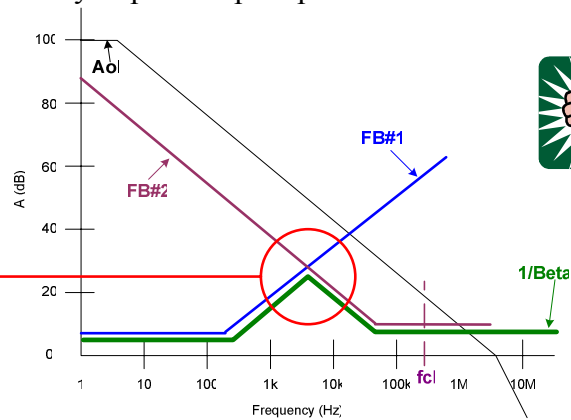


Fig. 4.12: Dual-Feedback Networks

When using dual-feedback paths around an op amp there is one extremely important case to avoid: the BIG NOT. There are op amp circuits (Fig. 4.13) which can result in feedback paths which contains a net $1/\beta$ slope changing abruptly from $+20$ dB/decade to -20 dB/decade, implying a complex conjugate pole -- which is therefore a complex conjugate zero in the loop-gain plot. Complex zeros and poles

create a $\pm 90^\circ$ phase shift at that frequency. In addition, the phase slope around a complex zero/complex pole can range from $\pm 90^\circ$ to $\pm 180^\circ$ in a narrow frequency band around the frequency of the occurrence. Complex zero/complex pole occurrences can cause severe gain peaking in the closed-loop op amp response. This can be very undesirable especially in power op amp circuits.

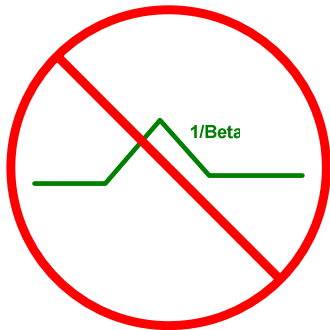WARNING: This can be hazardous to your circuit!




Dual Feedback and the **BIG NOT**:

1/β Slope changes from +20dB/decade to -20dB/decade

- Implies a “complex conjugate pole” in the $1/\beta$ Plot.
- Implies a “complex conjugate zero” in the $Aol\beta$ (Loop Gain Plot).
- $\pm 90^\circ$ phase shift at frequency of complex zero/complex pole.
- Phase slope from $\pm 90^\circ/\text{decade}$ slope to $\pm 180^\circ$ in narrow band near frequency of complex zero/complex pole depending upon damping factor.
- Complex zero/complex pole can cause **severe** gain peaking in closed loop response.

Fig. 4.13: Dual Feedback and the BIG NOT

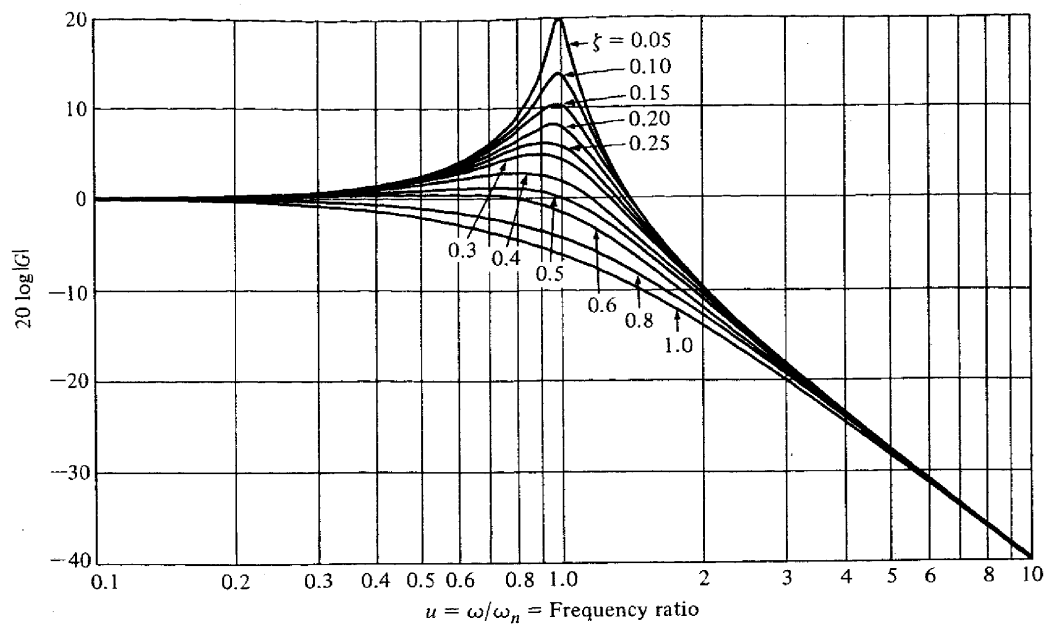Irrespective of the damping factor (Fig. 4.14) the magnitude plot for a complex conjugate pole appears to be two-pole with a -40 dB/decade slope. However, the phase will show a different story.




(a)

From: Dorf, Richard C. Modern Control Systems. Addison-Wesley Publishing Company. Reading, Massachusetts. Third Edition, 1981.

Fig. 4.14: Complex Conjugate Pole Magnitude Example

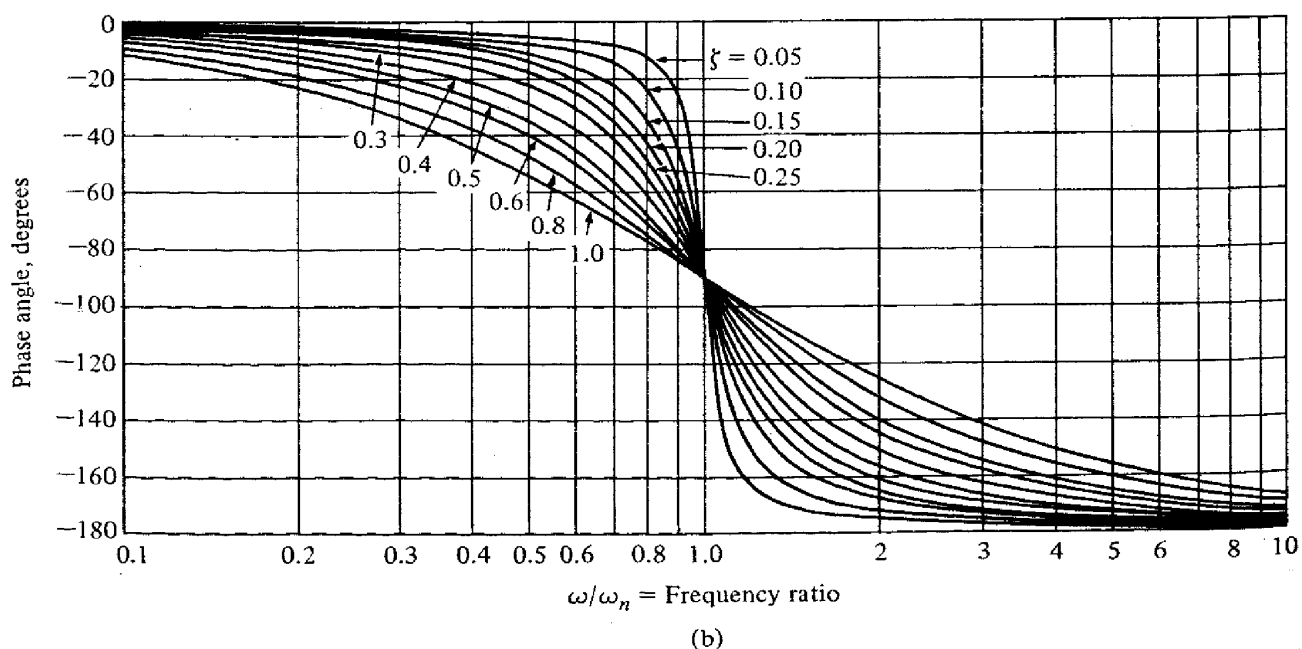In the phase plot for a complex conjugate pole (Fig. 4.15) it is clear that, depending upon the damping factor, the phase shift can be dramatically different than one for a simple double pole: which we would expect to be -90° shift at the frequency and a $-90^\circ/\text{decade}$ slope (damping factor = 1).




From: Dorf, Richard C. *Modern Control Systems*. Addison-Wesley Publishing Company. Reading, Massachusetts. Third Edition, 1981.

Fig. 4.15: Complex Conjugate Pole Phase Example

Real-World Stability Test

Once we complete our first-order hand analysis, do a SPICE simulation as a sanity check, we then build the op amp circuit. It would be convenient to have an easy way to confirm if our real-world phase margin is what we predicted. Most real-world circuits are dominated by a two-pole second-order system response (Fig. 4.16). A typical op amp Aol has a low-frequency pole in the 10 Hz to 100 Hz region and another high-frequency pole at its unity-gain crossover frequency, or soon after that in frequency. If pure resistive feedback is used we can see that the loop-phase plot would demonstrate the effects of a two-pole system. For more complicated op amp circuits the resultant loop-gain and loop-phase plots are usually dominated by a two-pole response. Closed-loop behavior of a second-order system is well defined and offers us a powerful technique for a real-world stability check.

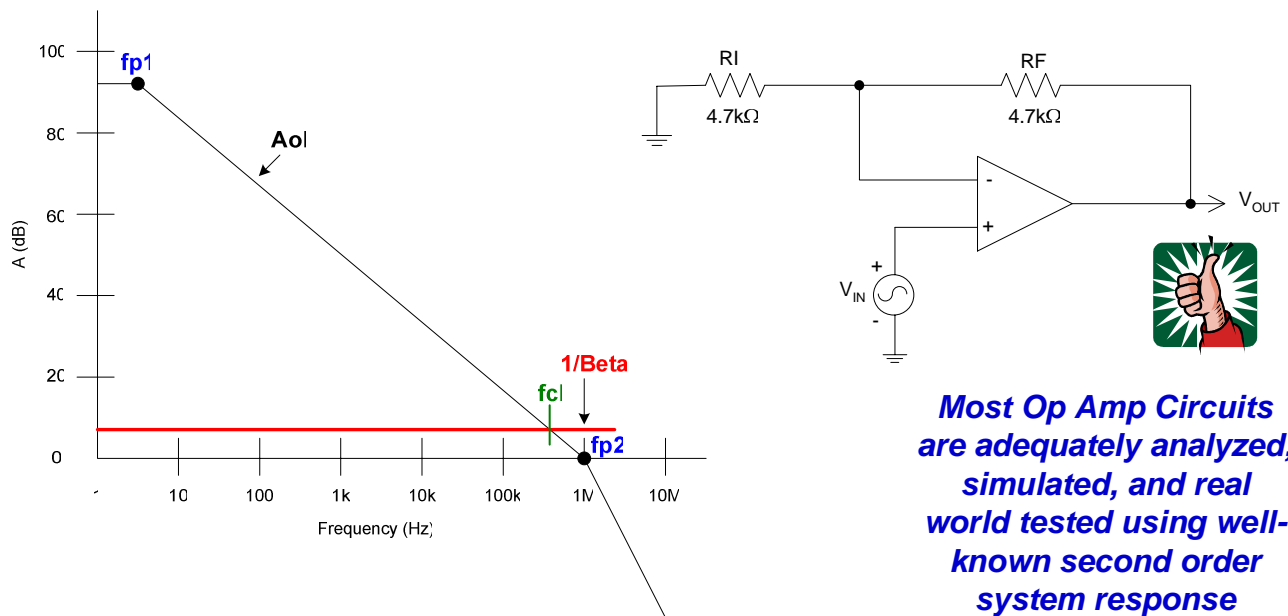

Most Op Amps are dominated by Two Poles:

Aol curve shows a low frequency pole, fp1

Aol curve also has a high frequency pole, fp2


Often fp2 is at fcl for unity gain

This yields 45 degrees phase margin at unity gain

Fig. 4.16: Op Amp Circuit Ac Behavior

In a transient real-world stability test (Fig. 4.17) a small amplitude square-wave is injected into the closed-loop op amp circuit as the V_{IN} source. A frequency is chosen well within the loop-gain bandwidth but also high enough to make triggering with an oscilloscope easy. 1 kHz is a good test frequency for most applications. V_{IN} is adjusted such that V_{OUT} is 200 mVpp or less. We are interested in the small signal ac behavior of the circuit to look for ac stability. To that end we do not want a large signal swing on the output which could also contain large signal limitations such as slew rate, output current limitations, or output stage voltage saturation. V_{offset} provides a mechanism to move the output voltage up and down through its entire output voltage range to look for ac stability under all operating point conditions. For many circuits, especially those that drive capacitive loads, the worst case for stability is when the output is near zero (for a dual-supply op amp application) and there is little or no dc load current since this results in the highest value of R_O , the op amp's open-loop small-signal


resistance. Record the amount of overshoot and ringing on the square-wave output and compare it to the 2nd-order transient curves (Fig. 4.18). From the curve that matches your measured circuit the closest, note the respective damping ratio and find this ratio in y-axis of the 2nd-order damping ratio vs phase margin curve (Fig. 4.19). The x-axis contains the phase margin of the second-order circuit.

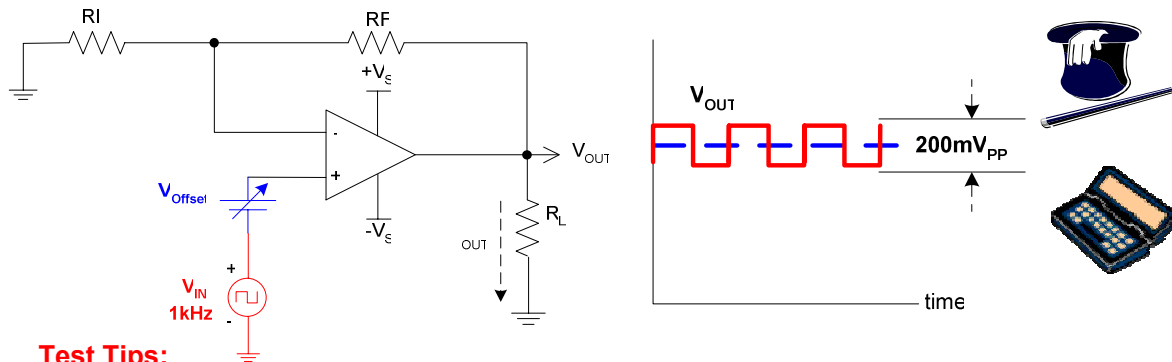

Test Tips:


- Choose test frequency $\ll f_{cl}$
- Adjust V_{IN} amplitude to yield “Small Signal” AC Output Square Wave
- Worst case is usually when $V_{Offset} = 0 \rightarrow$ Largest Op Amp R_O ($I_{OUT} = 0$)
- Use V_{Offset} as desired to check all output operating points for stability
- Set scope = AC Couple & expand vertical scope scale to look for amount of overshoot, undershoot, ringing on V_{OUT} small signal square wave

Fig. 4.17: Transient Real World Stability Test

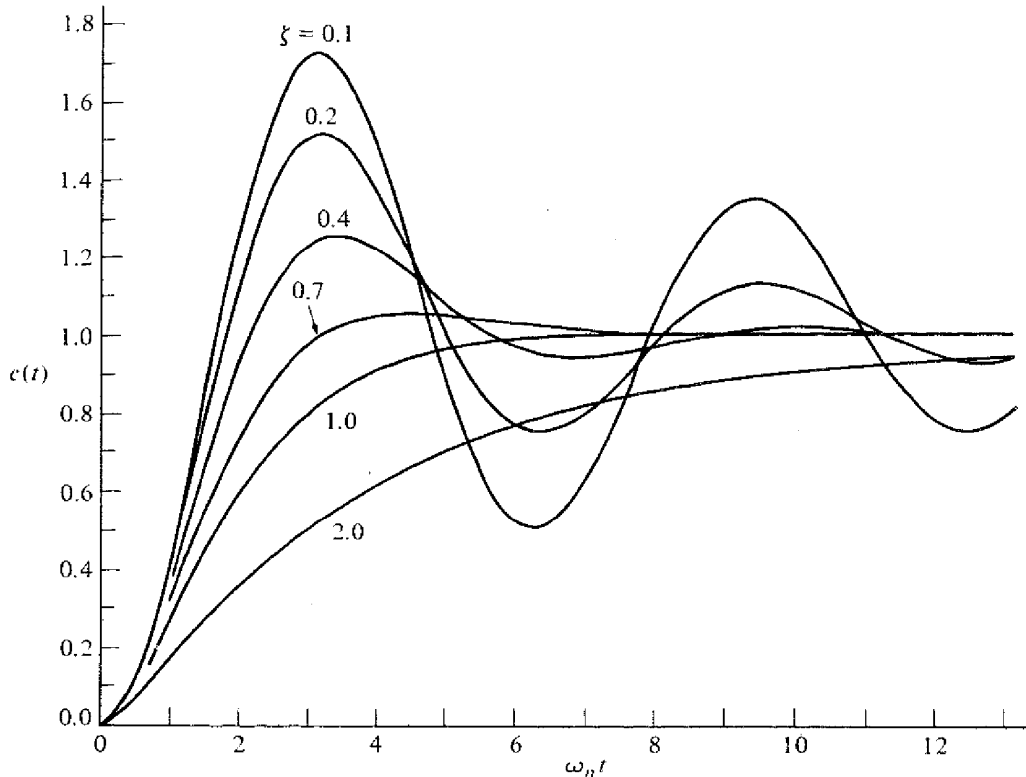

From: Dorf, Richard C. Modern Control Systems. Addison-Wesley Publishing Company. Reading, Massachusetts. Third Edition, 1981.

Fig. 4.18: 2nd-Order Transient Curves

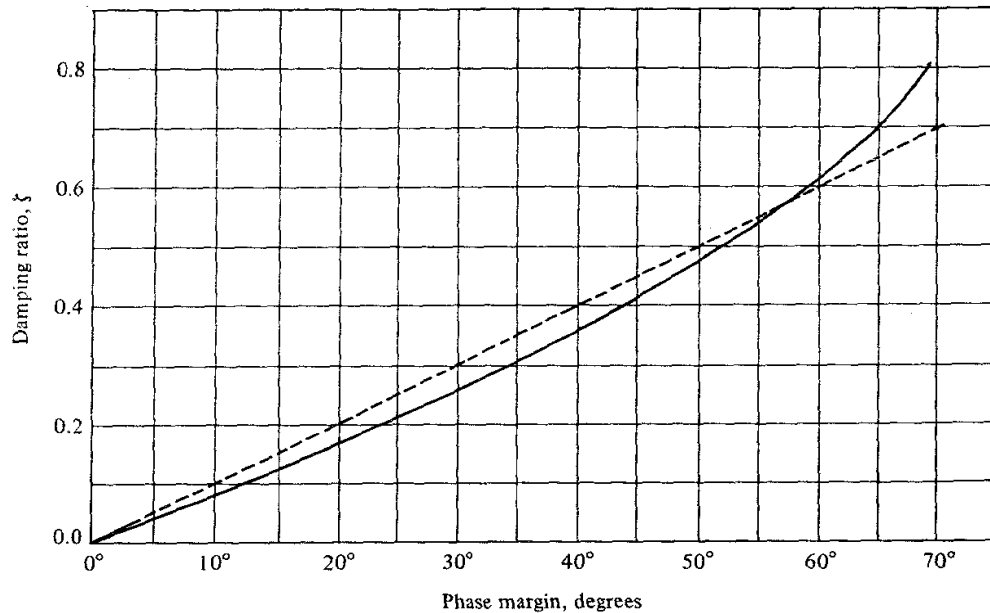

From: Dorf, Richard C. *Modern Control Systems*. Addison-Wesley Publishing Company. Reading, Massachusetts. Third Edition, 1981.

Fig. 4.19: 2nd Order Damping Ratio versus Phase Margin

References:

Frederiksen, Thomas M. *Intuitive Operational Amplifiers*, From Basics to Useful Applications, Revised Edition. McGraw-Hill Book Company. New York, New York. 1988

Dorf, Richard C. *Modern Control Systems*. Addison-Wesley Publishing Company. Reading, Massachusetts. Third Edition, 1981

Smith, Ralph J. *Circuits, Devices, And Systems*. John Wiley & Sons, Inc. New York. Third Edition, 1973.

About The Author

After earning a BSEE from the University of Arizona, Tim Green has worked as an analog and mixed-signal board/system level design engineer for over 23 years, including brushless motor control, aircraft jet engine control, missile systems, power op amps, data acquisition systems, and CCD cameras. Tim's recent experience includes analog & mixed-signal semiconductor strategic marketing. He is currently a Strategic Development Engineer at Burr-Brown, a division of Texas Instruments, in Tucson, AZ and focuses on instrumentation amplifiers and digitally-programmable analog conditioning ICs. He can be contacted at green_tim@ti.com

