

## Power Line Monitor

---


Power Quality Analyzer All in a single unit! Wide color screen [www.hiokiusa.com](http://www.hiokiusa.com)

Reliant - Official Site Reliant's Weekly Email Helps Manage Energy Use & Spend. Sign Up Now! [www.reliant.com/](http://www.reliant.com/)

Stop Wasting Electricity A power strip that shuts off automatically to save you money. [www.amazon.com](http://www.amazon.com)

Ads by Google

This node monitors the instantaneous current, voltage, frequency, and real power consumption of my home. Voltage is monitored with a dedicated miniature transformer, the current is measured using a home built current transformer that clamps around the incoming power feed, and the real power is calculated with an analog multiplier followed by a low pass filter to obtain the DC component (real power). These analog quantities are then fed to a 12-bit A/D converter driven by a '77 PIC. The circuit gains get me a resolution of 5 Watts. As a result I can even see the effect of turning on one lamp.

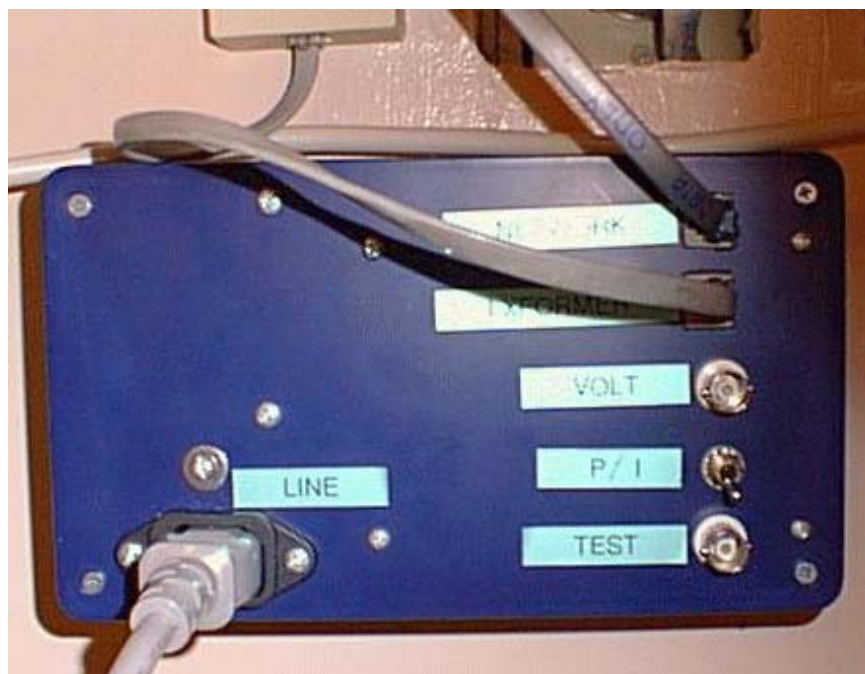


The power line monitor node. The two RJ11 connectors are the home automation network (top) and the current transformers (bottom). There are also two BNCs to plug in my 'scope to see the voltage, current and power waveforms.

The current transformers are key to this node. They are homemade from split ferrite cores with 100 turns into a 0.1 ohm 'burden' resistor. As a result, the output is 1mVolt per Ampere (each phase). Since the power service of the home is rated at 200 Amps (100 Amp / phase), the maximum output voltage is 0.1 Volt rms. Note that the transformers are made from split ferrite cores, clamped together by nylon hardware. This allows installation without having to remove the main power feeds from their connection on the breaker panel. By separating the halves and clamping them around the power feeds, I can sense current without disturbing the circuit.

An important consideration with the selection of the ferrite cores is if they can handle the magnetic field of the power feed without saturating. I confirmed this with a small space heater that I had. This unit draws approximately 11 Amps, and by winding nine turns around the core I saw that the resulting output current was linearly proportional to one turn. However adding just one more turn (12 turns) resulted in a slightly lower output (per turn), indicating that the core had started to saturate from the magnetic field. This proved that the cores should be able to handle the equivalent of a single conductor passing thru its hole carrying 100 Amps of current.

By the way, these cores were just some that I had lying around. I do not know a commercial source for them. They appear to be similar to TV flyback transformer cores, so TV repair shops may be a good source. [5/01 Update: It turns out that this suspicion was correct. I found an identically appearing transformer [here](#). The transformer that I used is in the center-top of the picture. Attempts to purchase small amounts of these have so far been unsuccessful.].

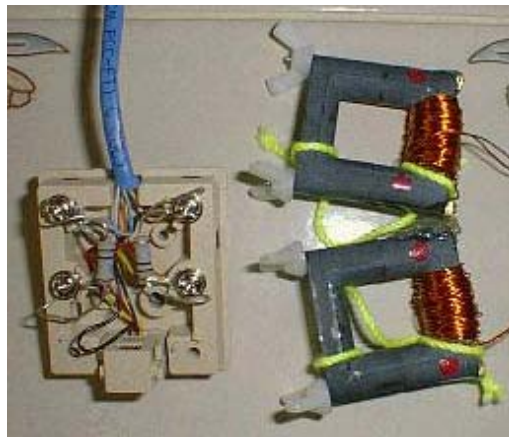

The current transformers. As is visible above, there are two transformers in the system, one for each power phase. Note that all parts that go inside the breaker panel are either tethered together or nonconductive. This prevents shorts should any parts fall during installation or use. The ferrite cores are split so that they can be installed without disturbing the power feeds to the house. This is done by unscrewing the nylon thumb screws and separating the two halves. Note that connection beyond this point is handled by RJ11 connectors, and the ['burden' resistors](#) inside the connector.

Calibration was performed by using an accurate clamp-on current meter, a DVM and a small electrical space heater. I first measured the voltage and current with the current meter and the DVM, noting the outputs of the A/D converter. I then turned on the space heater and measure the increase current. These two measurements (and assuming a linear system) allow me to calculate the gain and offset of the system. As mentioned above, each bit on the A/D results in a resolution of about 5 Watts.



The current transformers installed into the breaker panel. The two large black vertical conductors are the two main power feeds. Note the [CP303](#) signal blocker (with the four screw terminals) installed around the neutral (silver color) cable. This view should provide appreciation of using nonconductive wing nuts, if they should fall, they could touch the two large terminal blocks attaching the two main power cables.

## Energy Analysis


The main home control program was augmented with support for this node. The data on power, voltage, current and frequency is displayed on the home status window. Any TV in the house can now turn to the home control computer channel and see the current power line stats. After only a few minutes of use, I could already tell the power consumption of some major appliances in my home, for example:

- Refrigerator : 220 Watts
- Downstairs HVAC : 600 Watts (air handler), 3.6kWatt (compressor)
- Upstairs HVAC : 250 Watts (air handler).2.2kWatt (compressor)
- Sony 32" TV : 140 Watts
- Outside fountains : 100 Watts (for two pumps)
- Small space heater : 20 Watts (fan), 1.3kWatt (heating element)
- Home Automation PC : 40 Watts (monitor), 40 Watts (system unit)

The cost of [energy](#) (January 2005) ranges from 0.03 dollars/kWHR (winter night) to 0.08 dollars/kWHR (summer day).

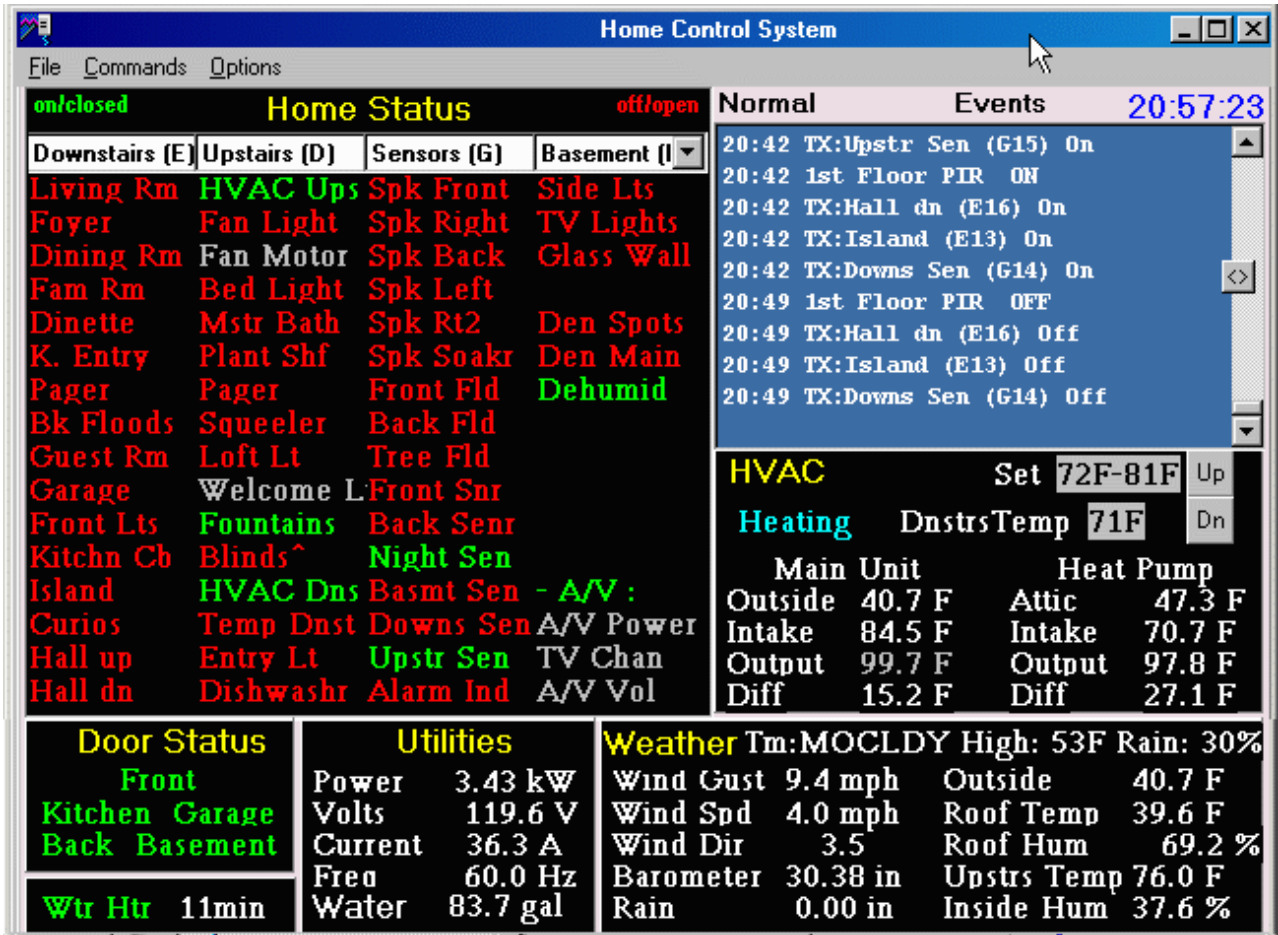
### Main System

The screenshot below shows the [home automation system](#)'s main screen. Note the power node's data in the 'Utilities' box.



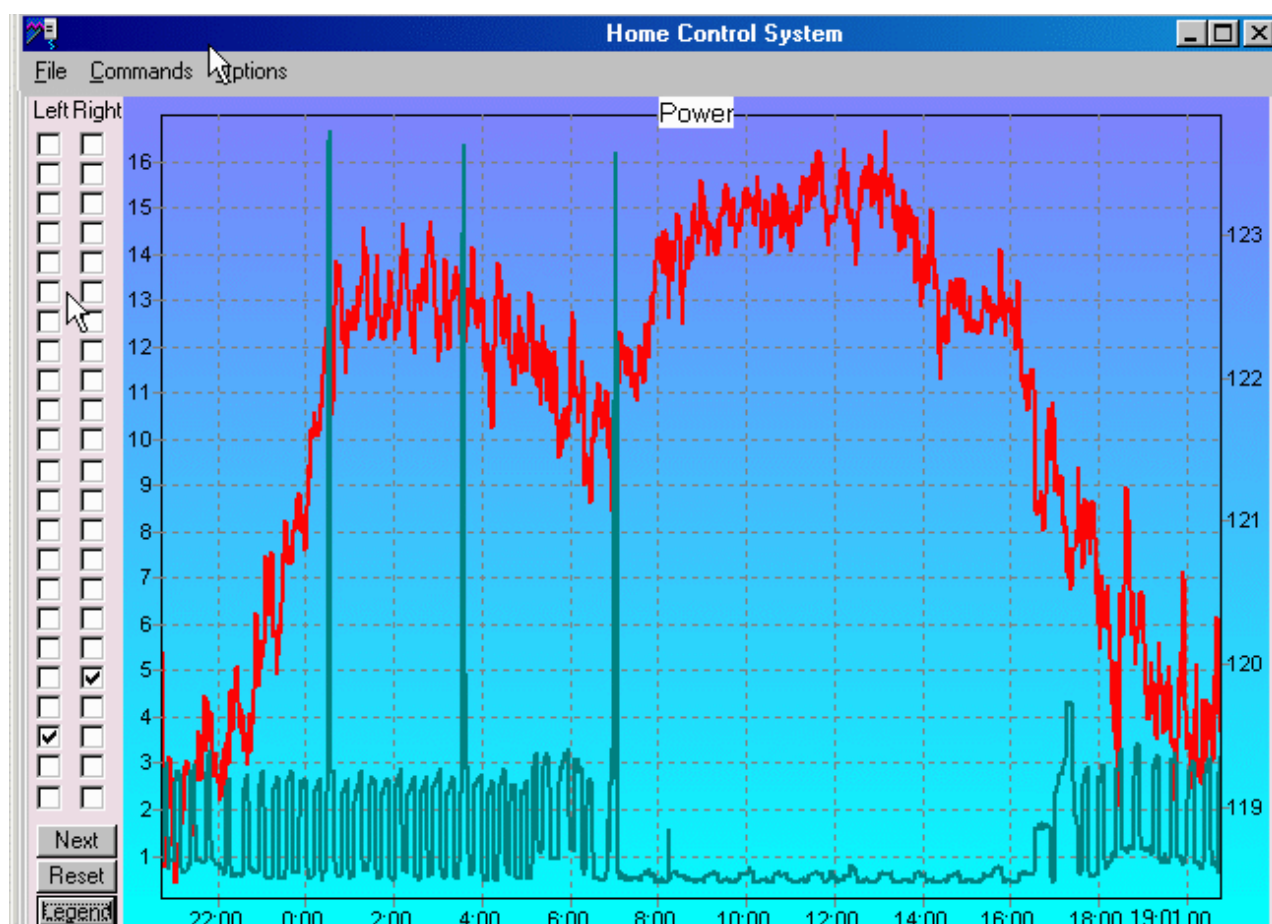Screenshot of the main control screen. Note the data of the power node displayed near the bottom. The heating system is shown to be running. The main unit has a temp rise of 15.2F, and the Heat Pump has a temp rise of 27.1F.





24 hour graph of the power data. Voltage is in red (right vertical axis) and power (left vertical axis). The large spikes are the defrost cycles on the heat pump, the 2kW ripple is the heat pump compressor. The user can position the cursor anywhere on the data to read the actual value.

One additional interesting observation is that the voltage level seems to be a good indicator of the power draw of my neighborhood. This quantity increases to about 122 Volts rms in the early morning hours (summer) to a low of 115 Volts rms in the hottest part of the late afternoon. This voltage seems unaffected by the instantaneous power draw of my own home (thus remains largely unchanged by my own HVAC units cycling), but is closely correlated to the current time and temperature conditions.

During the winter of 2000-2001, I was able to estimate the source impedance that the house sees from the power company. The line voltage changed by about 0.75Vrms when the power draw of the house changed from 3.5kW to 20kW. This translates into a source impedance of about 5.5milliOhms. Thus (measured at my breaker panel inside the home), the power company looks like a 5.5milliOhm source. Most of this is probably the wiring from the breaker panel to the neighborhood transformer (about 100 feet).

I am making circuit schematics and source code available for this project (for noncommercial use only). I hope you will [write to me](#) if you build your own version of my power node.

## Links:

- [Source code in C](#). Using [CCS](#) compiler.
- [Schematics](#) in Adobe pdf format
- Off-the-shelf [current transformers](#), including split-core and innovative flexible core units. Thanks to Arthur Hoey, NY
- Off-the-shelf [current transformers](#). Thanks to Carl Hunsinger.
- Another source of [split core transformers](#). Thanks to Duco Weytze.
- [Flyback transformer](#) cores. Including picture of unit identical to the one I am using.
- Commercial single outlet power monitor (Kill A Watt). [Here](#) and [here](#).

- Off-the-shelf [snap-on cores](#).
- Commercial [whole-home monitor](#) with graphing software.

## Long term update and log

- This node was installed on July 24, 1999.
- September 29 1999. Added an additional current transformer attached to an RJ11 jack for the [generator](#) current monitoring. By unplugging from one current transformer to the other, I can monitor power from the generator.
- November 23, 2000. Estimated the source impedance of the power company at 5.5 milliOhm.
- January 12, 2001. Added energy integrator in the software. This allows me to find out the total energy consumption over a specified period. This will be used to find the optimal operating mode of the upstairs HVAC system (heat pump).
- May 28, 2001. Power node working without a hitch.
- May 26, 2003. With the complete rewrite of the home automation system, I used the Kill-A-Watt meter (above) to calibrate the output of the power node. The commercial unit has a stated accuracy of 0.2%. In addition, I was unsatisfied with the diode-based peak detector in the current measurement (D1 in the schematic, and modified it by adding a spare op-amp. Currents are now measured down to 0 amps). The schematic was updated.
- July 28, 2003. Found Split-core AC current sensors on [digikey](#)'s website (part number 341-1052-ND) for a picture, click [here](#).
- Another source of split core transformers [here](#) (by Jeff Noxon).
- A complete fly-back transformer is part number IF313C8 from [Brigar](#) (by ericmagaha.at.adelphia.net).
- January 2005 - Energy analysis (see above).

Electric Power Meters Pulse Output Watt-Hour Meter Accurate, Easy Install, UL Listed [www.ccontrols.com](http://www.ccontrols.com)

TED The Energy Detective Monitor electricity usage of entire home in real-time. Accurate.Simple. [www.theenergy.com](http://www.theenergy.com)

Circuit Breaker Save time with push-in bridging. Reduce downtime! Request sample. [www.phoenixcontact.com](http://www.phoenixcontact.com)

Ads by Google

[Main Home Automation Web Page](#)

[Back Home](#)

(c) Edward Cheung, 2009