

BJT Frequency Response

Design a single stage common emitter with emitter bypass capacitor
Pre-amplifier circuit to amplify a 50mVp @ 10KHz input signal to up to 2Vp,
with cutoff frequency set to 1KHz and 50 KHz.

Use voltage divider circuit and $R_L = 10k\text{-ohm}$

Required:

- a) Design computation
- b) Simulation graphs (input and output comparison)
 - b1) 50mVp @ 60 Hz sine
 - b2) 50mVp @ 10 KHz sine
 - b3) 50mVp @ 100 KHz sine
 - b3) 50mVp @ 1MHz sine
- c) Low frequency response (bode plot and phase plot)
- d) Schematic and PCB foil pattern

DESIGN SOMPUTATION

$$V_{CC} := 10V \quad V_{in} := 50mV \quad V_{CE} := 7.5V \quad I_C := 8.69mA \quad C_C := 1\mu F \quad C_S := 1\mu F$$

$$V_O := 2V \quad V_{BE} := 0.7V \quad I_B := 50\mu A \quad f_1 := 10KHz \quad R_L := 10k\Omega \quad C_E := 15\mu F$$

$$V_E := \frac{V_{CC}}{10} = 1V \quad R_C := 475\Omega$$

$$V_B := V_{BE} + V_E = 1.7V$$

$$I_E := (\beta + 1)I_B = 8.74mA$$

$$R_E := \frac{V_E}{I_E} = 114.416\Omega$$

$$R_2 := \frac{\beta \cdot R_E}{10} = 1.989k\Omega$$

$$R_1 := \left(\frac{R_2 \cdot V_{CC}}{V_B} \right) - R_2 = 9.709k\Omega$$

$$r_e := \frac{26mV}{I_E} = 2.975\Omega$$

$$V_C := V_{CC} - I_C \cdot R_C = 8.5V$$

$$R_B := \frac{R_1 \cdot R_2}{R_1 + R_2} = 1.651 \times 10^3\Omega$$

$$Z_I := \frac{R_B \cdot (\beta \cdot r_e)}{R_B + (\beta \cdot r_e)} = 393.698\Omega$$

$$Z_O := \frac{R_C \cdot R_L}{R_C + R_L} = 169.683\Omega$$



Plate No. 3
BJT Frequency Response

Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13

1
7

DC TRANSFER CURVE

 


Plate No. 3
BJT Frequency Response


Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13

SIMULATION GRAPHS

50mVp @ 60 Hz

 

50mVp @ 10 KHz

 



Plate No. 3
BJT Frequency Response

Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13

50mVp @ 100 KHz

 

50mVp @ 1 MHz

 


Plate No. 3
BJT Frequency Response

Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13

LOW FREQUENCY RESPONSE

 



Plate No. 3
BJT Frequency Response

Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13

SCHEMATIC DIAGRAM

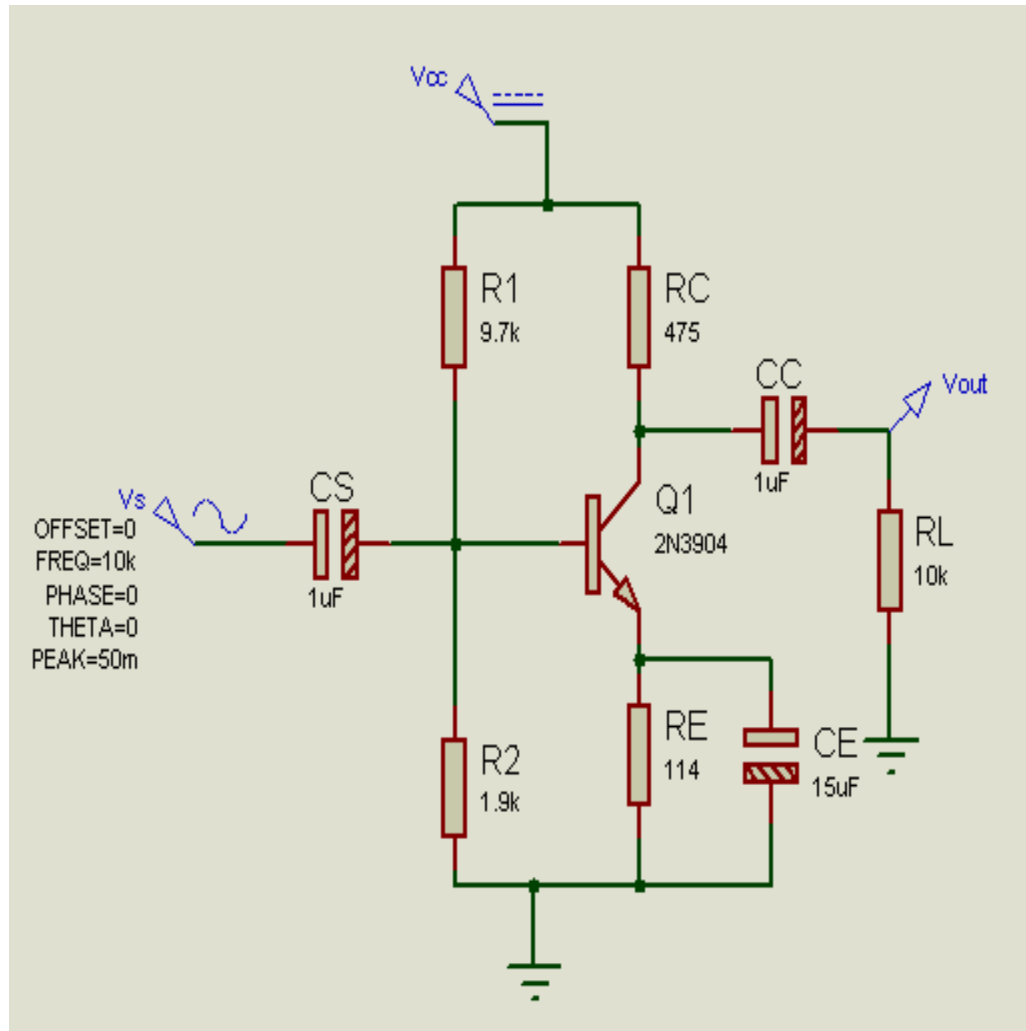

PCB FOIL PATTERN

 


Plate No. 3
BJT Frequency Response


Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13

6
7

3D DESIGN

 

SCHEMATIC DIAGRAM

 


Plate No. 3
BJT Frequency Response

Instructor:
Engr. Edgardo Martinez

Student:
Jomerey P. Sioson

Date:
4 / 28 /13