

sribalaji asked on 24-12-11, 03:03: "I learnt that maximum power transfer occurs when load impedance is equal to source impedance. Can anyone explain the reason why?"

I'll try to explain it to you.

First I have to correct your statement slightly (**pico** also did it before):

The *load impedance* must be **conjugate** (not equal) with the *source impedance* (at used frequency), i.e. the *real components* of $\mathbf{Z}_I (=R_I)$ and of $\mathbf{Z}_{LOAD} (=R_{LOAD})$ must be equal (\mathbf{Z}_I and R_I stand for the internal impedance and resistance of the source, respectively) and the *imaginary components* must be equal as to their absolute value but they must have opposite signs (it results in nullifying the reactive part of the total impedance \mathbf{Z} within the circuit).

Note: In general both the impedances are functions of frequency (the same holds for their real/imaginary components), so the condition can usually meet at only one (used) frequency (I suppose that a harmonic (=sine) waveform is used).

I'll offer you below the proof of the above statement:

Let's consider the simplest case first, i.e. when $\mathbf{Z}_I = R_I$ and $\mathbf{Z}_{LOAD} = R_{LOAD}$ (the imaginary components X_I and X_{LOAD} of both impedances are zero; see Fig.1):

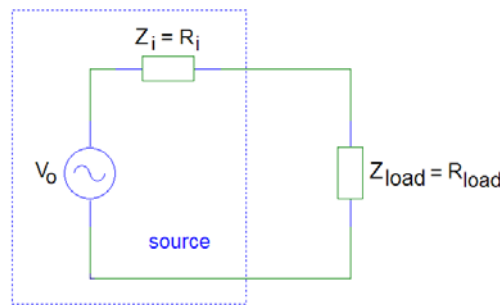


Fig. 1: Both internal and load impedances are purely active (real component $\neq 0$; imaginary component = 0)

The current flowing through R_I and R_{LOAD} is as follows:

$$I = \frac{V_0}{R_I + R_{LOAD}} \quad (1)$$

(the voltage drop over R_{LOAD} equals $V = V_0 \cdot \frac{R_{LOAD}}{R_I + R_{LOAD}}$) (2)

The active power P_{LOAD} dissipated in R_{LOAD} ('transferred' from source to load) is given as:

$$P_{LOAD} = R_{LOAD} \cdot I^2 = V_0^2 \cdot \frac{R_{LOAD}}{(R_I + R_{LOAD})^2} \quad (3)$$

As P_{LOAD} is the simple function of R_{LOAD} shown above, it is easy to find its local extremes by

- a) setting its first derivative to zero ($P_{LOAD}' = dP_{LOAD} / dR_{LOAD} = 0$), and
- b) inspecting the polarity of its second derivative to find out if the extreme found is maximum ($P_{LOAD}'' < 0$) or minimum ($P_{LOAD}'' > 0$):

$$\text{ad a)} \quad \frac{dP_{LOAD}}{dR_{LOAD}} = V_0^2 \cdot \frac{(R_I + R_{LOAD})^2 - 2R_{LOAD} \cdot (R_I + R_{LOAD})}{(R_I + R_{LOAD})^4} = V_0^2 \cdot \frac{R_I^2 - R_{LOAD}^2}{(R_I + R_{LOAD})^4} = 0 \quad (4)$$

Because $R_I^2 - R_{LOAD}^2$ equals $(R_I - R_{LOAD}) \cdot (R_I + R_{LOAD})$, the expression can be simplified as follows (both R_I and R_{LOAD} are **always positive**):

$$\frac{dP_{LOAD}}{dR_{LOAD}} = P_{LOAD}' = V_0^2 \cdot \frac{R_I - R_{LOAD}}{(R_I + R_{LOAD})^3} = 0 \quad (5)$$

The equation holds true if the numerator is zero, then its solution is:

$$\mathbf{R_{LOAD} = R_I} \quad (6)$$

$$\text{ad b)} \quad \frac{d^2 P_{LOAD}}{dR_{LOAD}^2} = P_{LOAD}'' = V_0^2 \cdot \frac{-(R_I + R_{LOAD})^3 - 3 \cdot (R_I - R_{LOAD}) \cdot (R_I + R_{LOAD})^2}{(R_I + R_{LOAD})^6} = \quad (7)$$

$$= V_0^2 \cdot \frac{-(R_I + R_{LOAD}) - 3 \cdot (R_I - R_{LOAD})}{(R_I + R_{LOAD})^4} = V_0^2 \cdot \frac{2R_{LOAD} - 4R_I}{(R_I + R_{LOAD})^4} \quad (8)$$

Substituting $\mathbf{R_{LOAD} = R_I}$, we obtain:

$$P_{LOAD}'' (@ R_{LOAD} = R_I) = V_0^2 \cdot \frac{-2R_I}{(2R_I)^4} = -\frac{V_0^2}{8R_I^3} < 0 \quad (9)$$

This result (9) determines that the extreme found at $R_{LOAD} = R_I$ (6) is the **maximum of P_{LOAD} with respect to R_{LOAD}** and the maximum itself equals:

$$P_{LOAD_MAX} = \frac{V_0^2}{4R_I} = \frac{V_0^2}{4R_{LOAD}} = \frac{\left(\frac{V_0}{2}\right)^2}{R_{LOAD}} \quad (10)$$

A slightly more complicated situation takes place if the imaginary components of impedances are not zero – the current is determined by the absolute value of the total impedance \mathbf{Z} within the circuit:

$$\mathbf{Z = Z_I + Z_{LOAD} = (R_I + R_{LOAD}) + j(X_I + X_{LOAD})}, \quad (11)$$

where \mathbf{j} stands for the imaginary unit ($\sqrt{-1}$)

$$\text{The absolute value of the complex quantity } \mathbf{Z}: |\mathbf{Z}| = \sqrt{(R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2} \quad (12)$$

So the current equals:

$$I = \frac{V_0}{|Z|} = \frac{V_0}{\sqrt{(R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2}} \quad (13)$$

The active power P_{LOAD} dissipated in R_{LOAD} ('transferred' from source to load) will be:

$$P_{LOAD} = R_{LOAD} \cdot I^2 = V_0^2 \cdot \frac{R_{LOAD}}{(R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2} \quad (14)$$

We have a function of **two variables** R_{LOAD} and X_{LOAD} now. Calculating its first partial derivative with respect to R_{LOAD} and setting it to zero we obtain:

$$\frac{\partial P_{LOAD}}{\partial R_{LOAD}} = V_0^2 \cdot \frac{(R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2 - 2R_{LOAD} \cdot (R_I + R_{LOAD})}{((R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2)^2} = 0 \quad (15)$$

Again, the equation holds true if the numerator is zero:

$$(R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2 - 2R_{LOAD} \cdot (R_I + R_{LOAD}) = 0, \quad \text{simplifying it:}$$

$$R_{LOAD}^2 = R_I^2 + (X_I + X_{LOAD})^2 \quad (16)$$

Similarly, calculating the first partial derivative with respect to X_{LOAD} now and setting it to zero we obtain:

$$\frac{\partial P_{LOAD}}{\partial X_{LOAD}} = V_0^2 \cdot \frac{-2R_{LOAD} \cdot (X_I + X_{LOAD})}{((R_I + R_{LOAD})^2 + (X_I + X_{LOAD})^2)^2} = 0 \quad (17)$$

It means, that $(X_I + X_{LOAD})$ must be zero (for the whole expression to be zero), therefore:

$$X_{LOAD} = -X_I \quad (18)$$

Substituting this result (18) in the above (16) we obtain the **final conditions for max. power transfer**:

$$R_{LOAD} = R_I \quad \text{and} \quad (19)$$

$$X_{LOAD} = -X_I \quad (20)$$

Let's believe that the second derivatives are less than zero ;-) (you can rely on it)
Well, that's it...

I believe it's helped you to understand "*the reason why*" (what you have asked).

Best Regards,
Eric

Appendix

Rules needed to calculate derivatives in the proof:

(independent variable here ... x)

$$\text{a) } (\text{constant})' = \frac{d\text{constant}}{dx} = 0$$

$$\text{b) } (\text{constant} \cdot x^n)' = \frac{d(\text{constant} \cdot x^n)}{dx} = \text{constant} \cdot n \cdot x^{n-1}$$

$$\text{c) } (u(x) \cdot v(x))' = \frac{d(u(x) \cdot v(x))}{dx} = u'(x) \cdot v(x) + u(x) \cdot v'(x) = v(x) \cdot \frac{du(x)}{dx} + u(x) \cdot \frac{dv(x)}{dx}$$

$$\text{d) } \left(\frac{u(x)}{v(x)} \right)' = \frac{d\left(\frac{u(x)}{v(x)} \right)}{dx} = \frac{u'(x) \cdot v(x) - u(x) \cdot v'(x)}{v^2} = \frac{v(x) \cdot \frac{du(x)}{dx} - u(x) \cdot \frac{dv(x)}{dx}}{v^2}$$

$$\text{e) } u''(x) = \frac{d}{dx} u'(x)$$

Conditions for local extremes of a function $u(x)$:

Maximum:

$$1. \quad u'(x) = \frac{du(x)}{dx} = 0$$

$$2. \quad u''(x) = \frac{d^2 u(x)}{dx^2} = \frac{du'(x)}{dx} < 0$$

Minimum:

$$1. \quad u'(x) = \frac{du(x)}{dx} = 0$$

$$2. \quad u''(x) = \frac{d^2 u(x)}{dx^2} = \frac{du'(x)}{dx} > 0$$