

## FLY-BACK CONVERTER DESIGN AND CIRCUIT

Circuit diagram and design calculations are given to convert 12V DC to fixed 12.5V DC and 18V isolated DC. Fly-back converter works in self oscillating mode.

Ferrite core selected: E 25/10/6

Core Cross section Area  $A_e = 39.5\text{mm}^2$

$A_L = 1600\text{ nH}$  (from core datasheet)

Max flux density  $B_{\text{max}} = 0.35\text{ Wb/m}^2$


Minimum input voltage  $V_{\text{min}} = (10.5\text{V} - 0.7\text{V}(\text{Diode}) - 0.7\text{V}(\text{Transistor})) = 9.1\text{ V}$

Minimum switching frequency  $F_s = 25\text{ KHz}$

Maximum duty cycle  $D_{\text{max}} = 0.5$  (for self oscillating mode)

Total output power  $P_o = 5\text{ W}$

Efficiency  $\eta = 0.7$

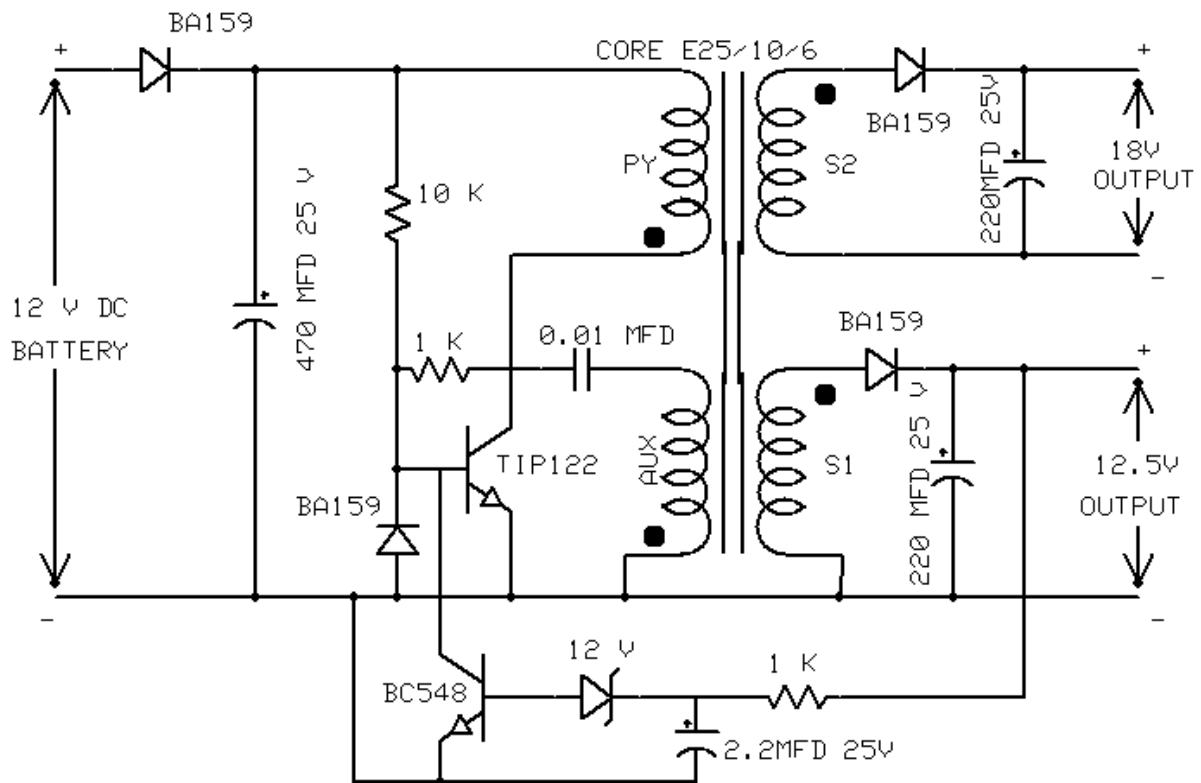

Peak Primary Current  $I_{\text{ppk}} = (2 \times P_o) / (\eta \times D_{\text{max}} \times V_{\text{min}})$

$$= (2 \times 5) / (0.7 \times 0.5 \times 9.1)$$

$$= 3.1 \text{ A}$$

$$\text{Primary RMS Current } I_{rms} = I_{ppk} \times \sqrt{D_{max} / 3}$$

$$= 3.1 \times \sqrt{0.5 / 3}$$

$$= 1.26 \text{ A (Wire selected 24 SWG enameled copper wire)}$$

$$\text{Primary Inductance } L_p = (V_{min} \times D_{max}) / (F_s \times I_{ppk})$$

$$= (9.1 \times 0.5) / (25000 \times 3.1)$$

$$= 58 \mu\text{H}$$

$$\text{No. of Primary turns } N_p = (V_{min} \times D_{max}) / (F_s \times B_{max} \times A_e)$$

$$= (9.1 \times 0.5) / (25000 \times 0.35 \times 39.5 \times 10^{-6})$$

$$\text{No. of Primary turns } \mathbf{N_p = 13 \text{ Turns}}$$

$$\text{Auxiliary winding voltage} = 6 \text{ V}$$

$$\text{No. of Aux Turns} = (6/9.1) \times 13 = \mathbf{9 \text{ Turns (30 SWG enameled wire)}}$$

(This 12.5 V may be used to supply KA3525 in push-pull converter to give constant gate drive to MOSFETs when input voltage decreases due to load)

$$S1 \text{ winding voltage} = 12.5\text{V} + 1 \text{ V} = 13.5 \text{ V}$$

$$\mathbf{S1 \text{ winding Turns} = (13.5/9.1) \times 13 = 19 \text{ Turns (30 SWG enameled wire)}}$$

(This isolated 18 V may be used to supply TLP250 drivers driving IGBTs)

$$S2 \text{ winding voltage} = 18 \text{ V} + 1 \text{ V} = 19 \text{ V}$$

$$\mathbf{S2 \text{ winding Turns} = (19/9.1) \times 13 = 27 \text{ Turns (30 SWG PVC insulated wire)}}$$

**(Note: Winding directions are important in self oscillating Fly-back converter)**

$$\text{Air gap required } L_g = \mu_o \times A_e ((N_p^2 / L_p) - (1 / A_L))$$

$$= 4 \times \pi \times 10^{-7} \times 39.5 \times 10^{-6} \times ((13^2/58 \times 10^{-6}) - (1/1600 \times 10^{-9}))$$

$$= 0.1 \text{ mm}$$

$$\text{Per limb air gap} = 0.1 / 2 = 0.05 \text{ mm}$$