

# **Lecture 25**

## **Multistage Amplifiers (II)**

### **DC VOLTAGE AND CURRENT SOURCES**

#### **Outline**

1. DC Voltage Sources
2. DC Current Sources and Sinks

#### **Reading Assignment:**


Howe and Sodini, Chapter 9, Sections 9-3-9.4

# 1. DC Voltage Sources

Characteristics of DC Voltage Sources :

- A well controlled output voltage
- Output voltage does not depend on current drawn from source  $\Rightarrow$  **Low Thevenin Resistance**

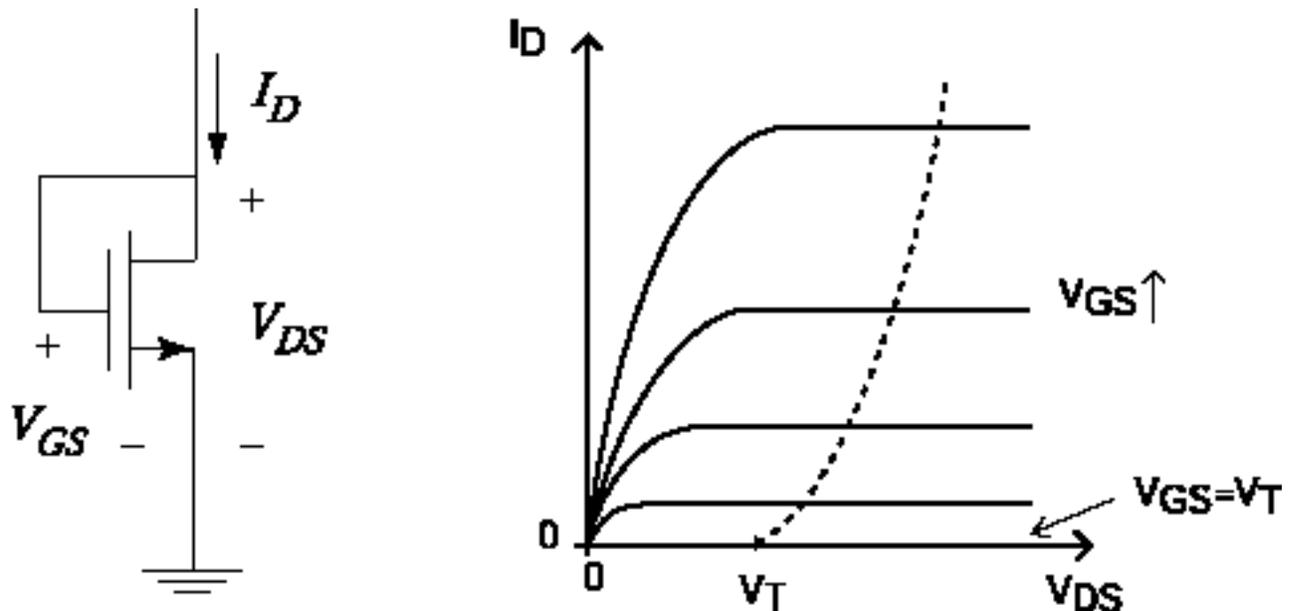Consider a MOSFET connected in “diode configuration”




I-V characteristics:

$$I_D = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_{Tn})^2 = \frac{W}{2L} \mu_n C_{ox} (V_{DS} - V_{Tn})^2$$

Beyond the threshold voltage, the MOSFET looks like a “diode” with quadratic I-V characteristics

## How does one synthesize a voltage source with this?

Assume a current source is available

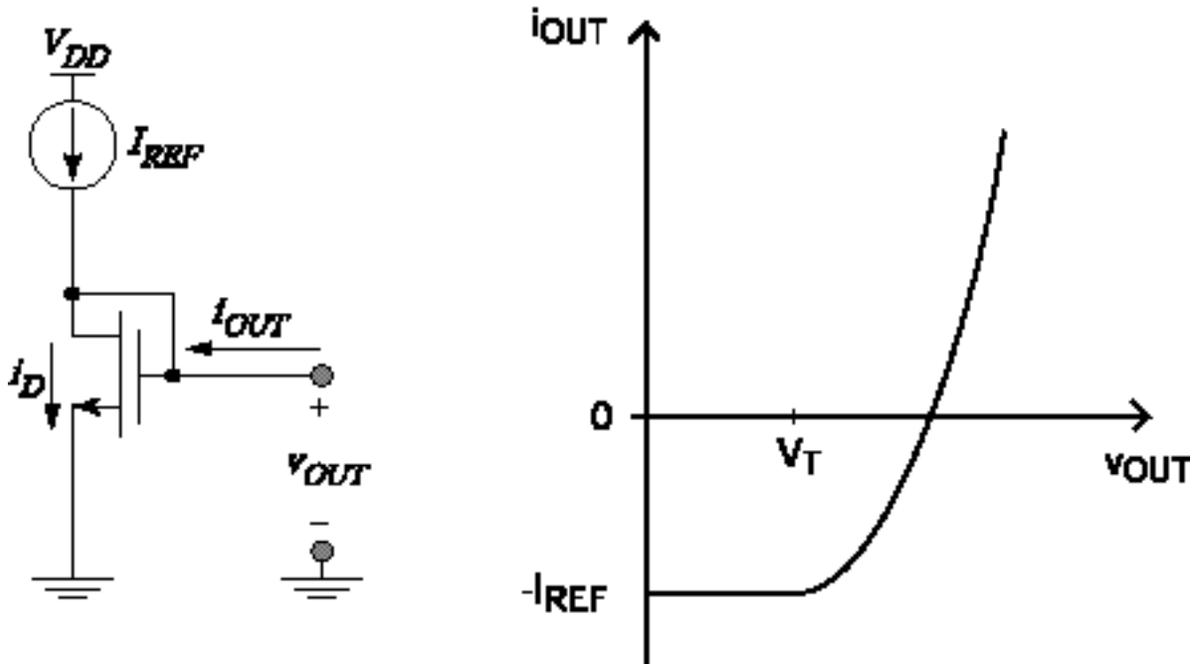

$V_{GS} = V_{DS}$  takes a value needed to sink current

$$i_D = I_{REF} + i_{OUT} = \frac{W}{2L} \mu_n C_{ox} (v_{OUT} - V_{Tn})^2$$

Then:

$$i_{OUT} = \frac{W}{2L} \mu_n C_{ox} (v_{OUT} - V_{Tn})^2 - I_{REF}$$


Solving for  $v_{OUT}$ :

$$v_{OUT} = V_{Tn} + \sqrt{\frac{I_{REF} + i_{OUT}}{\frac{W}{2L} \mu_n C_{ox}}}$$

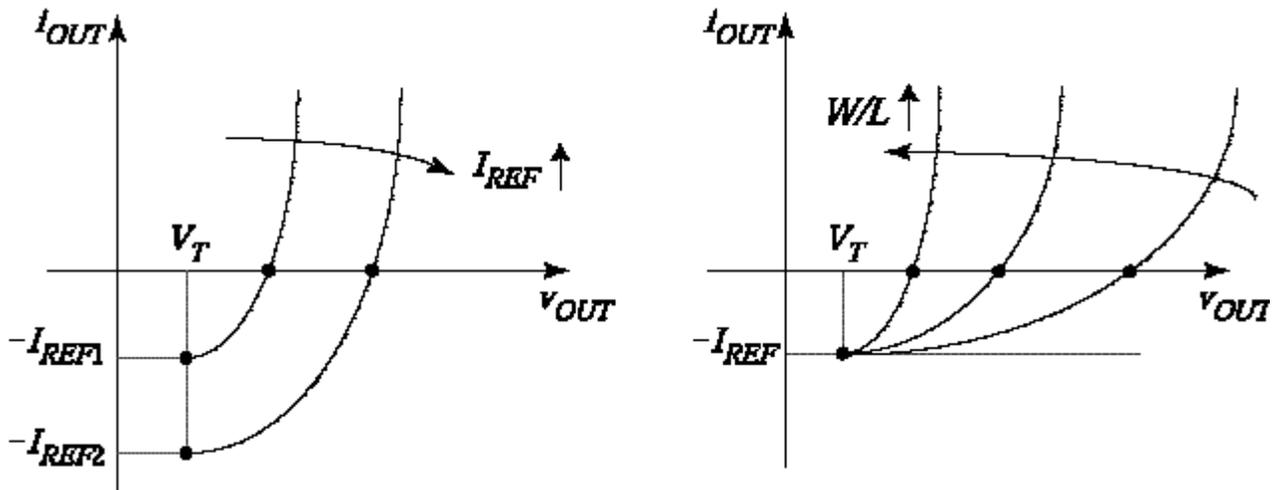
## Synthesizing Voltage Sources (contd.)

$v_{OUT}$  is a function of  $I_{REF}$  and  $W/L$  of MOSFET:

- $I_{REF} \uparrow \Rightarrow v_{OUT} \uparrow$
- $W/L \uparrow \Rightarrow v_{OUT} \downarrow$




Small Signal Equivalent Circuit Model:

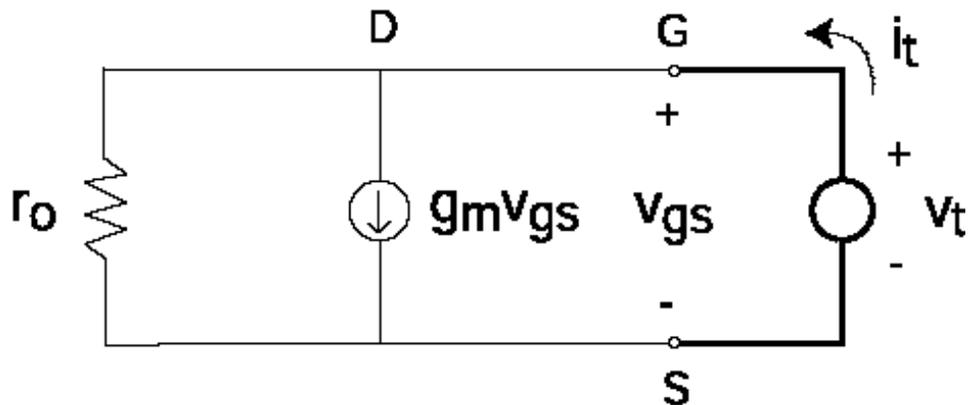

$$R_{out} = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

$R_{out}$  is small (good!)

## PMOS voltage source

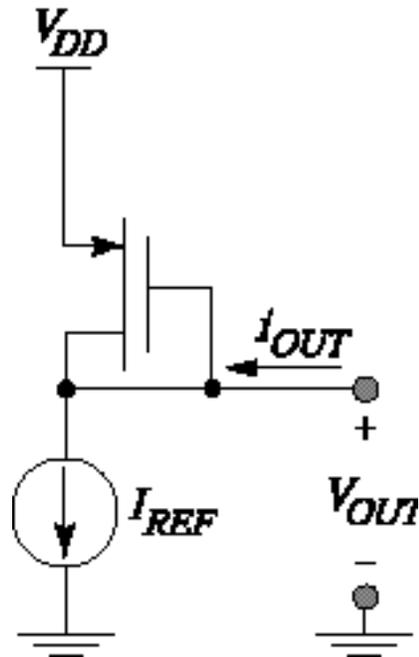

Same operation and characteristics as NMOS voltage source. PMOS needs to be larger to attain the same  $R_{out}$ .

### 3. DC Current Sources and Sinks


#### Characteristics of Current Sources

- A well controlled output current
- Supplied current does not depend on output voltage  
 $\Rightarrow$  *High Norton Resistance*

Connect a voltage source to the gate of another MOSFET:

$$I_{OUT} \approx \frac{1}{2} \left( \frac{W}{L} \right)_2 \mu_n C_{ox} (V_{REF} - V_{Tn})^2$$
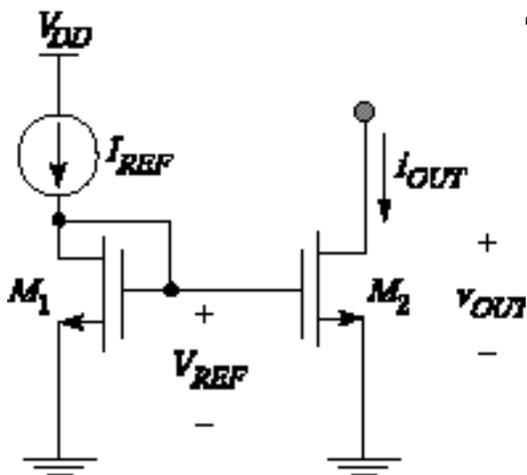
$$I_{REF} \approx \frac{1}{2} \left( \frac{W}{L} \right)_1 \mu_n C_{ox} (V_{REF} - V_{Tn})^2$$



Then:


$$I_{OUT} = I_{REF} \frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1}$$

$I_{OUT}$  scales with  $I_{REF}$  by  $W/L$  ratios of two MOSFETs  
 $\Rightarrow$  *Current Mirror Circuit*

Well “matched” transistors important.


## DC Current Sources and Sinks (contd.)
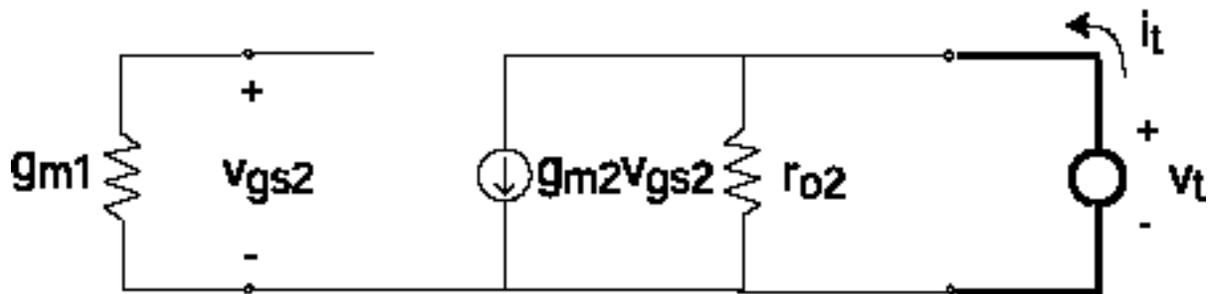
### Small Signal Equivalent Circuit Model:



$$R_{out2} = r_{o2}$$

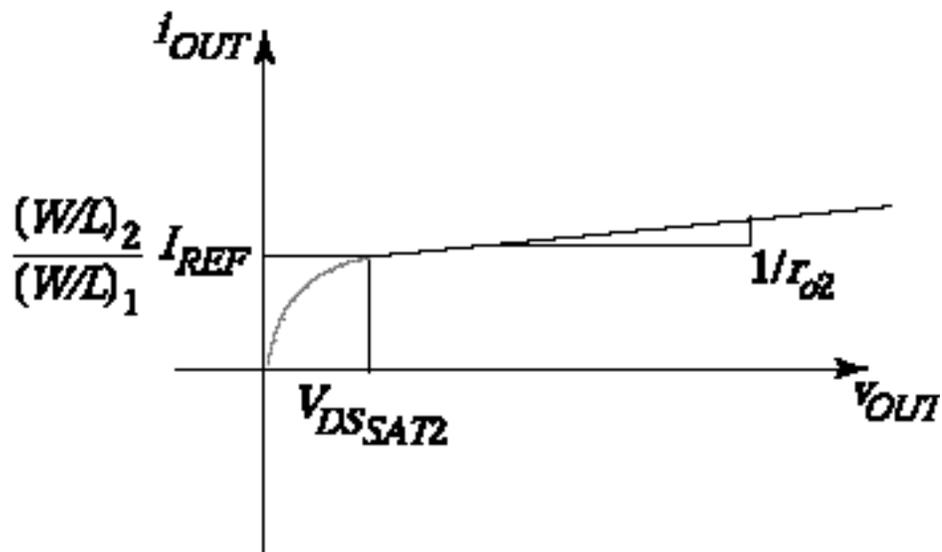
I-V characteristics of NMOS current source:



## PMOS Current Source


- NMOS current source sinks current to ground
- PMOS current source sources current from positive supply

PMOS Current Mirror:

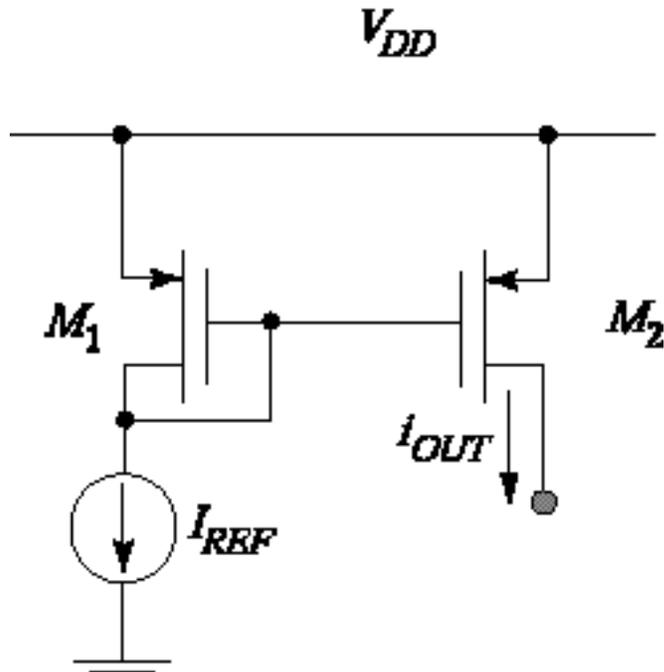

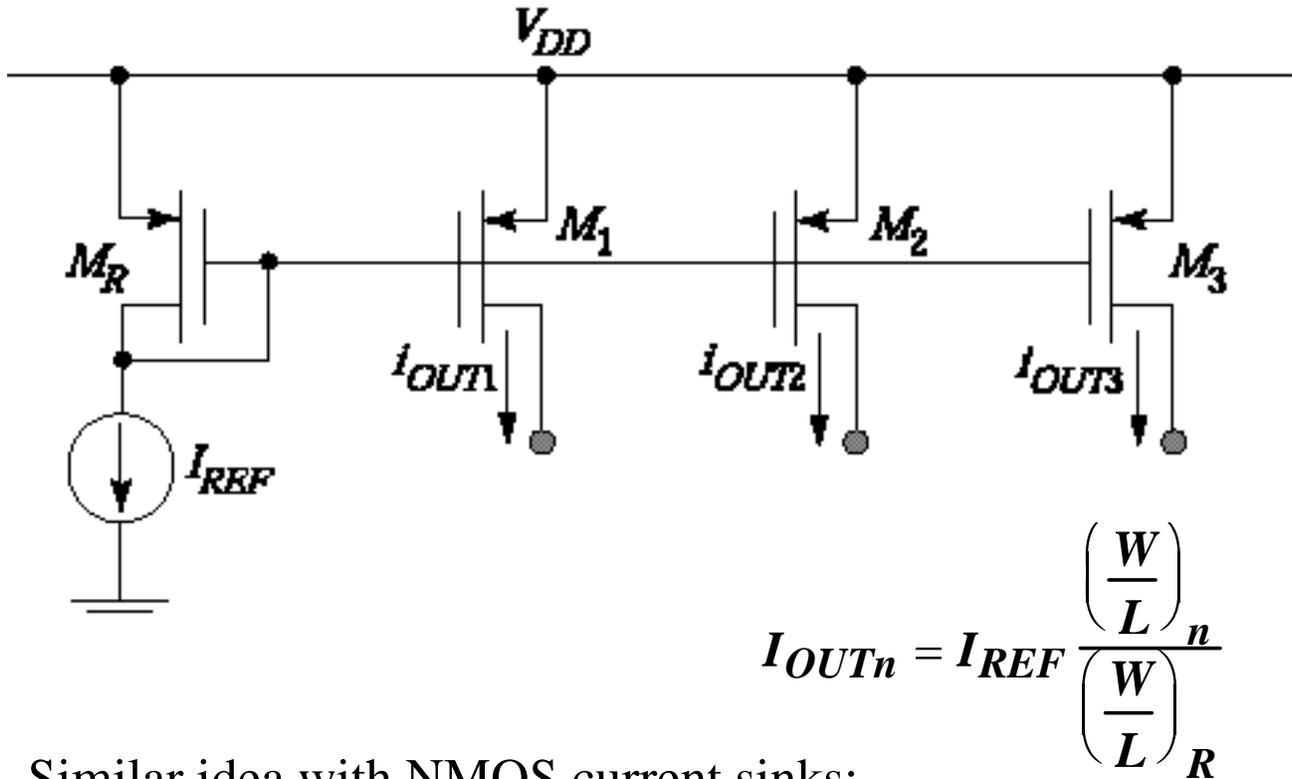
### 3. Multiple Current Sources

Since there is no DC gate current in MOSFET, we can tie up multiple current mirrors to single current source:




Similar idea with NMOS current sinks:

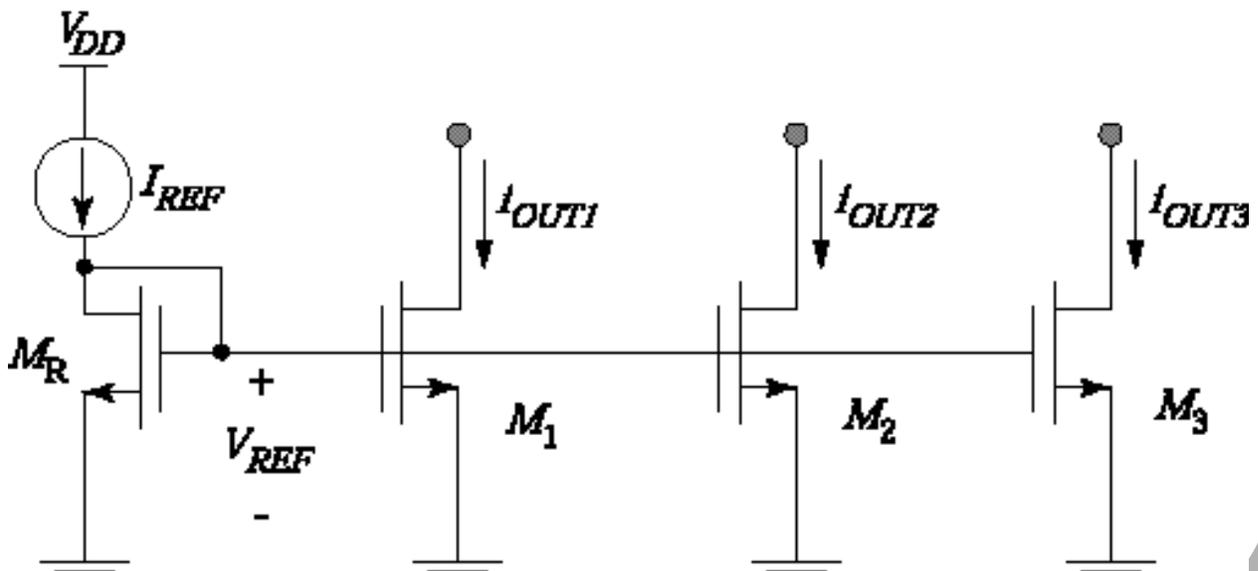
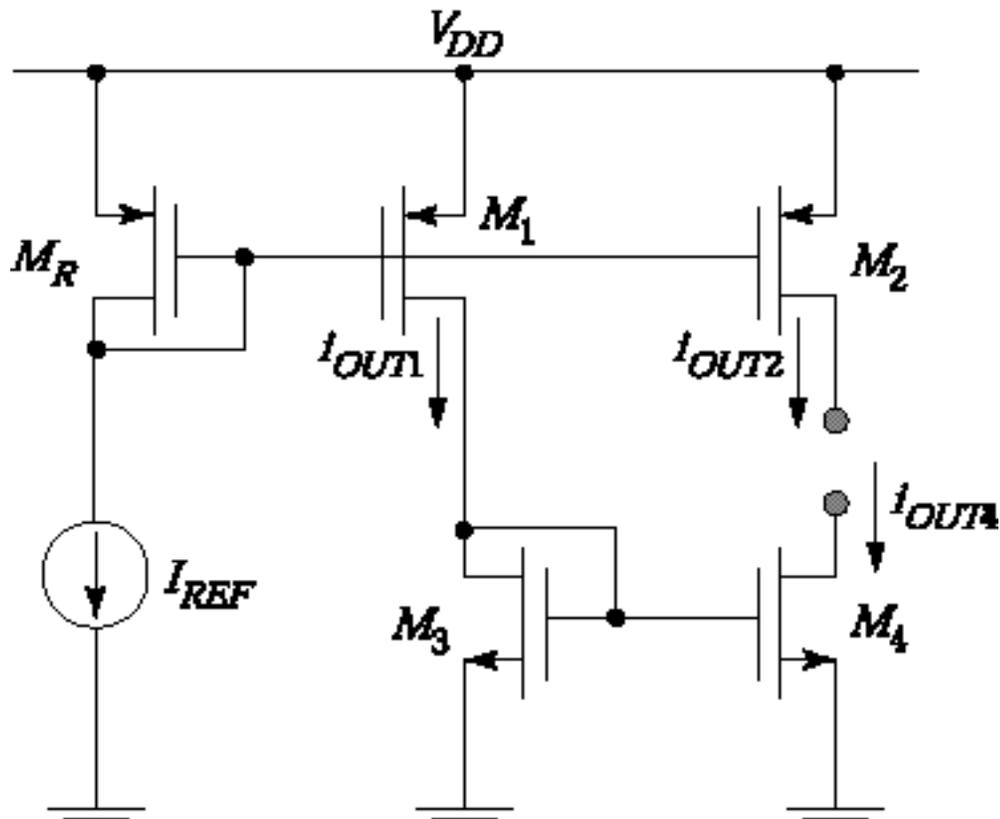
# Multiple Current Sources and Sinks

Often, in a given circuit, we need current sources and sinks. We can build them all out of a single current source.




$$I_{OUT1} = I_{REF} \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_R}$$

$$I_{OUT2} = I_{REF} \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_R}$$

$$I_{OUT4} = I_{OUT1} \frac{\left(\frac{W}{L}\right)_4}{\left(\frac{W}{L}\right)_3} = I_{REF} \frac{\left(\frac{W}{L}\right)_4 \left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_3 \left(\frac{W}{L}\right)_R}$$

# Generating $I_{REF}$

Simple circuit:

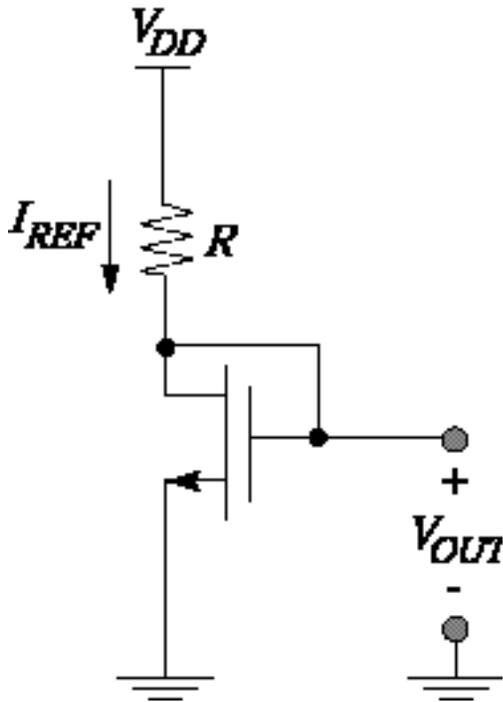

$$I_{REF} = \frac{V_{DD} - V_{OUT}}{R}$$

$$V_{OUT} = V_{Tn} + \sqrt{\frac{I_{REF}}{\frac{W}{2L} \mu_n C_{ox}}}$$

For large  $W/L$ : 
$$I_{REF} \approx \frac{V_{DD} - V_{Tn}}{R}$$

- Advantages
  - $I_{REF}$  set by value of resistor
- Disadvantages
  - $V_{DD}$  also affects  $I_{REF}$ .
  - $V_{Tn}$  and  $R$  are functions of temperature  $\Rightarrow I_{REF}(T)$ .

In the real world, more sophisticated circuits are used to generate  $I_{REF}$  that are  $V_{DD}$  and  $T$  independent.

# What did we learn today?

## Summary of Key Concepts

- *Voltage source* easily synthesized from **reference current source** using MOSFET in diode configuration
- *Current source* easily synthesized from *current source* using **current mirror** circuit.
- Multiple current sources and sinks with different magnitudes can be synthesized from a single current source.
- Voltage and current sources rely on the availability of well “matched” transistors in IC technology.