



# Selection of MOSFETs for DC/DC Synchronous Buck Controllers: SiP12201 Single 10 A Controller and SiP12203 Triple Step Down Controller IC for 2 Synchronous and 1 Linear Power Rail

## Simon Foley

This application note is intended to help designers select the best MOSFETs to use with the SiP12201 and SiP12203 synchronous buck dc-to-dc controller ICs.

The SiP12201 is a single 10 A controller (fig. 1a). The SiP12203 is a triple step down controller IC for 2 synchronous and 1 linear power rail (fig. 1b). Both have

an input voltage range of 4.2 V to 26 V, an output voltage range of 0.6 V to 20 V, and a 500 kHz fixed switching frequency. The dead time and MOSFET driving capabilities of both ICs are similar as well. Thus the choice of MOSFETs for a particular dc-to-dc conversion application will be similar for each IC.

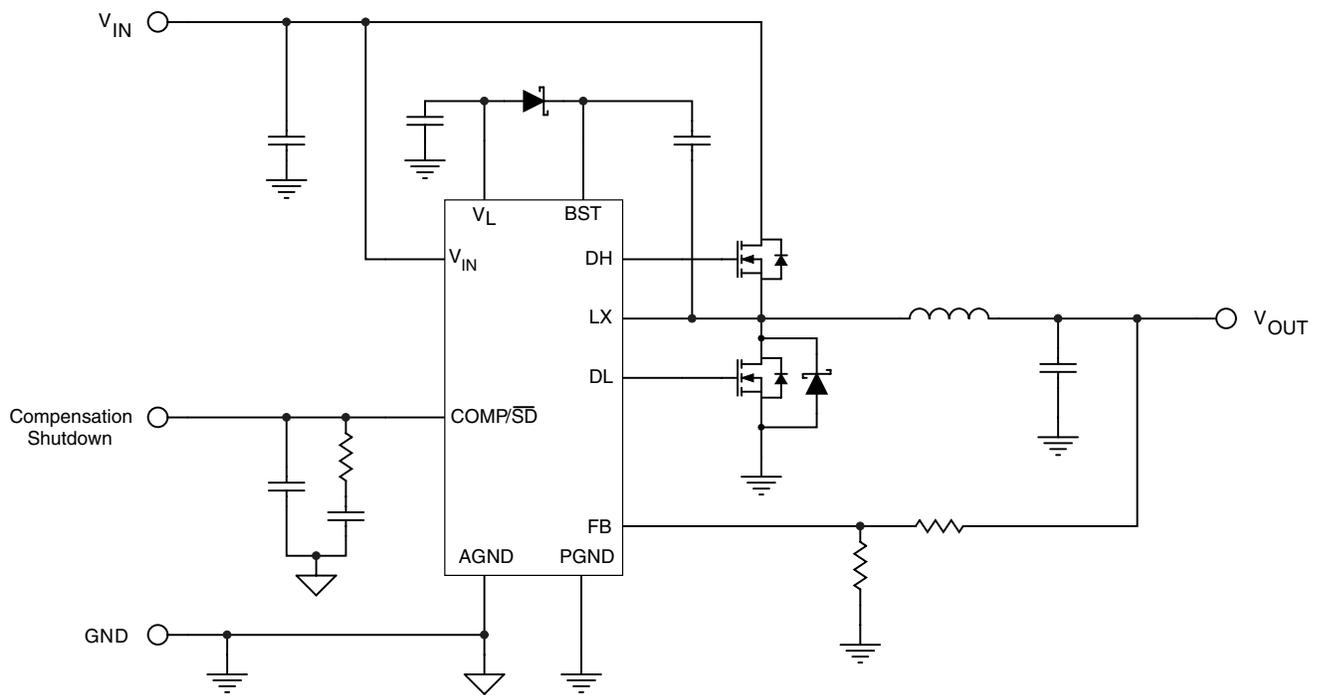


Fig. 1a

## Selection of MOSFETs for DC/DC Synchronous Buck Controllers: SiP12201 Single 10 A Controller and SiP12203 Triple Step Down Controller IC for 2 Synchronous and 1 Linear Power Rail

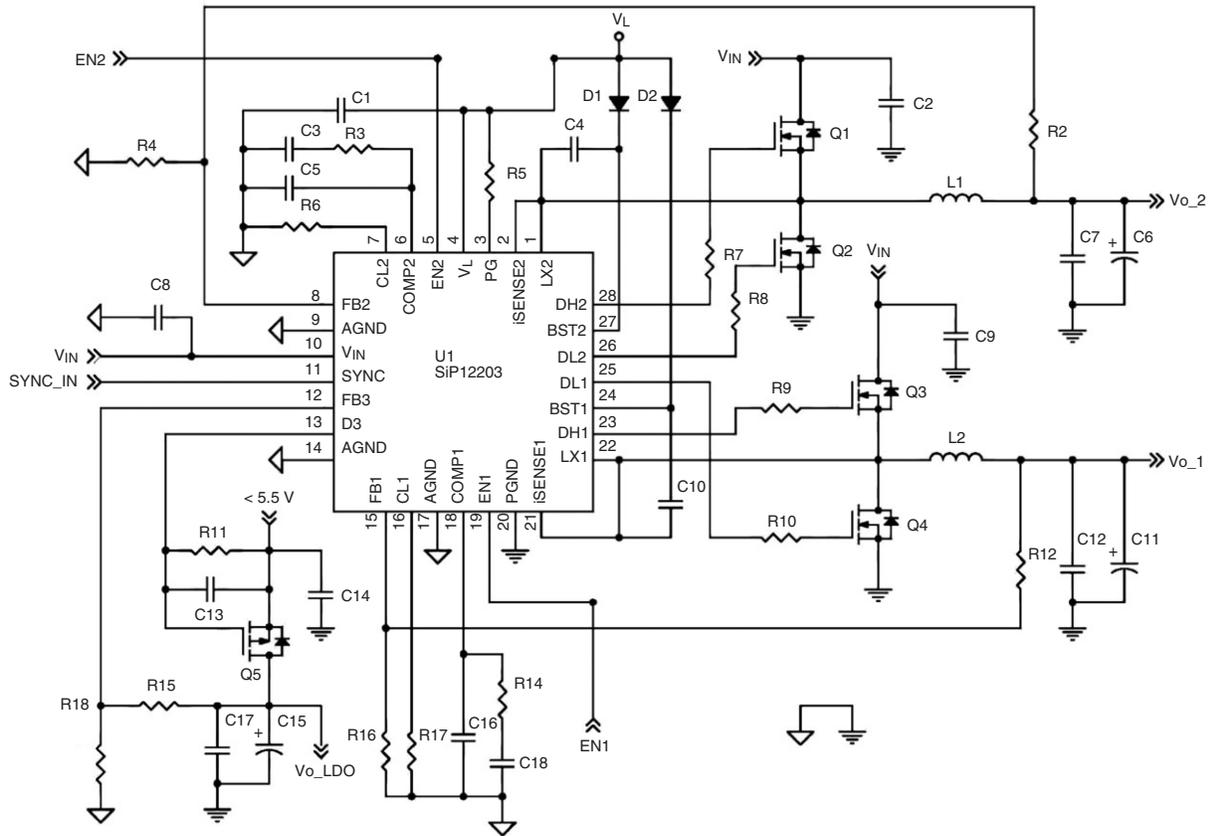


Fig. 1b

For the most efficient solution (duty cycle ( $\delta$ ) < 0.5), the high-side MOSFET would have the lowest  $Q_g$  and  $Q_{gd}$  rating (for the lowest  $V_I$  power losses) and the low-side MOSFET would have the lowest  $R_{DS(on)}$  and  $Q_{rr}$  rating (for the lowest  $I^2R$  losses). When the duty cycle is 0.5 then the  $R_{DS(on)}$  and  $Q_g$  values would be the same. However, this is not always practical, and the selection of high- and low-side MOSFETs thus depends on five key factors - input voltage, efficiency, size, output current, and cost. **AN607** and **AN608** covers gate losses and the switching characteristics of MOSFETs extensively.

- Input voltage** - this determines the max.  $V_{DS}$  of MOSFET needed.  
5 V input -  $V_{DS} = 12$  V or 20 V needed  
12 V input -  $V_{DS} = 20$  V, 25 V, or 30 V needed etc.....
- Efficiency** - switching losses  $V_I$  losses ( $Q_{gd}$ ) and conduction losses  $I^2R$  losses ( $R_{DS(on)}$ ). This is covered comprehensively in Vishay's application note **AN607**.
- Size** - this depends on the current output, duty cycle and thermal properties of the MOSFET ( $R_{th(j-c)}$ ) and pcb board ( $R_{th(c-a)}$ ).

- Output current** - this determines the package and  $R_{DS(on)}$  needed and is covered below in "Choosing the Correct MOSFET" below.
- Cost** - this depends on the package, die size, and production volume.

### CHOOSING THE CORRECT MOSFETS

Once the MOSFET  $V_{DS}$  is chosen from the input voltage range, there is now a huge range of MOSFETs to choose from. To narrow the choice, follow these steps, each of which is described in further detail below:

- Calculate the current requirement of the high- and low-side MOSFET. This will give an idea of smallest package needed.
- Consider and calculate the thermal values from junction to ambient.
- Calculate the maximum  $R_{DS(on)}$  for the MOSFET at the required  $V_{GS}$ , for the current handling required.
- Considering  $Q_g$ ,  $Q_{gs}$ ,  $Q_{gd}$  ratings for the high side MOSFET Q1.

## Selection of MOSFETs for DC/DC Synchronous Buck Controllers: SiP12201 Single 10 A Controller and SiP12203 Triple Step Down Controller IC for 2 Synchronous and 1 Linear Power Rail

5. Determine requirements for shoot-through immunity.
6. Choose a device that improves efficiency at higher switching frequencies and light loads.

### 1. Calculating the Current Requirement of the MOSFET: High Side (Q1) and Low Side (Q2)

Consider 12 V is converted to 3 V out at 10 A.

#### A. Calculating the Duty Cycle:

$$V_{OUT} = V_{IN} \times t_{(on)}/T = V_{IN} \delta$$

e.g. a 12 V input with 3 V output would have a  $\delta = 0.25$

#### B. Calculating the Current Requirement of the MOSFET:

High-side (controlling MOSFET) Q1 RMS current requirement =  $I_o \sqrt{\delta}$

e.g. RMS current = 10 A  $\times \sqrt{0.25} = 5$  A

Low-side (freewheel MOSFET) Q2 RMS current requirement =  $I_o \sqrt{1-\delta}$

e.g. RMS current = 10A  $\times \sqrt{1 - 0.25} = 8.66$  A

From this we can see that the smaller the duty cycle, the less RMS current the high-side MOSFET and the more the low-side MOSFET needs to handle.

The RMS current requirement will give you an idea of the package needed. The following specifications are package limited:


60 A = PowerPAK<sup>®</sup> SO-8 and PolarPAK<sup>®</sup>50 A = PowerPAK 1212-8

12 A = PowerPAK ChipFET<sup>®</sup>
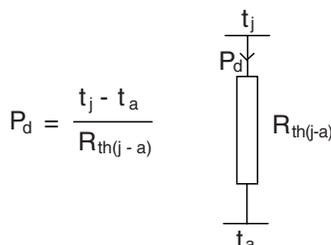
### 2. Consider and Calculate the Thermal Values from Junction To Ambient

Junction to ambient thermal rating ( $R_{th(j-a)}$ ) is the sum of the thermal rating junction to case ( $R_{th(j-c)}$ ) and case to ambient ( $R_{th(c-a)}$ ).  $R_{th(j-c)}$  can be found on the MOSFET datasheet. This rating is fixed. However, the  $R_{th(c-a)}$  depends on the pcb and amount of copper used. The lower the  $R_{th(j-a)}$ , the more current and more power dissipation the MOSFET can handle.\*

\*The only figures that are "arbitrary" are when manufacturers use different  $R_{th(j-a)}$  for calculations. Although nominally based on the data sheet on a 1" copper PCB variation in this value is often seen. The only true thermal ( $R_{th}$ ) figures to compare different MOSFETs is the junction to case rating ( $R_{th(j-c)}$ ).



### 3. Calculating the Max. $R_{DS(on)}$ at the required $V_{GS}$

The choice of  $R_{DS(on)}$  value will depend on your requirements for efficiency, cost, and size. The lower the  $R_{DS(on)}$ , the higher the cost of the MOSFET, but the more efficient the dc-to-dc conversion. The bigger the package, the bigger the die which can fit into the package and therefore the bigger packages have the lowest  $R_{DS(on)}$  ratings.

We first need to calculate the highest  $R_{DS(on)}$  for the application and consider that a lower  $R_{DS(on)}$  will offer a more efficient solution.

$$R_{DS(on) \text{ max.}} = \frac{t_j - t_a}{I^2_{\text{max.}} \times RK \times R_{th(j-a)} \times \delta \text{ K (duty cycle constant)}}$$

For a rough  $R_{DS(on)}$  this calculation can be used:

$$R_{DS(on) \text{ max.}} = \frac{t_j - t_a}{I^2_{\text{max.}} \times 1.7 \times R_{th(j-a)}}$$

- A.  $T_{amb}$  = ambient temperature (usually 25 °C for calculation)
- B. RK = increase in  $R_{DS(on)}$  factor with respect to temperature (normally 1.6 to 1.8) (fig. 2).
- C.  $R_{th(j-a)}$  = thermal impedance junction to ambient for the MOSFET - controlled by package type and pcb ( $R_{th(c-a)}$ ). There is a typical  $R_{th(j-a)}$  depending on the package preferred (fig. 3). Vishay recommends using the max.  $R_{th(j-a)}$  steady-state, to allow a safety margin.
- D. Max. junction temperature of the MOSFET (normally 150 °C).
- E.  $\delta$  K = normal thermal impedance duty cycle constant depending on pulse duration (fig. 4).

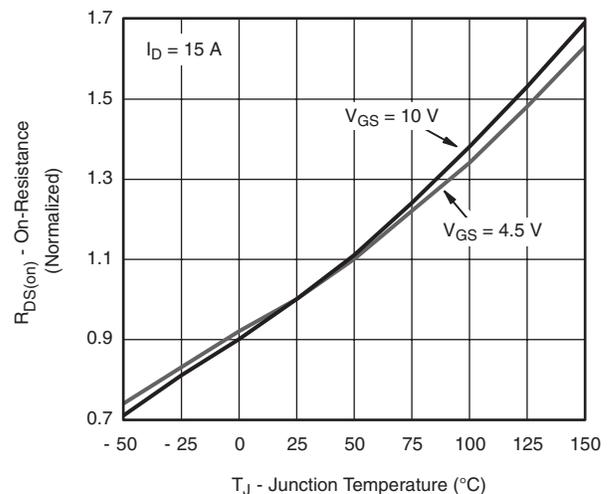


Fig. 2

## Selection of MOSFETs for DC/DC Synchronous Buck Controllers: SiP12201 Single 10 A Controller and SiP12203 Triple Step Down Controller IC for 2 Synchronous and 1 Linear Power Rail

THERMAL RESISTANCE RATINGS					
PARAMETER		SYMBOL	TYPICAL	MAXIMUM	UNIT
Maximum Junction-to-Ambient	$t \leq 10$ s	$R_{thJA}$	19	24	°C/W
Maximum Junction-to-Case (Drain)	Steady State	$R_{thJC}$	1.2	1.8	

Fig. 3

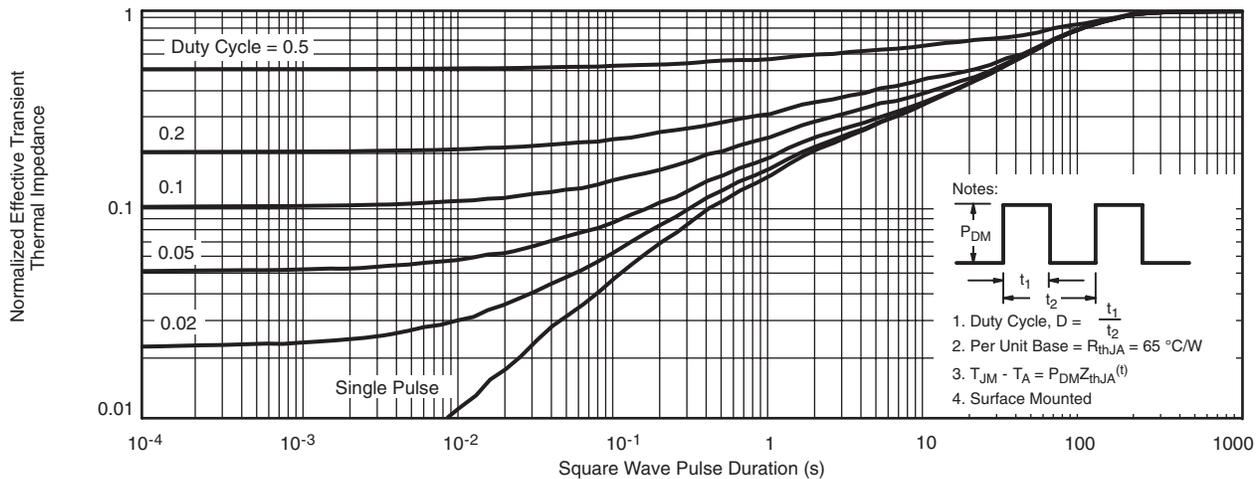


Fig. 4

Considering 12 V is converted to 3 V out at 10 A (50 °C ambient) and the low-side (freewheel MOSFET) RMS current requirement is 8.66 A

$$R_{DS(on) \text{ max.}} = \frac{150 - 50}{75 \times 1.7 \times 24}$$

$$R_{DS(on) \text{ max.}} = 32.7 \text{ m}\Omega$$

### 4. Using Gate Charge to Determine Switching Time

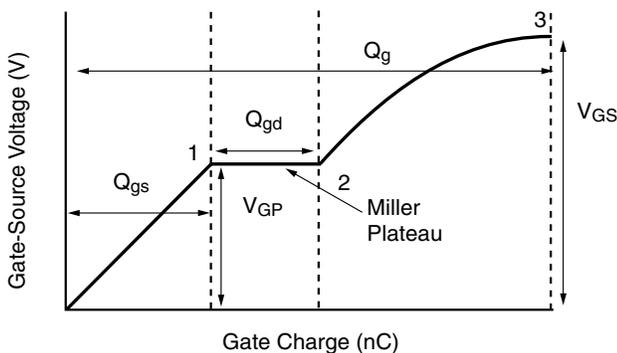


Fig. 5

Looking at the gate charge waveform in fig. 5,  $Q_{gs}$  is defined as the charge from the origin, to the start of the Miller Plateau  $V_{GP}$ .  $Q_{gd}$  is defined as the charge from  $V_{GP}$  to the end of the plateau.  $Q_g$  is defined from the origin, to the point on the curve at which the driving voltage equals the actual gate voltage of the device.

The rise in  $V_{GS}$  during  $t_2$  (fig. 5) is brought about by charging  $C_{gs}$  and  $C_{gd}$ . During this time  $V_{DS}$  does not change and as such  $C_{gd}$  and  $C_{gs}$  stay relatively constant, since they vary as a function of  $V_{DS}$ . At this time  $C_{gs}$  is generally larger than  $C_{gd}$  and therefore the majority of the drive current flows into  $C_{ds}$  rather than into  $C_{gd}$ . This current through  $C_{gd}$  and  $C_{ds}$  depends on the time derivative of the product of the capacitance and its voltage. The gate charge can therefore be assumed to be  $Q_{gs}$ .

The next part of the waveform is the Miller Plateau. It is generally accepted that the point at which the gate charge figure goes into the plateau region coincides with the peak value of the peak current. However, the knee in the gate charge depends on the product of  $C_{gd}V_{gd} = Q_{gd}$ , with respect to time. This means that there is a very small value of drain current and a large value of output impedance; thus the  $I_{DS}$  can actually reach its maximum value after the knee occurs.

Once the plateau is finished (when  $V_{DS}$  reaches its on-state value),  $C_{gd}$  becomes constant again and the bulk of the

## Selection of MOSFETs for DC/DC Synchronous Buck Controllers: SiP12201 Single 10 A Controller and SiP12203 Triple Step Down Controller IC for 2 Synchronous and 1 Linear Power Rail

current flows into  $C_{gs}$  again. The gradient is not as steep as it was in the first period ( $t_2$ ), because  $C_{gd}$  is much larger and closer in magnitude to that of  $C_{gs}$ .

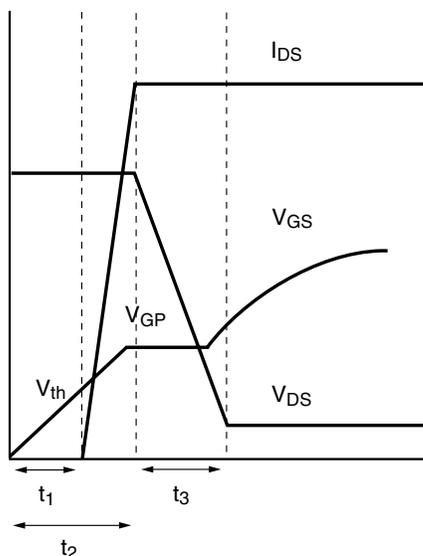


Fig. 6

### 5. Shoot-Through Immunity

The lower the  $Q_{gd}/Q_{gs}$  ratio in the low-side MOSFET, the more robust the synchronous buck will be to  $dV/dt$  shoot-through. A ratio of  $< 1$  is a good indicator.

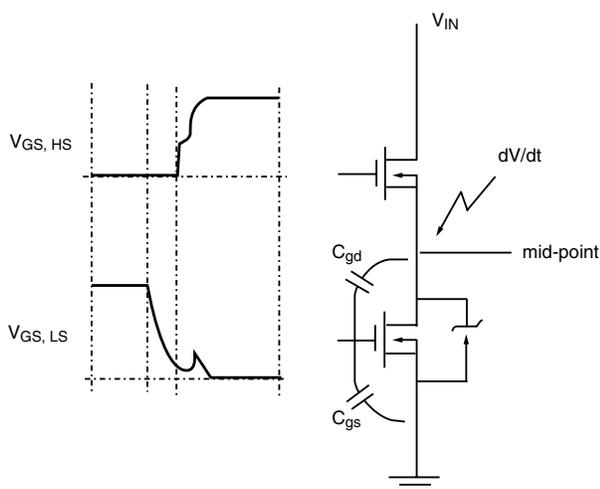


Fig. 7

### 6. Improving Efficiency at Higher Switching Frequencies and Light Loads

There is a demand for higher efficiency in point-of-load (POL) converters, especially at higher switching frequencies and light loads. One solution is to use a low-side MOSFET in parallel with a Schottky diode. This allows the current to flow through the diode before the low-side MOSFET turns on, reducing the losses of the body drain diode (bdd) in the MOSFET.

Vishay's SkyFET® Power MOSFETs combine the MOSFET and Schottky in one monolithic die, with two major benefits over two-component (MOSFET and Schottky) solutions. First, the power losses associated with the reverse-recovery current in the low-side MOSFET are defined as  $V_{IN} \times Q_{rr} \times f_{sw}$ . Therefore a reduction in  $Q_{rr}$  (reverse recovery charge) reduces the power losses, proportional to the switching frequency. The  $Q_{rr}$  of Vishay Siliconix SkyFETs is about 40 % lower than traditional trench MOSFETs.

Second, there is a time when the transformer current travels through the bdd, before the low-side MOSFET turns on. At this time, there will be power losses in the diode ( $P = VI$ ). Reducing the  $V_F$  of the body drain diode, reduces this power loss. Vishay's SkyFETs offer a 38 % reduction in  $V_F$  to 0.44 V, compared to 0.72 V for a standard TrenchFET.

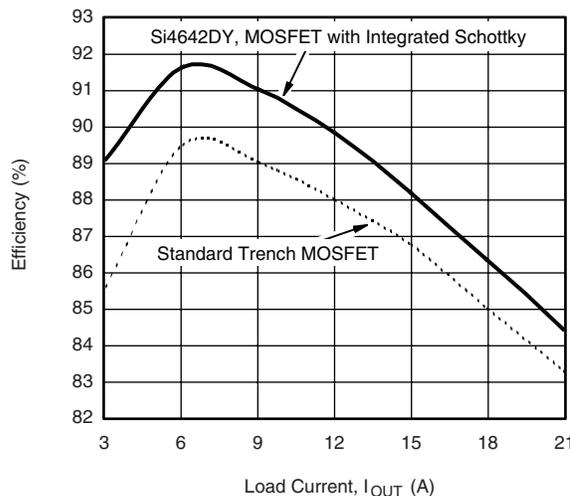


Fig. 8 MOSFET with Integrated Schottky as Low Side Switch Efficiency Performance Comparison, 300 kHz  $V_{IN} = 19$  V,  $V_{OUT} = 1.3$  V

At a 300 kHz switching frequency, the Si4624DY SkyFET, used as a low-side MOSFET, delivers improved efficiency compared to a standard trench MOSFET. (Fig. 8).

Figure 9 highlights the improvement of efficiency at 550 kHz.

## Selection of MOSFETs for DC/DC Synchronous Buck Controllers: SiP12201 Single 10 A Controller and SiP12203 Triple Step Down Controller IC for 2 Synchronous and 1 Linear Power Rail

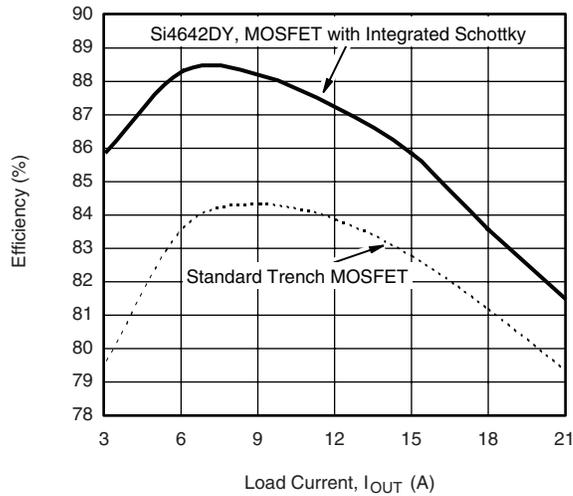


Fig. 9 - MOSFET with Integrated Schottky as Low Side Switch Efficiency Performance Comparison, 550 kHz  
 $V_{IN} = 19\text{ V}$ ,  $V_{OUT} = 1.3\text{ V}$

### SUGGESTED DUAL $V_{DS} = 30\text{ V}$ MOSFET FOR $< 6.5\text{ A}$ OUTPUT (PER CHANNEL)

DEVICE	PKG	POL	CONFIG.	$V_{DS}$ (V)	$V_{GS}$ (V)	$R_{DS(ON)}$ MAX. AT $V_{GS}$ (m $\Omega$ )	$Q_G$ TYP. AT 4.5 V (nC)	$Q_{GS}$ TYP. (nC)	$Q_{GD}$ TYP. (nC)
Si7994DP	PowerPAK SO8	Dual N	High Side	30	20	33	5	2.3	1.6
			Low Side						
Si7218DN	PowerPAK 1212-8	Dual N	High Side	30	20	33	5	2.3	1.6
			Low Side						
Si4816BDY	SO8	Dual N	High Side	30	20	22.5	7.8	2.9	2.3
			Low Side and Schottky						
Si4618DY	SO8	Dual N	High Side	30	12	19.5	12.5	4.1	3.4
			Low Side and Schottky						
Si4622DY	SO8	Dual N	High Side	30	20	18.6	19	8	6
			Low Side SKYFET						
Si4618DY	SO8	Dual N	High Side	30	20	22	10.5	5	2.5
			Low Side and Schottky						