

# Network Parameters

# Impedance and Admittance matrices

For n ports network we can relate the voltages and currents by impedance and admittance matrices

Impedance matrix

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{21} & \cdot & \cdot & Z_{n1} \\ Z_{12} & Z_{22} & \cdot & \cdot & Z_{n2} \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ Z_{1n} & Z_{2n} & \cdot & \cdot & Z_{nn} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \cdot \\ \cdot \\ I_n \end{bmatrix}$$

Admittance matrix

$$\begin{bmatrix} I_1 \\ I_2 \\ \cdot \\ \cdot \\ I_n \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{21} & \cdot & \cdot & Y_{n1} \\ Y_{12} & Y_{22} & \cdot & \cdot & Y_{n2} \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot & \cdot \\ Y_{1n} & Y_{2n} & \cdot & \cdot & Y_{nn} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \cdot \\ \cdot \\ V_n \end{bmatrix}$$

where  $[Y] = [Z]^{-1}$

# Reciprocal and Lossless Networks

**Reciprocal** networks usually contain nonreciprocal media such as ferrites or plasma, or active devices. We can show that the impedance and admittance matrices are symmetrical, so that.


$$Z_{ij} = Z_{ji} \text{ or } Y_{ij} = Y_{ji}$$

**Lossless** networks can be shown that  $Z_{ij}$  or  $Y_{ij}$  are imaginary

Refer to text book Pozar pg193-195
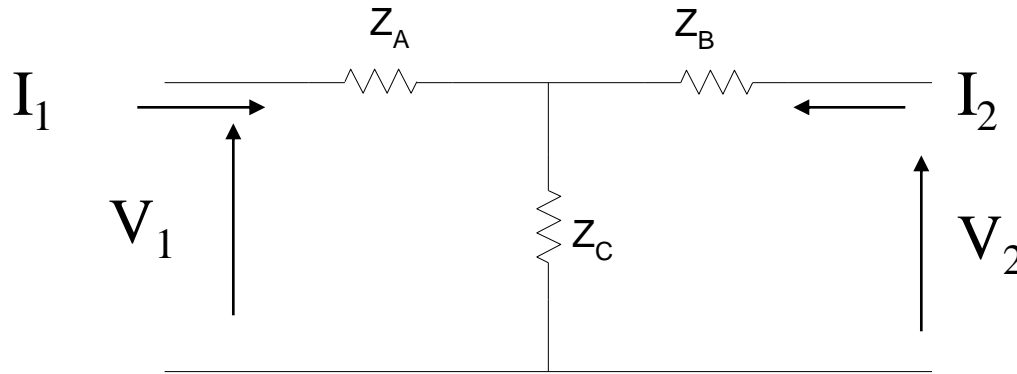
# Example

Find the Z parameters of the two-port T –network as shown below



Solution

Port 2 open-circuited

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_A + Z_C$$

Similarly we can show that

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_C$$


Port 1 open-circuited

This is an example of reciprocal network!!

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{V_2}{I_2} \frac{Z_C}{Z_B + Z_C} = (Z_B + Z_C) \frac{Z_C}{Z_B + Z_C} = Z_C$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_B + Z_C$$

# S-parameters

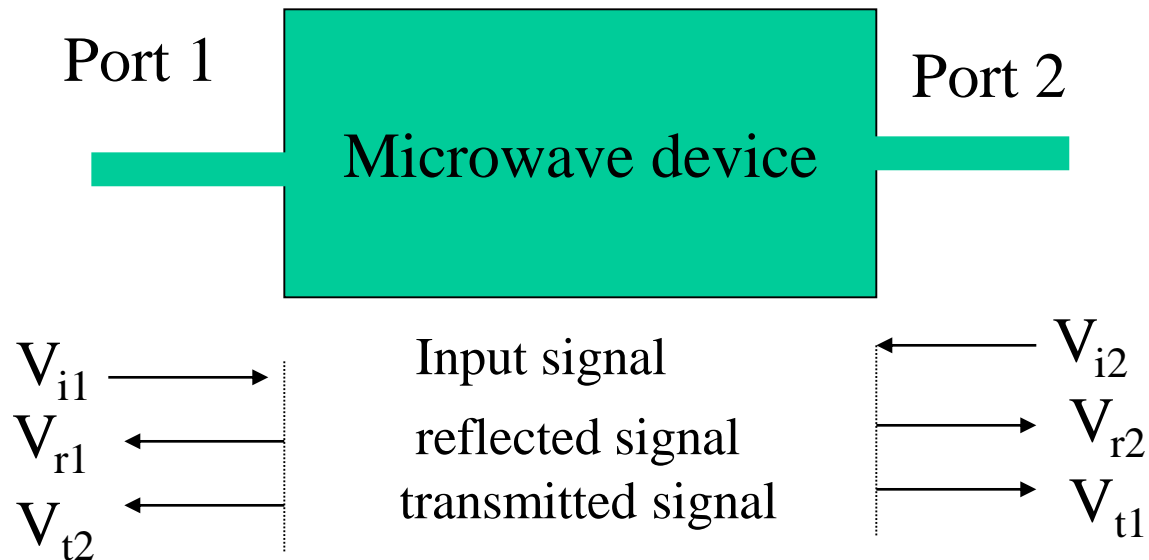

Transmission and reflection coefficients

$$\tau = \frac{V_t}{V_i}$$

$$\rho = \frac{V_r}{V_i}$$

# S-parameters

Voltage of traveling wave away from port 1 is

$$V_{b1} = \frac{V_{r1}}{V_{i1}} V_{i1} + \frac{V_{t2}}{V_{i2}} V_{i2}$$

Voltage of  
Reflected wave  
From port 1

Voltage of  
Transmitted wave  
From port 2

Voltage of transmitted wave away from port 2 is

$$V_{b2} = \frac{V_{t1}}{V_{i1}} V_{i1} + \frac{V_{r2}}{V_{i2}} V_{i2}$$

Let  $V_{b1} = b_1$ ,  $V_{i1} = a_1$ ,  $V_{i2} = a_2$ ,  $\rho_1 = \frac{V_{r1}}{V_{i1}}$ ,  $\tau_{12} = \frac{V_{t2}}{V_{i2}}$ ,  $\tau_{21} = \frac{V_{t1}}{V_{i1}}$

and  $\rho_2 = \frac{V_{r2}}{V_{i2}}$

Then we can rewrite

# S-parameters

Hence

$$b_1 = \rho_1 a_1 + \tau_{12} a_2$$

$$b_2 = \tau_{21} a_1 + \rho_2 a_2$$

In matrix form

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} \rho_1 & \tau_{12} \\ \tau_{21} & \rho_2 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

S-matrix

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

- $S_{11}$  and  $S_{22}$  are a measure of reflected signal at port 1 and port 2 respectively
- $S_{21}$  is a measure of gain or loss of a signal from port 1 to port 2.
- $S_{12}$  is a measure of gain or loss of a signal from port 2 to port 1.

Logarithmic form

$$S_{11} = 20 \log(\rho_1)$$

$$S_{22} = 20 \log(\rho_2)$$

$$S_{12} = 20 \log(\tau_{12})$$

$$S_{21} = 20 \log(\tau_{21})$$

# S-parameters

$$S_{11} = \left. \frac{V_{r1}}{V_{i1}} \right|_{V_{r2}=0}$$

$$S_{12} = \left. \frac{V_{t2}}{V_{i2}} \right|_{V_{r2}=0}$$

$V_{r2}=0$  means port 2 is matched


$$S_{21} = \left. \frac{V_{t1}}{V_{i1}} \right|_{V_{r1}=0}$$

$$S_{22} = \left. \frac{V_{r2}}{V_{i2}} \right|_{V_{r1}=0}$$

$V_{r1}=0$  means port 1 is matched




# Multi-port network

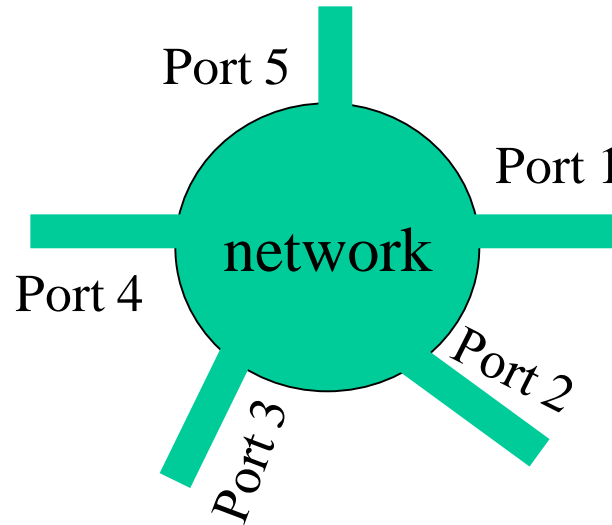

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \\ b_5 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} & S_{15} \\ S_{21} & S_{22} & S_{23} & S_{24} & S_{25} \\ S_{31} & S_{32} & S_{33} & S_{34} & S_{35} \\ S_{41} & S_{42} & S_{43} & S_{44} & S_{45} \\ S_{51} & S_{52} & S_{53} & S_{54} & S_{55} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \\ a_5 \end{bmatrix}$$
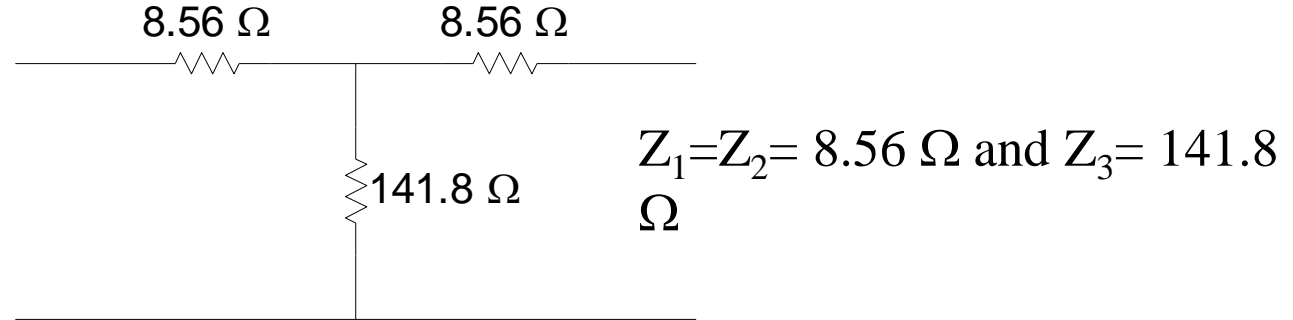
# Example

Below is a matched 3 dB attenuator. Find the S-parameter of the circuit.



Solution

$$S_{11} = \left. \frac{V_{r1}}{V_{i1}} \right|_{V_{r2}=0} = \rho = \frac{Z_{in} - Z_o}{Z_{in} + Z_o}$$

By assuming the output port is terminated by  $Z_o = 50 \, \Omega$ ,

then  $Z_{in} = Z_1 + [Z_3 \parallel (Z_2 + Z_o)]$


$$= 8.56 + [141.8(8.56 + 50) / (141.8 + 8.56 + 50)] = 50 \, \Omega$$

$$S_{11} = \frac{50 - 50}{50 + 50} = 0$$

Because of symmetry , then  $S_{22}=0$

# Continue

$$S_{21} = \left. \frac{V_{t2}}{V_{i2}} \right|_{V_{r2}=0}$$

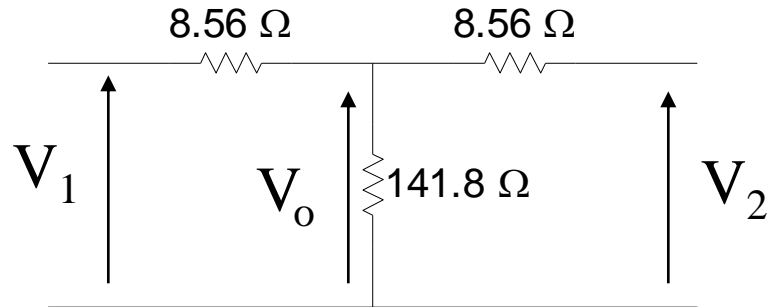

From the fact that  $S_{11}=S_{22}=0$ , we know that  $V_{r1}=0$  when port 2 is matched, and that  $V_{i2}=0$ . Therefore  $V_{i1}=V_1$  and  $V_{t2}=V_2$

$$\begin{aligned} V_{t2} = V_2 &= V_1 \left( \frac{Z_2 // Z_3}{Z_2 // Z_3 + Z_1} \right) \left( \frac{Z_o}{Z_3 + Z_o} \right) = V_o \left( \frac{Z_o}{Z_3 + Z_o} \right) \\ &= V_1 \left( \frac{41.44}{41.44 + 8.56} \right) \left( \frac{50}{50 + 8.56} \right) = 0.707 V_1 \end{aligned}$$

Therefore  $S_{12} = S_{21} = 0.707$

$$[S] = \begin{bmatrix} 0 & 0.707 \\ 0.707 & 0 \end{bmatrix}$$

# Lossless network

For lossless n-network , total input power = total output power. Thus

$$\sum_{i=1}^n a_i a_i^* = \sum_{i=1}^n b_i b_i^* \quad \text{Where } a \text{ and } b \text{ are the amplitude of the signal}$$

Putting in matrix form

$$\begin{aligned} a^t a^* &= b^t b^* \\ &= a^t S^t S^* a^* \end{aligned}$$

Note that  $b^t = a^t S^t$  and  $b^* = S^* a^*$

$$\text{Thus} \quad a^t (I - S^t S^*) a^* = 0 \quad \text{This implies that} \quad S^t S^* = I$$

Called unitary matrix

In summation form

$$\sum_{k=1}^n S_{ki} S_{kj}^* = \begin{cases} 1 & \text{for } i = j \\ 0 & \text{for } i \neq j \end{cases}$$

# Conversion of Z to S and S to Z

$$[S] = ([Z] + [U])^{-1}([Z] - [U])$$

$$[Z] = ([U] - [S])^{-1}([U] + [S])$$

where

$$[U] = \begin{bmatrix} 1 & 0 & . & 0 \\ 0 & . & . & . \\ . & . & 1 & . \\ 0 & . & . & 1 \end{bmatrix}$$

# Reciprocal and symmetrical network

Since the  $[U]$  is diagonal , thus  $[U] = [U]^t$

For reciprocal network

$$[Z] = [Z]^t$$

Since  $[Z]$  is symmetry

Thus it can be shown that

$$[S] = [S]^t$$

# Example

A certain two-port network is measured and the following scattering matrix is obtained:

$$[S] = \begin{bmatrix} 0.1 \angle 0^\circ & 0.8 \angle 90^\circ \\ 0.8 \angle 90^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

From the data, determine whether the network is reciprocal or lossless. If a short circuit is placed on port 2, what will be the resulting return loss at port 1?

## Solution

Since  $[S]$  is symmetry, the network is reciprocal. To be lossless, the  $S$  parameters must satisfy

$$\sum_{k=1}^n S_{ki} S_{kj}^* = \begin{cases} 1 & \text{for } i = j \\ 0 & \text{for } i \neq j \end{cases}$$

For  $i=j$

$$|S_{11}|^2 + |S_{12}|^2 = (0.1)^2 + (0.8)^2 = 0.65$$


Since the summation is not equal to 1, thus it is not a lossless network.

# continue

Reflected power at port 1 when port 2 is shorted can be calculated as follow and the fact that  $a_2 = -b_2$  for port 2 being short circuited, thus

$$b_1 = S_{11}a_1 + S_{12}a_2 = S_{11}a_1 - S_{12}b_2 \quad (1)$$
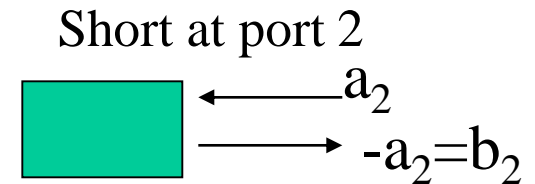
$$b_2 = S_{21}a_1 + S_{22}a_2 = S_{21}a_1 - S_{22}b_2 \quad (2)$$



From (2) we have

$$b_2 = \frac{S_{21}}{1 + S_{22}} a_1 \quad (3)$$

Dividing (1) by  $a_1$  and substitute the result in (3), we have

$$\rho = \frac{b_1}{a_1} = S_{11} - S_{12} \frac{b_2}{a_1} = S_{11} - \frac{S_{12}S_{21}}{1 + S_{22}} = 0.1 - \frac{(j0.8)(j0.8)}{1 + 0.2} = 0.633$$

$$\text{Return loss} \quad -20 \log \rho = -20 \log(0.633) = 3.97 \text{ dB}$$



# ABCD parameters



Voltages and currents in a general circuit

$$I_2 \propto V_2 - V_1 \quad V_2 \propto I_1 - I_2$$

This can be written as

$$V_1 \propto V_2 - I_2 \quad I_1 \propto V_2 + I_2$$

Or

$$V_1 = AV_2 - BI_2 \quad I_1 = CV_2 - DI_2$$


A -ve sign is included in the definition of D

In matrix form

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Given  $V_1$  and  $I_1$ ,  $V_2$  and  $I_2$  can be determined if ABCD matrix is known.

# Cascaded network

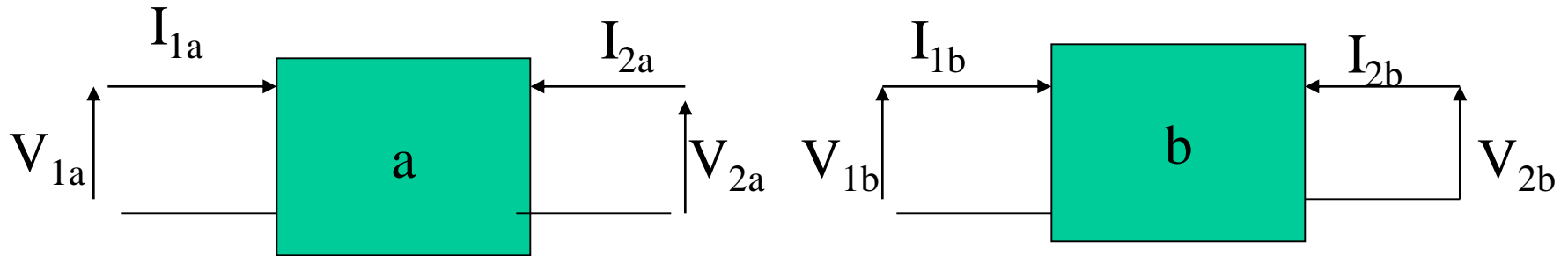

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

However  $V_{2a} = V_{1b}$  and  $-I_{2a} = I_{1b}$  then

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

The main use of ABCD matrices are for chaining circuit elements together

Or just convert to one matrix

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

Where

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

# Determination of ABCD parameters


$$V_1 = AV_2 - BI_2 \qquad I_1 = CV_2 - DI_2$$

Because A is independent of B, to determine A put  $I_2$  equal to zero and determine the voltage gain  $V_1/V_2=A$  of the circuit. In this case port 2 must be open circuit.

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit} \qquad B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit} \qquad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

# ABCD matrix for series impedance

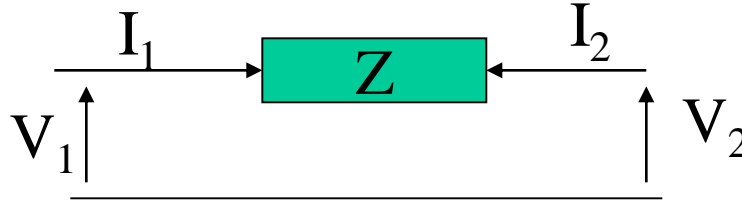

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

$$V_1 = V_2 \text{ hence } A=1$$

$$V_1 = -I_2 Z \text{ hence } B=Z$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$


$$I_1 = -I_2 = 0 \text{ hence } C=0$$

$$I_1 = -I_2 \text{ hence } D=1$$

The full ABCD matrix can be written

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

# ABCD for T impedance network

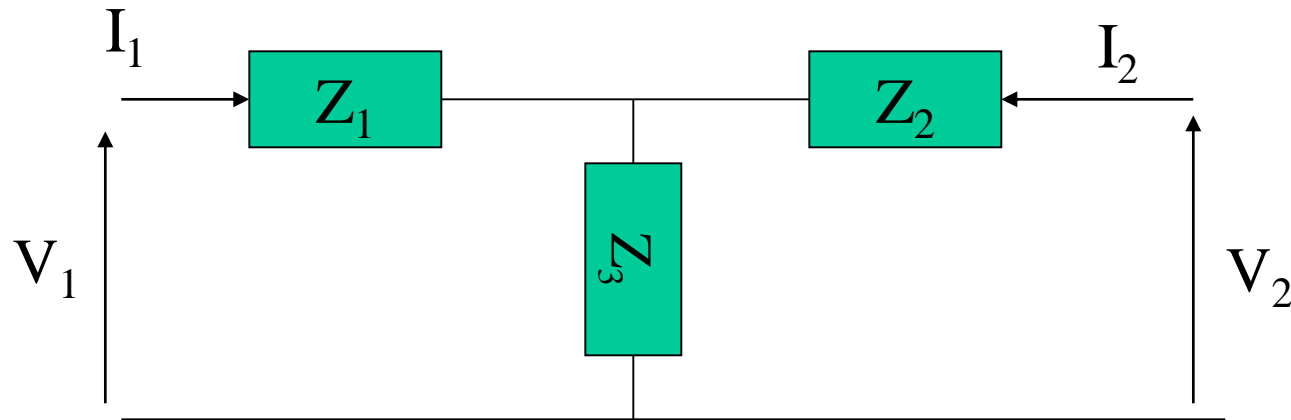

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit}$$

then

$$V_2 = \frac{Z_3}{Z_1 + Z_3} V_1$$

therefore

$$A = \frac{V_1}{V_2} = \frac{Z_1 + Z_3}{Z_3} = 1 + \frac{Z_1}{Z_3}$$

# Continue


$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

Solving for voltage in  $Z_2$

$$V_{Z_2} = \frac{\frac{Z_2 Z_3}{Z_2 + Z_3}}{Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3}} V_1$$

But

$$V_{Z_2} = -I_2 Z_2$$

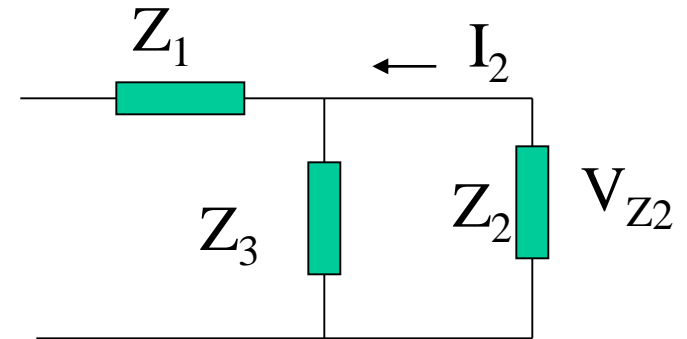


Hence

$$B = \frac{V_1}{-I_2} = Z_2 + Z_1 + \frac{Z_1 Z_2}{Z_3}$$

# Continue

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit}$$

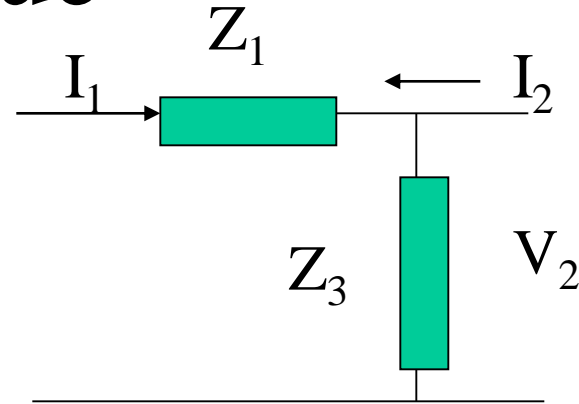

Analysis

$$-I_2 = I_1$$

$$V_2 = -I_2 Z_3 = I_1 Z_3$$

Therefore

$$C = \frac{I_1}{V_2} = \frac{1}{Z_3}$$

# Continue


$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

$I_1$  is divided into  $Z_2$  and  $Z_3$ , thus

$$I_2 = \frac{-Z_3}{Z_2 + Z_3} I_1$$

Hence
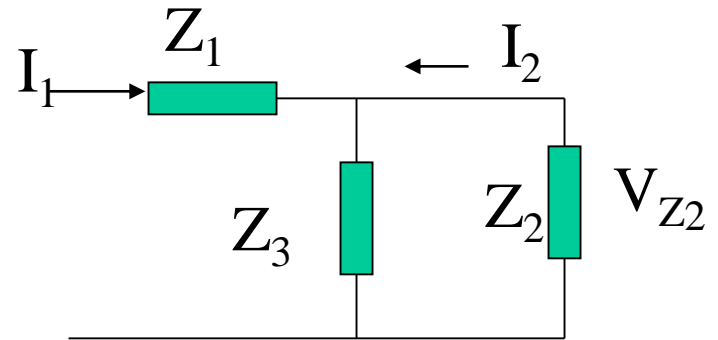
$$D = \frac{I_1}{-I_2} = 1 + \frac{Z_2}{Z_3}$$




Full matrix

$$\begin{bmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3} \\ \frac{1}{Z_3} & 1 + \frac{Z_2}{Z_3} \end{bmatrix}$$



# ABCD for transmission line

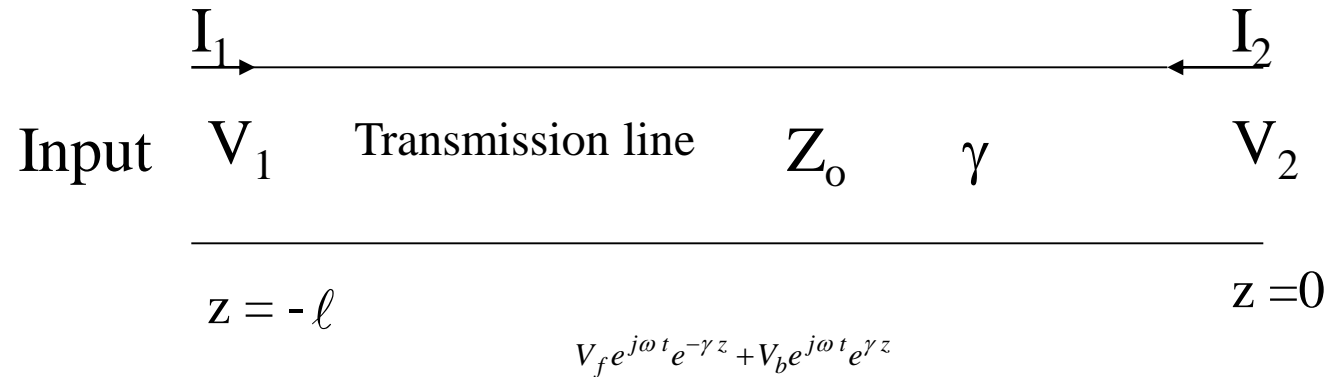

For transmission line

$$V(z) = V_f e^{j\omega t} e^{-\gamma z} + V_b e^{j\omega t} e^{\gamma z}$$

$$Z_o = \frac{V_f}{I_f} = \frac{V_b}{I_b}$$

$$I(z) = \frac{1}{Z_o} (V_f e^{j\omega t} e^{-\gamma z} - V_b e^{j\omega t} e^{\gamma z})$$

f and b represent forward and backward propagation voltage and current Amplitudes. The time varying term can be dropped in further analysis.

# continue

At the input  $z = -\ell$

$$V_1 = V(-\ell) = V_f e^{+\gamma \ell} + V_b e^{-\gamma \ell} \quad (1) \quad I_1 = I(-\ell) = \frac{1}{Z_o} (V_f e^{\gamma \ell} - V_b e^{-\gamma \ell}) \quad (2)$$

At the output  $z = 0$

$$V_2 = V(0) = V_f + V_b \quad (3) \quad I_2 = I(0) = \frac{1}{Z_o} (V_f - V_b) \quad (4)$$

Now find A,B,C and D using the above 4 equations

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit}$$

For  $I_2 = 0$  Eq.( 4 ) gives  $V_f = V_b = V_o$  giving

# continue

From Eq. (1) and (3) we have

$$A = \frac{V_o(e^{\gamma \ell} + e^{-\gamma \ell})}{2V_o} = \cosh(\gamma \ell)$$

---

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

For  $V_2 = 0$ , Eq. (3) implies  $-V_f = V_b = V_o$ . From Eq. (1) and (4) we have

$$B = \frac{Z_o V_o(e^{\gamma \ell} - e^{-\gamma \ell})}{2V_o} = Z_o \sinh(\gamma \ell)$$

Note that

$$\cosh(x) = \frac{(e^x + e^{-x})}{2}$$

$$\sinh(x) = \frac{(e^x - e^{-x})}{2}$$

# continue

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \text{for port 2 open circuit}$$

For  $I_2=0$  , Eq. (4) implies  $V_f = V_b = V_o$  . From Eq.(2) and (3) we have

$$C = \frac{V_o(e^{\gamma \ell} - e^{-\gamma \ell})}{2V_o Z_o} = \frac{\sinh(\gamma \ell)}{Z_o}$$

---

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} \quad \text{for port 2 short circuit}$$

For  $V_2=0$  , Eq. (3) implies  $V_f = -V_b = V_o$  . From Eq.(2) and (4) we have

$$D = \frac{-Z_o V_o(e^{\gamma \ell} + e^{-\gamma \ell})}{-2Z_o V_o} = \cosh(\gamma \ell)$$

# continue

The complete matrix is therefore

$$\begin{bmatrix} \cosh(\gamma \ell) & Z_o \sinh(\gamma \ell) \\ \frac{\sinh(\gamma \ell)}{Z_o} & \cosh(\gamma \ell) \end{bmatrix}$$

When the transmission line is lossless this reduces to

$$\begin{bmatrix} \cos(k \ell) & jZ_o \sin(k \ell) \\ j \frac{\sin(k \ell)}{Z_o} & \cos(k \ell) \end{bmatrix}$$

Note that

$$\gamma = \alpha + jk$$

Where

$\alpha$ = attenuation

$k$ =wave propagation  
constant

Lossless line

$$\alpha = 0$$

$$\cosh(jk \ell) = \cos(k \ell)$$

$$\sinh(jk \ell) = j \sin(k \ell)$$

# Table of ABCD network

Transmission line

$$\begin{bmatrix} \cosh(\gamma \ell) & Z_o \sinh(\gamma \ell) \\ \frac{\sinh(\gamma \ell)}{Z_o} & \cosh(\gamma \ell) \end{bmatrix}$$


$Z$   
Series impedance

$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$


$Z$  Shunt impedance

$$\begin{bmatrix} 1 & 0 \\ \frac{1}{Z} & 1 \end{bmatrix}$$


# Table of ABCD network

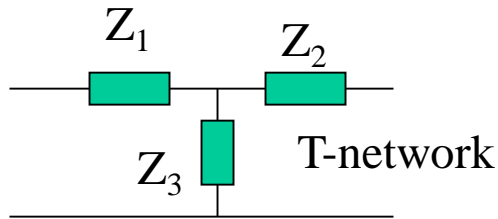
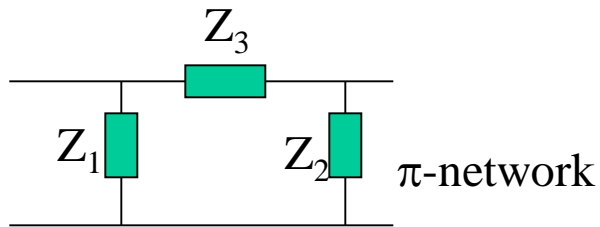
$$\begin{bmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3} \\ \frac{1}{Z_3} & 1 + \frac{Z_2}{Z_3} \end{bmatrix}$$


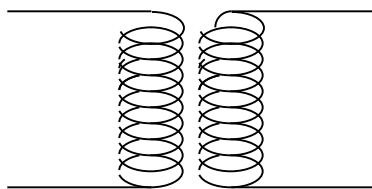
$$\begin{bmatrix} 1 + \frac{Z_3}{Z_2} & Z_3 \\ \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{Z_3}{Z_1 Z_2} & 1 + \frac{Z_3}{Z_1} \end{bmatrix}$$



n:1

$$\begin{bmatrix} n & 0 \\ 0 & \frac{1}{n} \end{bmatrix}$$

Ideal transformer

# Short transmission line

Lossless transmission line  $ABCD|_{tline} = \begin{bmatrix} \cos(k \ell) & jZ_o \sin(k \ell) \\ j \frac{\sin(k \ell)}{Z_o} & \cos(k \ell) \end{bmatrix}$

If  $\ell \ll \lambda$  then  $\cos(k\ell) \simeq 1$  and  $\sin(k\ell) \simeq k\ell$  then

$$ABCD|_{tlineshort} = \begin{bmatrix} 1 & jZ_o k \ell \\ j \frac{1}{Z_o} k \ell & 1 \end{bmatrix}$$



# Embedded short transmission line



$$ABCD|_{embed} = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z_1} & 1 \end{bmatrix} \begin{bmatrix} 1 & jZ_o k \ell \\ j \frac{1}{Z_o} k \ell & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{Z_1} & 1 \end{bmatrix}$$

Solving, we have

$$ABCD|_{embed} = \begin{bmatrix} 1 + \frac{jZ_o k \ell}{Z_1} & jZ_o k \ell \\ \frac{2}{Z_1} + \frac{jZ_o k \ell}{Z_1^2} + j \frac{k \ell}{Z_o} & 1 + \frac{jZ_o k \ell}{Z_1} \end{bmatrix}$$

# Comparison with $\pi$ -network

$$ABCD_{\pi-net} = \begin{bmatrix} 1 + \frac{Z_3}{Z_2} & Z_3 \\ \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{Z_3}{Z_1 Z_2} & 1 + \frac{Z_3}{Z_1} \end{bmatrix}$$

$$ABCD|_{embed} = \begin{bmatrix} 1 + \frac{jZ_o k \ell}{Z_1} & jZ_o k \ell \\ \frac{2}{Z_1} + \frac{jZ_o k \ell}{Z_1^2} + j \frac{k \ell}{Z_o} & 1 + \frac{jZ_o k \ell}{Z_1} \end{bmatrix}$$

It is interesting to note that if we substitute in ABCD matrix in  $\pi$ -network,  $Z_2=Z_1$  and  $Z_3=jZ_o k \ell$  we see that the difference is in C element where we have extra term i.e  $j \frac{k \ell}{Z_o}$

Both are almost same if  $\frac{Z_o k \ell}{Z_1^2} \gg \frac{k \ell}{Z_o}$

So the transmission line exhibit a  $\pi$ -network

# Comparison with series and shunt

## Series

If  $Z_o \gg Z_1$  then the series impedance  $Z = jZ_o k \ell$

This is an inductance which is given by  $L = \frac{Z_o \ell}{c}$



Where  $c$  is a velocity of light

## Shunt

If  $Z_o \ll Z_1$  then the series impedance  $Z = j \frac{k \ell}{Z_o}$

This is a capacitance which is given by  $C = \frac{\ell}{Z_o c}$

# Equivalent circuits

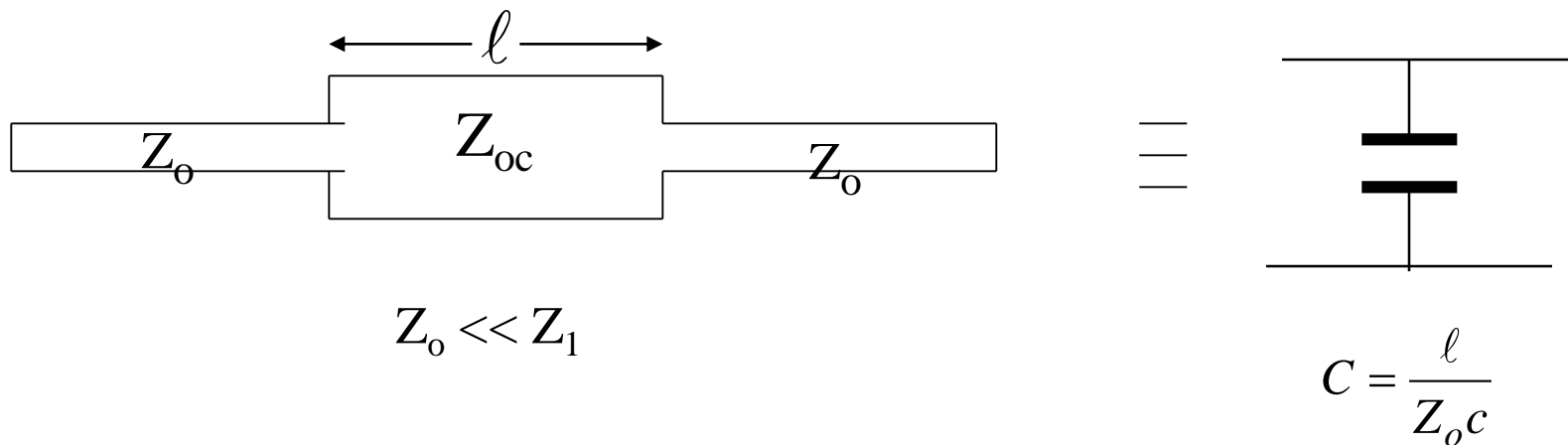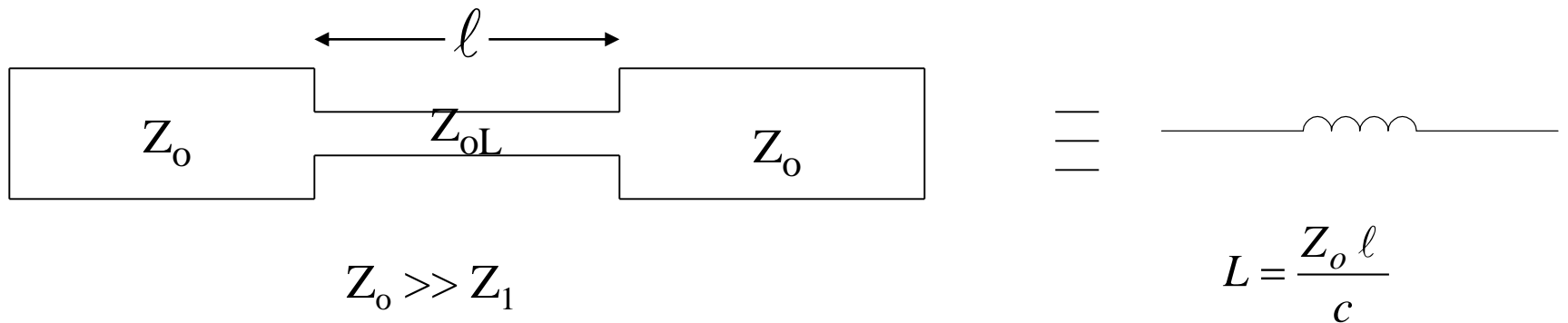

# Transmission line parameters

It is interesting that the characteristic impedance and propagation constant of a transmission line can be determined from ABCD matrix as follows

$$Z_o = \sqrt{\frac{B}{C}}$$

$$\gamma = \frac{1}{\ell} \cosh^{-1}(A) = \frac{1}{\ell} \ln \left( A \pm \sqrt{A^2 - 1} \right)$$

# Conversion S to ABCD

For conversion of ABCD to S-parameter

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \frac{1}{Z_o A + B + Z_o^2 C + Z_o D} \begin{bmatrix} Z_o A + B - Z_o^2 C - Z_o D & 2Z_o (AD - BC) \\ 2Z_o & -Z_o A + B - Z_o^2 C + Z_o D \end{bmatrix}$$

For conversion of S to ABCD-parameter

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{2S_{21}} \begin{bmatrix} (1 + S_{11})(1 - S_{22}) + S_{12}S_{21} & Z_o((1 + S_{11})(1 + S_{22}) - S_{12}S_{21}) \\ \frac{1}{Z_o}((1 - S_{11})(1 - S_{22}) - S_{12}S_{21}) & (1 - S_{11})(1 + S_{22}) + S_{12}S_{21} \end{bmatrix}$$

$Z_o$  is a characteristic impedance of the transmission line connected to the ABCD network, usually 50 ohm.

# MathCAD functions for conversion

For conversion of ABCD to S-parameter

$$S(A) = \frac{1}{Z.A_{1,1} + A_{1,2} + Z.Z.A_{2,1} + Z.A_{2,2}} \begin{bmatrix} Z.A_{1,1} + A_{1,2} - Z.Z.A_{2,1} - Z.A_{2,2} & 2.Z.(A_{1,1}.A_{2,2} - A_{1,2}.A_{2,1}) \\ 2.Z & -Z.A_{1,1} + A_{1,2} - Z.Z.A_{2,1} + Z.A_{2,2} \end{bmatrix}$$

For conversion of S to ABCD-parameter

$$A(S) = \frac{1}{2.S_{2,1}} \cdot \begin{bmatrix} (1 + S_{1,1})(1 - S_{2,2}) + S_{1,2}.S_{2,1} & Z.((1 + S_{1,1})(1 + S_{2,2}) - S_{1,2}.S_{2,1}) \\ \left(\frac{1}{Z_o}\right).((1 - S_{1,1})(1 - S_{2,2}) - S_{1,2}.S_{2,1}) & (1 - S_{1,1})(1 + S_{2,2}) + S_{1,2}.S_{2,1} \end{bmatrix}$$


# Odd and Even Mode Analysis

**Usually use for analyzing a symmetrical four port network**

- (1) Excitation
  - Equal ,in phase excitation – even mode
  - Equal ,out of phase excitation – odd mode
- (2) Draw intersection line for symmetry and apply
  - short circuit for odd mode
  - Open circuit for even mode
- (3) Also can apply EM analysis of structure
  - Tangential E field zero – odd mode
  - Tangential H field zero – even mode
- (4) Single excitation at one port= even mode + odd mode



# Example 1

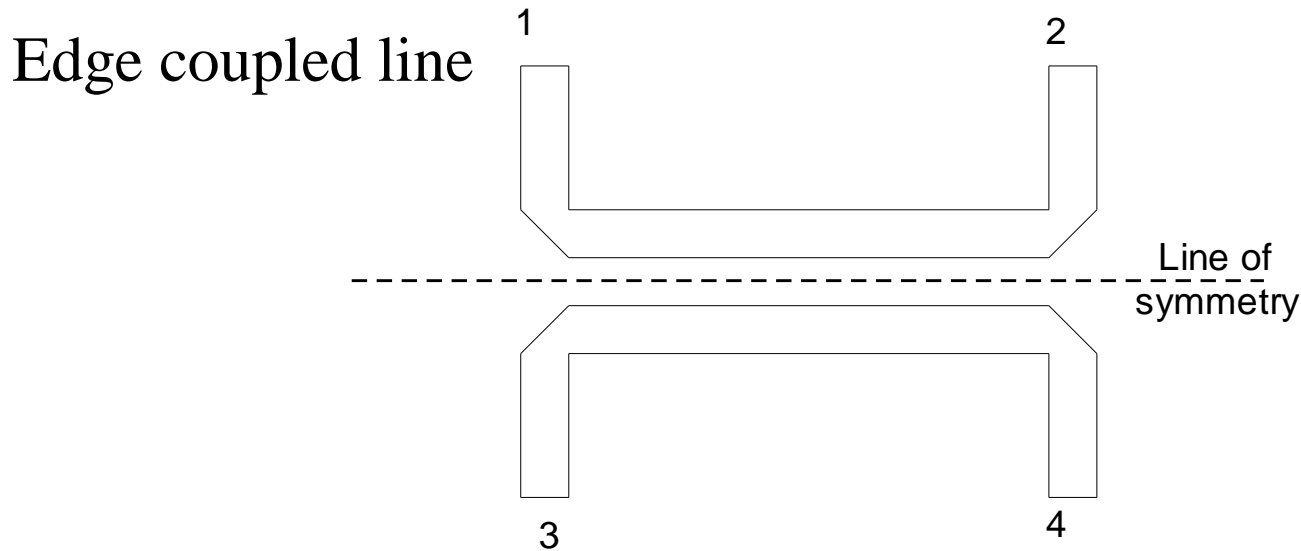

The matrix contains the odd and even parts

$$[S] = \frac{1}{2} \begin{bmatrix} S_{11ev} + S_{11od} & S_{12ev} + S_{12od} & S_{13ev} - S_{13od} & S_{14ev} - S_{14od} \\ S_{21ev} + S_{21od} & S_{22ev} + S_{22od} & S_{23ev} - S_{23od} & S_{24ev} - S_{24od} \\ S_{31ev} - S_{31od} & S_{32ev} - S_{32od} & S_{33ev} + S_{33od} & S_{34ev} + S_{34od} \\ S_{41ev} - S_{41od} & S_{42ev} - S_{42od} & S_{43ev} + S_{43od} & S_{44ev} + S_{44od} \end{bmatrix}$$

Since the network is symmetry, Instead of 4 ports , we can only analyze 2 port

# continue

We just analyze for 2 transmission lines with characteristic  $Z_e$  and  $Z_o$  respectively. Similarly the propagation coefficients  $\beta_e$  and  $\beta_o$  respectively. Treat the odd and even mode lines as uniform lossless lines. Taking ABCD matrix for a line , length  $l$ , characteristic impedance  $Z$  and propagation constant  $\beta$ , thus

$$ABCD|_{tline} = \begin{bmatrix} \cos(\beta l) & jZ \sin(\beta l) \\ j \frac{\sin(\beta l)}{Z} & \cos(\beta l) \end{bmatrix}$$

Using conversion

$$[S] = \frac{1}{Z_o A + B + Z_o^2 C + Z_o D} \begin{bmatrix} Z_o A + B - Z_o^2 C - Z_o D & 2Z_o (AD - BC) \\ 2Z_o & -Z_o A + B - Z_o^2 C + Z_o D \end{bmatrix}$$

# continue

$$[S] = \frac{1}{2Z \cos \beta \ell + j \sin \beta \ell \left( \frac{Z^2 + Z_o^2}{Z^2} \right)} \begin{bmatrix} j \sin \beta \ell \left( \frac{Z^2 - Z_o^2}{Z} \right) & 2Z_o \\ 2Z_o & j \sin \beta \ell \left( \frac{Z^2 - Z_o^2}{Z} \right) \end{bmatrix}$$

Taking  $\beta \ell = \frac{\pi}{2}$  (equivalent to quarter-wavelength transmission line)

Then


$$[S] = \frac{1}{Z^2 + Z_o^2} \begin{bmatrix} Z^2 - Z_o^2 & -j2ZZ_o \\ -j2ZZ_o & Z^2 - Z_o^2 \end{bmatrix}$$

continue

Odd ± even

$S_{11}$	$S_{12}$
$S_{21}$	$S_{22}$

## Convert to

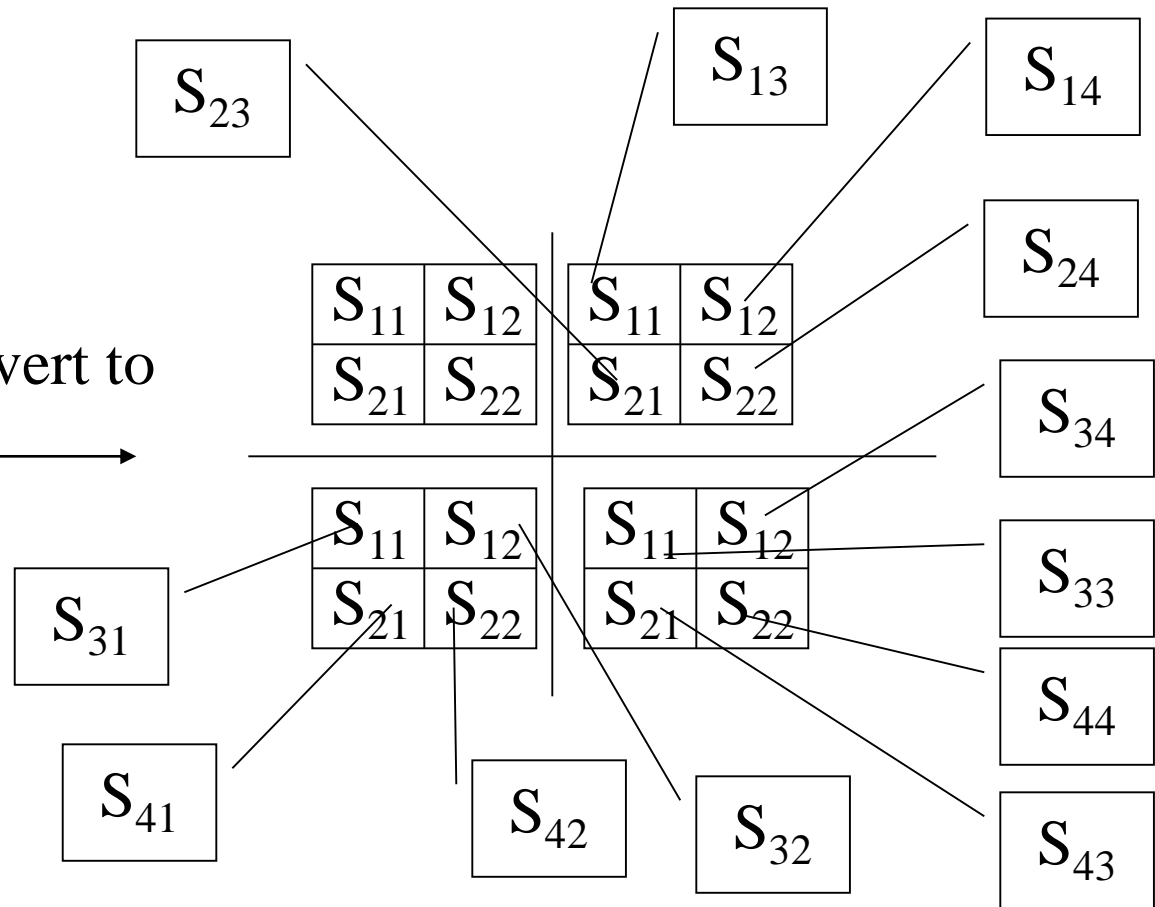

## 2-port network matrix

## 4-port network matrix

# continue

Follow symmetrical properties

ev+ od	$S_{11}$	$S_{12}$	$S_{13}$	$S_{14}$	ev- od
	$S_{21}$	$S_{22}$		$S_{24}$	
ev- od	$S_{31}$	$S_{32}$	$S_{33}$	$S_{34}$	ev+ od
	$S_{41}$	$S_{42}$		$S_{44}$	

Assuming  $\beta_{ev} = \beta_{od} = \frac{\pi}{2\ell}$   
Then

$$\begin{aligned}
 S_{41} = S_{14} = S_{32} = S_{23} &= -\frac{jZ_o}{2} \left( \frac{Z_{ev}}{Z_{ev}^2 + Z_o^2} - \frac{Z_{od}}{Z_{od}^2 + Z_o^2} \right) \\
 &= -\frac{jZ_o}{2} \left( \frac{(Z_{ev}Z_{od} - Z_o^2)(Z_{od} - Z_{ev})}{(Z_{ev}^2 + Z_o^2)(Z_{od}^2 + Z_o^2)} \right)
 \end{aligned}$$

For perfect isolation (I.e  $S_{41}=S_{14}=S_{32}=S_{23}=0$  ),we choose  $Z_{ev}$  and  $Z_{od}$  such that  $Z_{ev} Z_{od}=Z_o^2$ .

# continue

ev+ od	$S_{11}$	$S_{12}$	$S_{13}$	$S_{14}$	ev- od
	$S_{21}$	$S_{22}$		$S_{24}$	
ev- od	$S_{31}$	$S_{32}$	$S_{33}$	$S_{34}$	ev+ od
	$S_{41}$	$S_{42}$		$S_{44}$	

Similarly we have

$$\begin{aligned}
 S_{11} = S_{22} = S_{33} = S_{44} &= \frac{1}{2} \left( \frac{Z_{ev}^2 - Z_o^2}{Z_{ev}^2 + Z_o^2} + \frac{Z_{od}^2 - Z_o^2}{Z_{od}^2 + Z_o^2} \right) \\
 &= \frac{1}{2} \left( \frac{Z_{ev}^2 Z_{od}^2 - Z_o^4}{(Z_{ev}^2 + Z_o^2)(Z_{od}^2 + Z_o^2)} \right)
 \end{aligned}$$

Equal to zero if  $Z_{ev} Z_{od} = Z_o^2$ .

# continue

ev+ od	$S_{11}$	$S_{12}$	$S_{13}$	$S_{14}$	ev- od
	$S_{21}$	$S_{22}$		$S_{23}$	
<hr/>					
ev- od	$S_{31}$	$S_{32}$	$S_{33}$	$S_{34}$	ev+ od
	$S_{41}$	$S_{42}$		$S_{43}$	

We have

$$\begin{aligned}
 S_{31} = S_{13} = S_{24} = S_{42} &= \frac{1}{2} \left( \frac{Z_{ev}^2 - Z_o^2}{Z_{ev}^2 + Z_o^2} - \frac{Z_{od}^2 - Z_o^2}{Z_{od}^2 + Z_o^2} \right) \\
 &= \left( \frac{(Z_{ev}^2 - Z_{od}^2) Z_o^2}{(Z_{ev}^2 + Z_o^2)(Z_{od}^2 + Z_o^2)} \right) \\
 &= \left( \frac{Z_{ev} - Z_{od}}{Z_{ev} + Z_{od}} \right)
 \end{aligned}$$

if  $Z_{ev} Z_{od} = Z_o^2$ .

# continue

ev+ od	$S_{11}$	$S_{12}$	$S_{13}$	$S_{14}$	ev- od
	$S_{21}$	$S_{22}$		$S_{24}$	
ev- od	$S_{31}$	$S_{32}$	$S_{33}$	$S_{34}$	ev+ od
	$S_{41}$	$S_{42}$	$S_{43}$	$S_{44}$	

$$\begin{aligned}
 S_{21} = S_{12} = S_{34} = S_{43} &= -\frac{jZ_o}{2} \left( \frac{Z_{ev}}{Z_{ev}^2 + Z_o^2} + \frac{Z_{od}}{Z_{od}^2 + Z_o^2} \right) \\
 &= -jZ_o \left( \frac{1}{Z_{ev} + Z_{od}} \right) \quad \text{if } Z_{ev} Z_{od} = Z_o^2.
 \end{aligned}$$



# continue

This S-parameter must satisfy network characteristic:

(1) Power conservation

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 = 1$$

Reflected  
power

transmitted  
power to  
port 2

transmitted  
power to  
port 3

transmitted  
power to  
port 4

Since  $S_{11}$  and  $S_{41}=0$  , then

$$|S_{21}|^2 + |S_{31}|^2 = 1$$

(2) And quadrature condition

$$\text{Arg}\left(\frac{S_{11}}{S_{21}}\right) = \pm \frac{\pi}{2}$$

# continue

For 3 dB coupler

$$\left( \frac{Z_{ev} - Z_{od}}{Z_{ev} + Z_{od}} \right)^2 = \frac{1}{2} \quad \text{or} \quad \left( \frac{Z_{ev} - Z_{od}}{Z_{ev} + Z_{od}} \right) = \pm \sqrt{\frac{1}{2}}$$

Rewrite we have

$$\frac{Z_{ev}}{Z_{od}} = \left( \frac{1 + (\pm\sqrt{2})}{1 - (\pm\sqrt{2})} \right) = 3 \pm 2\sqrt{2}$$


In practice  $Z_{ev} > Z_{od}$  so  $\frac{Z_{ev}}{Z_{od}} = 3 + 2\sqrt{2} = 5.83$

However the limitation for coupled edge

$$\frac{Z_{ev}}{Z_{od}} < 2 \quad (\text{Gap size}) \quad \text{also} \quad \beta_{ev} \text{ and } \beta_{od} \text{ are not pure TEM}$$

thus not equal

# A $\lambda/4$ branch line coupler

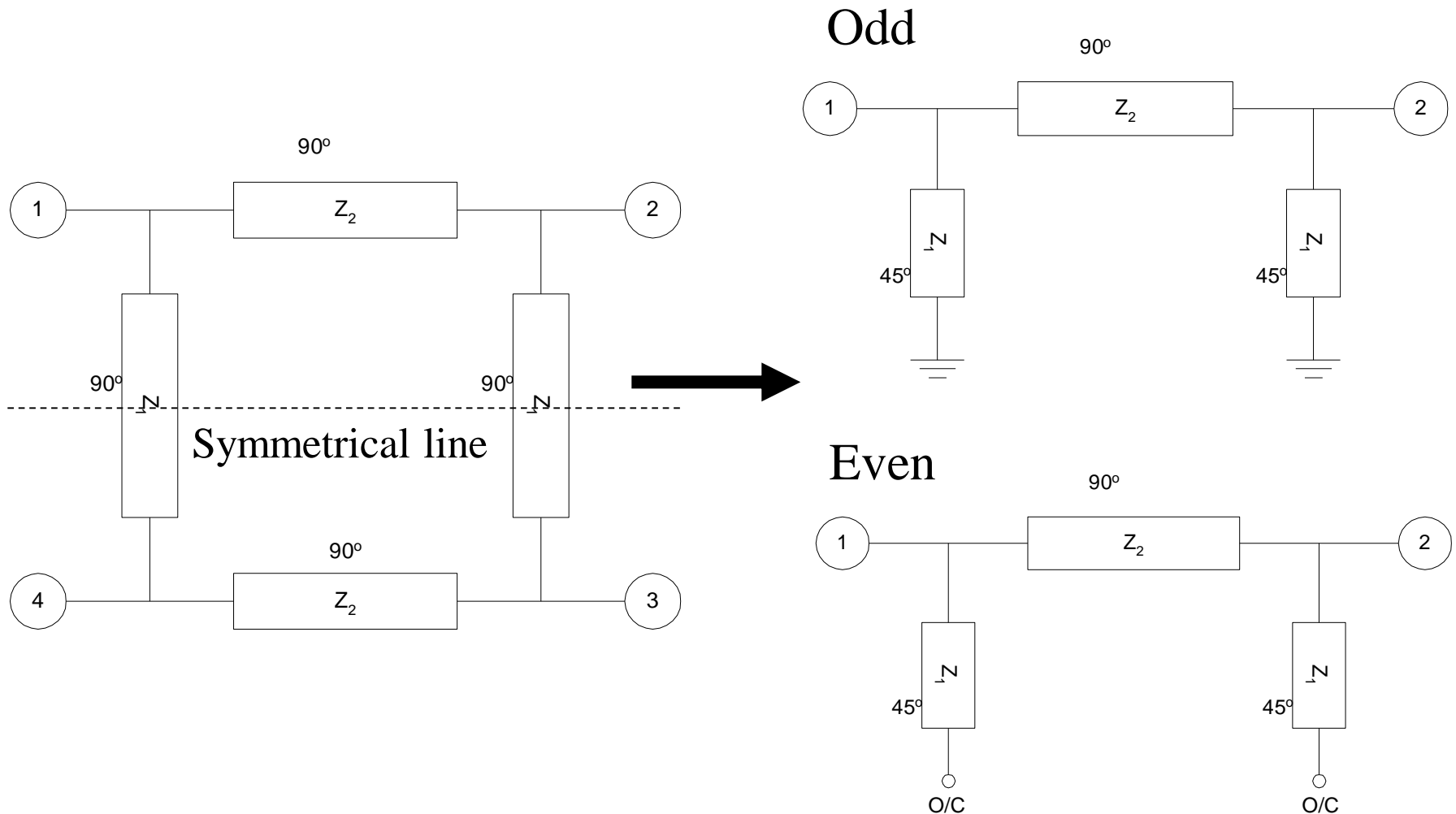

# Analysis

Stub odd (short circuit)  $X_{s,od} = Z_1 \tan\left(\frac{\pi}{4}\right) = Z_1$

Stub even (open circuit)  $X_{s,ev} = -Z_1 \cot\left(\frac{\pi}{4}\right) = -Z_1$

The ABCD matrices for the two networks may then found :

$$ABCD \Big| = \begin{bmatrix} 1 & 0 \\ \frac{1}{jX_s} & 1 \end{bmatrix} \begin{bmatrix} 0 & jZ_2 \\ \frac{j}{Z_2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{jX_s} & 1 \end{bmatrix} = \begin{bmatrix} \frac{Z_2}{X_s} & jZ_2 \\ \frac{j}{Z_2} - \frac{jZ_2}{X_s^2} & \frac{Z_2}{X_s} \end{bmatrix}$$

stub

Transmission  
line

stub

# continue

Convert to S

$$[S] = \frac{1}{Z_o A + B + Z_o^2 C + Z_o D} \begin{bmatrix} Z_o A + B - Z_o^2 C - Z_o D & 2Z_o(AD - BC) \\ 2Z_o & -Z_o A + B - Z_o^2 C + Z_o D \end{bmatrix}$$

$$= \frac{1}{\frac{2Z_o Z_2}{X_s} + jZ_2 - j\frac{Z_o^2 Z_2}{X_s^2} + j\frac{Z_o^2}{Z_2}} \begin{bmatrix} jZ_2 + j\frac{Z_o^2 Z_2}{X_s^2} - j\frac{Z_o^2}{Z_2} & 2Z_o \\ 2Z_o & jZ_2 + j\frac{Z_o^2 Z_2}{X_s^2} - j\frac{Z_o^2}{Z_2} \end{bmatrix}$$

For perfect isolation we require

$$S_{11ev} + S_{11od} = S_{11ev} - S_{11od} = 0 \quad \text{Thus} \quad S_{11ev} = S_{11od} = 0$$

$$S_{11} = jZ_2 + j\frac{Z_o^2 Z_2}{X_s^2} - j\frac{Z_o^2}{Z_2} = 0 \quad \text{or} \quad X_s = \mp \frac{Z_o Z_2}{\sqrt{Z_o^2 - Z_2^2}} = Z_1$$

From previous definition

# continue

Substituting into S-parameter gives us

$$[S]_{odd} = \frac{1}{\sqrt{Z_o^2 - Z_2^2 + jZ_2}} \begin{bmatrix} 0 & Z_o \\ Z_o & 0 \end{bmatrix} \quad \text{and} \quad [S]_{even} = -\frac{1}{\sqrt{Z_o^2 - Z_2^2 + jZ_2}} \begin{bmatrix} 0 & Z_o \\ Z_o & 0 \end{bmatrix}$$

Therefore for full four port

$$S_{21} = S_{12} = S_{43} = S_{34} = \frac{1}{2}(S_{21ev} + S_{21od}) = -j \frac{Z_2}{Z_o}$$

$$S_{41} = S_{14} = S_{32} = S_{23} = \frac{1}{2}(S_{21ev} - S_{21od}) = -\sqrt{1 - \frac{Z_2^2}{Z_o^2}}$$

$$S_{11} = S_{22} = S_{33} = S_{44} = 0$$

And  $S_{31} = S_{13} = S_{42} = S_{24} = 0$

# continue

For power conservation and quadrature conditions to be met

Equal split S

$$|S_{21}| = \frac{Z_2}{Z_o} = \frac{1}{\sqrt{2}} \quad \text{or} \quad Z_2 = \frac{Z_o}{\sqrt{2}}$$

And

$$X_s = Z_1 = \frac{Z_o Z_2}{\sqrt{Z_o^2 - Z_2^2}} = \frac{Z_o \frac{Z_o}{\sqrt{2}}}{\sqrt{Z_o^2 - \left(\frac{Z_o}{\sqrt{2}}\right)^2}} = Z_o$$

If  $Z_o = 50 \, \Omega$  then  $Z_2 = 35.4 \, \Omega$