

Advanced Current Mirrors and Opamps

David Johns and Ken Martin
University of Toronto
(johns@eecg.toronto.edu)
(martin@eecg.toronto.edu)



University of Toronto

slide 1 of 35

-

Wide-Swing Current Mirrors

- Q3 and Q4 act like a single transistor

$$V_{eff} = V_{eff2} = V_{eff3} = \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)}} \quad (1)$$

- Q₅ has same drain current but $(n + 1)^2$ times smaller

$$V_{eff5} = (n + 1)V_{eff} \quad (2)$$

- Similarly

$$V_{eff1} = V_{eff4} = nV_{eff} \quad (3)$$

$$V_{G5} = V_{G4} = V_{G1} = (n + 1)V_{eff} + V_{tn} \quad (4)$$

$$V_{DS2} = V_{DS3} = V_{G5} - V_{GS1} = V_{G5} - (nV_{eff} + V_{tn}) = V_{eff} \quad (5)$$

- Puts Q2 and Q3 right at edge of triode



Wide-Swing Current Mirrors

- Min allowable output voltage

$$V_{\text{out}} > V_{\text{eff1}} + V_{\text{eff2}} = (n + 1)V_{\text{eff}} \quad (6)$$

- If $n = 1$

$$V_{\text{out}} > 2V_{\text{eff}} \quad (7)$$

- With typical value of V_{eff} of 0.2 V, wide-swing mirror can operate down to 0.4 V
- Analyzed with $I_{\text{bias}} = I_{\text{in}}$. If I_{in} varies, setting I_{bias} to max I_{in} will ensure transistors remain in active region
- Setting I_{bias} to nominal I_{in} will result in low output impedance during slewing (can often be tolerated)




Design Hints

- Usually designer would take $(W/L)_5$ smaller to bias Q_2 and Q_3 slightly larger than minimum
- To save power, bias Q_5 with lower currents while keeping same current densities (and V_{eff})
- Choose lengths of Q_2 and Q_3 close to minimum allowable gate length (since V_{ds} are quite small)
 - maximizes freq response
- Choose Q_1 and Q_4 to have longer gate lengths since Q_1 often has larger voltages (perhaps twice minimum allowable gate length)
 - Reduces short-channel effects



Enhanced Output-Impedance Current Mirror

 


- Use feedback to keep V_{ds} across Q_2 stable

$$R_{out} \cong g_{m1} r_{ds1} r_{ds1} (1 + A) \quad (8)$$

- Limited by parasitic conductance between drain and substrate of Q_1



 Simplified Enhanced Output-Impedance Mirror



- Rather than build extra opamps, use above
- Feedback amplifier realized by common-source amplifier of Q_3 and current source I_{B1}



Simplified Enhanced Output-Impedance Mirror

- Assuming output impedance of I_{B1} is equal to r_{ds3} , loop gain will be $(g_{m3}r_{ds3})/2$, resulting in


$$r_{out} \cong \frac{g_{m1}g_{m3}r_{ds1}r_{ds2}r_{ds3}}{2} \quad (9)$$

- Circuit consisting of Q_4 , Q_5 , Q_6 , I_{in} , and I_{B2} operates like a diode-connected transistor — results in accurate matching of I_{out} to I_{in}
- Note that shown circuit is NOT wide-swing — requires output to be $2V_{eff} + V_{tn}$ above lower supply



Wide-Swing with Enhanced Output Impedance

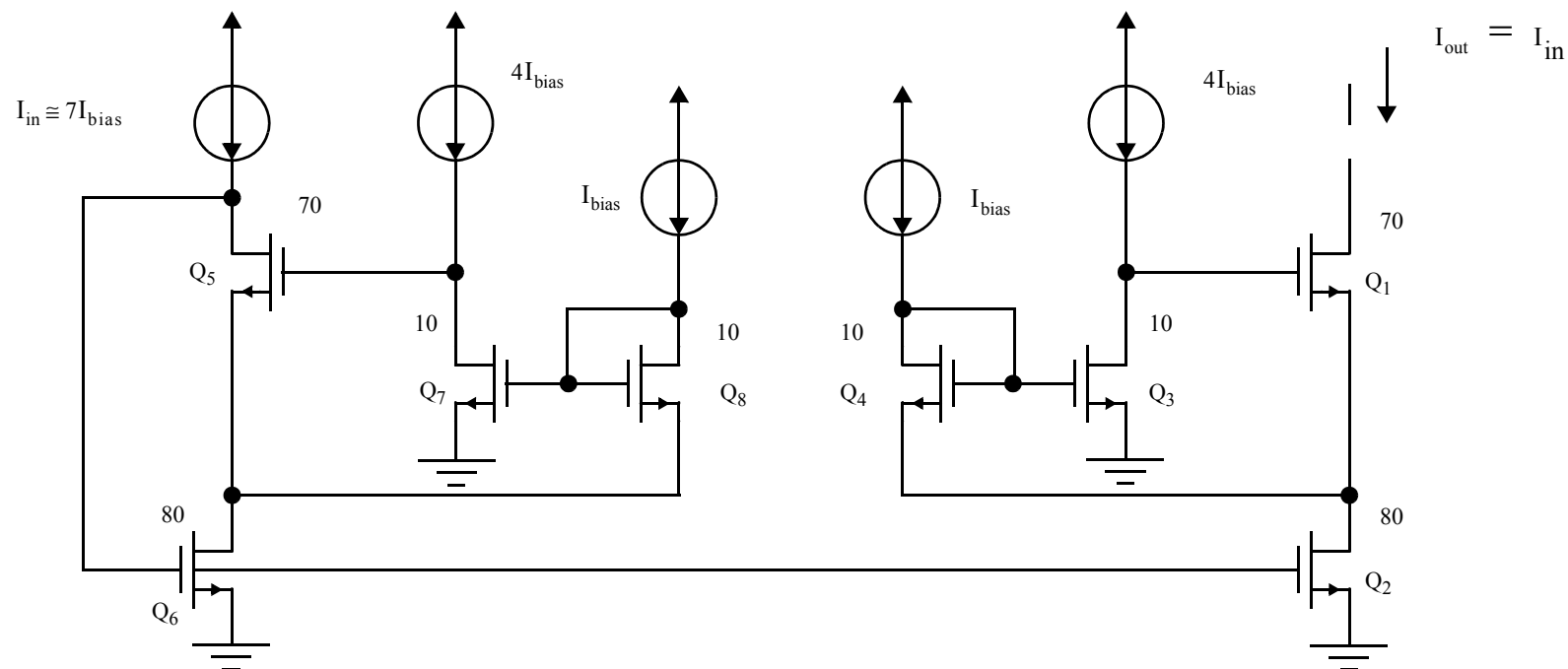
- Add wide-swing to improve output voltage swing



- Q_3 and Q_7 biased at 4 times current density — $2V_{eff}$
- Requires roughly twice power dissipation
- Might need local compensation capacitors



Folded-Cascode Opamp

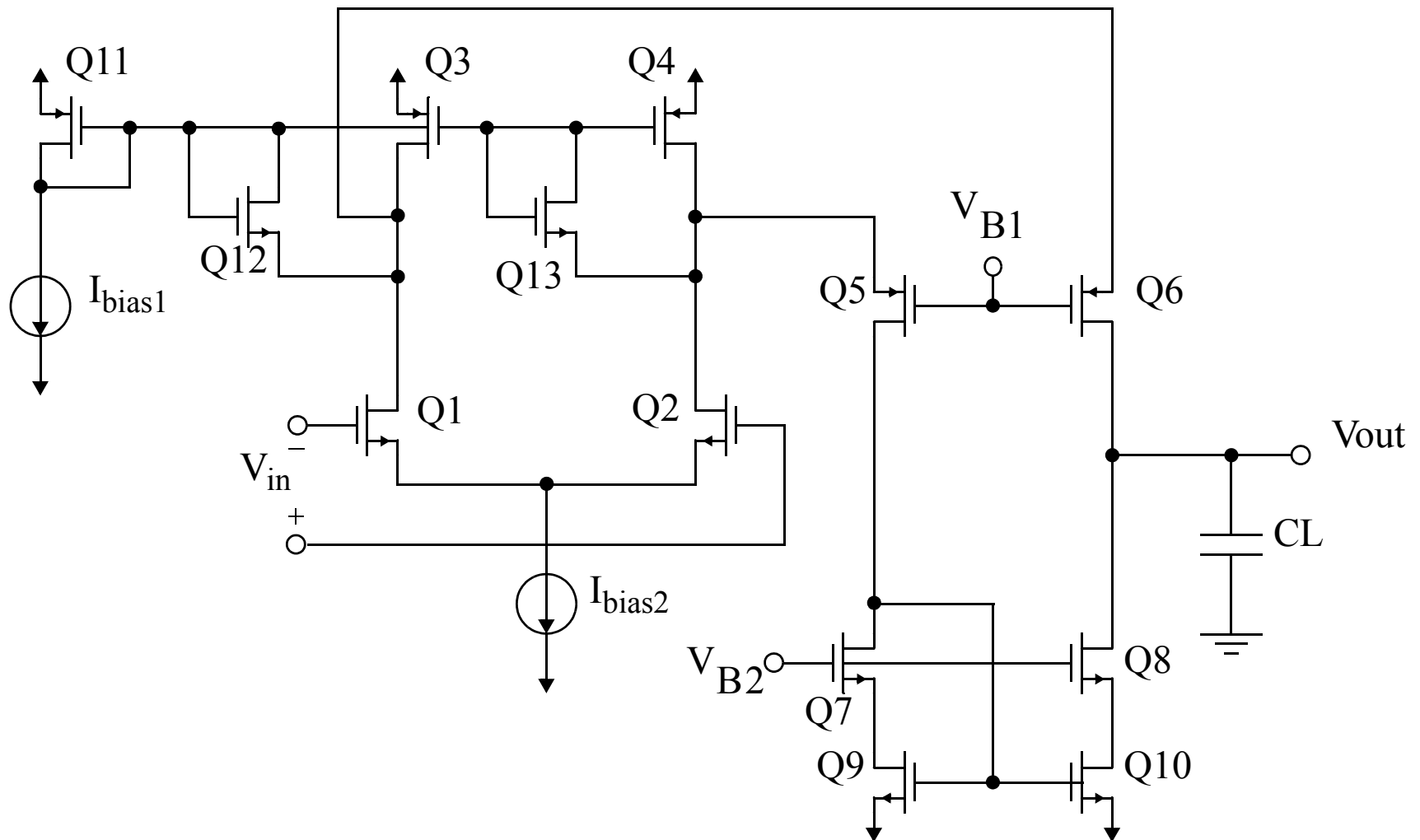

Folded-Cascode Opamp

- Compensation achieved using load capacitor
- As load increases, opamp slower but more stable
- Useful for driving capacitive loads only
- Large output impedance (not useful for driving resistive loads)
- Single-gain stage but dc gain can still be quite large (say 1,000 to 3,000)
- Shown design makes use of wide-swing mirrors
- Simplified bias circuit shown
- Inclusion of Q12 and Q13 for improved slew-rate



Folded-Cascode Opamp

$$A_V = \frac{V_{out}(s)}{V_{in}(s)} = g_{m1} Z_L(s) \quad (10)$$

$$A_V = \frac{g_{m1} r_{out}}{1 + s r_{out} C_L} \quad (11)$$

- r_{out} is output impedance of opamp (roughly $g_m r_{ds}^2 / 2$)
- For mid-band freq, capacitor dominates

$$A_V \cong \frac{g_{m1}}{s C_L} \quad (12)$$

$$\omega_t = \frac{g_{m1}}{C_L} \quad (13)$$



Folded-Cascode Opamp

- Maximizing gm of input maximizes freq response (if not limited by second-poles)
- Choose current of input stage larger than output stage (also maximizes dc gain)
- Might go as high as 4:1 ratio
- Large input gm results in better thermal noise
- Second poles due to nodes at sources of Q5 and Q6
- Minimize areas of drains and sources at these nodes with good layout techniques
- For high-freq, increase current in output stage



Folded-Cascode Slew-Rate

- If Q2 turned off due to large input voltage

$$SR = \frac{I_{D4}}{C_L} \quad (14)$$

- But if $I_{bias2} > I_{D3}$, drain of Q1 pulled near negative power supply
- Would require a long time to recover from slew-rate
- Include Q12 (and Q13) to clamp node closer to positive power supply
- Q12 (and Q13) also dynamically increase bias currents during slew-rate limiting (added benefit)
- They pull more current through Q11 thereby increasing bias current in Q3 and Q4



Folded-Cascode Example

Design Goals

- $\pm 2.5\text{V}$ power supply and 2mW opamp with 4:1 ratio of current in input stage to output stage
- Set bias current in Q11 to be 1/30 of Q3 (or Q4)
- Channel lengths of $1.6\mu\text{m}$ and max width of $300\mu\text{m}$ with $V_{\text{eff}}=0.25$ (except input transistors)
- Load cap = 10pF

Circuit Design

$$I_{\text{total}} = 2(I_{D1} + I_{D6}) = 2(4I_B + I_B) = 10I_B \quad (15)$$

$$I_B = I_{D5} = I_{D6} = \frac{I_{\text{total}}}{10} = \frac{(2\text{mW})/5\text{ V}}{10} = 40\text{ }\mu\text{A} \quad (16)$$

$$I_{D3} = I_{D4} = 5I_{D5} = 200\text{ }\mu\text{A} \quad (17)$$



$$I_{D1} = I_{D2} = 4I_{D5} = 160 \mu\text{A} \quad (18)$$

- To find transistor sizing:

$$\left(\frac{W}{L}\right)_i = \frac{2I_{Di}}{\mu_i C_{ox} V_{effi}^2} \quad (19)$$

rounding to nearest factor of 10 (and limiting to 300um width) results in

Q ₁	300/1.6	Q ₆	60/1.6	Q ₁₁	10/1.6
Q ₂	300/1.6	Q ₇	20/1.6	Q ₁₂	10/1.6
Q ₃	300/1.6	Q ₈	20/1.6	Q ₁₃	10/1.6
Q ₄	300/1.6	Q ₉	20/1.6		
Q ₅	60/1.6	Q ₁₀	20/1.6		

- Widths of Q_{12} and Q_{13} were somewhat arbitrarily chosen to equal the width of Q_{11}
- Transconductance of input transistors



$$g_{m1} = \sqrt{2I_{D1}\mu_n C_{ox}(W/L)_1} = 2.4 \text{ mA/V} \quad (20)$$

- Unity-gain frequency

$$\omega_t = \frac{g_{m1}}{C_L} = 2.4 \times 10^8 \text{ rad/s} \Rightarrow f_t = 38 \text{ MHz} \quad (21)$$

- Slew rate *without* clamp transistors

$$\text{SR} = \frac{I_{D4}}{C_L} = 20 \text{ V}/\mu\text{s} \quad (22)$$

- Slew rate *with* clamp transistors

$$I_{D12} + I_{D3} = I_{bias2} = 320 \mu\text{A} \quad (23)$$

$$I_{D3} = 30I_{D11} \quad (24)$$

$$I_{D11} = 6.6 \mu\text{A} + I_{D12} \quad (25)$$



- Solving above results in

$$I_{D11} = 10.53 \mu\text{A} \quad (26)$$

which implies

$$I_{D3} = I_{D4} = 30I_{D11} = 0.32 \text{ mA} \quad (27)$$


leading to slew-rate

$$\text{SR} = \frac{I_{D4}}{C_L} = 32 \text{ V}/\mu\text{s} \quad (28)$$


- More importantly, time to recover from slew-rate limiting is decreased.



Current-Mirror Opamp

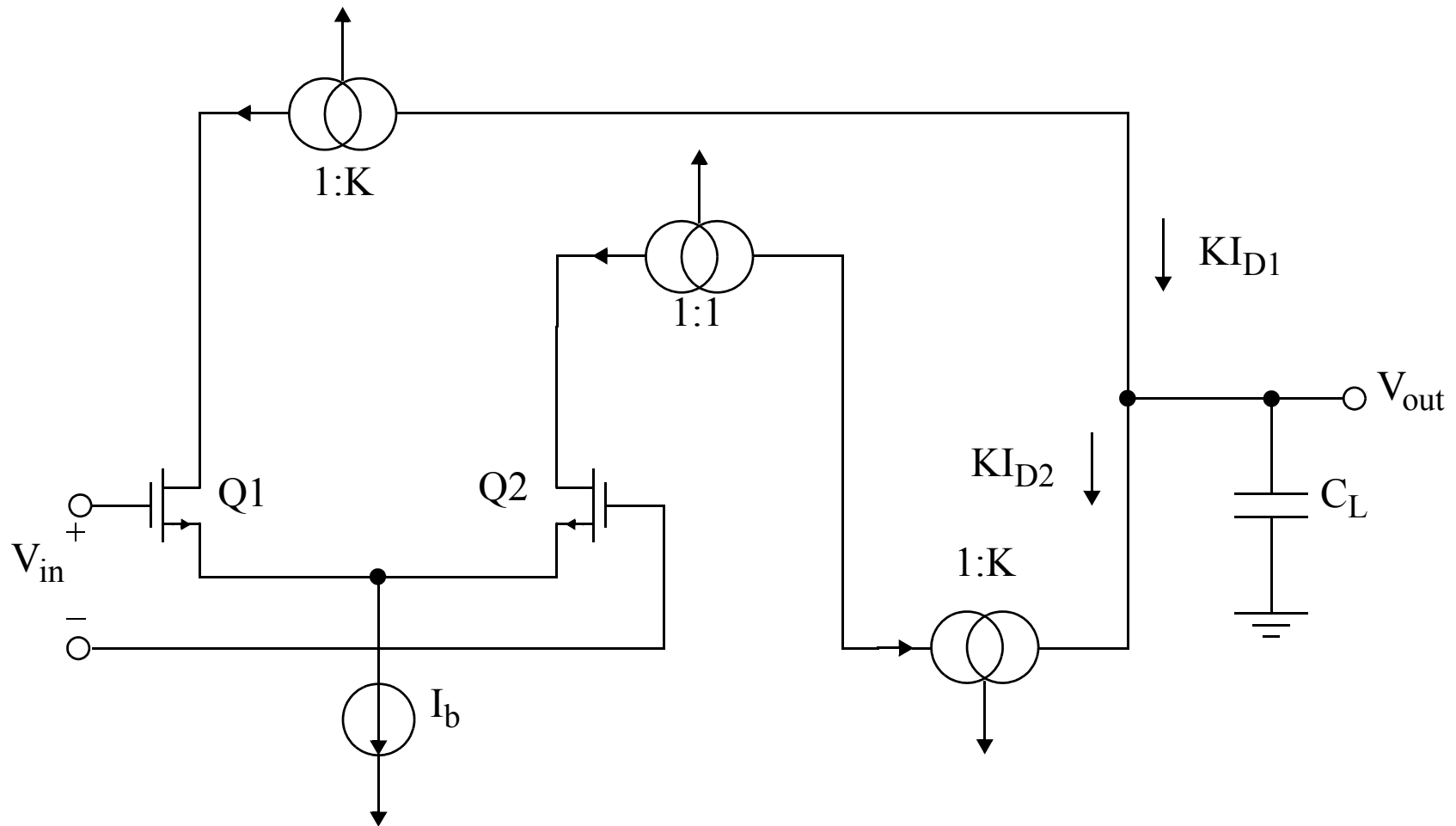

Current-Mirror with Wide-Swing Cascodes

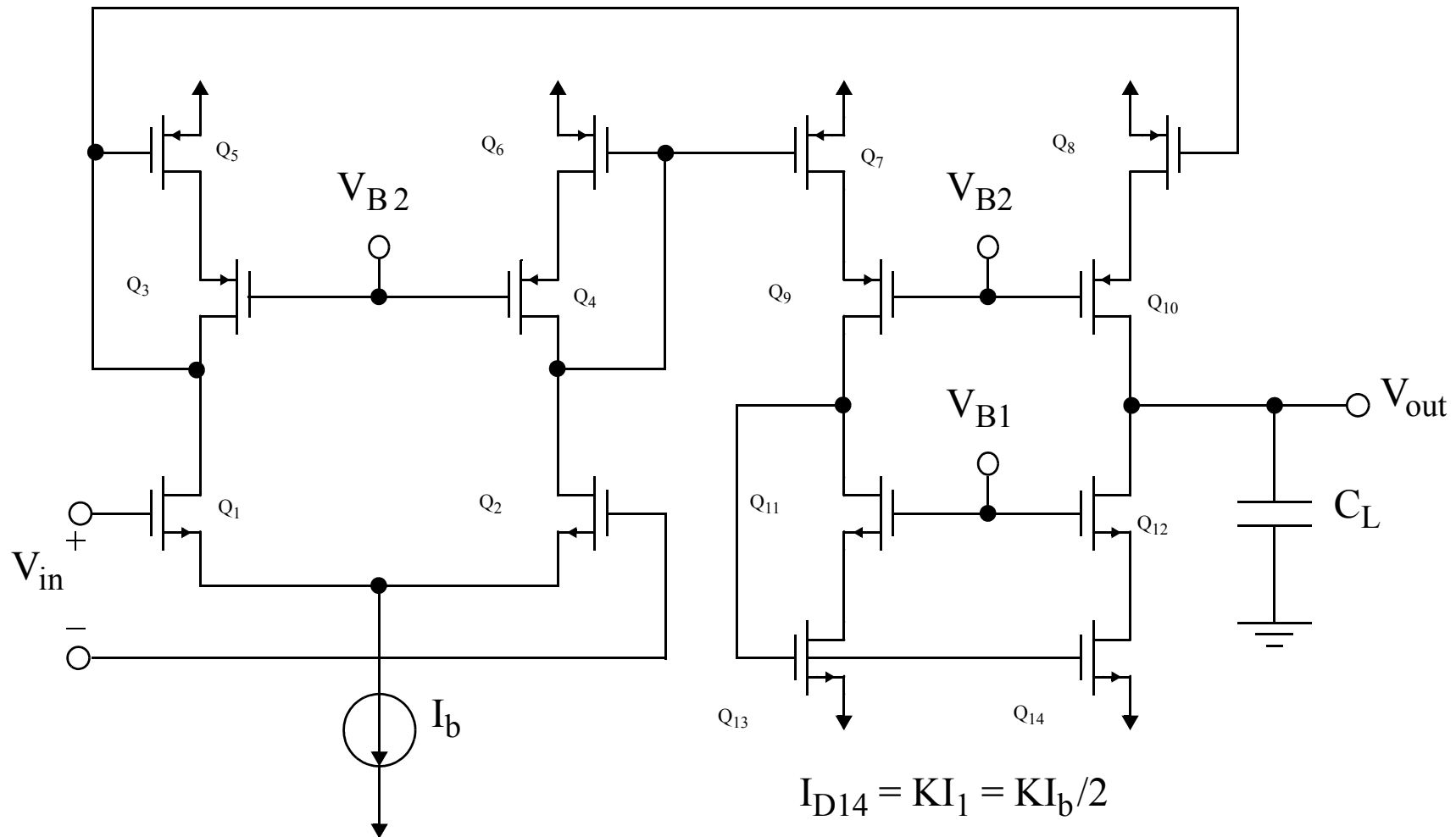

Current-Mirror Opamp

$$A_V = \frac{V_{out}(s)}{V_{in}(s)} = Kg_{m1}Z_L(s) = \frac{Kg_{m1}r_{out}}{1 + sr_{out}C_L} \cong \frac{Kg_{m1}}{sC_L} \quad (29)$$

- K factor is the current gain from mirrors

$$\omega_t = \frac{Kg_{m1}}{C_L} = \frac{K\sqrt{2I_{D1}\mu_n C_{ox}(W/L)_1}}{C_L} \quad (30)$$

- If output capacitance set max speed, higher K results in higher speed
- If second-poles set max speed, higher K results in lower speed (increases capacitances of nodes)
- A reasonable choice for a general-purpose opamp is $K = 2$ (for max speed, $K = 1$)



Current-Mirror Opamp Slew-Rate

$$SR = \frac{KI_b}{C_L} \quad (31)$$

- For given power, SR maximized by large K
- Example: $K = 4$ results in 4/5 of total bias current used in charging C_L
- Usually has better SR than folded-cascode
- Usually has better bandwidth than folded-cascode
- Folded-cascode has better thermal noise



Current-Mirror Opamp Example

Design goals

Same as in folded-cascode. Use $K=2$

Circuit Design

- With 2mW power limit and 5V supply, $I_{\text{total}} = 400 \mu\text{A}$

$$I_{\text{total}} = (3 + K)I_{D1} \quad (32)$$

$$I_{D1-7} = I_{D9} = I_{D11} = I_{D13} = 80 \mu\text{A} \quad (33)$$

$$I_{D8} = I_{D10} = I_{D12} = I_{D14} = 160 \mu\text{A} \quad (34)$$

$$I_b = 160 \mu\text{A} \quad (35)$$

and setting V_{eff} around 0.25V, we find transistor sizes...

- Resulting in:



Q ₁	300/1.6	Q ₇	60/1.6	Q ₁₃	30/1.6
Q ₂	300/1.6	Q ₈	120/1.6	Q ₁₄	60/1.6
Q ₃	60/1.6	Q ₉	60/1.6		
Q ₄	60/1.6	Q ₁₀	120/1.6		
Q ₅	60/1.6	Q ₁₁	30/1.6		
Q ₆	60/1.6	Q ₁₂	60/1.6		

$$g_{m1} = \sqrt{2I_{D1}\mu_n C_{ox}(W/L)_1} = 1.7 \text{ mA/V} \quad (36)$$

$$\omega_t = \frac{Kg_{m1}}{C_L} = 3.4 \times 10^8 \text{ rad/s} \Rightarrow f_t = 54 \text{ MHz} \quad (37)$$

$$SR = (KI_b)/C_L = 32 \text{ V}/\mu\text{s} \quad (38)$$

- which is better than 20 V/ μ s for the folded-cascode opamp without clamp transistors



Linear Settling Time

- Time constant for linear settling time equals inverse of closed-loop 3dB freq, $\omega_{3\text{dB}}$ where


$$\omega_{3\text{dB}} = \beta \omega_t \quad (39)$$

where β is feedback factor and ω_t is unity-gain freq of amplifier (not including feedback factor)

- For 2-stage opamp, ω_t is relatively independent of load capacitance
- This is NOT the case where load capacitor is compensation capacitor (folded-cascode and current-mirror opamps)
- Need to find equivalent load capacitance



Linear Settling Time

 

$$\beta = \frac{1/[s(C_1 + C_p)]}{1/[s(C_1 + C_p)] + 1/(sC_2)} = \frac{C_2}{C_1 + C_p + C_2} \quad (40)$$

$$C_L = C_C + C_{load} + \frac{C_2(C_1 + C_p)}{C_1 + C_p + C_2} \quad (41)$$



Linear Settling Time Example

- Given $C_1 = C_2 = C_C = C_{\text{load}} = 5 \text{ pF}$ and $C_p = 0.46 \text{ pF}$, find settling time for 0.1 percent accuracy (i.e. 7τ) for the current-mirror opamp

Solution:

- Equivalent load capacitance

$$C_L = 5 + 5 + \frac{5(5 + 0.46)}{5 + 5 + 0.46} = 12.61 \text{ pF} \quad (42)$$

which results in a unity gain freq of

$$\omega_t = \frac{Kg_{m1}}{C_L} = \frac{2 \times 1.7 \text{ mA/V}}{12.61 \text{ pF}} = 2.70 \times 10^8 \text{ rad/s} \quad (43)$$



Linear Settling Time Example

- Feedback factor given by

$$\beta = \frac{5}{5 + 0.46 + 5} = 0.48 \quad (44)$$

causing a first-order time constant

$$\tau = \frac{1}{\beta\omega_t} = 7.8 \text{ ns} \quad (45)$$

- For 0.1 percent accuracy, we need a linear settling time of 7τ or 54 ns.
- This does not account for any slew-rate limiting time.



Fully Differential Opamps

Advantages


- Use of fully-differential signals helps to reject common-mode noise and even-order linearities
 - rejection only partial due to non-linearities but much better than single-ended designs
- Fast since no extra current mirror needed

Disadvantages


- Requires common-mode feedback (CMFB) circuitry
 - sets average output voltage level, should be fast
 - adds some capacitance to output stage
 - might limit output signal swing
- Negative going single-ended slew-rate slower since set by bias current — not dynamic




Fully Differential Folded-Cascode Opamp

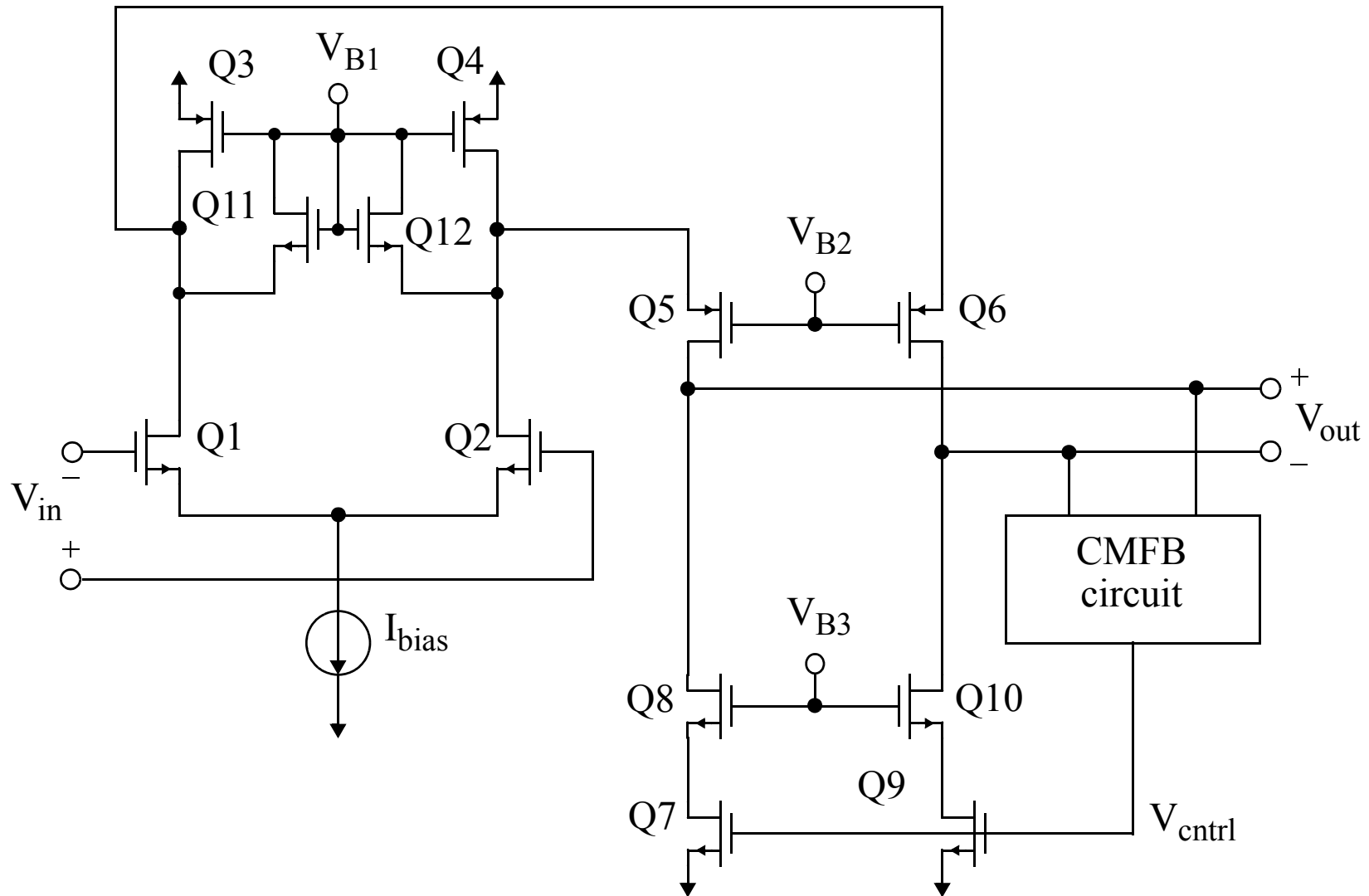


Fully-Diff Current-Mirror Opamp

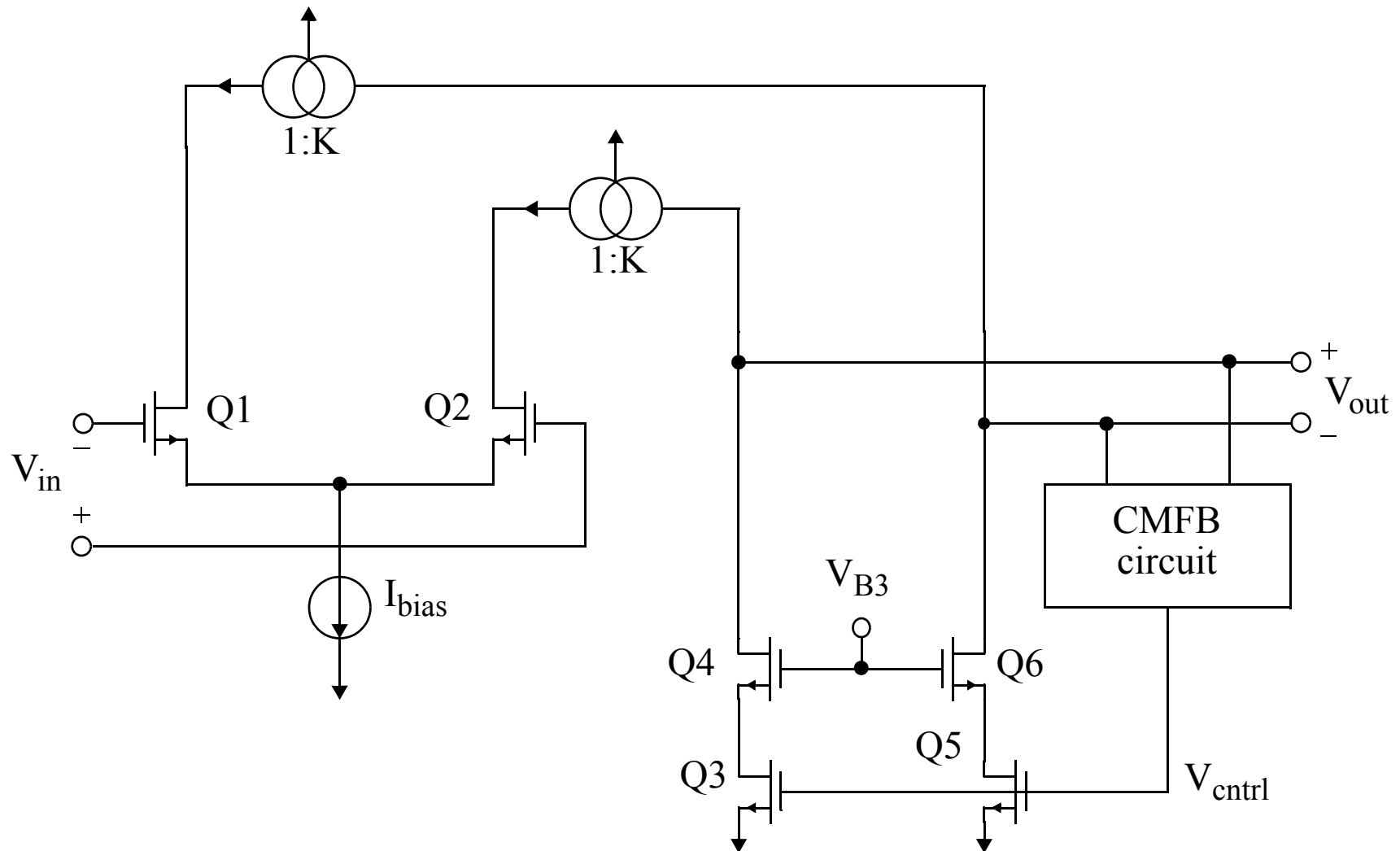

Other Fully-Diff Opamps

 

Using 2 single-ended opamps

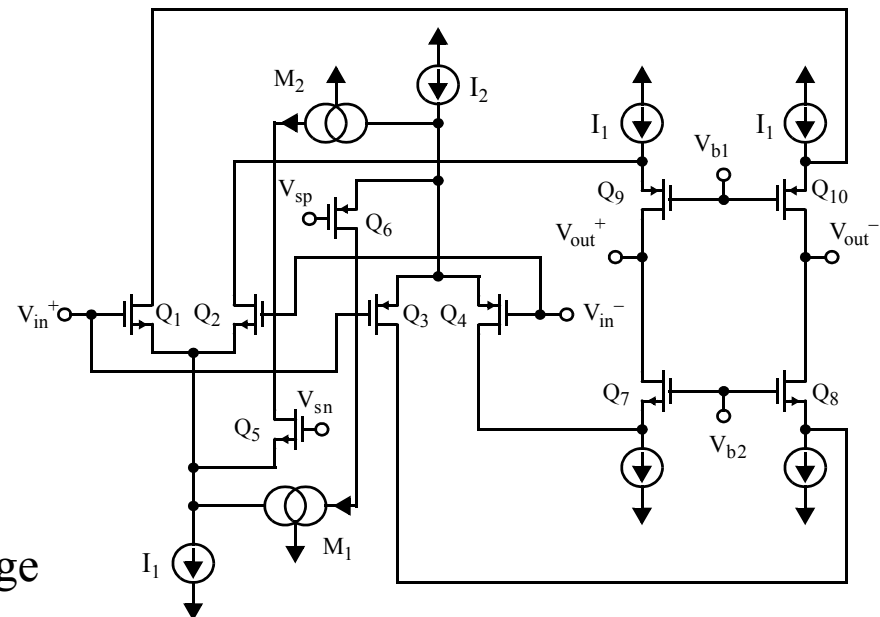

Rail-to-rail input common-mode range




University of Toronto

slide 32 of 35

-


Common-Mode Feedback Circuits

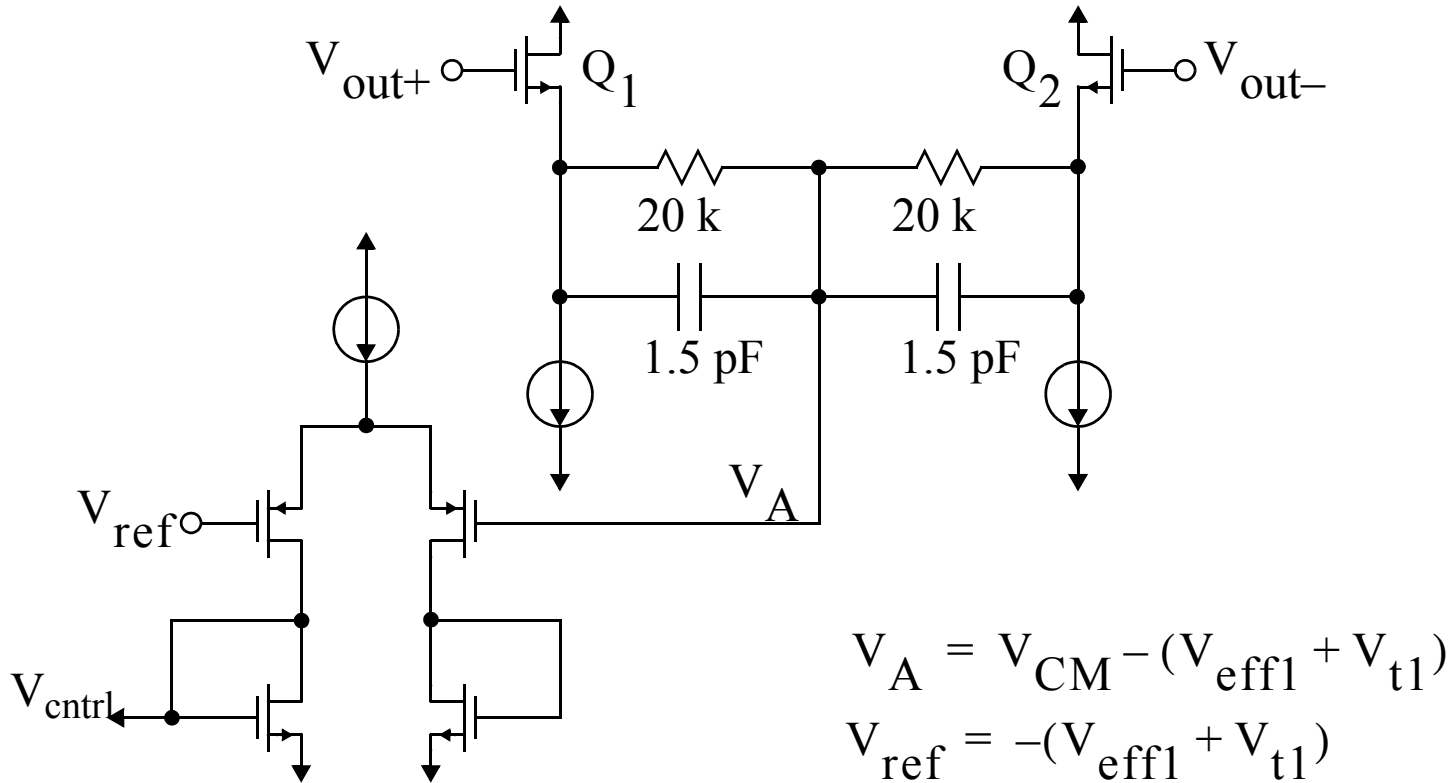

- Limited differential swing
- Should ensure CMFB loop is stable



Common-Mode Feedback Circuits

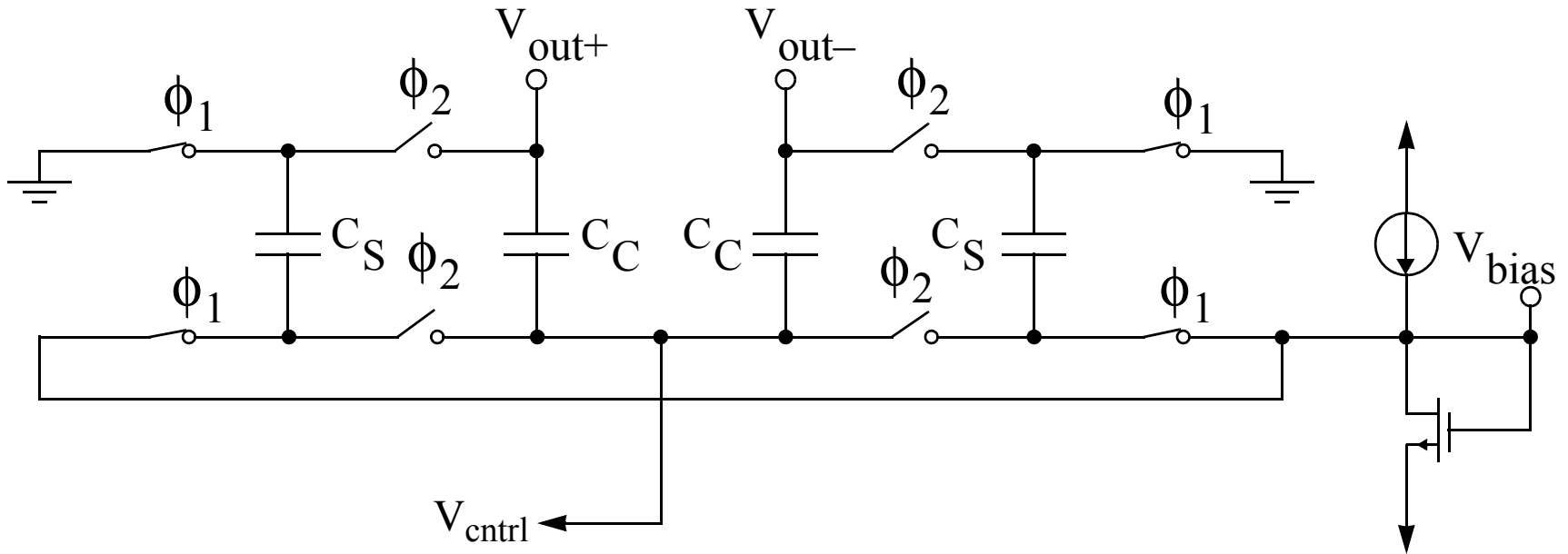

- Useful for switched-capacitor circuits
- Caps C_s set nominal dc bias at bottom of C_c
- Large output signal swing allowed

