

Electronics Exercise 2: The 555 Timer and it's applications

Mechatronics Instructional Laboratory
Woodruff School of Mechanical Engineering
Georgia Institute of Technology
Lab Director: I. Charles Ume, Professor
Author: Kita , Development TA Summer 2004
Revised by Jie, TA Fall 2011:

Objective:

1. Learn about the 555 timer integrated circuit and applications
2. Apply the 555 timer to build an infrared (IR) transmitter and receiver

1. The 555 Timer

The 555 timer integrated circuit (IC) has become a mainstay in electronics design. A 555 timer will produce a pulse when a trigger signal is applied to it. The pulse length is determined by charging then discharging a capacitor connected to a 555 timer. A 555 timer can be used to debounce switches, modulate signals, create accurate clock signals, create pulse width modulated (PWM) signals, etc. A 555 timer can be obtained from various manufacturers including Fairchild Semiconductor and National Semiconductor.

A 555 timer is shown below in Fig 1.

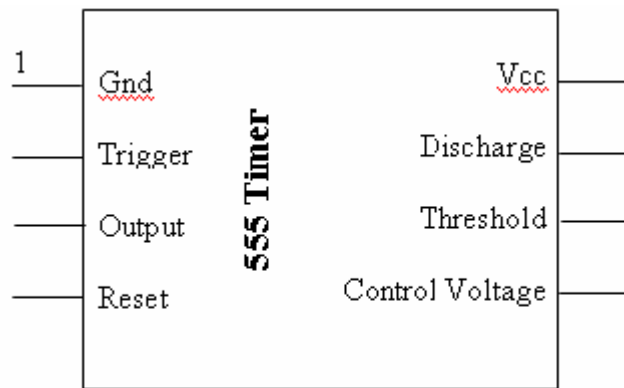


Fig. 1 555 Timer

Pins of the 555 timer are as follows:

- Gnd Ground connection for chip
- Trigger 555 timer triggers when this pin transitions from voltage at Vcc to 33% voltage at Vcc. Output pin goes high when triggered
- Output Output pin of 555 timer
- Reset Resets 555 timer when low
- Vcc 5V to 15 V supply input
- Discharge Used to discharge a capacitor
- Threshold Used to detect when the capacitor has charged. The Output pin goes low when capacitor has charged to 66.6% of Vcc.
- Control Voltage Used to change Threshold and Trigger set point voltages and is rarely used

1.1 555 Timer Monostable Circuit

Fig. 2 shows a monostable 555 timer circuit. The monostable circuit outputs one pulse for each high to low transition of the trigger pin.

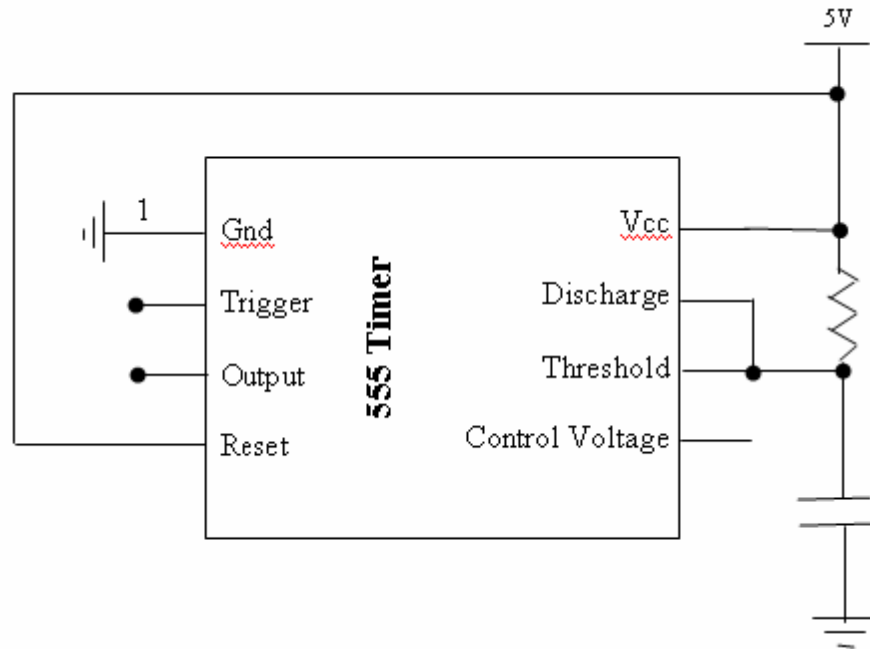


Fig. 2 Monostable 555 Timer Circuit

The discharge pin is internally connected to ground. The discharge pin is disconnected from ground and output pin is set high when the trigger pin transitions from V_{cc} to 33% V_{cc} Voltage. The capacitor, C , starts to charge through resistor, R . The threshold pin is used to detect when the voltage across the capacitor reaches 66.6% V_{cc} voltage. When the voltage across the capacitor reaches 66.6% V_{cc} voltage, the output pin is set low and the discharge pin is connected back to ground. When the discharge pin is connected back to ground, the capacitor is discharged.

The length of the output pulse depends on when the capacitor reaches 66.6% V_{cc} voltage. This rate is determined by the charge capacity of the capacitor, C , and resistance, R . The length of the output pulse, t_p , is:

$$t_p = 1.1 RC$$

The monostable 555 timer circuit can be used in the following applications:

1. Debounce a momentary/pushbutton switch
2. Turning on an actuator for a set period of time
3. Turn an output from a resistive sensor from analog signal to digital signal. ([Example: A potentiometer is a variable resistor. A project requires determining the position of a potentiometer used for user input. All analog to digital \(A/D\) converters on a microcontroller have already been used but there are some digital inputs and outputs available. The potentiometer can be used as the resistor in a monostable 555 timer circuit. The microcontroller can then trigger the monostable circuit and measure \$t_p\$ since \$t_p\$ now depends on the position of the potentiometer.](#))

1.2 555 Timer Astable Circuit

Fig. 3 shows an astable 555 timer circuit. The astable 555 timer circuit outputs a series of pulses.

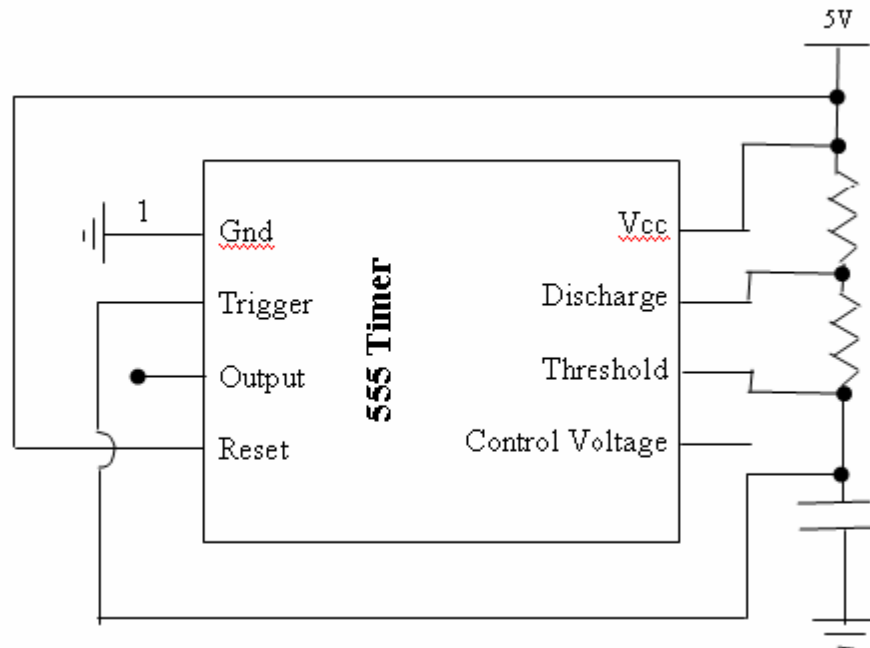


Fig. 3 Astable 555 Timer Circuit

When the circuit is first turned on, the discharge pin is disconnected from ground and output pin is set high because the trigger pin is below 33% V_{cc} Voltage. The capacitor, C , starts to charge through resistors R_1 and R_2 . The threshold pin is used to detect when the voltage across the capacitor reaches 66.6% V_{cc} voltage. When the voltage across the capacitor reaches 66.6% V_{cc} voltage, the output pin is set low and the discharge pin is connected back to ground. When the discharge pin is connected back to ground, the capacitor starts discharging through resistor R_2 . When the voltage across the capacitor reaches 33.3% V_{cc} voltage, the cycle repeats and creates a series of output pulses. An astable circuit triggers from previous output pulse whereas a monostable circuit requires an externally applied trigger.

The output pin oscillates from high to low creating a series of output pulses. The duration the output pin stays high, t_{HIGH} , is given below:

$$t_{HIGH} = .693 \cdot C \cdot (R_1 + R_2)$$

The duration the output pin stays low, t_{LOW} , is given below:

$$t_{LOW} = .693 \cdot C \cdot R_2$$

The frequency, f , of the series of pulses is:

$$f = \frac{1}{t_{HIGH} + t_{LOW}}$$

The astable 555 timer circuit can be used in the following applications:

1. Modulate transmitters such as ultrasonic and IR transmitters
2. Create an accurate clock signal (Example: There is a pulse accumulator pin on the 68HC11 microcontroller that counts pulses. You can apply an astable 555 timer circuit set at 1 Hz frequency to the pulse accumulator pin and create a seconds counter within the microcontroller. The pulse accumulator will be covered in later in the course.)
3. Turn on and off an actuator at set time intervals for a fixed duration

2. 555 timer to modulate infrared (IR) light

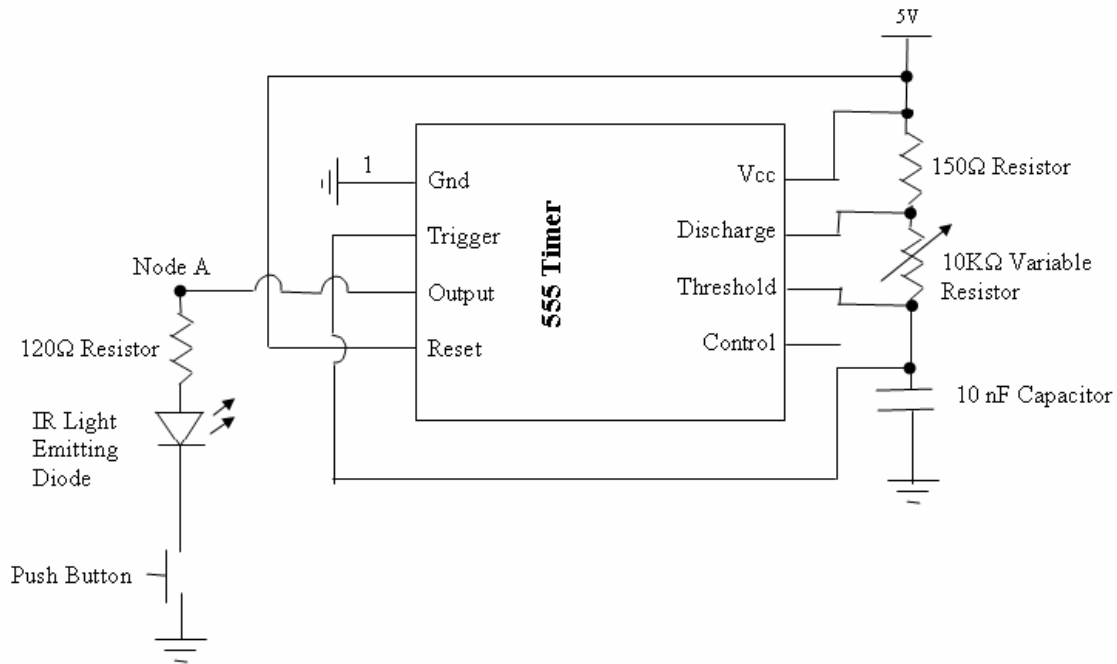


Fig. 4 modulated IR transmitter

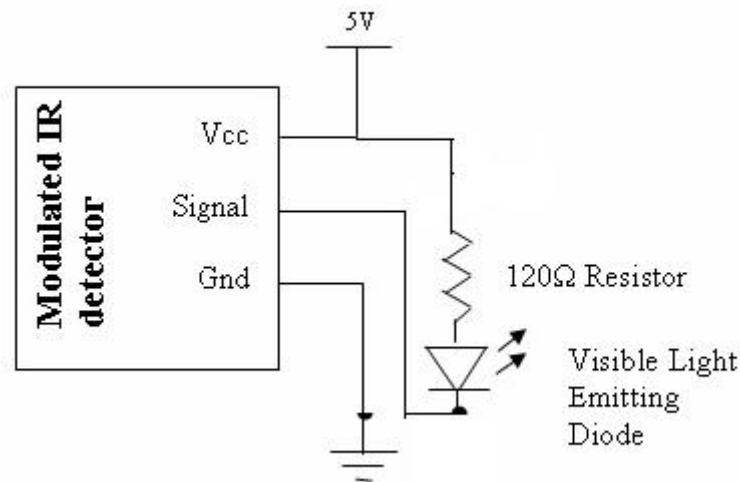


Fig. 5 modulated IR receiver

Apply power to the transmitter circuit. Use an oscilloscope to observe the signal at node A. Adjust the 10kΩ variable resistor until the signal at node A is a 38 kHz series of pulses. Apply power to the receiver circuit. Point the IR light emitting diode (LED) on the transmitter to the detector on the receiver. When the pushbutton is depressed the visible LED on the receiver should blink. Try to turn off the ambient light when you want to test the circuit in case of the ambient noise. If the visible led is blinking randomly, put exposed 35 mm camera film around the IR detector. (Note: Exposed 35 mm camera film blocks out visible light but is transparent to IR)

Questions:

- 1 How far away can the transmitter and receiver be before the signal from the transmitter to receiver is lost?
- 2 What applications can this circuit be used for?