
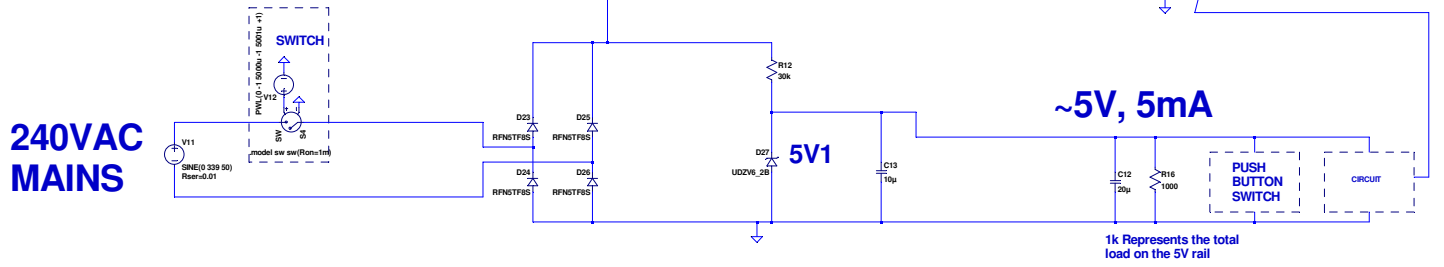


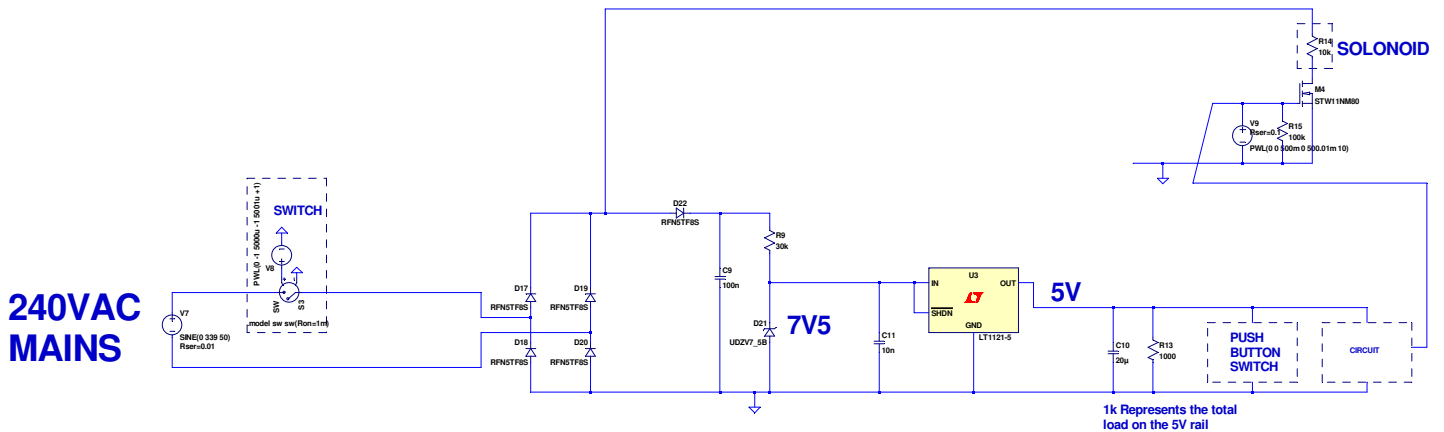
Linear regulator (R/Zener) power supply (5V, 5mA)




Linear regulator (R/Zener) power supply (5V, 5mA)



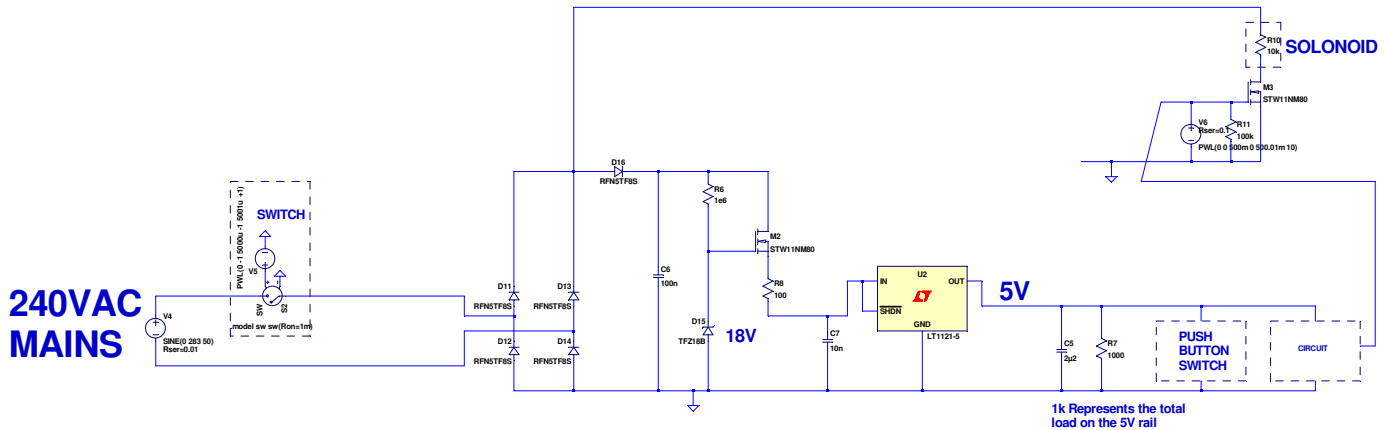Linear regulator (Zener/FET) power supply (5V, 5mA)



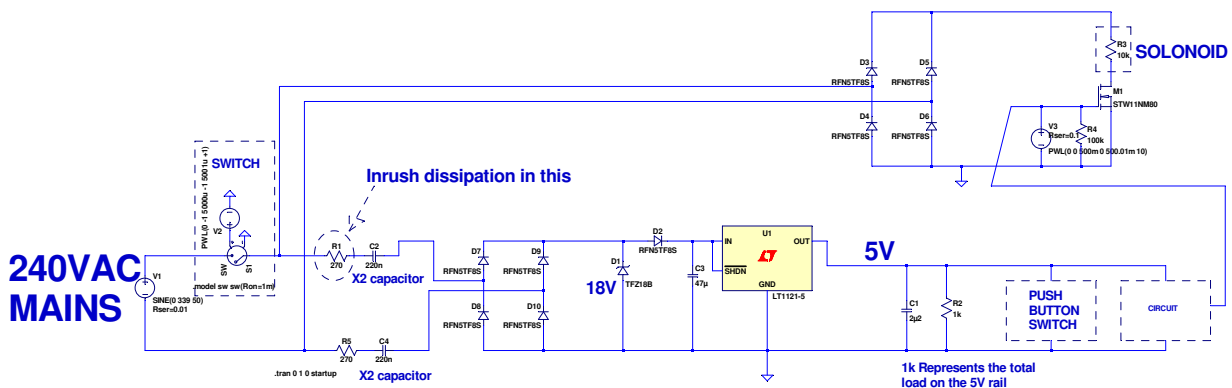Capacitive dropper power supply (5V, 5mA)



--- C:\forum\cap droper\5V 5mA from the mains.asc ---