

# Course on CMOS Data Converters for Communications

Bellaterra, Barcelona (Spain) May 6-10, 2002

## A Sigma-Delta modulator design example: From specs to measurements

*Fernando Medeiro, R. del Río,  
J.M. de la Rosa, B. Pérez-Verdú and Ángel Rodríguez-Vázquez*



**MIXMODEST**



*Mixed-Signal Design Cluster*

- Solution of a design exercise and practical considerations on the selection of:
  - ◆ **Architecture**
  - ◆ **Reference voltages**
  - ◆ **Integrator weights**
  - ◆ **Oversampling ratio**
  - ◆ **Sampling capacitors**
  - ◆ **Opamp DC-gain**
  - ◆ **Comparator hysteresis**
  - ◆ **Integrator and comparator dynamics**
  - ◆ **Switches**
  - ◆ **Component non-linearity**
- Simulating  $\Sigma\Delta$  modulators
- Circuit-level design
- Layout for mixed-signal performance
- From layout to measurements
- Measurements

• Modulator specifications:


- ◆ Effective resolution: **17bit**
- ◆ Signal Bandwidth: **4.8kHz**
- ◆ Maximum input signal: **2Vpp**
- ◆ Minimum **power consumption**

$$FOM = \frac{\text{Power(W)}}{2^{\text{resolution(bit)}} \times \text{DOR(S/s)}} \times 10^{12} \text{pJ}$$

[Goodenough ED'96]


Intended technology: 5-V 0.7 $\mu\text{m}$  CMOS

2nd-order  $\Sigma\Delta$  Modulator

 

[Candy, Trans. Comm. 85]

 Architecture selection [Medeiro, Kluwer98]



Minimum: 2nd-order  $\Delta\Sigma\text{M}$  with  $M \sim 300$

• When resolution is high

- ◆ In-band error power dominated by other error sources than quantization (for instance, thermal noise)
- ◆ Assume that  $P_{\text{error}} = P_Q + P_{th}$

$X_{FS}$  = modulator full scale       $L$  = modulator order

$$P_Q = \frac{X_{FS}^2}{12} \cdot \frac{\pi^{2L}}{(2L+1)M^{(2L+1)}}$$

$M$  = oversampling ratio

$$P_{th} \cong kT/(MC_s)$$


$C_s$  = sampling cap.

$$DR(X_{FS}, L, M, C_s) \cong \frac{(X_{FS}/2)^2/2}{\frac{X_{FS}^2}{12} \cdot \frac{\pi^{2L}}{(2L+1)M^{(2L+1)}} + kT/(MC_s)}$$

$$N_{\text{eff}} = \frac{DR|_{\text{dB}} - 1.76}{6.02} \text{ in bits}$$


- ◆ The larger  $X_{FS}$ , the better, but it is limited by output swing and dynamic requirements

• If quantization error dominates

 

$$DR \cong DR(X_{FS}, L, M, C_s)$$

• If white noise dominates

 

$$DR \cong DR(X_{FS}, M, C_s)$$

**DR does not depend on modulator order**


$$\left. \begin{aligned} P_Q &= \frac{X_{FS}^2}{12} \cdot \frac{\pi^4}{5M^5} \\ \Delta P_{Q(A_V)} &= \frac{X_{FS}^2}{12} \cdot \frac{(g_1 + g_2 + g_2')^2}{A_V^2} \cdot \frac{\pi^2}{3M^3} \\ \Delta P_{Q(h)} &= 4h^2 \cdot \frac{\pi^4}{5M^5} \end{aligned} \right\} \longrightarrow \text{Quantization error power}$$

$$\left. \begin{aligned} P_{smp} &= \frac{X_{FS}^2}{9M} \left(1 + \frac{C_p}{C_o}\right)^2 \left(\frac{C_{l1}}{C_{eq,1}}\right)^2 \exp\left(-\frac{g_m}{C_{eq,1}} \frac{1}{f_S}\right) \\ P_{int} &= \frac{X_{FS}^2}{9M} \left(1 + \frac{C_p}{C_s}\right)^2 \left(\frac{C_s}{C_{eq,2}}\right)^2 \left(1 + \frac{C_{l2}}{C_o}\right)^2 \exp\left(-\frac{g_m}{C_{eq,2}} \frac{1}{f_S}\right) \\ P_{sw} &= \frac{X_{FS}^2}{9M} \left(\frac{C_s}{C_o}\right)^2 \exp\left(-\frac{1}{2r_{on}C_s f_S}\right) \end{aligned} \right\} \text{Settling error power}$$

$$P_{th} = \frac{kT}{2MC_s} + \frac{kT}{M(C_s + C_p)} \left(\frac{1}{3} + g_m r_{on}\right) \longrightarrow \text{Thermal noise power}$$

• • •  $\longrightarrow$  Distortion, jitter noise ...

⇒ How to select the reference voltages?

 

⇒ **Input Full-Scale**,  $X_{FS} = E_{refp} - E_{refn}$

( $X_{FS} = 2E_{ref}$ ) for symmetrical references


⇒ **Specification: Max. signal = 2Vpp**

If

$$E_{ref} = 1.5V, X_{FS} = 3V$$


Max. input signal = **80%  $X_{FS} = 2.4V_{pp}$**

OK

 
 
## ⇒ Take into account:

- **Stability of the loop:**  $g_2' / (g_1 g_2) > 1.25$
- **Maximum SNR peak:**
  - ◆ Available integrator output swing
  - ◆ Required integrator dynamic
  - ◆ SC implementation: size and number of capacitors
  - ◆ ...



Weight	Bosse,88	Yin,94	Marques, 97	Medeiro, 98
$g_1, g_1'$	0.5	0.25	1/3	0.25
$g_2$	0.5	0.5	0.6	1
$g_2'$	0.5	0.25	0.4	0.5
Total int. OS / $E_{ref}$	3.5	2	2.4	2
# unitary caps.	6	10	12	9

➤ For an ideal  $\Delta\Sigma$  (Quantization error only)  $\rightarrow N_{\text{eff}} = \frac{1}{2} \log_2 [(2^N - 1)^2 (2L + 1) M^{2L+1} / (\pi^{2L})]$

➤ In our case,  $N = 1$   $L = 2$

➤ So,  $M$ ?

- For  $M = 128$ ,  $N_{\text{eff}} = 15.3\text{bit}$
- For  $M = 256$ ,  $N_{\text{eff}} = 17.8\text{bit}$ , **OK**


**$M = 256$**

➤ Thus,

$$P_Q = \frac{X_{FS}^2}{12} \cdot \frac{\pi^4}{5M^5} = -108.8\text{dB}$$

$$DR = \frac{E_{\text{ref}}^2/2}{P_Q} = 109.2\text{dB}$$

 
$$N_{\text{eff}} = \frac{DR(\text{dB}) - 1.76}{6.02} = 17.8\text{bit}$$



**$f_S = 2f_B M = 2.4576\text{MHz}$**

4.8kHz





 

➡ The choice of  $C_s$  is mainly related to:

- Thermal noise
- Integrator dynamics

## Folded-back noise in a SH circuit

  

$$P_{th} = \frac{kT}{2MC_s} + \frac{kT}{M(C_s + C_p)} \left( \frac{1}{3} + g_m r_{on} \right)$$

$$P_{th} @ kT \propto (MC_s)$$

$$C_s = 1\text{pF}$$


$$DR = \frac{E_{ref}^2/2}{(P_Q + P_{th})}$$

-107.9dB

17.3bit OK

$$C_o = C_s / g_1 = 4\text{pF}$$

⇒ Opamp finite DC-gain

 

$$H(z) = \frac{z^{-1}}{1 - z^{-1}} \quad Y(z) = z^{-2}X(z) + (1 - z^{-1})^2 E(z)$$


Implies infinite DC-gain! Not possible in practice

In practice: “Lossy” integrator

$$H(z) \stackrel{A_V \gg 1}{=} \frac{g_1 z^{-1}}{1 - (1 - \mu)z^{-1}}$$

$$m \approx \frac{1}{A_V}$$
 
$$Y(z) \cong z^{-2}X(z) + (1 - z^{-1} + \mu z^{-1})^2 E(z)$$




$$\Delta P_Q(A_V) = \frac{X_{FS}^2}{12} \cdot \frac{(g_1 + g_2 + g_2')^2}{A_V^2} \cdot \frac{\pi^2}{3M^3}$$

Quite insensitive to the finite opamp DC-gain

## ➤ Comparator hysteresis

**Hysteresis and offset**

 

**Offset**

Attenuated by the integrator DC-gain

**Hysteresis**

$$\Delta P_Q(h) = 4h^2 \cdot \frac{\pi^4}{5M^5}$$

Quite insensitive to hysteresis

We do not need precise comparators

➤ If we set




$$A_V = 500 \quad h = 50\text{mV}$$

$$DR = \frac{E_{ref}^2/2}{(P_Q + \Delta P_Q(A_V) + \Delta P_Q(h) + P_{th})} \longrightarrow 17.2\text{bit OK}$$


$\swarrow$   $\searrow$   
 -128.3dB      -127.5dB



➡ We already set
 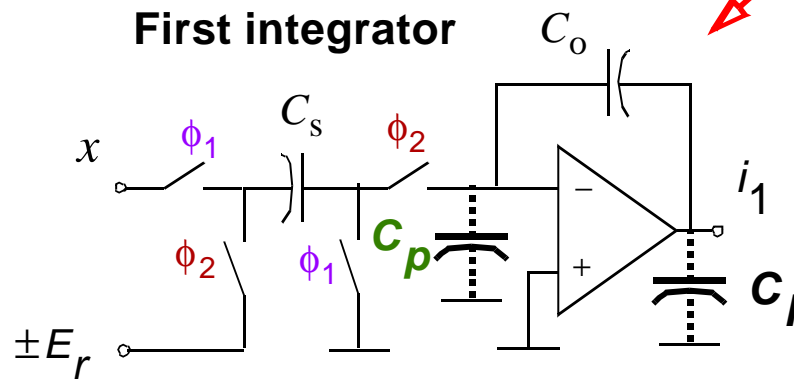 
$$C_s = 1\text{pF} \quad C_o = 4\text{pF}$$



➡  $C_p$  ?

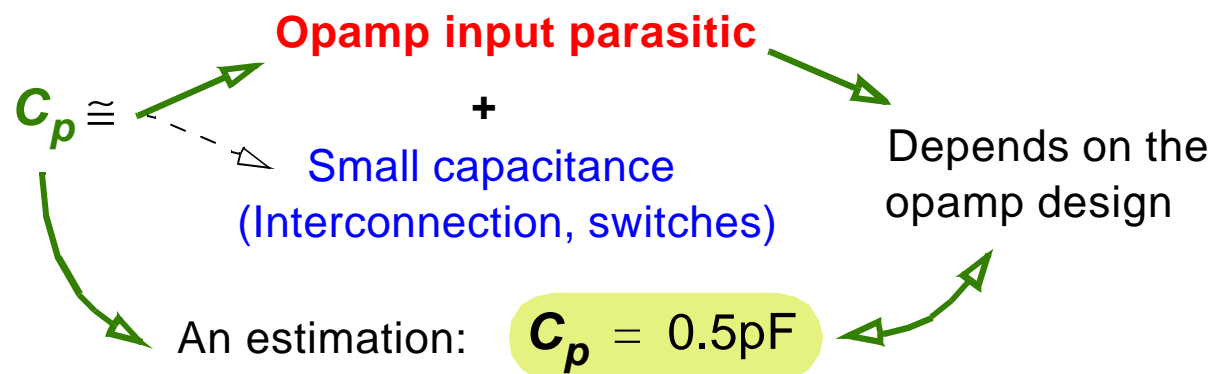

  


$$C_{s2} = C_{s2'} = 0.5\text{pF}$$

$$C_{o2} = 2\text{pF}$$


$$g_2 = \frac{C_{s2}}{C_{o2}} + \frac{C_{s2'}}{C_{o2}} = 0.5$$

$$g_2' = \frac{C_{s2'}}{C_{o2}} = 0.25$$




### Second integrator

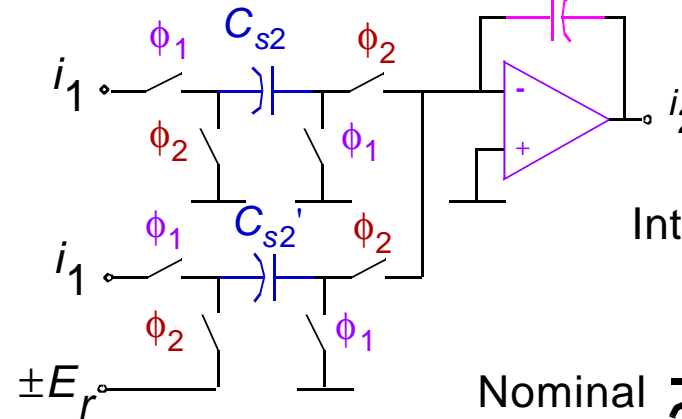

### First integrator


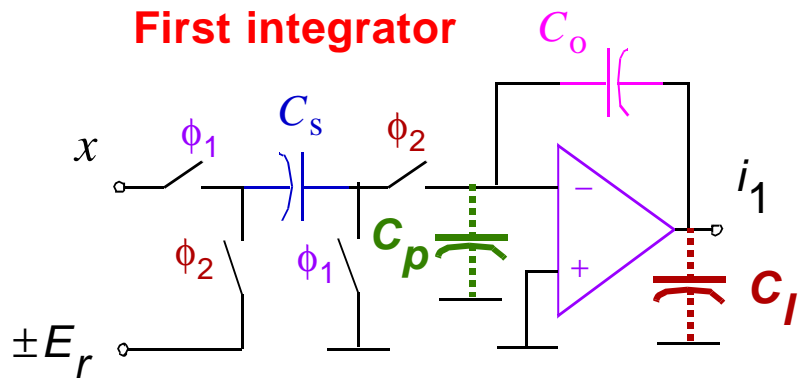


### Integrated capacitors

   

$$C_{I1} = 3.5\text{pF}$$

$$C_{I2} = 2\text{pF}$$

  

$$P_{samp} = \frac{X_{FS}^2}{9M} \left(1 + \frac{C_p}{C_o}\right)^2 \left(\frac{C_{I1}}{C_{eq,1}}\right)^2 \exp\left(-\frac{g_m}{C_{eq,1}} \frac{1}{f_S}\right)$$

$$P_{int} = \frac{X_{FS}^2}{9M} \left(1 + \frac{C_p}{C_s}\right)^2 \left(\frac{C_s}{C_{eq,2}}\right)^2 \left(1 + \frac{C_{I2}}{C_o}\right)^2 \exp\left(-\frac{g_m}{C_{eq,2}} \frac{1}{f_S}\right)$$

Valid for linear (no slew-rate) settling, or non-linear (slew-rate) if

$$I_o = g_m (C_s / C_{eq,2}) (1 + C_{I2} / C_o) (X_{FS} / 4)$$


$$C_{eq,1} = C_p + C_{I1} (1 + C_p / C_o) = 4.4375 \text{ pF}$$

$$C_{eq,2} = C_s + C_p + C_{I2} [1 + (C_s + C_p) / C_o] = 4.25 \text{ pF}$$

$$g_m = 220 \mu\text{A/V}$$

$$\Rightarrow I_o = 58 \mu\text{A}$$

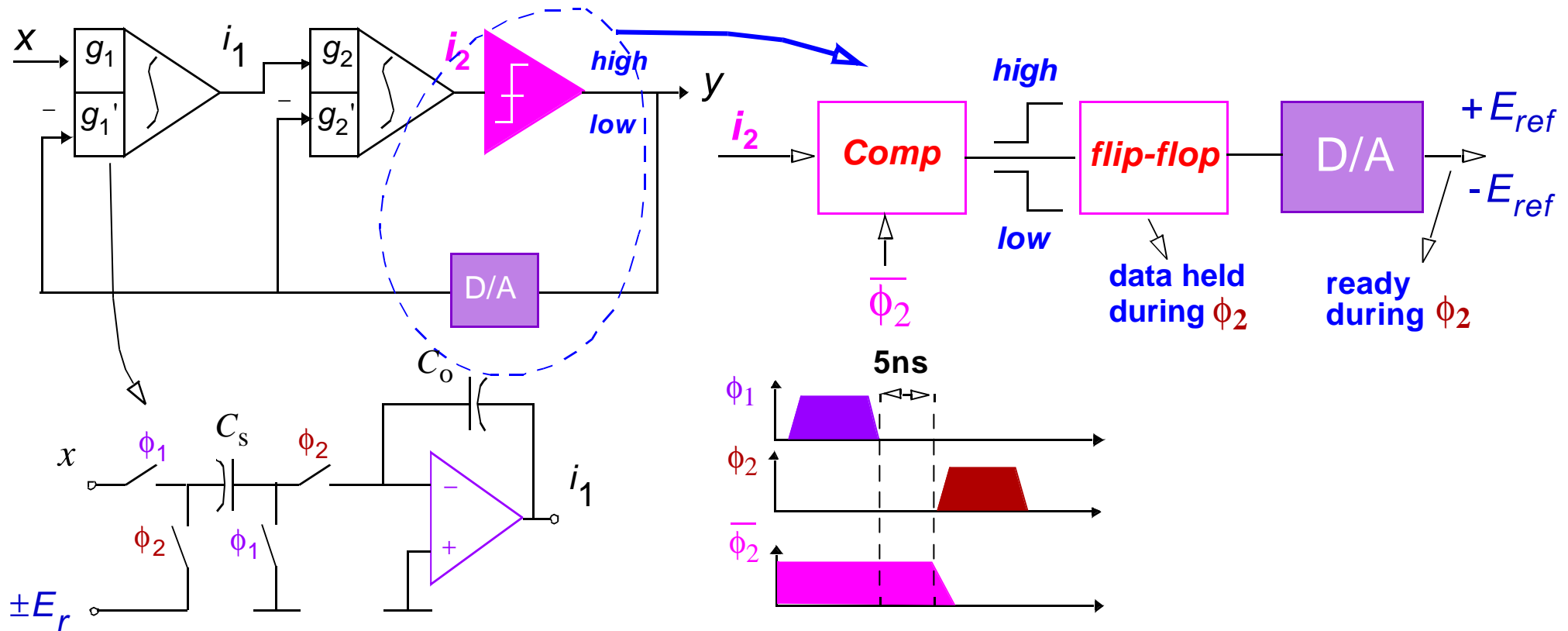
$$DR = \frac{E_{ref}^2 / 2}{(P_Q^* + P_{th} + P_{samp} + P_{int})} \rightarrow 17.1 \text{ bit OK}$$



⇒ The comparator does not have to be very precise (50mV is OK), but it must be fast enough

⇒ Usual choice: to make the comparator resolve in 1/8 of the clock period = 50ns

Use a latched comparator

 

### Thermal noise

$$P_{th} = \frac{kT}{2MC_s} + \frac{kT}{M(C_s + C_p)} \left( \frac{1}{3} + g_m r_{on} \right)$$

### Incorrect sampling error

$$P_{sw} = \frac{X_{FS}^2}{9M} \left( \frac{C_s}{C_o} \right)^2 \exp \left( -\frac{1}{2r_{on} C_s f_s} \right) \times \text{Circuit Diagram}$$

The circuit diagram shows a red zigzag line labeled  $2r_{on}$  in series with a capacitor  $C_s$ .

$$r_{on} = 2k\Omega$$

$$P_{th} = -107.8\text{dB}$$

$$P_{sw} = -478\text{dB}$$

Previously, we estimated

$$P_{th} = -107.9\text{dB}$$

OK



## Non-linear capacitors

Voltage coefficient  $k_v$  Weak non-linearity  $k_v \ll 1$


$$C(v) = C \exp(k_v v) \approx C(1 + k_v v)$$

$A_{inp} \cos(\omega t)$   $\Delta\Sigma$   $\approx A_{inp} \cos(\omega t + \phi_1)$



$$P_{cni} \approx \begin{cases} \frac{1}{8} k_v^2 A_{inp}^4 & \text{Singed-end circuitry} \\ 0 & \text{Fully-differential circuitry} \end{cases}$$

$+ \frac{1}{2} k_v A_{inp}^2 \cos(2\omega t + \phi_2)$
 
## Some integrated capacitor are not weakly non-linear!!



### Non-linear opamp DC-gain

  

$$A(i_1) = A_V(1 + \gamma_1 i_1 + \gamma_2 i_1^2)$$

$$A_{inp} \cos(\omega t) \rightarrow \Delta\Sigma \rightarrow A_{inp} \cos(\omega t + \varphi_1) + \frac{2|\gamma_1|}{A_V} g_1^2 A_{inp}^2 \cos(2\omega t + \varphi_2) + \frac{2|\gamma_2|}{A_V} g_1^3 A_{inp}^3 \cos(3\omega t + \varphi_2)$$

⇒ In fully-differential mode,  $\gamma_1 \ll 1$

⇒ Remember that  $A_V = 500 \rightarrow \gamma_2 \leq 5\%$  to keep resolution above 17bit



Very demanding !

⇒ Solution: increase DC-gain

$$A_V = 1000 \rightarrow \gamma_1 = 1\%, \gamma_2 = 10\% \quad \text{OK}$$

## Non-uniform sampling

$$T_S = 1/f_S$$

  


nearly gaussian

$$P_j = \frac{A_{inp}^2}{2} \frac{(2\pi f_B \sigma_T)^2}{M}$$

$$\sigma_T \leq 1\text{ns}$$

17bit ok

 

$$DR = \frac{E_{ref}^2/2}{(P_Q^* + P_{th} + P_{smp} + P_{int} + P_{HD} + P_j)}$$




Example for high-frequency application

➤ **Simulating  $\Sigma\Delta$  modulators...**

**Non-linear  
operation**

**Need for time-domain  
simulation**


**Lots of samples  
required**

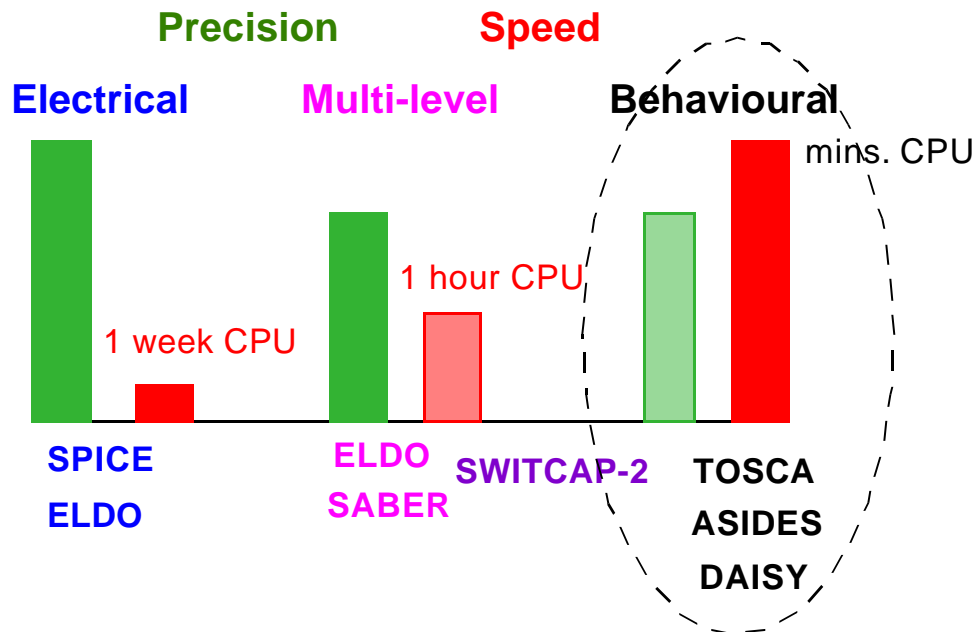  

**Use behavioural simulation  
but, it must precise:**

- Non-ideal simulation
- Practice-founded behavioural models
- IC-oriented

**Dedicated behavioural simulators**

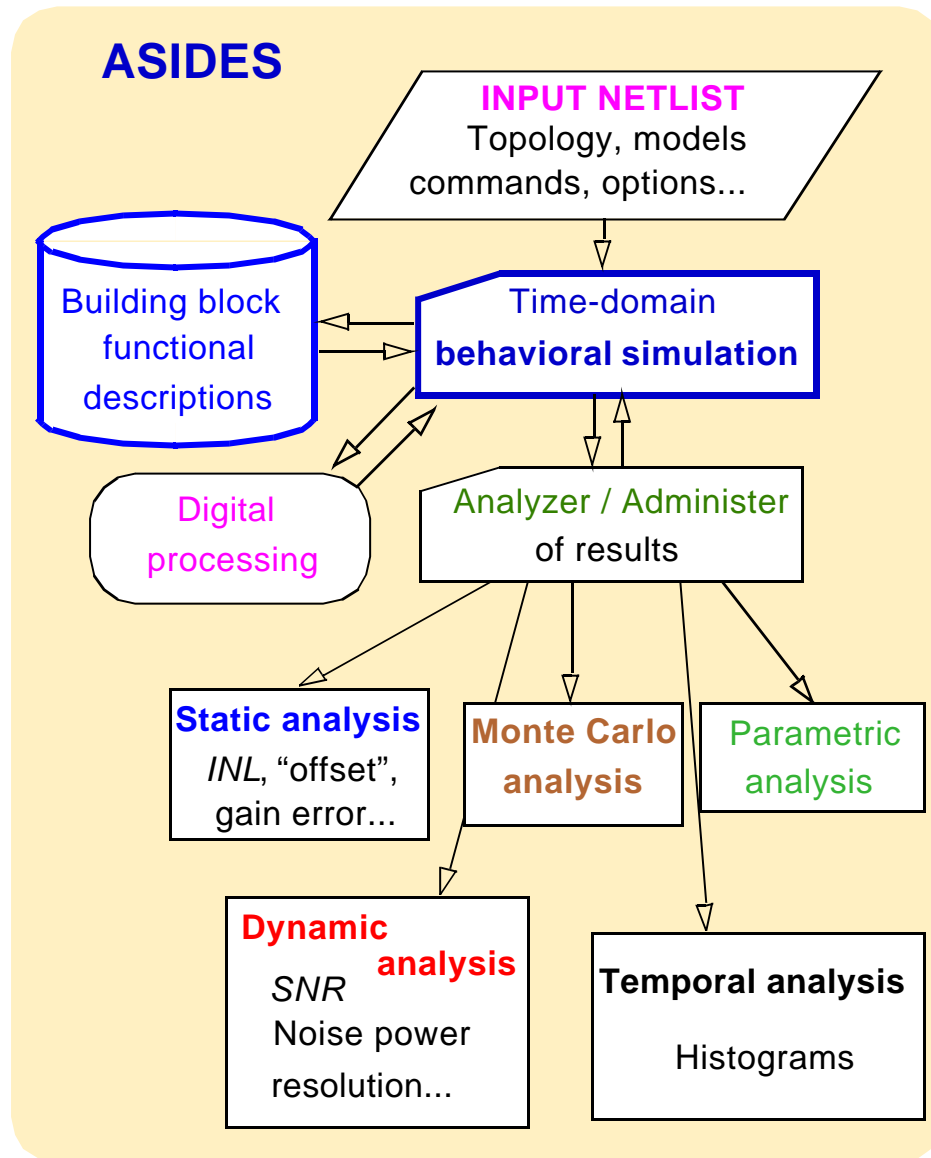

### Covered non-idealities

Building Blocks		Non-idealities	Consequences
Integrators	Opamps	DC-gain, finite and non-linear	Increased quantization error, harmonic distortion.
		Dynamic limitations	Settling error, harmonic distortion.
		Output range	Overloading.
		Thermal noise	White noise.
	Switches	ON-resistance, thermal noise	Settling error, white noise.
	Capacitors	Non-linearity, mismatch	Increased quantization error, harmonic distortion.
	Clock	Jitter	Jitter Noise.
	Comparators	Hysteresis, offset	Increased quantization error.
	Multi-bit ADC, DAC	Non-linearity, gain error, offset	Increased quantization error. Harmonic distortion.

Vin **inp** ampl=0.5 freq=1.2k;


Comp1 **out** (**oi2**) real cm;

I1 **oi1** (inp,out\*0.25) real im1;

I2 **oi2** (**oi1**,0\*0.25 **oi1**,out\*0.25) real im2;

.output spc(out);  
 .clock freq=2.4576x jitter=1n;  
 .oversamp 256;  
 .nsamp 65536;  
 .options fullydiff;

...

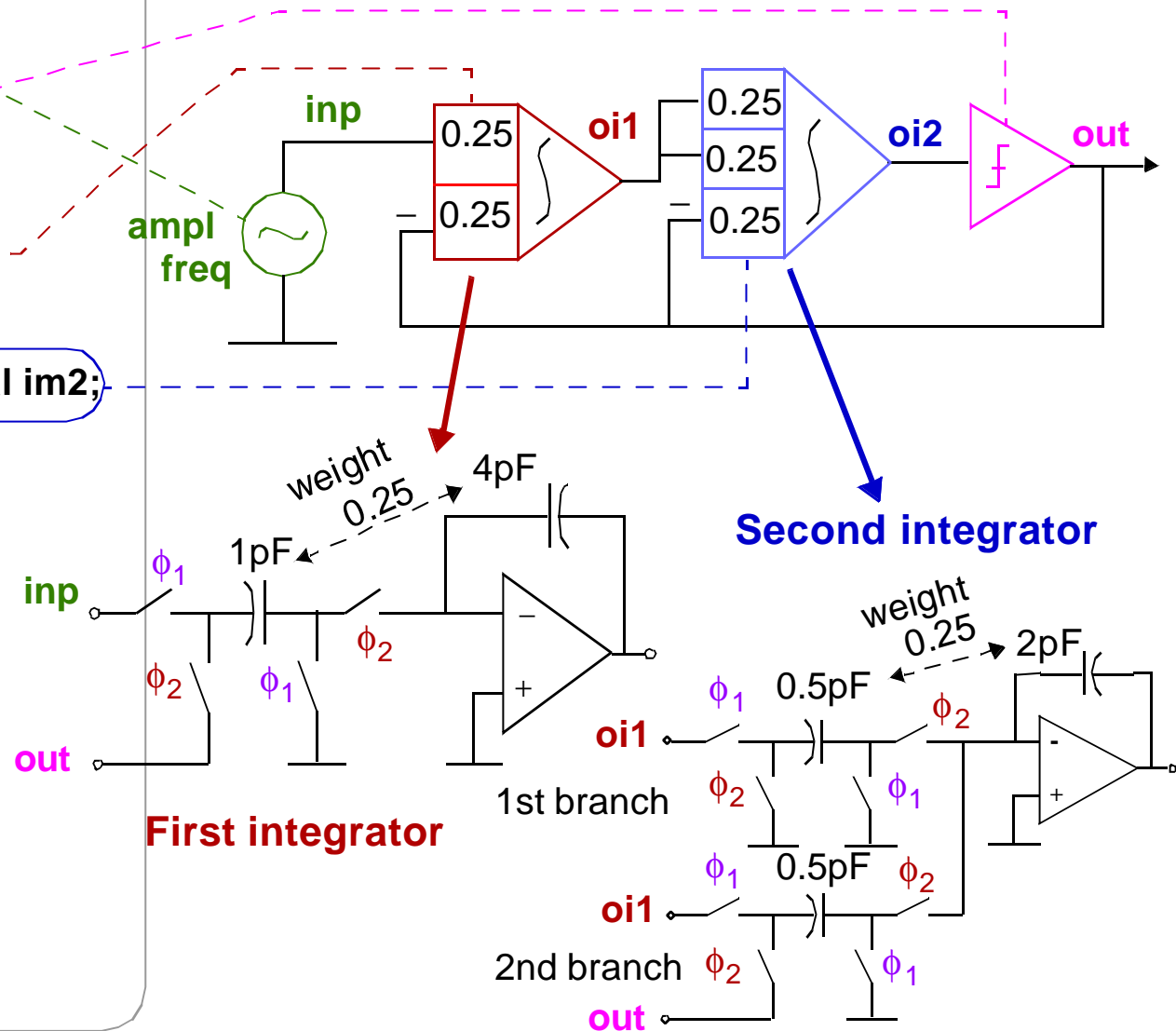

Vin inp ampl=0.5 freq=2.4k;

Comp1 out (oi2) real **cm**;  
 I1 oi1 (inp,out\*0.25) real **im1**;  
 I2 oi2 (oi1,0\*0.25 oi1,out\*0.25) real **im2**;

.output spc(out);  
 .clock freq=2.4576x jitter=1n;  
 .oversamp 256;  
 .nsamp 65536;  
 .options fullydiff;

**.model cm Comparator**

vhigh=1.5 vlow=-1.5 hys=50m;

**.model im1 Integrator**

cfb=4p ron=2k cload=0.5p  
 dcgain=60d dcgnl1=1 dcgnl1=-10  
 gm=220u imax=58u btpar=0.5  
 osp=1.5 osn=-1.5 cpa=0.5p;

**.model im2 Integrator**

cfb=4p ron=2k cload=0.5p  
 dcgain=60d dcgnl1=1 dcgnl1=-10  
 gm=220u imax=58u btpar=0.5  
 osp=1.5 osn=-1.5 cpa=0.5p;

### Manual sizing results

Topology	2nd-order	Modulator
Sampling frequency	2.4576MHz	
Oversampling ratio	256	
DAC output high, Low	$\pm 1.5V$	Quantizer
Hysteresis	$< 50mV$	
$g_1, g_1', g_2, g_2'$	0.25, 0.25, 0.5, 0.25	Integrators
Integration capacitor (1st int.)	4pF	
Integration capacitor (2nd int.)	2pF	
MOS switch-ON resistance	2k $\Omega$	
Maximum clock jitter	$< 1ns$	
DC-gain	$> 60dB$	Opamps
DC-gain non-linearity	$< 1\%V^{-1}, 10\%V^{-2}$	
Transconductance	$> 220mA/V$	
Maximum output current	$> 58mA$	
Total output swing	$> 3V$	
Parasitic input capacitor	$< 0.5pF$	

● “cload” must include **only**:

- ◆ opamp output parasitic
- ◆ input parasitic of a possible quantizer

● Remaining contributions to  $C_{I1}$  and  $C_{I2}$  are automatically estimated by ASIDES, through “btpar” -> relative bottom parasitic

## ➤ Output spectrum


```

Vin inp ampl=1 freq=1.2k;
Comp1 out (oi2) real cm;
I1 oi1 (inp,out*0.25) real im1;
I2 oi2 (oi1,0*0.25 oi1,out*0.25) real im2;

.clock freq=2.4576x jitter=1n;
.options fullydiff; # Using differential circuitry

.nsamp 65536; # Number of samples
.output spc(out); # Amplitude spectrum

```

 


## ➤ Signal-to-noise vs. input amplitude

```

Vin inp ampl=(-100 4 2) freq=1.2k;
Comp1 out (oi2) real cm;
I1 oi1 (inp,out*0.25) real im1;
I2 oi2 (oi1,0*0.25 oi1,out*0.25) real im2;
.clock freq=2.4576x jitter=1n;
.options fullydiff; # Using differential circuitry
.nsamp 65536; # Number of samples

.output snr(out); # Signal-to-noise
.oversamp 256; # Oversampling ratio
.filtfile file=f256_1024 type=fir # FIR filter

```

 




## Relaxing 2nd integrator dynamics

```
.output ibn(out); # In-band error power

.option nother fullydiff; # disables thermal noise


 
.model im1 Integrator
      gm=220u      imax=58u
      ...
.model im2 Integrator
      gm=gm2      imax=58u
      ...
.param gm2=sweep(dec 20 5u 100u)
```


  
## Fine-tuning 1st integrator dynamics




```
.model im1 Integrator
      gm=220u      imax=io1
.param io1=sweep(lin 20u 80u 5u)

.model im1 Integrator
      gm=gm1      imax=40u
.param gm1=sweep(lin 100u 250u 2u)
```



   
### ➤ Fine-tuning DC gain

```
.model im1 Integrator
dcgain=dcg dcgnl1=1 dcgnl2=10
.param dcg=sweep(dec 10 10 1000)
```





	1st opamp		2nd opamp	
	Before	After	Before	After
gm	220 $\mu$ A/V	205 $\mu$ A/V	200 $\mu$ A/V	50 $\mu$ A/V
imax	58 $\mu$ A	40 $\mu$ A	58 $\mu$ A	12 $\mu$ A
dcgain	1000	800	1000	200

 

Fully-differential SC schematic

- Large common-mode rejection
- 3dB increase in SNR
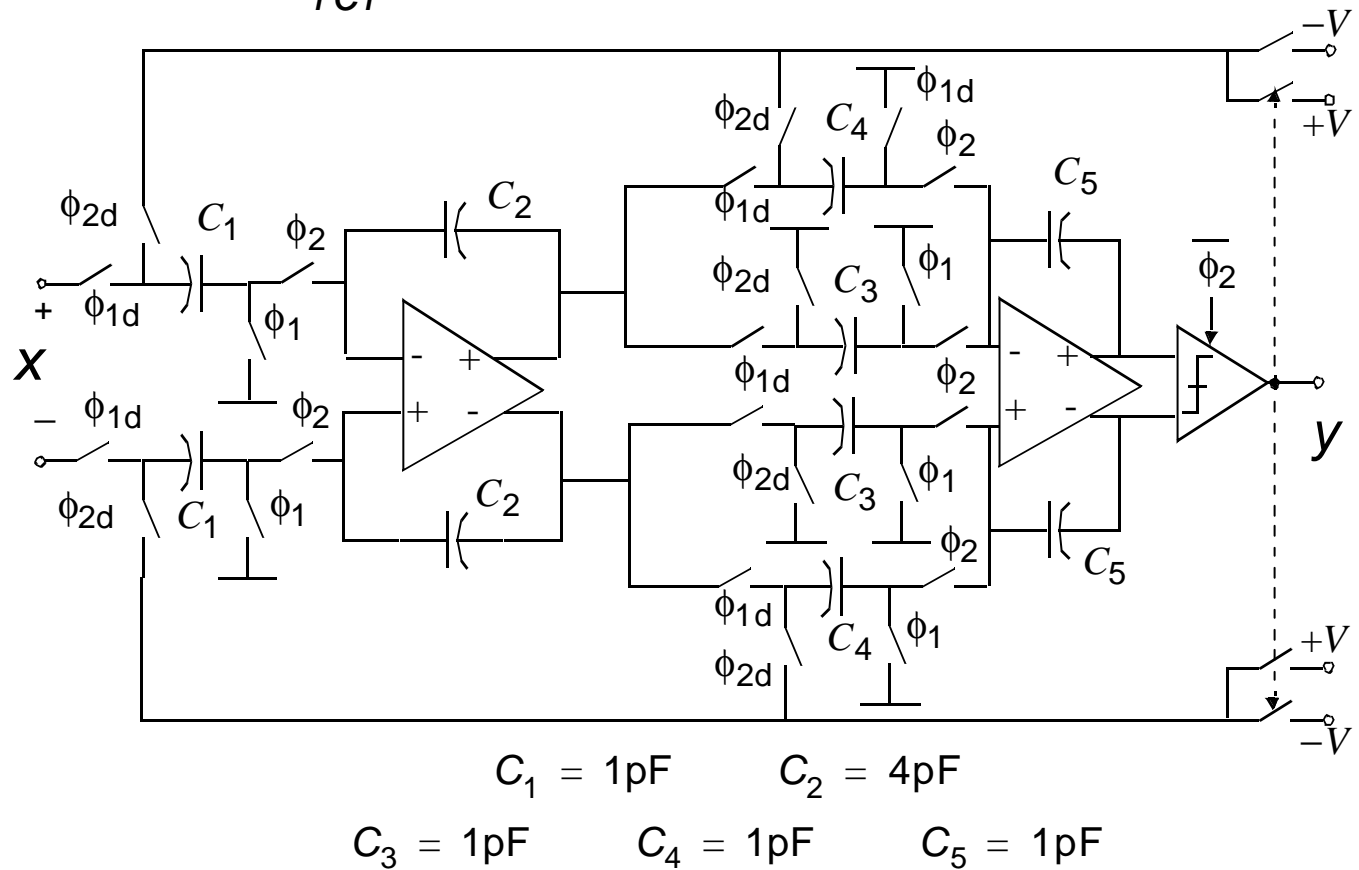 
$$\begin{aligned} +E_{ref} &= +V - (-V) = 2V \\ -E_{ref} &= -V - (+V) = -2V \end{aligned} \longrightarrow V = \frac{E_{ref}}{2}$$



⇒ **Opamp topology selection must primarily consider:**

● **Output swing requirement**

- ◆ **Remember:** it critically depends on the integrator weight
- ◆ Cascode techniques may not be valid

● **Open-loop DC gain requirement**

- ◆ Single, non-cascode stages may not be enough
- ◆ Cascode, and/or multi-stage topologies may be required


● **Dynamic requirements**

- ◆ Obtaining correct transient behaviour is harder in multi-stage topologies

● **Power dissipation and simplicity**

⇒ **In our case**

 
- ◆ Technology is 5-V Supply, O.S. = 3V differential => not tight
- ◆ Cascode techniques appropriate to obtain required DC gain



**Telescopic cascode**

**Best speed-power figure**

 **CM output voltage different from input**




**Folded cascode**

**Good speed-power figure**

**CM output = CM input**
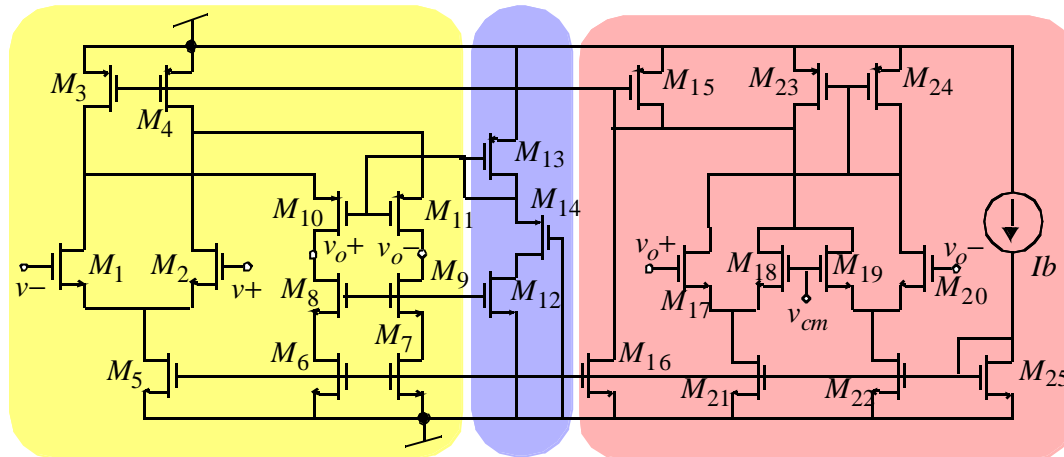
### ➤ Fully-differential folded-cascode OTA



OTA core

Biasing


Static Common-mode  
feed-back net

### ➤ Up to approx. 3V supply voltage


- Good trade-off performance/ power consumption
- Relatively easy to design
  - ◆ Single-stage amplifier
- Good supply rejection ratio figures
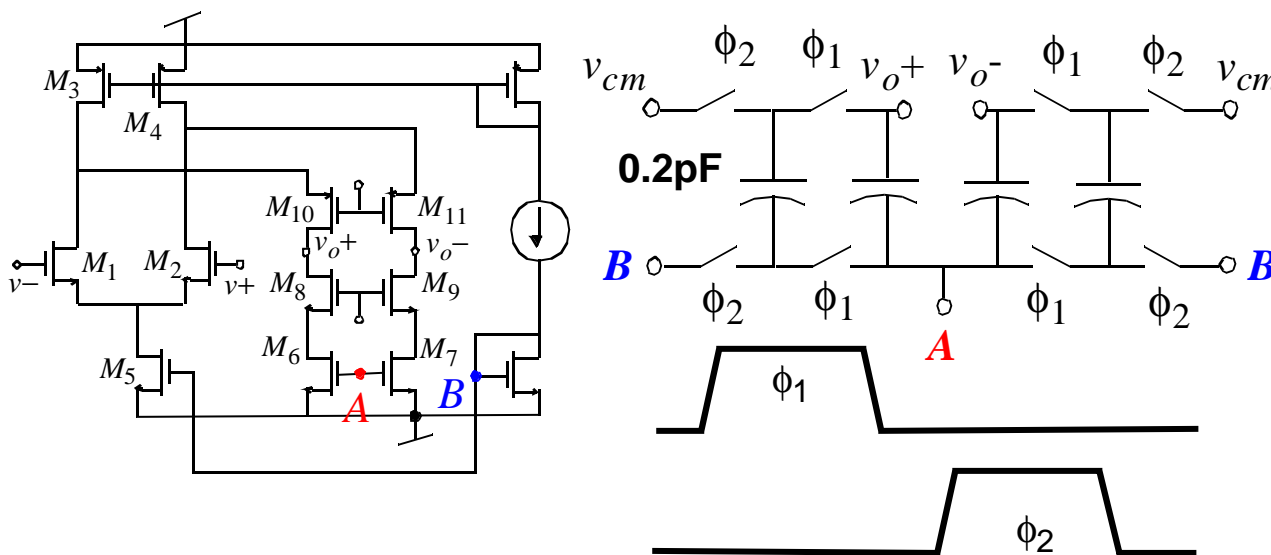
### Dynamic Common-mode feed-back net


- Lower power consumption
  - ◆ CMFB net practically does not consume
- but,
  - ◆ Larger difficulties in the test




➤ 1-bit Quantizer, latched comparator

 


**resolution  
around 50mV**

 

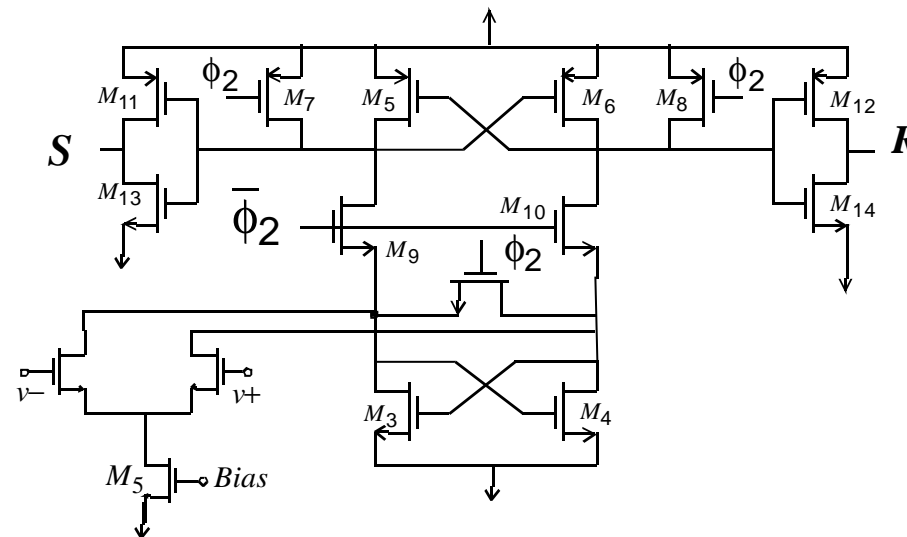➤ If a larger resolution is needed, use a differential pair as input transconductor



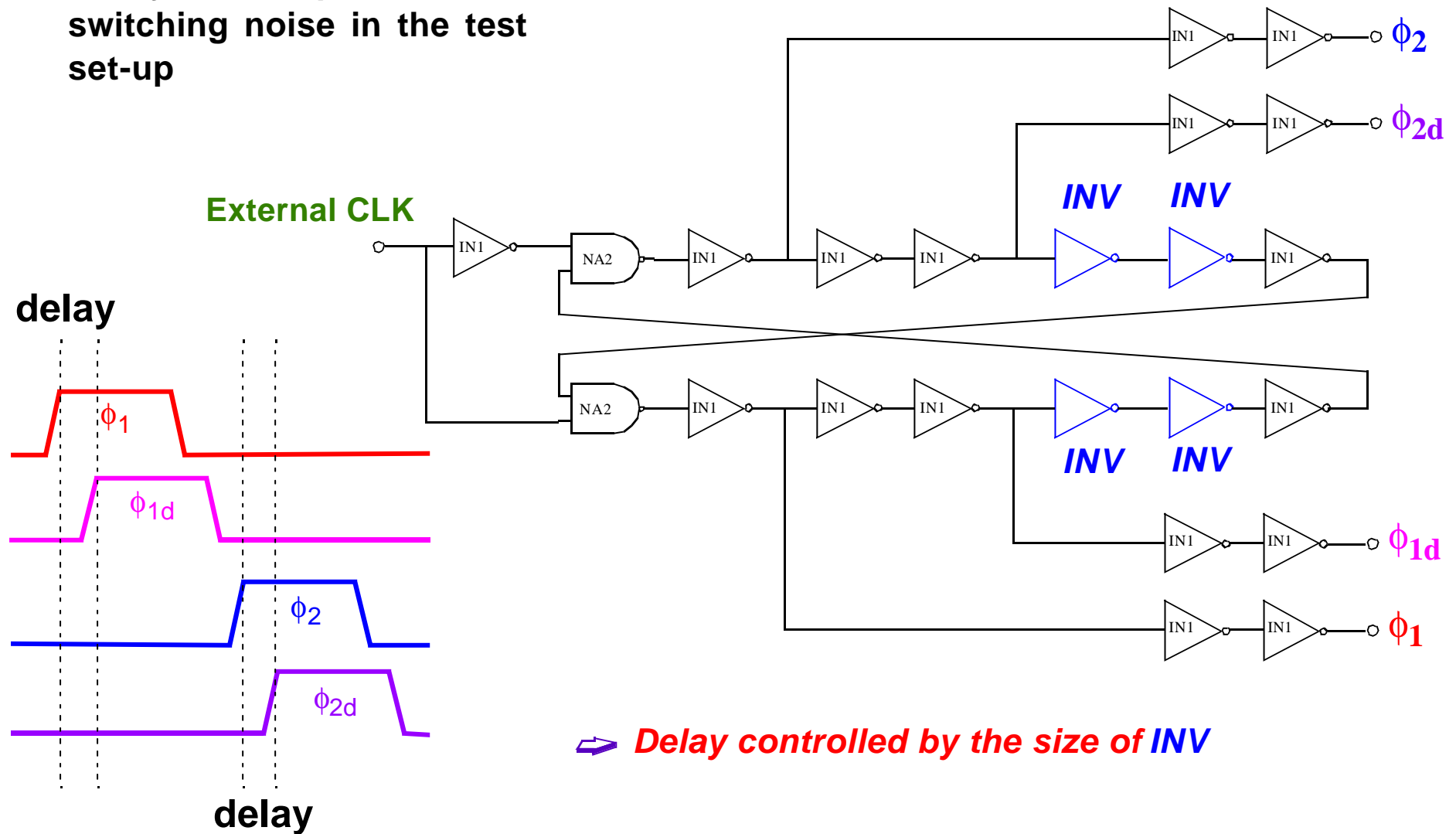- **Always on-chip to reduce switching noise in the test set-up**








# Layout for mixed-signal performance:
 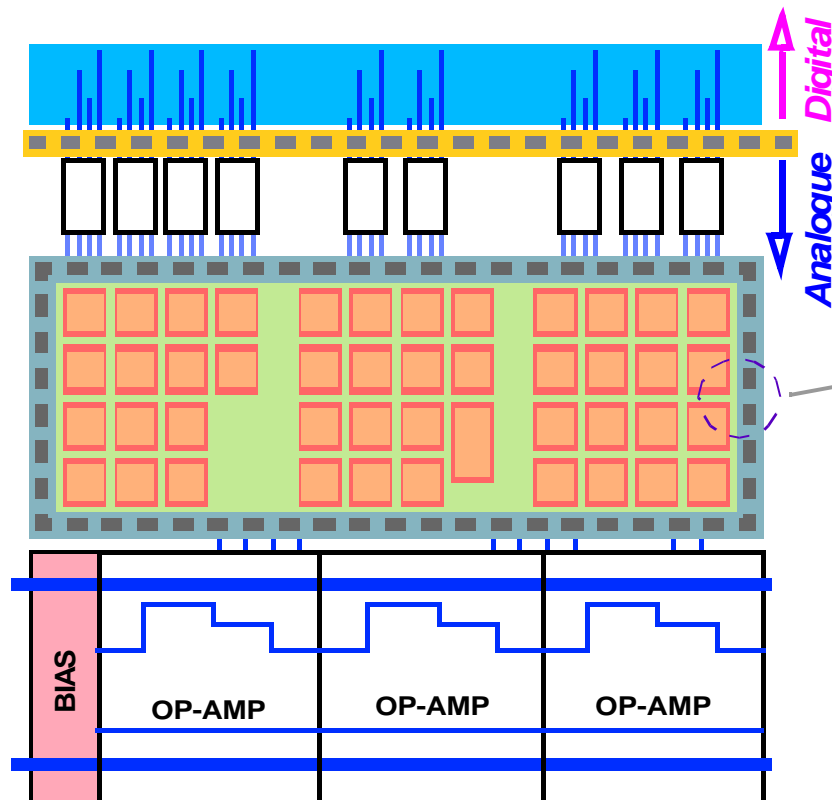   
## Requirements



- A good layout must

- ▶ Protect against interferences
- ▶ Ensure good matching / typical performance
- ▶ Reduce parasitics







⇒ **MOS transistors**

  


⇒ **Resistors**

 


⇒ **Capacitors**

 


⇒ **Inductors**

 


⇒ **Interconnects**



 


⇒ **Substrate contacts (p+ guard ring)**

 


⇒ **n+ in n-well guard ring**

 


 
 
 


$$\frac{W_u}{L} R_{\square \text{poly}} < \frac{1}{g_{m, \text{unitary}}} \Rightarrow \text{Th. noise}_{\text{poly}} < \text{Th. noise}_{\text{MOS}}$$



 
- ◆ Reduced area
- ◆ Reduced bottom junction capacitance (drain and source areas shared)
- ◆ Reduced side-wall junction capacitance (avoids contacting active area and channel-stop p implant)
- ◆ Usually well characterised except for parasitics



“Exotic”

    

⇒ Specific

   


## • Preserving symmetry helps a lot

- ◆ Even order non-linearity is suppressed
- ◆ Common-mode interferences are largely attenuated


➡ **Two devices are actually “equal” if**

✓ **Same structure**

 

✓ **Same temperature**


Constant  $T$

 


✓ **Same shape and size**

✓ **Minimum Distance**


✓ **Same Orientation**

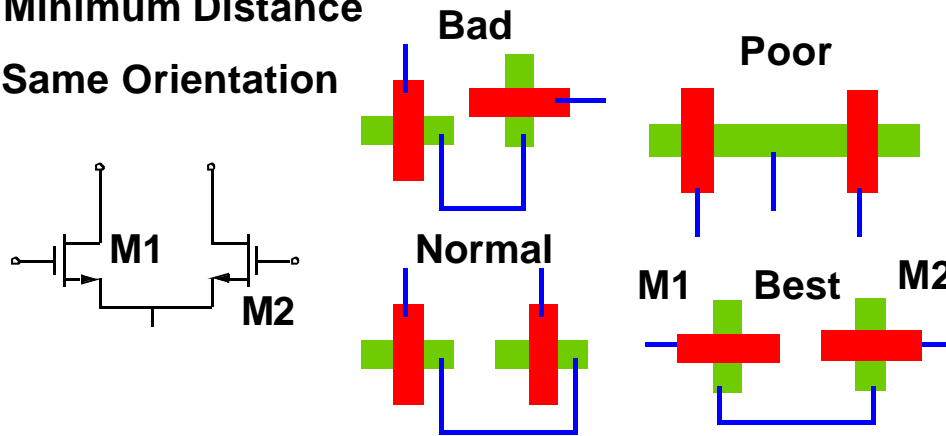

✓ **Cancel linear gradients**

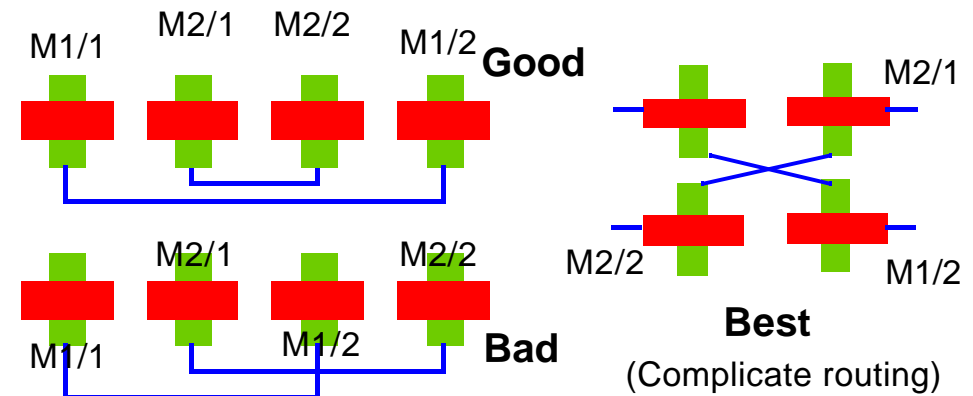

✓ **Same Surrounding**

 




## • There are still differences due to local errors

- ◆ Errors are inverse function of device size

$$\frac{\sigma_p^2}{p^2} \approx \frac{A_p^2}{WL} + \frac{B_p^2}{W^2L} + \frac{C_p^2}{WL^2}$$




- ◆ Use statistic models to estimate minimum dimensions

## Thin oxide capacitor ("analog" CMOS)

   




Density	<div><div></div></div>
Linearity	<div><div></div></div>
Temperature	<div><div></div></div>
Parasitics	<div><div></div></div>
Matching	<div><div></div></div>

## Digital CMOS compatible

   


Density	<div><div></div></div>
Linearity	<div><div></div></div>
Temperature	<div><div></div></div>
Parasitics	<div><div></div></div>
Matching	<div><div></div></div>

### Multi-layer

   

- 😊 Polishing after dielectric deposition improves matching
- 😞 Lack of models

### Lateral capacitors

 


- 😊 Large density (combination with multi-layer)
- 😞 Lack of models (value? variations? ...)

**Best choice!**

**M-i-M**

Density	<div><div></div></div>
Linearity	<div><div></div></div>
Temperature	<div><div></div></div>
Parasitics	<div><div></div></div>
Matching	<div><div></div></div>





## ● MOS capacitors

 

😊 Maximum density



😊 Good matching

😞 Very poor linearity

  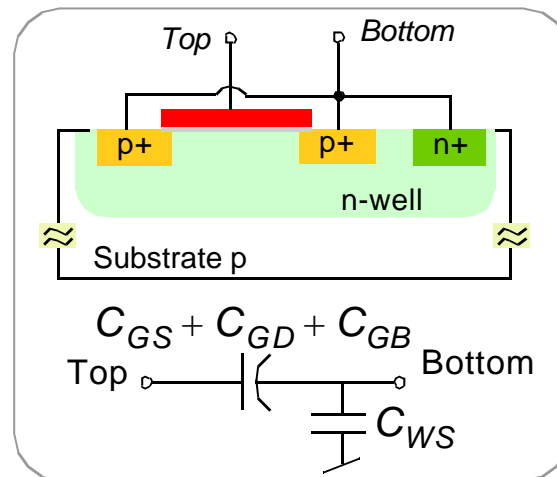 


Strong inversion

$C_{GS} + C_{GD}$

 
 


Strong inversion


Mainly used for decoupling

 

Accumulation

  

Accumulation

 




Non floating  $V_{SS}$
   
### ● Double-poly capacitors:

- ▶ Use **centroid** structure with **equally sized** unitary cap. or with the **same A/P** and locate then over an isotherm
- ▶ In non-integer ratios the non-unitary cap. must contribute to the largest capacitance and its value should be as close as possible to the unitary
- ▶ **Same surroundings** up to 50μm
- ▶ Make **interconnect capacitance** keep the same ratio as nominal
- ▶ Place grounded **decoupling lines** between interconnects
- ▶ If possible, place a **grounded metal** plane over the structure and a **well** below it connected to a “clean” voltage



Largely dependent on the process and capacitor type



Unitaries



90° angles






135° angles



No angles


### Diffused resistors

   


Less doping

- ▶  $R_{\square}$  larger (1-2 k $\Omega$ )
- ▶ Smaller parasitic cap
- ▶ Worse linearity
- ▶ Larger temperature coeff



### Deposited resistors

 



If salicided

 

Hypodoped ("Analog" CMOS)

 
 


  Proper combination of n- and p-poly may improve linearity and tempempature dependence





Large temperature dependence

### Channel resistors

  


### ⇒ High-precision resistor ladder

  

- ▶ **Folded structure** (if required) to reduce gradient effects
- ▶ **Contacts outside the resistive string**
- ▶ **Two contacts per tab** to compensate for mask displacement

### ⇒ High-speed resistor ladder

 

- ▶ **Small sheet resistance**
- ▶ **Small parasitic capacitance to substrate**
- ▶ **Good linearity**
- but...
- ▶ **Good matching requires large width**
- ▶ **Large temperature coefficient**



⇒ **Crosstalk**

- Capacitive and/or inductive coupling between interconnects

⇒ **Substrate noise**


- Coupled and propagated through the common substrate

⇒ **Power and ground supply bounce**

- Coupled and propagated through power and ground distribution




 
### Causes

- ◆ Capacitive coupling between routing lines
- ◆ Capacitive coupling to substrate
- ◆ Inductive coupling through package


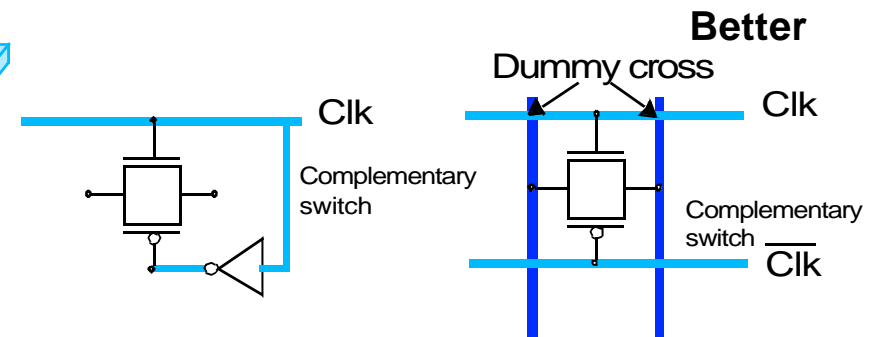  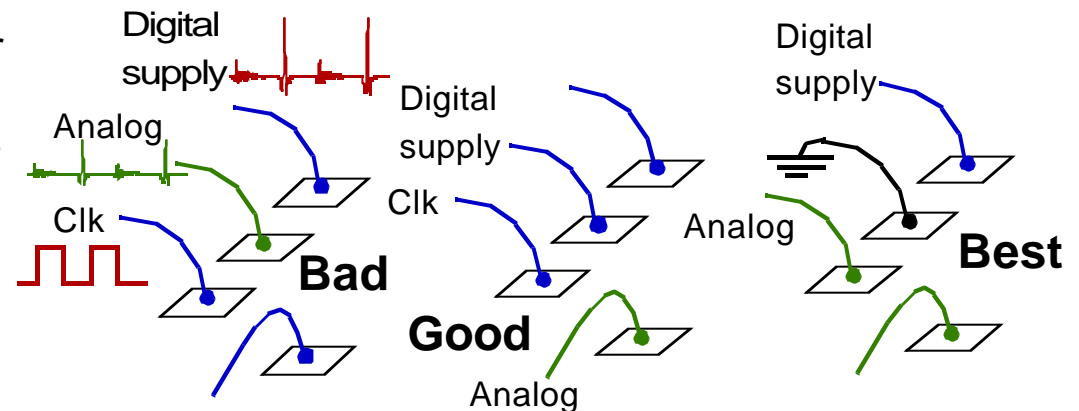
### Solutions


- ◆ Increase distance between pads/pins for noisy and sensitive signals
- ◆ Increase distance between noisy and sensitive lines
- ◆ Add shield between closely spaced lines
- ◆ Avoid crossing of noisy and sensitive lines
- ◆ Add shield to unavoidable crossings
- ◆ Use differential circuits and clocks



## Shielding metal lines

 
### Example:

Decoupling analog supply from a noisy substrate



- ▶ Attenuates on-chip and off-chip interferences
- ▶ Reduces capacitive coupling to substrate
- ▶ May increase capacitive loading
- ▶ **Requires a “clean” voltage**  
**Low-impedance path to ground**


## Shielding MOS transistors

 



n-well is not a good shield due to its high resistivity

Place contacts surrounding the device


## Shielding passive devices

 



Capacitors

  


Resistors

 


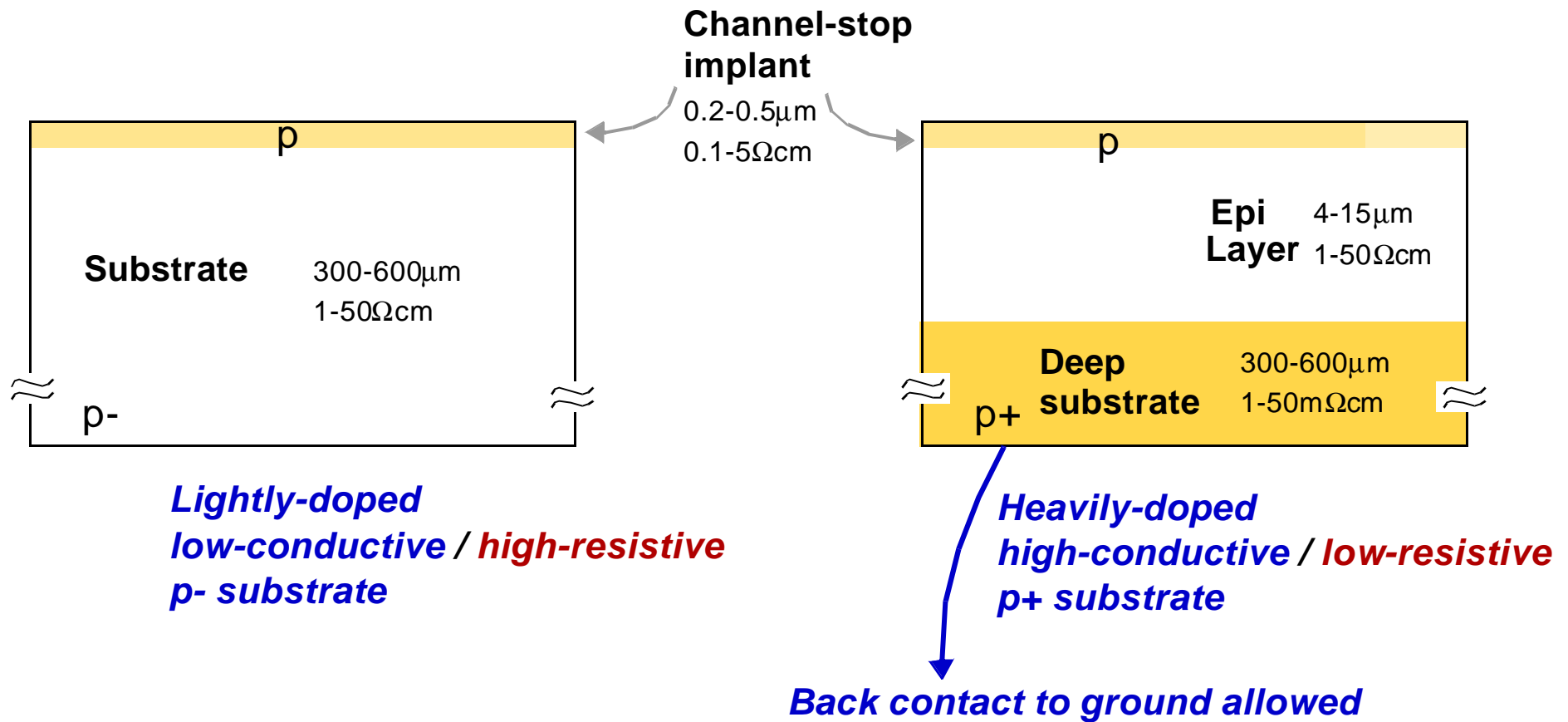

 


➤ **Substrate models** [Verg95]

 

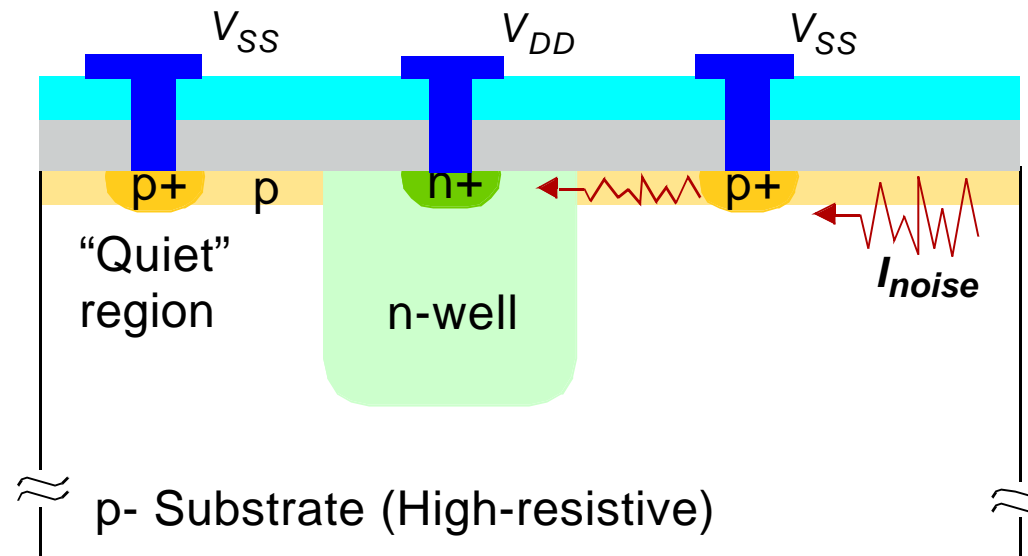

- **Noise current flows near surface** by a resistive material
  - ◆ Increase distance between noisy and sensitive
  - ◆ Provide a low impedance path to “drain” noise
- **Guard rings... (assume ideal pins)**
  - ◆ effectiveness depends on path impedance vs. substrate impedance. Place enough contacts.
  - ◆ position affects performance. Place p+ rings close to the noisy area. Place n+ and p+ rings surrounding sensitive area

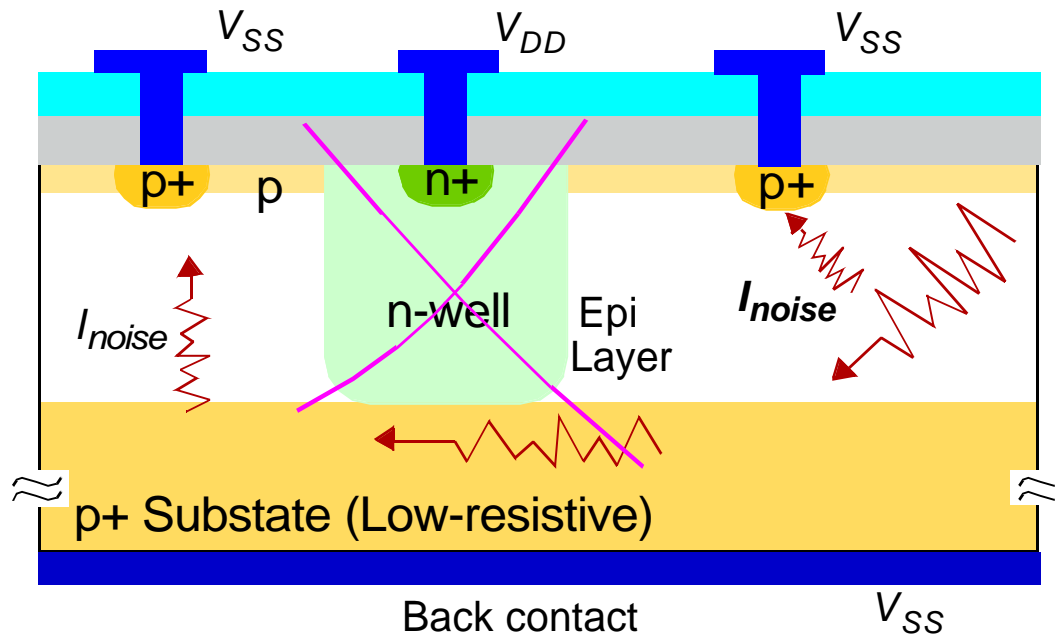

- **Noise current flows in deep substrate**, a highly conductive material
  - ◆ Noise almost the same everywhere
- **Guard rings...(assume ideal pins)**
  - ◆ n+ rings are useless. p+ rings may help if placed very close to the noisy/sensitive area. (farther than epi thickness => useless)
  - ◆ position does not affects performance. Only number of contacts (impedance) is important.
- **Back contact...**
  - ◆ provides a low-impedance path to noise
  - ◆ But in practice (skin effect, pin parasitics) may be useless

## ➡ Noise...

## Because...

- increases as device area increases larger devices => larger junction caps.
  - Use **adjusted sizes** for every application
  - Area reduction is also a matter of noise
- largely increases as rise/fall time decreases larger dV/dt => larger capacitive coupling
  - Use logic as **slow** as possible
- in p- bulk decreases with distance => larger resistance in the noise path
  - Maximise distance** between noisy and sensitive nodes
  - In practice, **not true in p+ subs**
- sensitivity varies with transistor design

$$\frac{\text{substrate noise gain}}{\text{signal gain}} \approx \sqrt{\underbrace{\left(\frac{2\pi f C_j}{g_m}\right)^2}_{\text{Capacitive coupling term}} + \underbrace{\frac{\gamma^2}{4(V_{SB} + \phi_B)}}_{\text{Body effect term}}}$$

Labels in diagram:  
 Transconductance (points to  $g_m$ )  
 Junction cap (points to  $C_j$ )  
 Body effect coeff. (points to  $\gamma$ )

◆ If  $V_{SB} = 0V$

$$\frac{\text{substrate noise gain}}{\text{signal gain}} \approx \frac{2\pi f C_j}{g_m}$$

◆ Sensitivity decreases if source and bulk are at the same effective voltage; e.g. short-circuit pMOS source and n-well

◆ Digital substrate → Digital VSS  
Analog substrate → Dedicated pin

◆ Digital substrate → Dedicated pin  
Analog substrate → Analog VSS

◆ Digital substrate → Dedicated pin  
Analog substrate → Another pin

◆ Digital substrate → Digital VSS  
Analog substrate → Analog VSS


◆ Digital substrate → Digital VSS  
Analog substrate → Digital VSS

◆ Digital substrate → Analog VSS  
Analog substrate → Analog VSS

[Arag99]

Best

• May produce latch-up in digital part

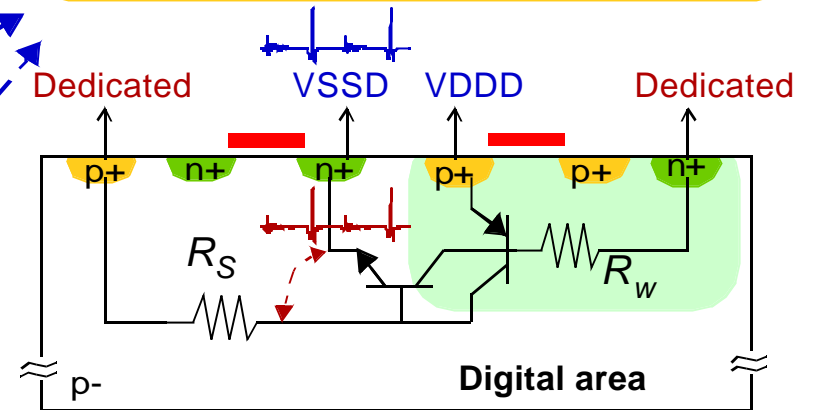



Normal

Bad

• Never bias a p- substrate with a single source


◆ It puts in contact noisy and quiet substrate areas, thus ruining substrate provided resistive isolation

Very bad

  




## Types

 


## Use and biasing

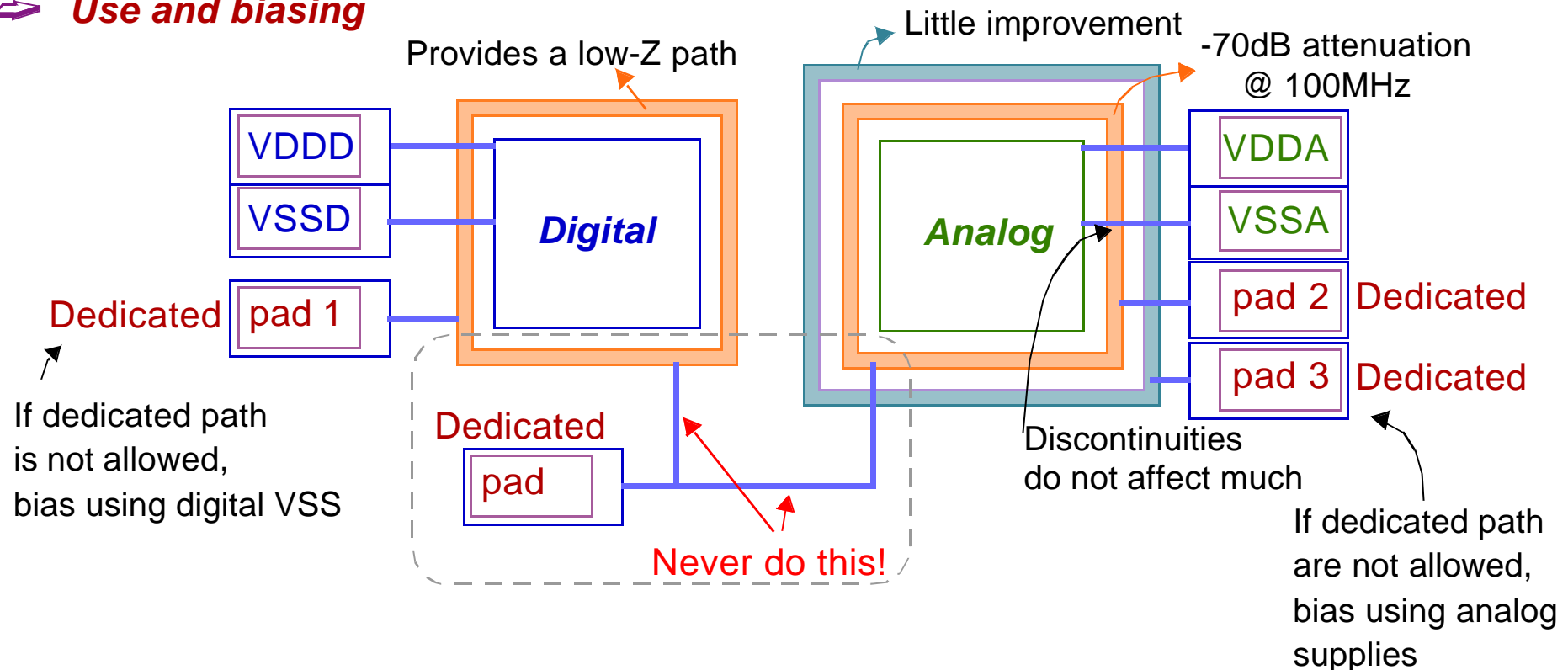
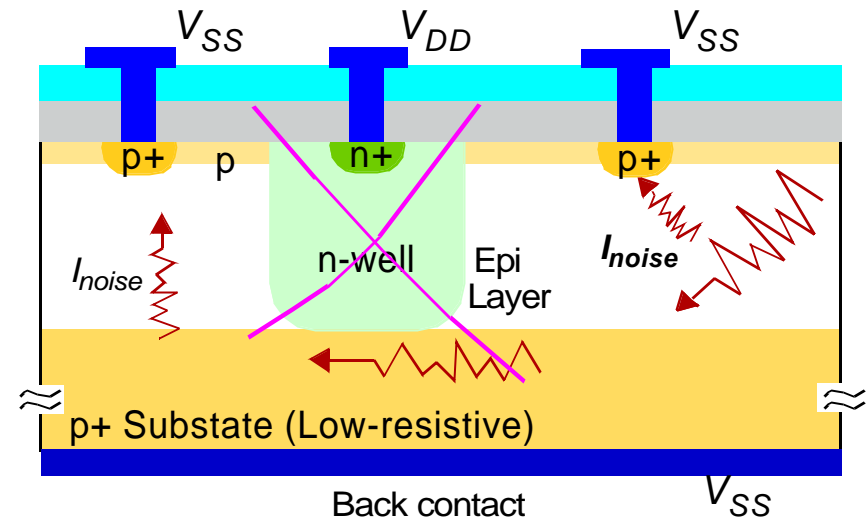
## Be careful

- ◆ This works only if (routing + pad + wirebond + lead + external interconnects) = **low-impedance path**


- **Noise is everywhere along the chip (through the high-conductive p+ substrate)**
  - ◆ Don't contact VSS analog to substrate! It will be quickly contaminated. Use a dedicated pad.
  - ◆ Minimize parasitic caps between analog supply and substrate: Shield
  - ◆ Even if this is avoided at the core level, the pad ring will do it!
  - ◆ Different biasing strategies show little difference
  - ◆ Back contact does not help much because of parasitics






**Non-general rules**, They may change a lot depending on size of the digital and analog part, application, technology, etc.

- **Guard rings?**
  - ◆ n+ in n-well rings are useless
  - ◆ p+ guard rings **surrounding** an analog block, not necessary. Only number of contacts and distance (impedance) are important.
  - ◆ If impedance is dominated by pad+package parasitics, then p+ guard rings are useless

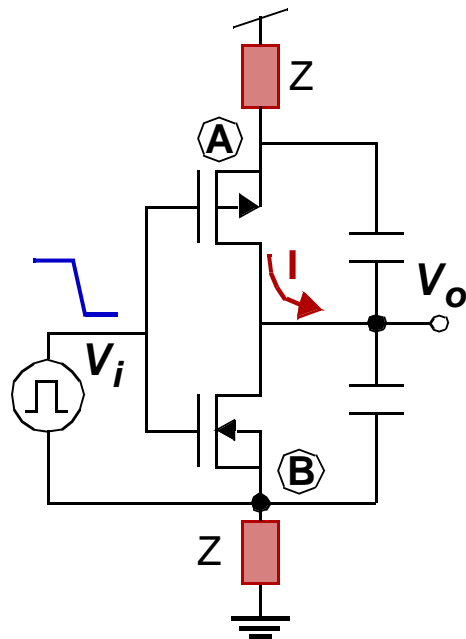- **In p+ substrates, noise is critically dependent on package inductance**
  - ◆ Not too much to do at the layout level
  - ◆ Solutions are at the package + board level
  - ◆ Use of circuit solutions as low-noise logic, trapezoidal digital buffers...
  - ◆ and on-chip decoupling devices may help



   Supply bounce or Delta-I noise  
Simultaneous switching noise (**SSN**)




- ◆ The larger the impedance, the larger the noise
- Try to minimize inductance + resistance**

- ◆ The larger the current peak, the larger the noise
- ◆ The shorter the rise (fall) time, the larger the noise

**Most SSN produced by I/O buffers**  
**Use separate supply for them**  
**(Dedicated pin + pad + routing)**

## Supply distribution


 


Typical supply distribution system

- Once in the power and ground supplies, SSN...

- is transmitted to any circuit connected to the same supply
- is coupled to substrate, other signal and/or biasing lines

## Types

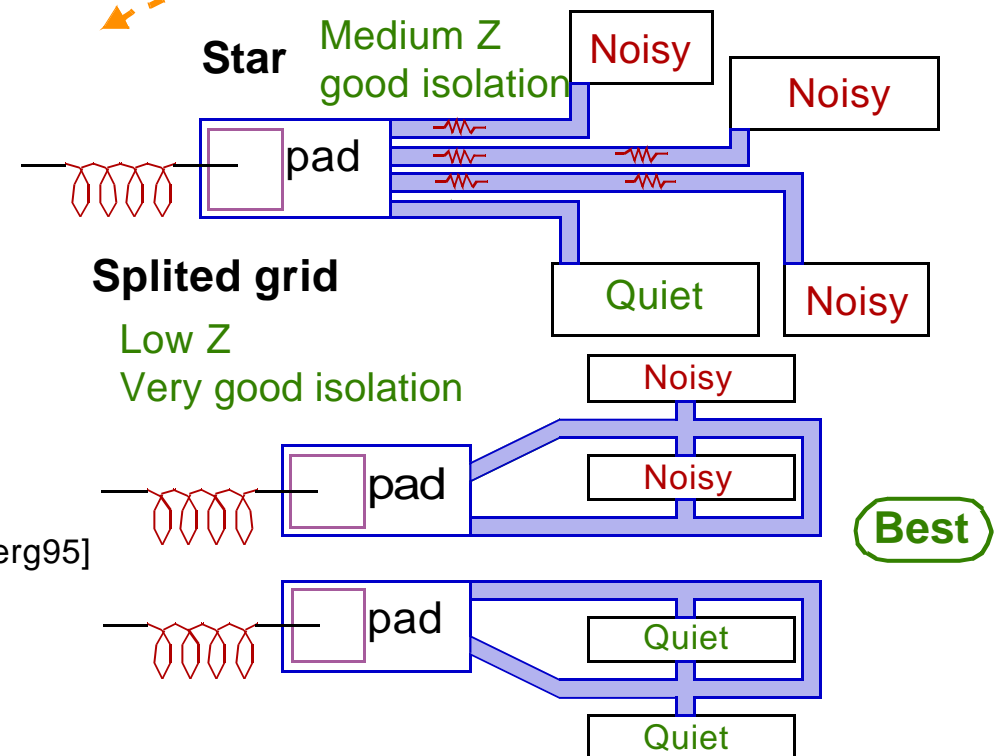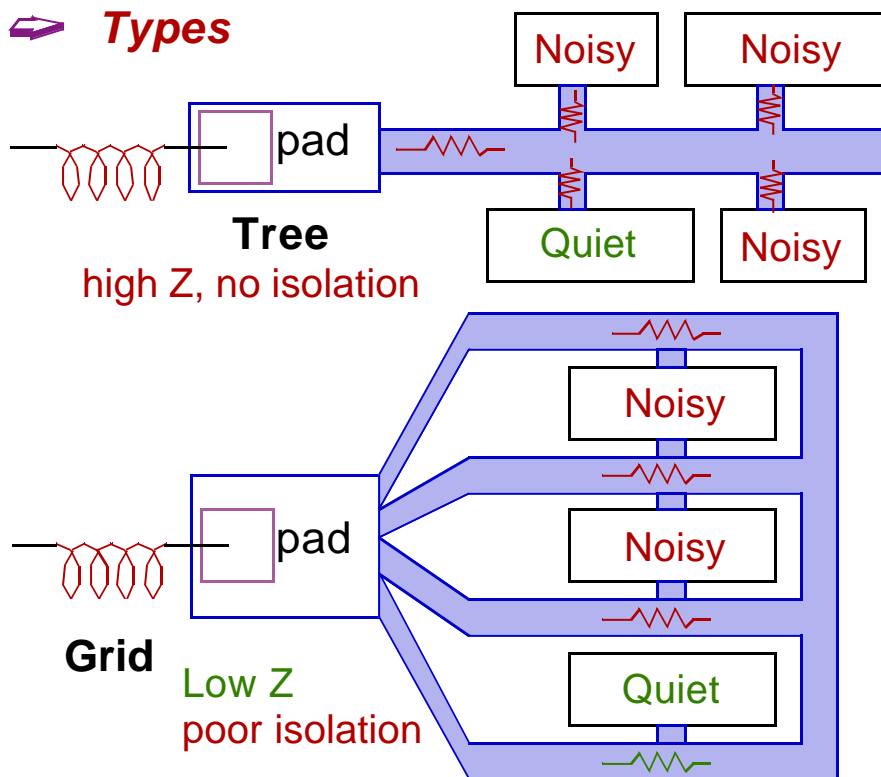


- Substrate (p+) is an excellent path for SSN

## Digital circuits
 
### SSN causes...

- ◆ delay to increase, through variation on current due to supply bounce
- ◆ false switching, due to changes in voltage driving a non-switching gate




## Analog and mixed-signal circuits

### SSN causes...

- ◆ Distortion and phase errors in linear circuits (Amplifiers, Filters, etc.)
- ◆ **Dynamic range reduction** in ADCs and DACs
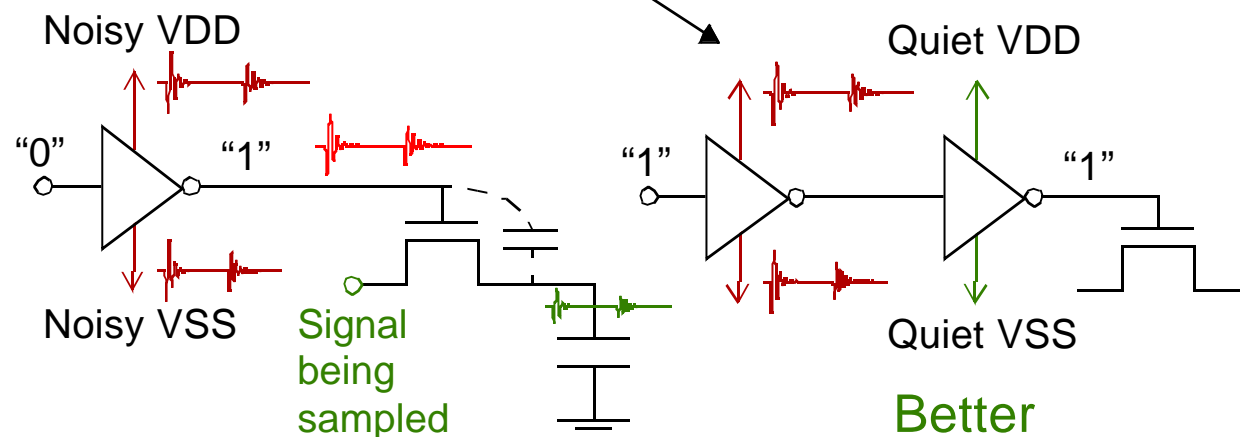
### Be careful with digital/analog interface points

- ◆ Clock phases controlling analog switches
- ◆ Supplying the last inverter with a clean voltage helps





### SSN reduction techniques

- |  |                                  |
|--|----------------------------------|
| <ul style="list-style-type: none"> <li>▶ Proper synthesis of the digital circuitry</li> <li>▶ Control of the digital buffer transition</li> <li>▶ Use of constant-current logic</li> </ul> | Trying to minimize SSN injection |
| <ul style="list-style-type: none"> <li>▶ Proper selection of packages and pin assignment</li> <li>▶ On chip decoupling</li> </ul>  | Trying to attenuate SSN impact   |



### Proper synthesis of digital circuitry [Arag99]


- **Reduce the number of gates switching simultaneously**
  - ◆ SSN is proportional to the number of gates switching
  - ◆ Keep digital blocks quiet when not used
- **Adjust timing to the application requirement**
  - ◆ SSN is inversely proportional to the rise (fall) time of the switching signal
  - ◆ Do not use oversized logic gates
  - ◆ Pay special attention to the transition at the input of the output buffers
- **Set the minimum cost (minimum area) option when synthesizing from VDHL**
- **Manually size critical blocks**

## ➡ Control of the digital buffer transition

### • Skewing


- ◆ Delay switching of a part of the output buffers with respect to the other part
- ◆ If the period of the ringing is known, delay can be adjusted to reduce overall ringing

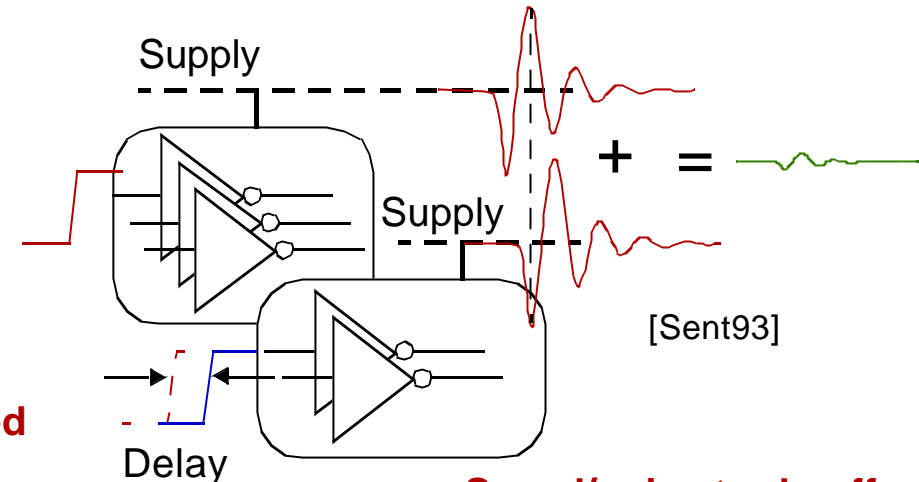**The value of the ringing period must be known a priori**


 
### • Controlling slew-rate

- ◆ Reduces the clock edge slope or changes it during the transition
- ◆ e.g.: resistor added in the switching current path to limit its peak value



**Speed/noise trade-off**

### • Damping resistor R,


- ◆ must be large to attenuate ringing
- ◆ must be small to keep speed

### • Reducing supply voltages (in prototyping)

- ◆ Reduces current peak => largely reduces SSN power
- ◆ Separately supply digitally buffers and reduce its voltage





**Be careful with latch-up!**

 **External timing and high/low levels must be readjusted**




    
## ➤ Use of constant-current logic

- ◆ Ideally, there are no current peaks => no SSN
- ◆ Used as a complement of the CMOS logic for high-speed digital blocks, I/O buffers



  - SSN two order of magnitude smaller than that of conventional CMOS
- Reduced output voltage swing
- Static power dissipation






### ➤ Proper selection of packages and pin assignment

 
#### • Target: minimum inductance

- ◆ Use surface mounting packages (SMT, SOIC, QFP, L~3-7nH)
- ◆ The larger the pin count, the larger the inductance
- ◆ Be careful with **DIL** or large **PGA** (typical L ~ 20nH)
- ◆ Assign power and ground to **centre pins** (corner pins have ~ 40% more inductance) [Will96]
- ◆ Assign several pins and pads to the critical voltages (supply, references, ...)
- ◆ Place a **grounded pin** between each pair of used pins
- ◆ If possible, **solder the die directly on PCB** (L < 1nH)



**Sockets largely  
increases inductance!**



## ➡ On-chip decoupling

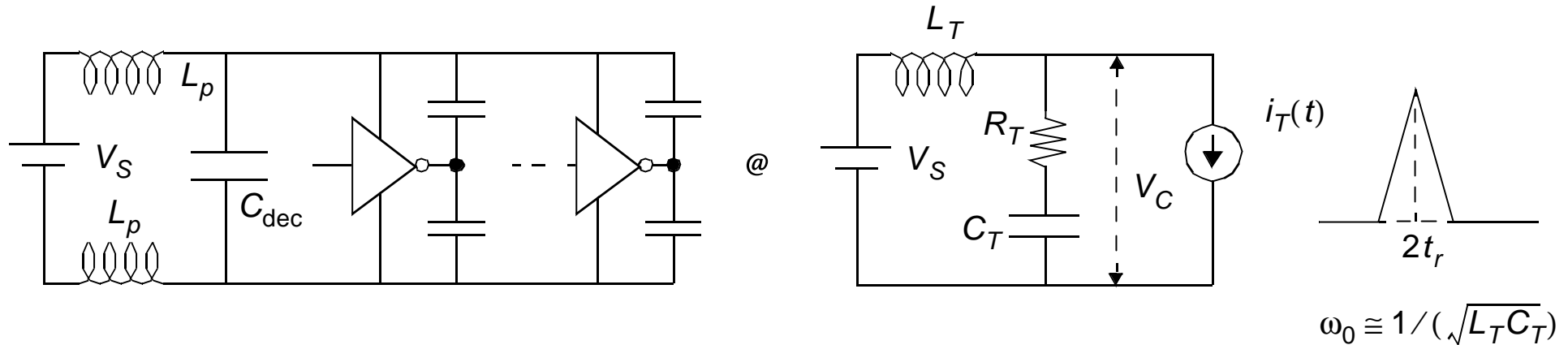

 
 
- **Problem:  $R_T$  usually small  $\Rightarrow$  low damping factor**
  - ◆ Ringing even more harmful than SSN itself
  - ◆ If any of the clock harmonics coincides with the resonant frequency, constructive SSN largely amplifies the effect
- **Simplest solution: increase  $R_T$** 
  - ◆ Add a resistor in series with the supply inductance, but then
    - Resistive switching noise is increased
    - Power dissipation is increased



➡ **More sophisticated on-chip decoupling techniques**

• **RCL decoupling method** [Inge97]

  
- ◆ Connecting a properly sized RLC net in parallel to the on-chip decoupling capacitor prevents oscillations
- ◆  $L_{RLC}$  can be implemented using wire parasitic inductance.  $C_{RLC}$  as an “in”-chip SDM cap.



**L and C choice**

$$L_{RCL} C_{RLC} \cong L_T C_T$$


The larger  $C_{RLC} / C_T$ , the better

 

• **Tank CMOS method** [Arag99]

- ◆ On-chip logic isolated from external supply and supplied directly by a tank capacitor
- ◆ Voltage across  $C_{tank}$  is kept by a controlled current source.  $I_C$  is connected only when  $V_{tank}$  drops below certain level

 
**70% reduction on SSN has been reported**



➡ **Final recommendation**

Avoid synchronizing critical analog operations with the clock edge

## Usual floorplane of a SC circuit


 


## Multiple supply


- ◆ VDDa, VSSa: Analog block supply
- ◆ VDDs, VSSs: Analog substrate and n-well biasing
- ◆ VDDd, VSSd: Digital core supply and substrate biasing
- ◆ VDDb, VSSb: Digital buffer supply and substrate
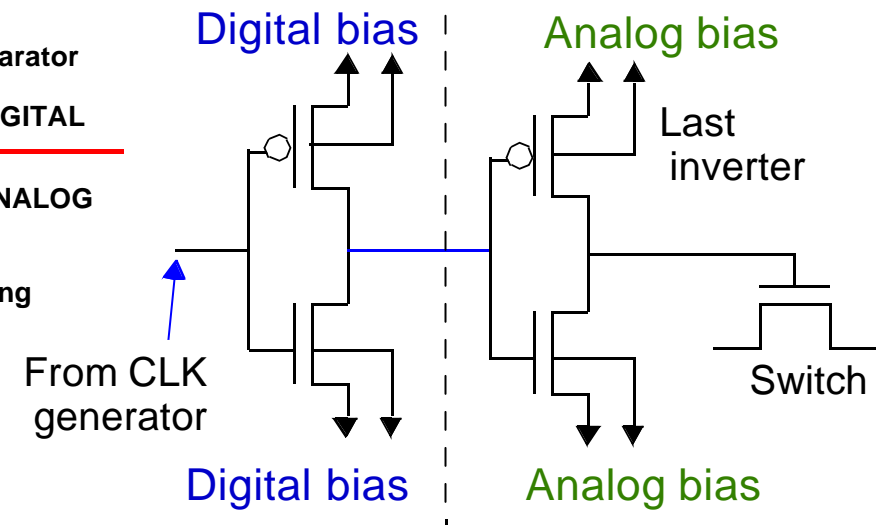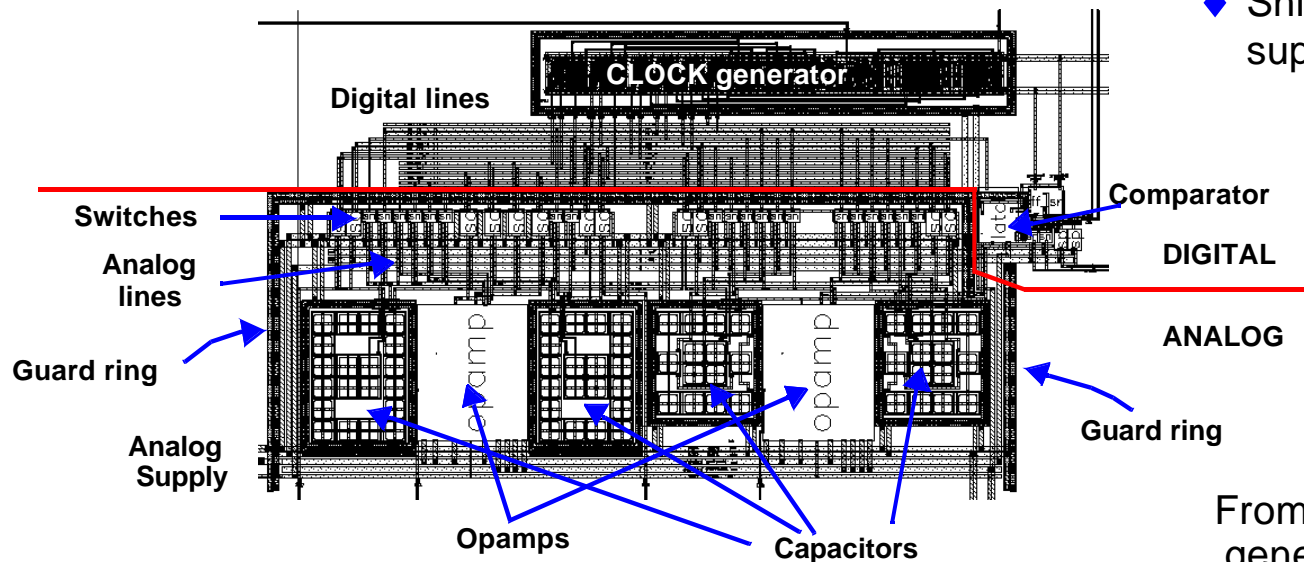
## Analog blocks

- ◆ Common-centroide techniques in opamp and latch transistors, and in capacitors
- ◆ Symmetrical routing
- ◆ Shielded capacitors and analog supply distribution




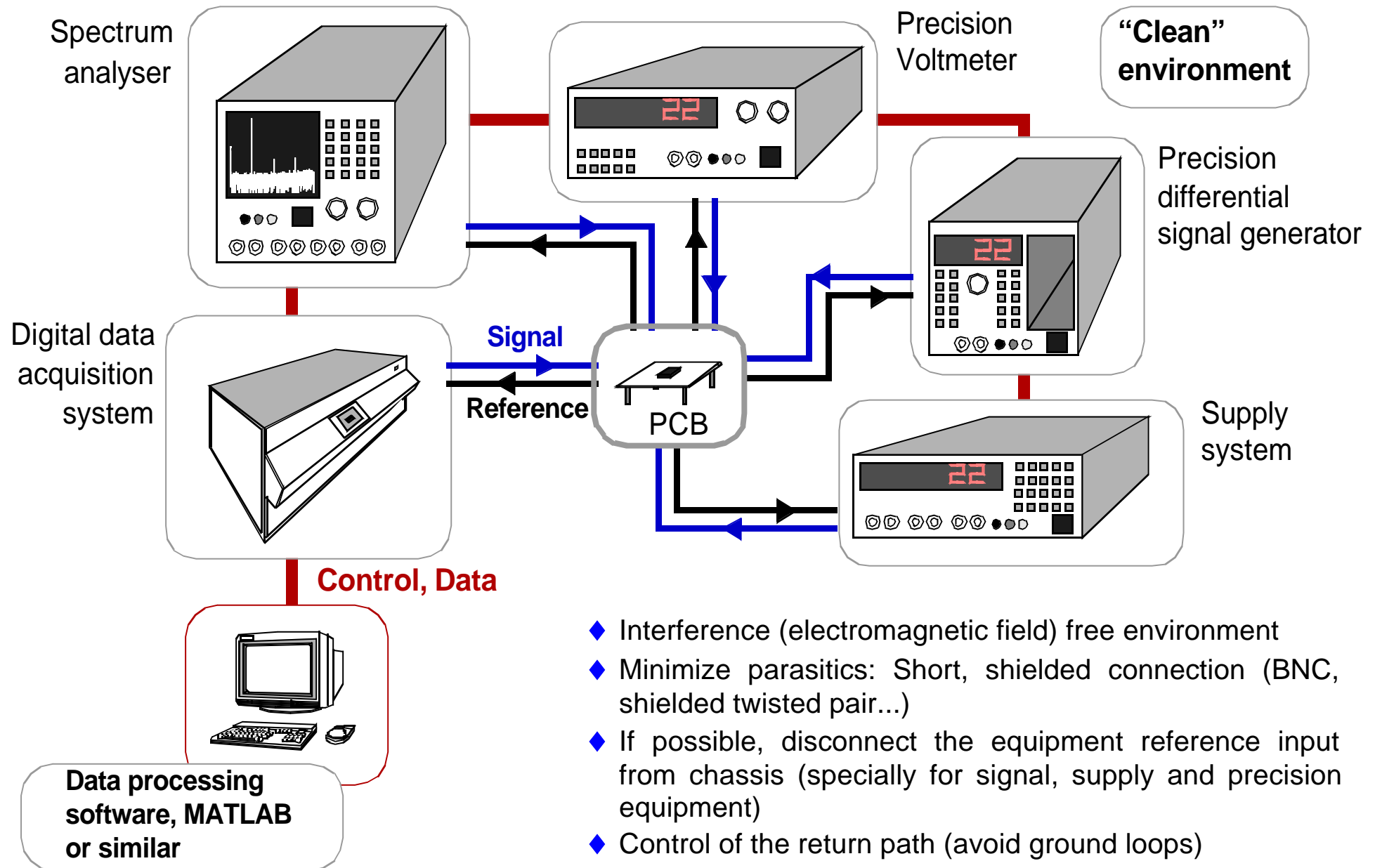0.7 $\mu$ m CMOS poly-diff caps 2-metal (p- substrate)  
0.42mm<sup>2</sup>




- ◆ Interference (electromagnetic field) free environment
- ◆ Minimize parasitics: Short, shielded connection (BNC, shielded twisted pair...)
- ◆ If possible, disconnect the equipment reference input from chassis (specially for signal, supply and precision equipment)
- ◆ Control of the return path (avoid ground loops)

## ➡ Ground loop effects

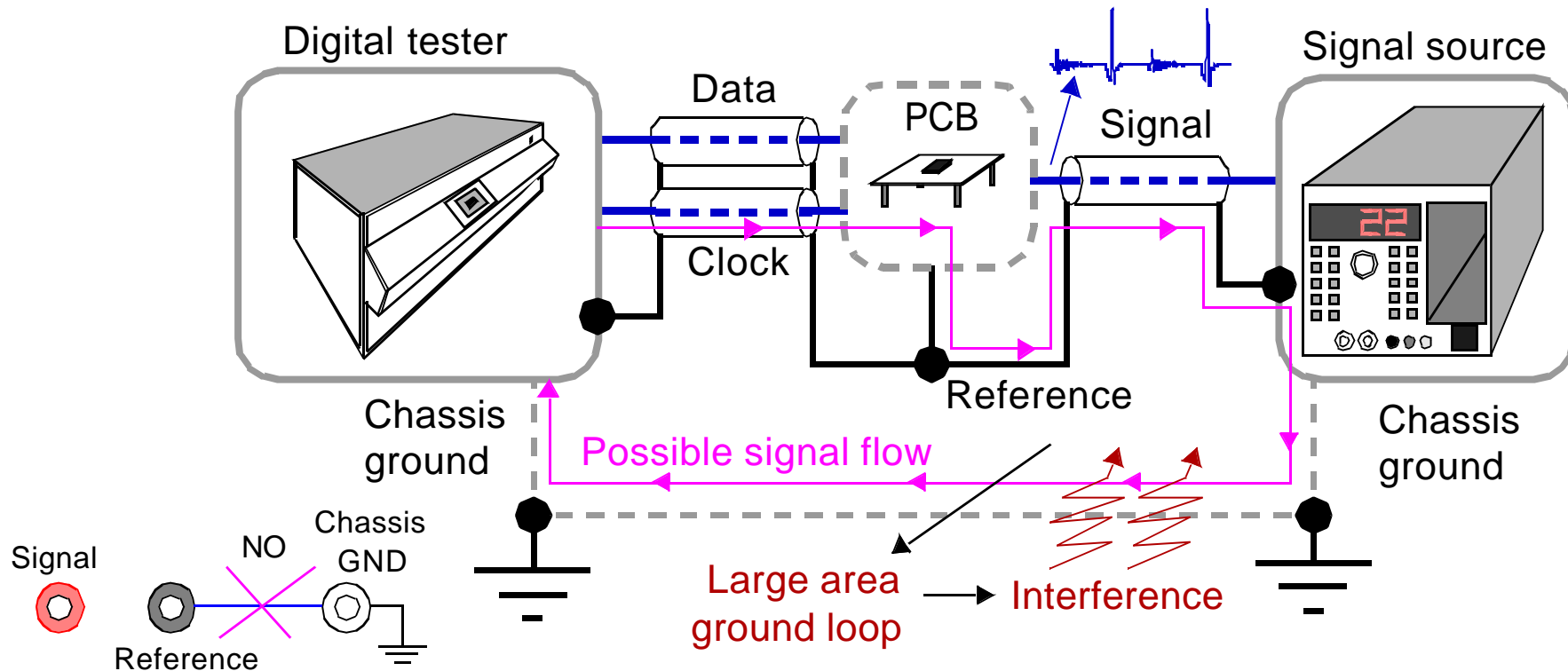
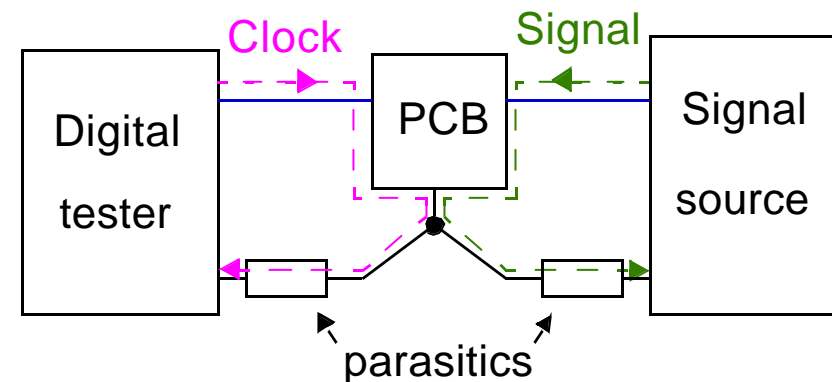
## ➡ How to avoid a ground loop? Open it

- ◆ Use floating input signal and supply sources (Do not connect signal reference to chassis)
- ◆ Make return path shared by noisy and sensitive signals as short as possible (a single point, ideally)



# ADC and DAC testing

## Static


Clock → max. rate  
Signal → DC or low frequency

## DC Accuracy

Offset

Gain error

Non-linearity  
INL, DNL

 

missing codes

non-monotonicity

## Dynamic

Clock → max. rate

Signal → variable freq. & amplitude


Dynamic non-linearity test

Noise


Signal-to-noise ratio

Distortion

Settling time, Glitches (DAC)

 


Conversion time (ADC)

 

SNDR (SINAD)  
Dynamic Range, ENOB

SFDR  
THD  
IP3

 



### ➡ Using MATLAB

- Windowing the signal...

```
>> Np = # points;
>> W = hanning(Np);
>> xw=W.*x;
```

- FFT...



```
>> pxx = abs(fft(xw/sqrt(Np))).^2;
>> pxx = 2*pxx/norm(W)^2; % factor 2 because
    only half of the spectrum is plotted
```

- Plotting...

```
>> f=(1:ceil(Np/2))*fs/Np;
>> pxx=pxx(1:ceil(Np/2));
>> semilogx(f,10*log10(pxx))
```

- SNDR estimation


 
 
```
>> [pxxm,index]=max(pxx(BAND));
>> SIGNAL=index-:index+5;
>> noise=sum(pxx(BAND))-sum(pxx(SIGNAL));
>> psignal=sum(pxx(SIGNAL));
>> SNDR=10*log10(psignal/pnoise)
```





   
## Data windowing

- Required when **sampled data do not contain an integer number of signal periods**
  - ◆ FFT assumes that sampled data are periodic with period equal to the sampled time slot
  - ◆ Such periodicity may require a “jump”, thus corrupting the results
  - ◆ Windowing alter start and end data to avoid discontinuities
- Windowing **reduces sidelobes** but also **reduces frequency resolution**



 - ◆ **Compromise between sidelobe suppression and frequency resolution**





➤ **Total harmonic distortion (dB)**

$$THD|_{dB} = 10\log_{10} \frac{\sum V_{harj}^2}{V_{sig}^2}$$

➤ **Spurious-free dynamic range (dB)**

$$SFDR|_{dB} = 20\log_{10} (V_{sig}/V_{sp})$$



**2-tone input**

  

### ➡ Minimum Sinusoidal Error (MSE) method
  
#### • Basis:

- ◆ Apply a sinusoidal input
- ◆ Fit the converter output to a sinewave of the same frequency + offset + some harmonics
- ◆ The fitting coefficients are **offset** and **harmonic amplitudes**
- ◆ The fitting error is **noise**



$$V_{\text{fit}} = V_{\text{off}} + \sum A_i \sin\left(2\pi j \frac{f_x}{f_s} + \phi_j\right)$$

$$V_{\text{off}} = 85.4\text{mV}$$

$$A_1 = 960\text{mV}$$

$$A_2 = 9.5\text{mV}$$

$$A_2 = 3.2\text{mV}$$

$$\text{Noise} = 0.1\text{mV}_{\text{rms}}$$

$$\text{SNR} = 37\text{dB}$$


$$\text{THD} = -40\text{dB}$$

#### Pros/Cons

- No FFT required
- Requires a reconstruction filter
- Slow for large number of harmonics
- Non-convergence for very corrupted data
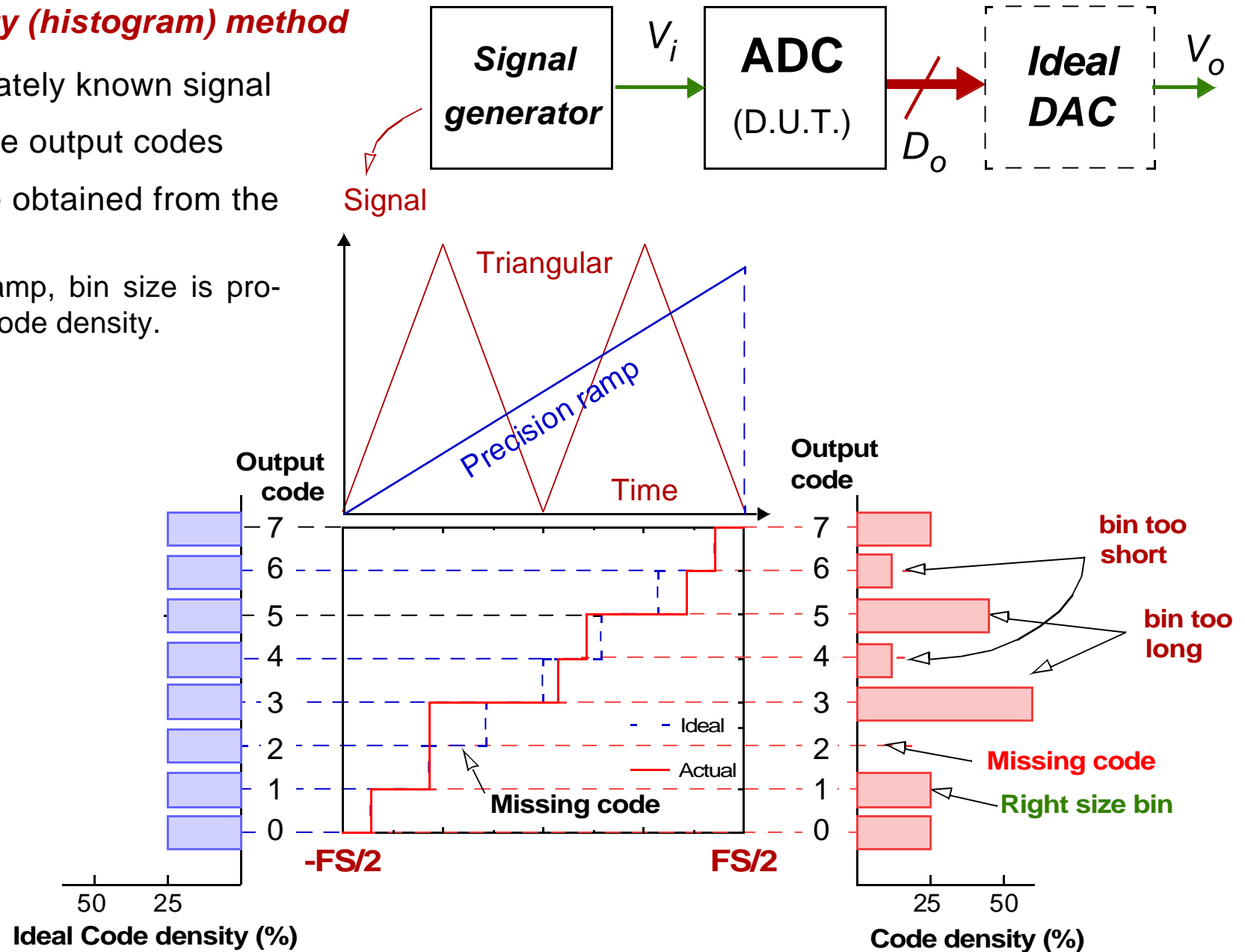
### Code density (histogram) method

- Apply an accurately known signal
- Histogram of the output codes
- Bin size can be obtained from the histogram data
  - ◆ If signal = ramp, bin size is proportional to code density.




## ➡ Code density method with sinewaves

- Peak-peak signal slightly above full-scale
- Signal frequency  $f_x = \frac{P}{M} f_s$ 
  - ◆  $f_s$  = sampling frequency
  - ◆  $P$  = number of signal period (odd, prime number: 1,3,5,7...)
  - ◆  $M$  = total number of samples taken
- If sinewave generator is not precise enough, divide ADC FS in sections
 
## Pros/Cons

- Allows evaluation of the accuracy of high-frequency converters
- Requires synchronisation for high resolution
- Otherwise, the number of samples needed may be prohibitive: 40Msamples for 16bit!, within 0.1LSB
- Slow for high resolution



$n \rightarrow n+1$  code transition point:

$$v_n = A \sin \left[ \pi \frac{n_{Cn}}{n_{\text{total}}} + \sin^{-1} \left( \frac{V_{n-1}}{A} \right) \right]$$

$$v_0 = A \sin \left[ \pi \left( \frac{n_{C0}}{n_{\text{total}}} - 1 \right) \right]$$



$n_{Cn}$  = number of occurrences of code  $n$





$n_{\text{total}}$  = total number of samples

Missing codes


5-bit ADC

10-bit ADC

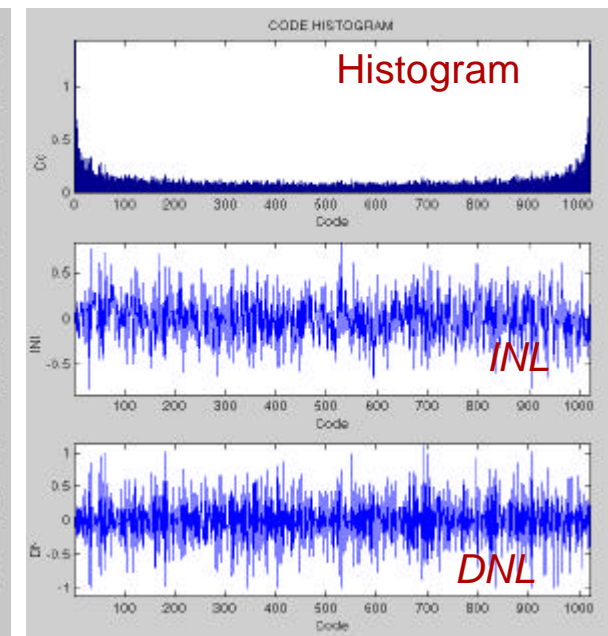 

    

 - ◆ Design on the border of the quantization noise limited and the white noise limited regions



**Efficient design**

## References

- [ALBU99] E. ALBUQUERQUE, M. SILVA: "A NEW LOW-NOISE LOGIC FAMILY FOR MIXED-SIGNAL INTEGRATED CIRCUITS," *IEEE TRANS. ON CIRCUITS AND SYSTEMS - I*, VOL. 46, PP. 1498-1500, DECEMBER 1999.
- [Allst93] D.J. Allstot, S. Kiaei, R.H. Zele: "Analog Logic Techniques Steer Around the Noise," *IEEE Circuits & Devices*, pp. 18-21, September 1993.
- [ARAG99] X. ARAGONÈS, J.L. GONZÁLEZ, A. RUBIO: *ANALYSIS AND SOLUTIONS FOR SWITCHING NOISE COUPLING IN MIXED-SIGNAL ICs*, KLUWER ACADEMIC PUBLISHERS, 1999.
- [FELD99] M. FELDER, J. GANGER: "ANALYSIS OF GROUND-BOUNCE INDUCED SUBSTRATE NOISE COUPLING IN A LOW RESISTIVE BULK EPITAXIAL PROCESS: DESIGN STRATEGIES TO MINIMIZE NOISE EFFECTS ON A MIXED-SIGNAL CHIP," *IEEE TRANS. ON CIRCUITS AND SYSTEMS - II*, VOL. 46 PP. 1427-1436, NOVEMBER 1999.
- [INGE97] M. INGELS, M.S.J. STEYAERT: "DESIGN STRATEGIES AND DECOUPLING TECHNIQUES FOR REDUCING THE EFFECTS OF ELECTRICAL INTERFERENCE IN MIXED-MODE IC'S," *IEEE JOURNAL OF SOLID-STATE CIRCUITS*, VOL. 32, PP. 1136-1141, JULY 1997.
- [LAMA92] J.L. LAMAY AND H.T. BOGARD: "HOW TO OBTAIN MAXIMUM PRACTICAL PERFORMANCE FROM STATE-OF-THE-ART DELTA-SIGMA ANALOG-TO-DIGITAL CONVERTERS," *IEEE TRANS. ON INSTRUMENTATION AND MEASUREMENT*, VOL. 41, PP. 861-867, DECEMBER 1992.
- [MEDE99] F. MEDEIRO, B. PEREZ-VERDU AND A. RODRIGUEZ-VAZQUEZ: *TOP-DOWN DESIGN OF HIGH-PERFORMANCE SIGMA-DELTA MODULATORS*, KLUWER ACADEMIC PUBLISHERS, 1999.
- [MONT96] M.I. MONTROSE: *PRINTED CIRCUIT BOARD DESIGN TECHNIQUES FOR EMC COMPLIANCE*, IEEE PRESS 1996.
- [NORS96] S. R. NORSWORTHY, R. SCHEREIER AND G. C. TEMES (EDITORS): *DELTA-SIGMA DATA CONVERTERS: THEORY, DESIGN AND SIMULATION*, IEEE PRESS, 1996.
- [RAZA95] B. RAZAVI: *PRINCIPLES OF DATA CONVERSION SYSTEM DESIGN*, IEEE PRESS, 1995
- [SENT93] R. SENTHINATHAN, J.L. PRINCE: "APPLICATION SPECIFIC CMOS OUTPUT DRIVER CIRCUIT DESIGN TECHNIQUES TO REDUCE SIMULTANEOUS SWITCHING NOISE," *IEEE JOURNAL OF SOLID-STATE CIRCUITS*, VOL. 28, PP. 1383-1388, DECEMBER 1993.
- [VERG95] N.K. VERGHESE, T.J. SHMERBECK, D.J. ALLSTOT: *SIMULATION TECHNIQUES AND SOLUTIONS FOR MIXED-SIGNAL COUPLING IN INTEGRATED CIRCUITS*, KLUWER ACADEMIC PUBLISHERS, 1995.
- [WILL96] J.M. WILLIAMSON, M.S. NAKHLA, Q.-J. ZHANG, P.D. VAN DER PUIJE: "GROUND NOISE MINIMIZATION IN INTEGRATED CIRCUIT PACKAGES THROUGH PIN ASSIGNMENT OPTIMIZATION," *IEEE TRANS. ON COMPONENTS, PACKAGING, AND MANUFACTURING TECHN.- B*, VOL. 19, PP. 361-371, MAY 1996.
- DYNAMIC CHARACTERIZATION OF A/D CONVERTERS WITH THE HP 82000M. HEWLETT PACKARD APPLICATION NOTES, 1992.
- "TERMS, DEFINITIONS, AND LETTER SYMBOLS FOR ANALOG-TO-DIGITAL AND DIGITAL-TO-ANALOG CONVERTERS". JEDEC STANDARD No. 99, ADDENDUM No.1, JULY 1989. (THERE IS AN IEEE STANDARD PUBLISHED IN 2001 AVAILABLE)