



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at
www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

Application Note AN-3003

Applications of Random Phase Crossing Triac Drivers

Construction

The MOC30XX family of random phase (non-zero crossing) triac drivers consist of an aluminum gallium arsenide infrared LED, optically coupled to a silicon detector chip. These two chips are assembled in a 6 pin DIP package, providing 7.5KV_{AC(PEAK)} of insulation between the LED and the output detector. These output detector chips are designed to drive triacs controlling loads on 115 and 220V AC power lines. The detector chip is a complex device which functions in the same manner as a small triac, generating the signals necessary to drive the gate of a larger triac such as Fairchild's FKPF12N80. The MOC30XX triacs are capable of controlling larger power triacs with a minimum number of additional components.

Table 1 lists the members of the MOC30XX random phase triac driver family. The family is divided by blocking voltage, V_{DM} , and input LED trigger sensitivity, I_{FT} . MOC3010/1/2 are rated at 250V, the MOC3020/1/2/3 are 400VAC, and the MOC3051/2 have a V_{DM} of 600V.

Basic Electrical Description

The AlGaAs LED has a nominal 1.3 V forward drop at 10 mA and a reverse breakdown voltage greater than 3 V. The maximum current to be passed through the LED is 60 mA.

The detector has a minimum blocking voltage of 250 Vdc in either direction in the off state. In the on state, the detector will pass 100 mA in either direction with less than 3 V drop

across the device. Once triggered into the on (conducting) state, the detector will remain there, even if no current flows through the LED, until the terminal current drops below the holding current (typically 100 μ A) at which time the detector reverts to the off (non-conducting) state. The detector may be triggered into the on state by exceeding the forward blocking voltage, by voltage ramps across the detector at rates exceeding the static dv/dt rating, or by photons from the LED. The LED is guaranteed by the specifications to trigger the detector into the on state when the current passing through the LED is equal to, or greater than the $I_{FT(max)}$ specification. For example the MOC3011M requires at least 10mA of LED current to guarantee turn-on. A similar device, the MOC3012M, has exactly the same characteristics except it requires only 5 mA to trigger.

Since these devices look essentially like a small optically triggered triac, we have chosen to represent it as shown in Figure 1.

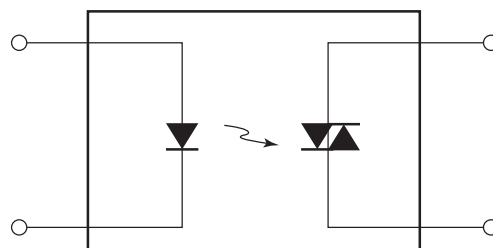


Figure 1. Schematic Representation of an Optically Coupled Random Phase Triac Driver

		Random Phase Triac Optocouplers						
		Part Number	I_{FT} (mA) max	V_{TM} (V) max	V_{DM} (V) min	I_H (μ A)	I_{DRM} (nA) max	V_{Iso} AC[PEAK]
<p>ANODE 1</p> <p>CATHODE 2</p> <p>NC 3</p> <p>6 MAIN TERM</p> <p>5 *</p> <p>4 MAIN TERM</p> <p>*Do not connect</p>	MOC3010M	15	3	250	100	100	7.5kV	
	MOC3011M	10	3	250	100	100	7.5kV	
	MOC3012M	5	3	250	100	100	7.5kV	
	MOC3020M	30	3	400	100	100	7.5kV	
	MOC3021M	15	3	400	100	100	7.5kV	
	MOC3022M	10	3	400	100	100	7.5kV	
	MOC3023M	5	3	400	100	100	7.5kV	
	MOC3051M	15	2.5	600	280	100	7.5kV	
	MOC3052M	10	2.5	600	280	100	7.5kV	

Table 1.


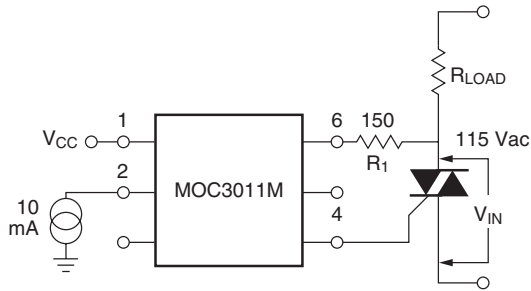


Figure 2. Simple Triac Gating Circuit

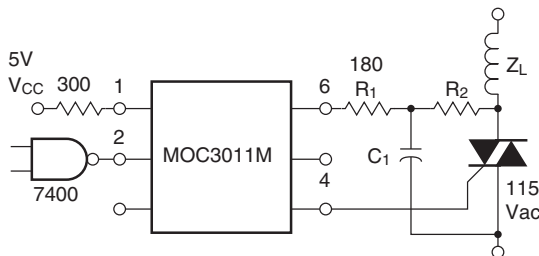

NOTE: Circuit supplies 25mA drive to gate of triac at $V_{in} = 25V$ and $T_A < 70^\circ C$

TRIAC		
I_{GT}	R_2	C
15 mA	2400	0.1
30 mA	1200	0.2
50 mA	800	0.3

Figure 3. Logic to Inductive Load Interface

Using the MOC3011M as a Triac Driver

Triac Driving Requirements

Figure 2 shows a simple triac driving circuit using the MOC3011M. The maximum surge current rating of the MOC3011M sets the minimum value of R_1 through the equation:

$$R_1 (\text{min}) = V_{in}(\text{pk})/1.2A$$

If we are operating on the 115 Vac nominal line voltage, $V_{in}(\text{pk}) = 180 V$, then

$$R_1 (\text{min}) = V_{in}(\text{pk})/1.2A = 150 \text{ ohms.}$$

In practice, this would be a 150 or 180 ohm resistor. If the triac has $I_{GT} = 100 \text{ mA}$ and $V_{GT} = 2 V$, then the voltage V_{in} necessary to trigger the triac will be given by,

$$V_{inT} = R_1 \cdot I_{GT} + V_{GT} + V_{TM} = 20 V.$$

Resistive Loads

When driving resistive loads, the circuit of Figure 2 may be used. Incandescent lamps and resistive heating elements are the two main classes of resistive loads for which 115 Vac is utilized. The main restriction is that the triac must be properly chosen to sustain the proper inrush loads. Incandescent lamps can sometimes draw a peak current known as “flash-over” which can be extremely high, and the triac should be protected by a fuse or rated high enough to sustain this current.

Line Transients-Static dv/dt

Occasionally transient voltage disturbances on the ac line will exceed the static dv/dt rating of the MOC3011M. In this case, it is possible the MOC3011M and the associated triac will be triggered on. This is usually not a problem, except in unusually noisy environments, because the MOC3011M and its triac will commute off at the next zero crossing of the line voltage, and most loads are not noticeably affected by an occasional single half-cycle of applied power. See Figure 4 for typical dv/dt versus temperature curves.

Inductive Loads-Commutating dv/dt

Inductive loads (motors, solenoids, magnets, etc.) present a problem both for triacs and for the MOC3011M because the voltage and current are not in phase with each other. Since the triac turns off at zero current, it may be trying to turn off when the applied current is zero but the applied voltage is high. This appears to the triac like a sudden rise in applied voltage, which turns on the triac if the rate of rise exceeds the commutating dv/dt of the triac or the static dv/dt of the MOC3011M.

Snubber Networks

The solution to this problem is provided by the use of “snubber” networks to reduce the rate of voltage rise seen by the device. In some cases, this may require two snubbers—one for the triac and one for the MOC3011M. The triac snubber is dependent upon the triac and load used and will not be discussed here. In many applications the snubber used for the MOC3011M will also adequately protect the triac.

In order to design a snubber properly, one should really know the power factor of the reactive load, which is defined as the cosine of the phase shift caused by the load. Unfortunately, this is not always known, and this makes snubbing network design somewhat empirical. However, a method of designing a snubber network may be defined, based upon a typical power factor. This can be used as a “first cut” and later modified based upon experiment.

Assuming an inductive load with a power factor of $PF = 0.1$ is to be driven. The triac might be trying to turn off when the applied voltage is given by

$$V_{to} = V_{pk} \sin \theta = V_{pk} = 180 V$$

First, one must choose R_1 (Figure 3) to limit the peak capacitor discharge current through the MOC3011M. This resistor is given by

$$R_1 = V_{pk}/I_{max} = 180/1.2 \text{ A} = 150\Omega$$

A standard value, 180 ohm resistor can be used in practice for R_1 .

It is necessary to set the time constant for $\tau = R_2C$. Assuming that the triac turns off very quickly, we have a peak rate of rise at the MOC3011M given by

$$dv/dt = V_{to}/\tau = V_{to}/R_2C$$

Setting this equal to the worst case dv/dt (static) for the MOC3011M which we can obtain from Figure 4 and solving for R_2C :

$$dv/dt(T_J = 70^\circ\text{C}) = 0.8 \text{ V}/\mu\text{s} = 8 \times 10^5 \text{ V/s}$$

$$R_2C = V_{to}/(dv/dt) = 180/(8 \times 10^5) = 225 \times 10^{-6}$$

The largest value of R_2 available is found, taking into consideration the triac gate requirements. Using Fairchild's power triac, FKPF12N80, $I_{GT} = 30 \text{ mA}$. If the triac is to be triggered when $V_{in} \leq 40\text{V}$:

$$(R_1 + R_2) = V_{in}/I_{GT} = 40/0.030 \approx 1.33 \text{ k}$$

If we let $R_2 = 1200 \Omega$ and $C = 0.1 \mu\text{F}$, the snubbing requirements are met. Triacs having less sensitive gates will require that R_2 be lower and C be correspondingly higher as shown in Figure 3.

Input Circuitry

Resistor Input

When the input conditions are well controlled, as for example when driving the MOC3011M from a logic gate, only a single resistor is necessary to interface the gate to the input LED of the MOC3011M. The resistor should be chosen to set the current into the LED to be a minimum of 10 mA but no more than 50 mA. 15 mA is a suitable value, which allows for considerable degradation of the LED over time, and assures a long operating life for the coupler. Currents higher than 15 mA do not improve performance and may hasten the aging process inherent in LED's. Assuming the forward drop to be 1.5 V at 15 mA allows a simple formula to calculate the input resistor.

$$R_I = (V_{CC} - 1.5)/0.015$$

Examples of resistive input circuits are seen in Figures 1 and 5.

Increasing Input Sensitivity

In some cases, the logic gate may not be able to source or sink 15 mA directly. CMOS, for example, is specified to have only 0.5 mA output, which must then be increased to drive the MOC3011M. There are numerous ways to increase this current to a level compatible with the MOC3011M input requirements; an efficient way is to use the Fairchild TinyLogic™, NC7SZ04 shown in Figure 5.

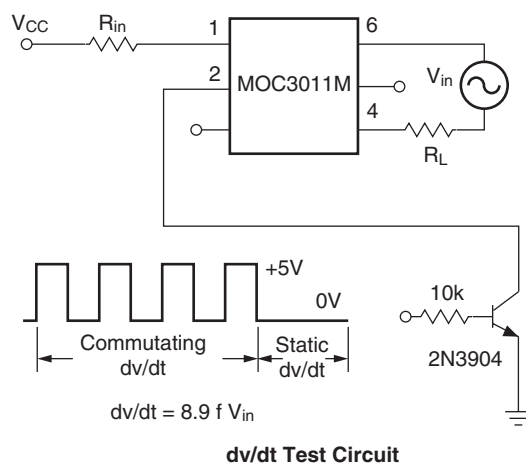
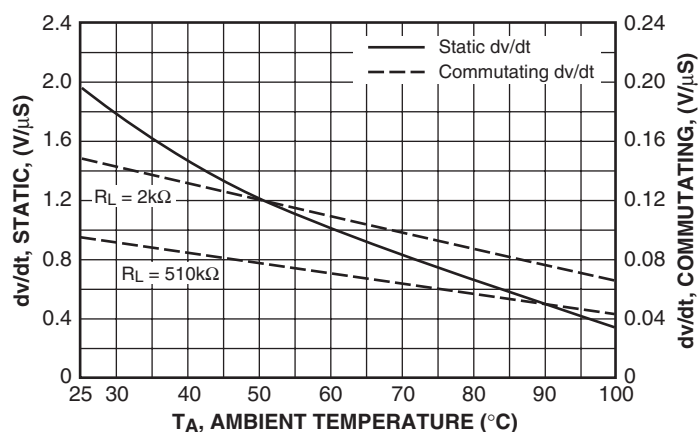


Figure 4. dv/dt versus Temperature

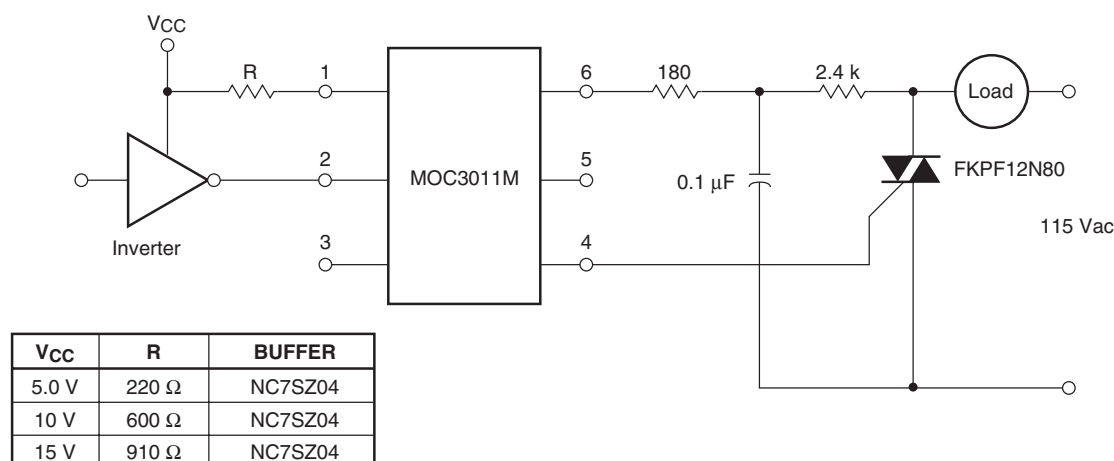


Figure 5. MOS to AC Load Interface

Input Protection Circuits

In some applications, such as solid state relays, in which the input voltage varies widely the designer may want to limit the current applied to the LED of the MOC3011M. The circuit shown in Figure 6 allows a non-critical range of input voltages to properly drive the MOC3011M and at the same time protects the input LED from inadvertent application of reverse polarity.

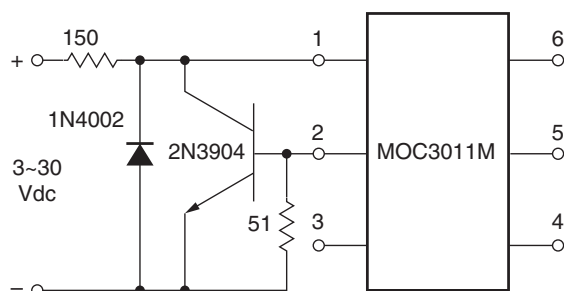


Figure 6. MOC3011M Input Protection Circuit

LED Lifetime

All light emitting diodes slowly decrease in brightness during their useful life, an effect accelerated by high temperature and high LED currents. To allow a safety margin and ensure long service life, the MOC3011M is actually tested to trigger at a value lower than the specified 10 mA input

threshold current. The designer can therefore design the input circuitry to supply 10 mA to the LED and still be sure of satisfactory operation over a long operating lifetime. On the other hand, care should be taken to ensure that the maximum LED input current (50 mA) is not exceeded or the lifetime of the MOC3011M may be shortened.

Applications Examples

Using the MOC3011M on 240 Vac Lines

The rated voltage of a MOC3011M is not sufficiently high for it to be used directly on 240 Vac line; however, the designer may attach two of them in series. When used this way, two resistors are required to equalize the voltage dropped across them as shown in Figure 7.

Remote Control of ac Voltage

Local building codes frequently require all 115 Vac light switch wiring to be enclosed in conduit. By using a MOC3011M, a triac, and a low voltage source, it is possible to control a large lighting load from a long distance through low voltage signal wiring which is completely isolated from the ac line. Such wiring usually is not required to be put in conduit, so the cost savings in installing a lighting system in commercial or residential buildings can be considerable. An example is shown in Figure 8. Naturally, the load could also be a motor, fan, pool pump, etc.

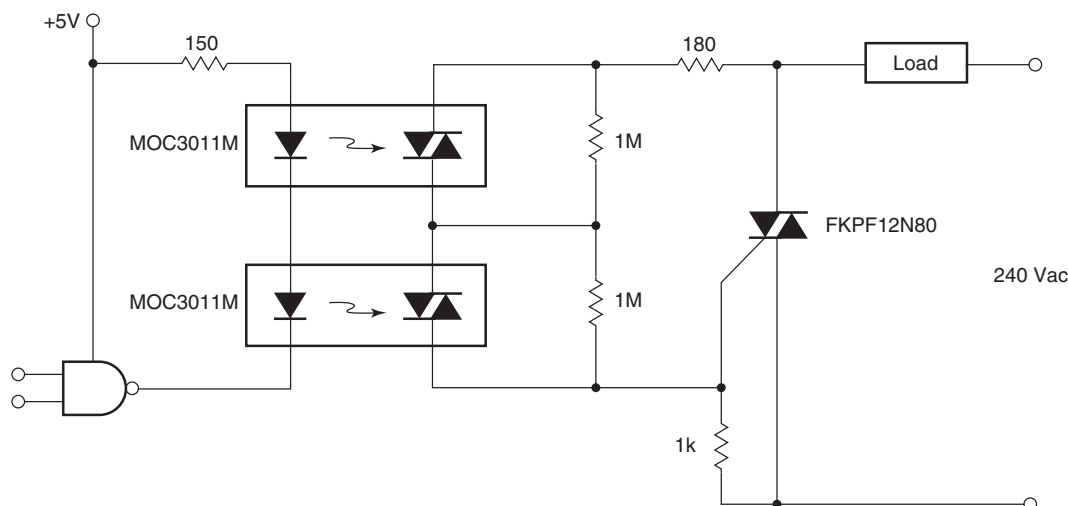


Figure 7. 2 MOC3011M Triac Drivers in Series to Drive 240 V Triac

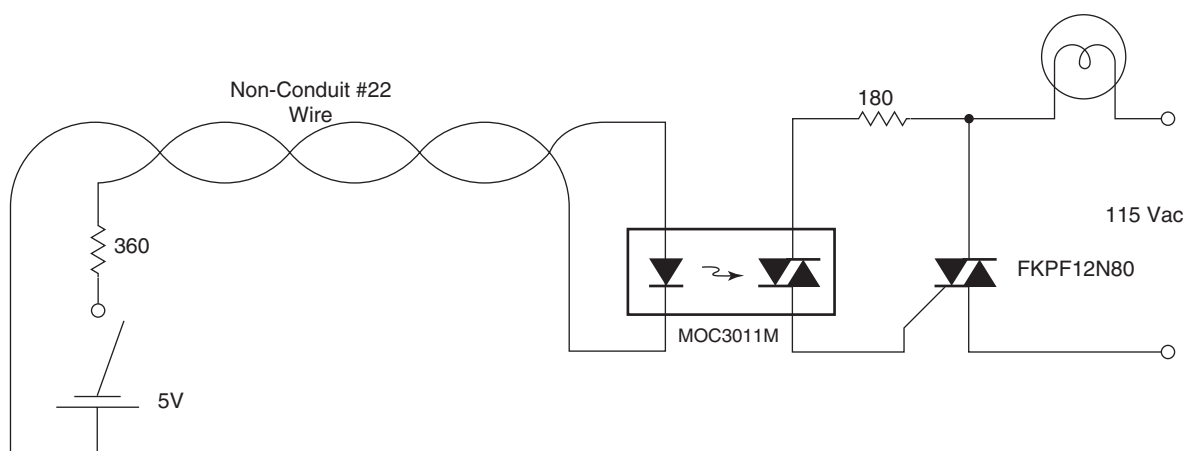


Figure 8. Remote Control of AC Loads through Low Voltage Non-Conduit Cable

Solid State Relay

Figure 9 shows a complete general purpose, solid state relay snubbed for inductive loads with input protection. When the designer has more control of the input and output conditions, he can eliminate those components which are needed for his particular application to make the circuit more cost effective.

Interfacing Microprocessors to 115 Vac Peripherals

The output of a typical microcomputer input-output (I/O) port is a TTL-compatible terminal capable of driving one or two TTL loads. This is not quite enough to drive the MOC3011M, nor can it be connected directly to an SCR or

triac, because computer common is not normally referenced to one side of the ac supply. The Fairchild TinyLogic™ NC7SZ04 UHS inverter can provide the LED current drive required by the MOC3011M family. If the second input of a 2 input gate is tied to a simple timing circuit, it will also provide energization of the triac only at the zero crossing of the ac line voltage as shown in Figure 10. This technique extends the life of incandescent lamps and reduces EMI generated by load switching. Of course, zero crossing can be generated within the micro-computer itself, but this requires considerable software overhead and usually just as much hardware to generate the zero-crossing timing signals.

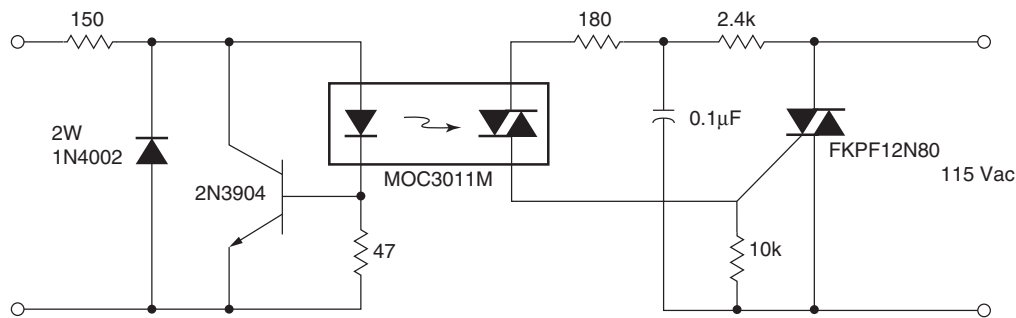


Figure 9. Solid-State Relay

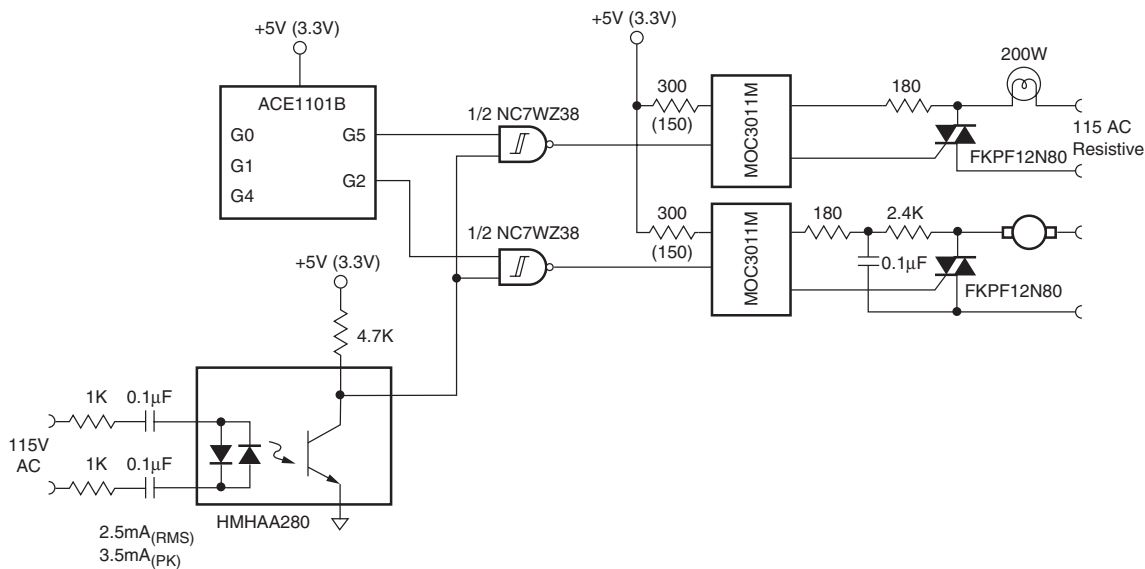


Figure 10. Interfacing an Arithmetic Controller Engine to 115 Vac Loads

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada

Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910

Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local
Sales Representative