

# Voltage reference and bandgap circuits




# Basic blocks for voltage reference circuits

What characteristic can be used to generate a reference voltage?

---


Bipolar

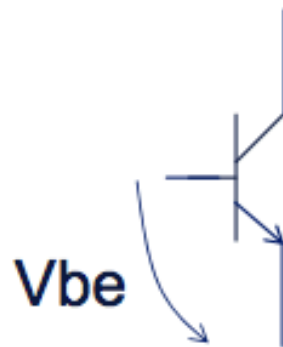

Base-emitter-voltage  $V_{be}$ :  
depends on temperature, but is not  
sensitive to process variation.

⇒ Bipolar device is the key  
component for accurate  
voltage reference circuits

MOS

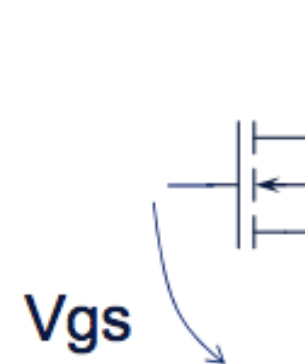



Gate-source-voltage  $V_{gs}$ :  
Depends strong on process variation

⇒ MOS device based voltage  
reference circuits will not  
achieve high accuracy

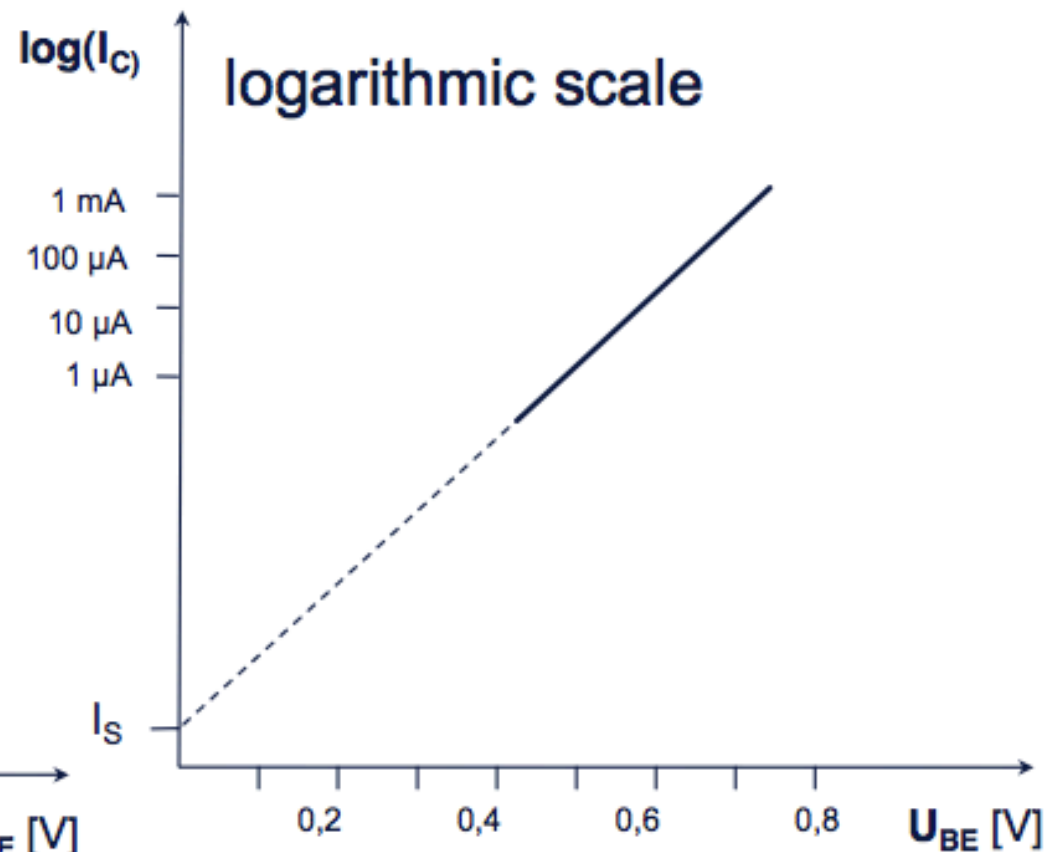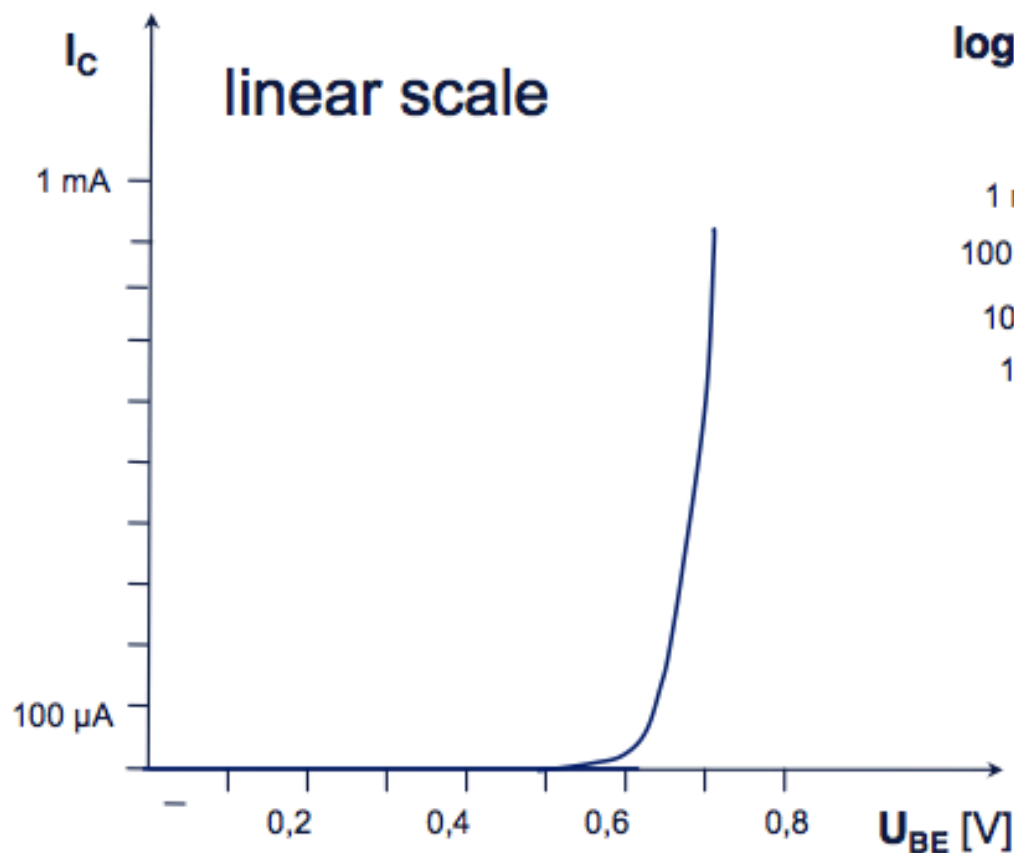
# Characteristics of bipolar transistors

$$I_C = I_S \cdot \left( e^{\frac{V_{BE}}{V_t}} - 1 \right)$$


$$V_t = \frac{k \cdot T}{q} \approx 26 \text{ mV} [25^\circ \text{C}]$$


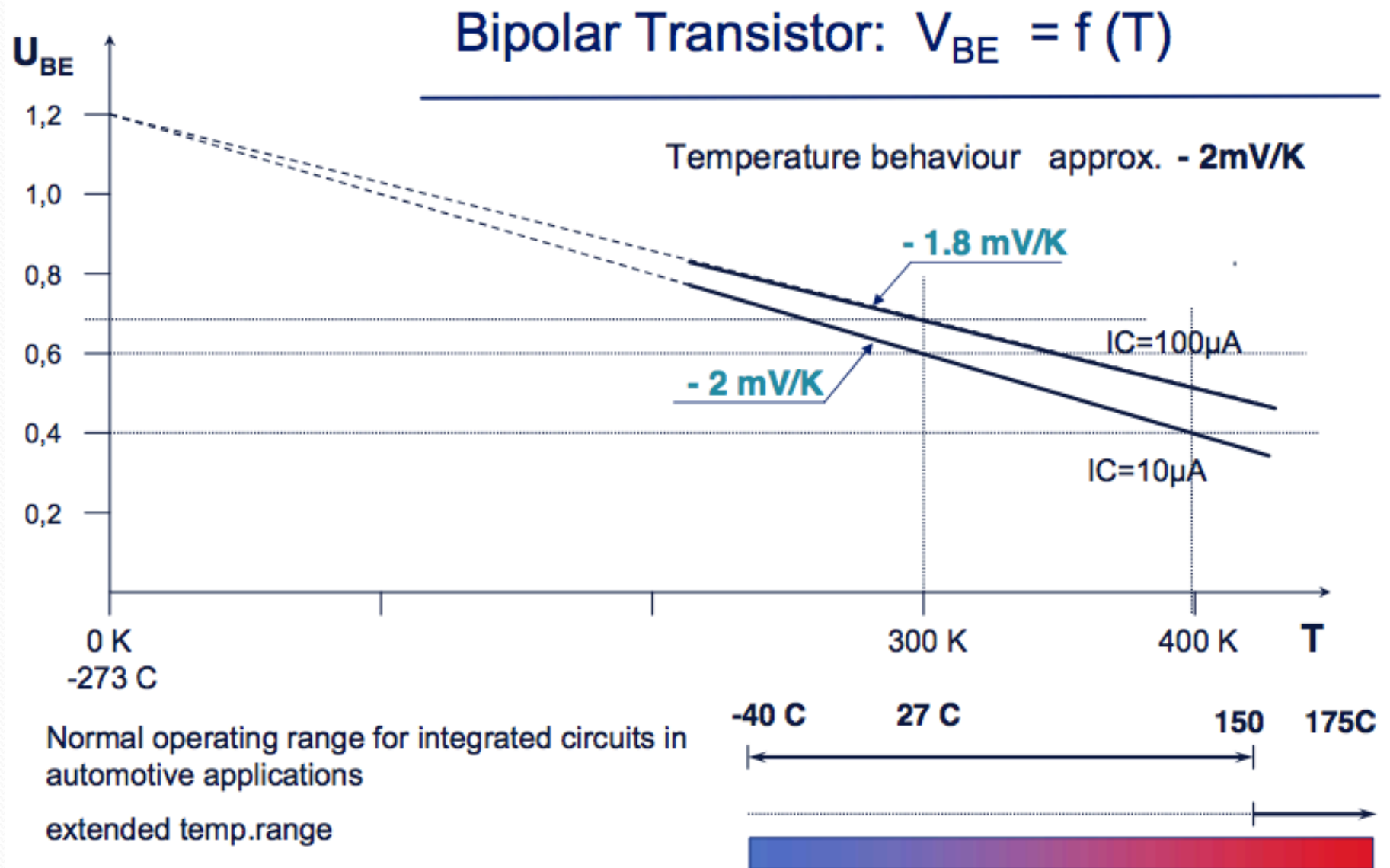
# Temperature dependence of BJT characteristics


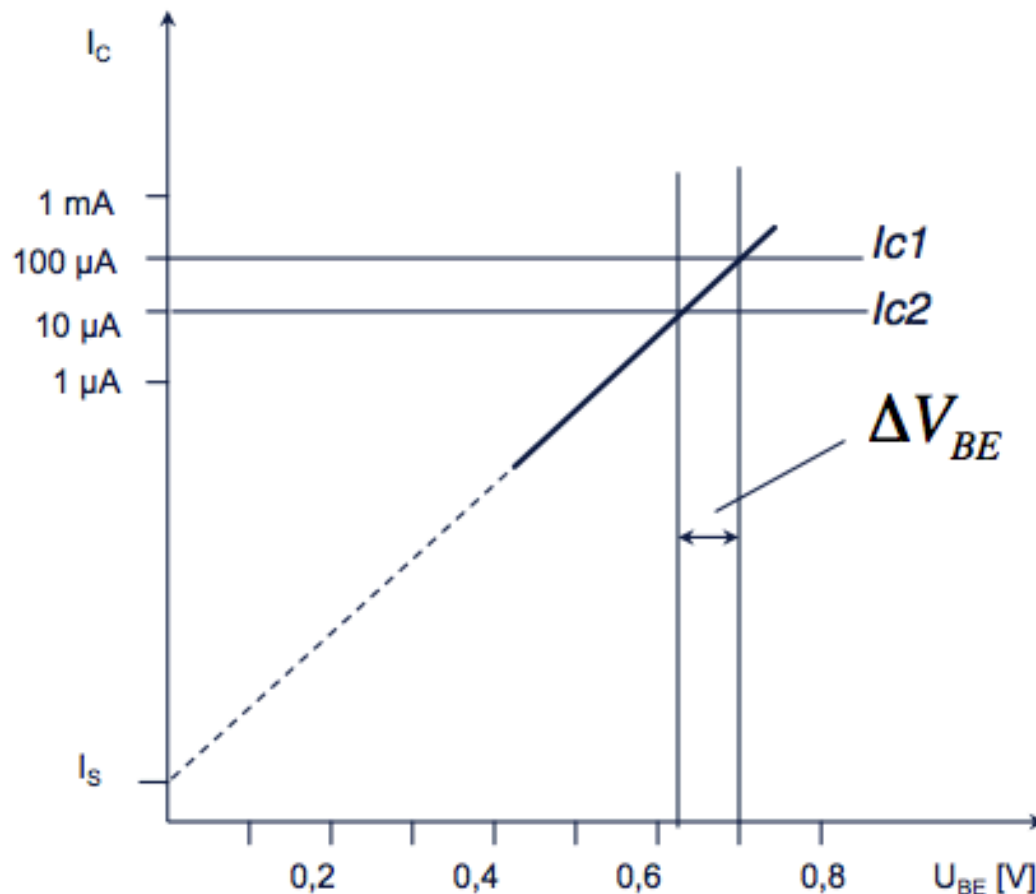
# Temperature dependence of $\Delta V_{BE}$



absolute value of  $V_{BE}$  depends on transistor parameter  $I_S$ ,  
 $\Delta V_{BE}$  is independent of individual transistor parameter

$$V_{BE} = \ln \left( \frac{I_C}{I_S} \right) \cdot V_t$$

$$\Delta V_{BE} = \ln \left( \frac{I_{C1}}{I_{C2}} \right) \cdot V_t$$


$$V_t = \frac{k \cdot T}{q} \approx 26 mV [25^\circ C]$$

$$k = 1,38 \cdot 10^{-23} J/K$$

$$q = 1,602 \cdot 10^{-19} As$$



| T [°C] | T [K] | V <sub>T</sub> [mV] |
|--------|-------|---------------------|
| -40    | 233   | 20,1                |
| 25     | 298   | 25,7                |
| 100    | 373   | 32,1                |
| 150    | 423   | 36,4                |
| 200    | 473   | 40,7                |
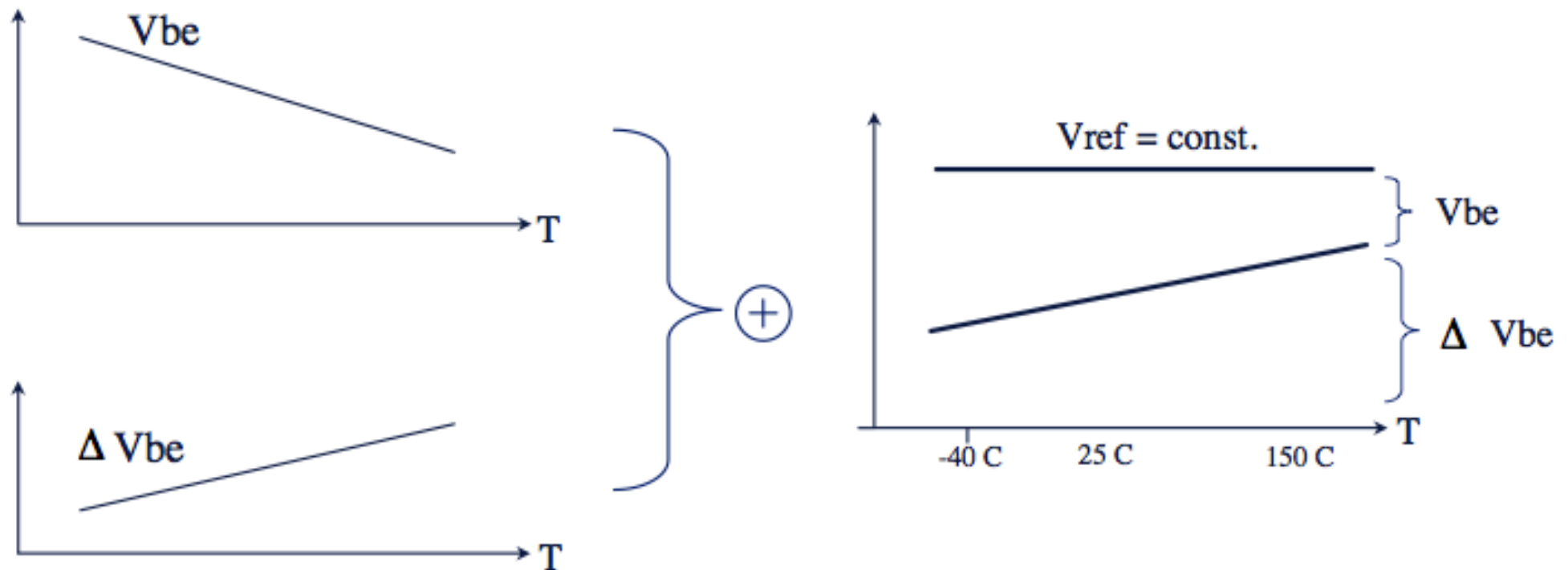
# Temperature-compensation of $V_{BE}$ voltage



The negative temperature dependence of  $V_{be}$  can be compensated by the positive temperature dependence of  $\Delta V_{be}$
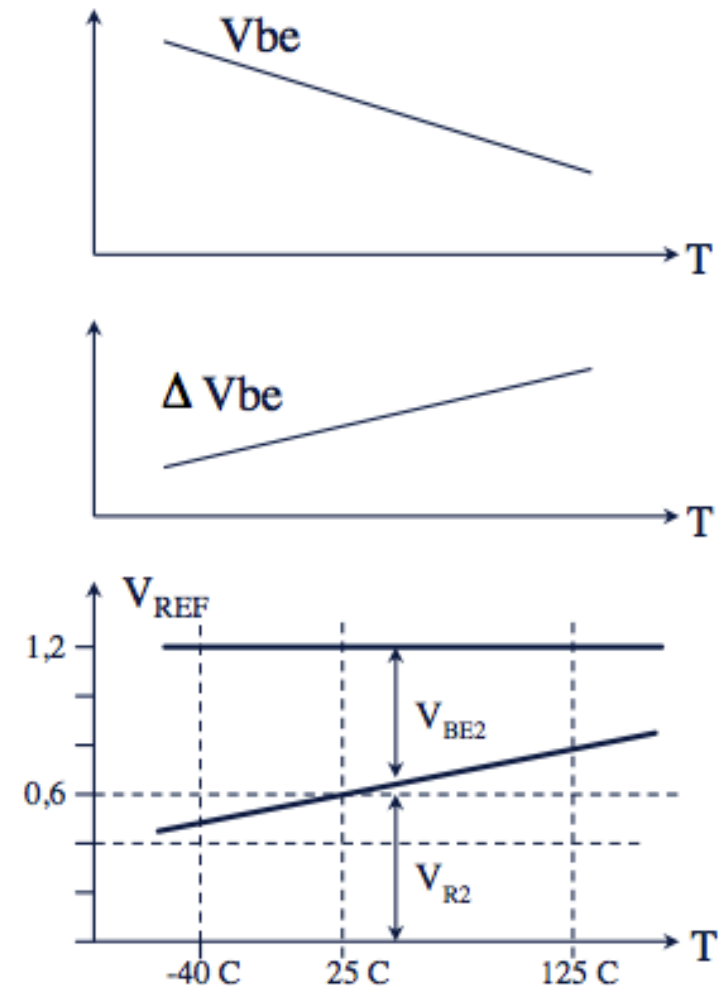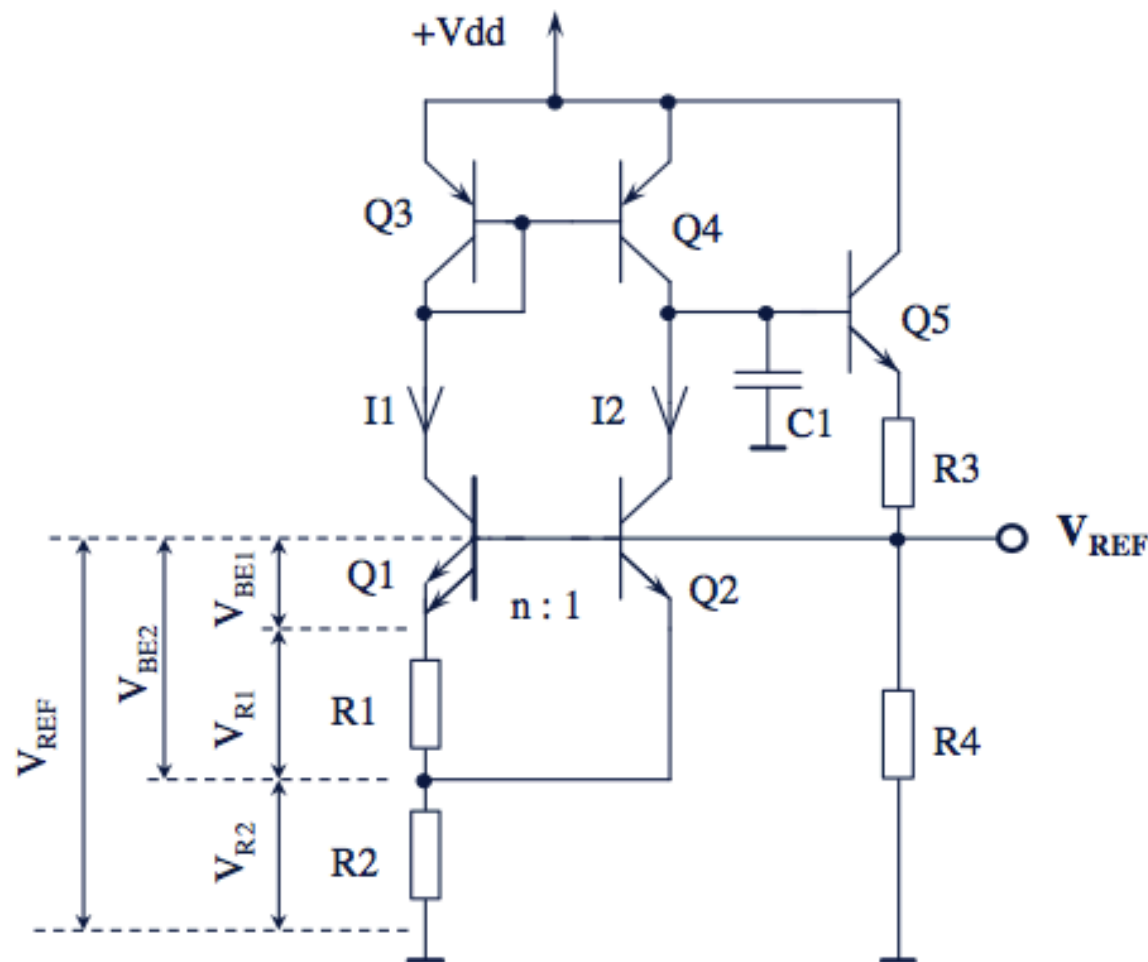
# Temperature-constant Reference Voltage: “Bandgap-Reference”



*This topology was first published by P.Brokaw, IEEE Journal of solid-state circuits, Dec. 1974*

# Operation of Bandgap-Reference Circuit

Assumption:  $I_1 = I_2$ , this is done by current mirror Q3, Q4.

Q1, Q2 have different emitter areas (AE) with  $AE(Q1) > AE(Q2)$ .

Ratio  $n$  is chosen as integer.

If collector-currents are equal, the base-emitter-voltages ( $V_{BE}$ ) of Q1, Q2 are different.

$$\Delta V_{BE} = V_t \cdot \ln(n) \quad n = \frac{AE(Q1)}{AE(Q2)} \quad V_t = \frac{k}{q} \cdot T$$

$$V_{R1} = \Delta V_{BE} = I_1 \cdot R_1$$

$$V_{R2} = (I_1 + I_2) \cdot R_2 = 2 \cdot I_1 \cdot R_2 = 2 \cdot \frac{R_2}{R_1} \cdot \Delta V_{BE}$$

$$V_{REF} = V_{BE2} + V_{R2} = 1,20 \dots 1,25V \text{ for optimal temp. comp.}$$

## Example:

$$n=10$$

$$\Delta V_{BE} = 60 \text{ mV } [25^\circ \text{C}]$$

$$R2/R1 = 5$$

$$V_{R2} = 600 \text{ mV}$$


$$V_{BE2} = 600 \text{ mV}$$

$$V_{REF} = 1,2 \text{ V}$$


Voltage drop at  $R1$  equals  $\Delta V_{BE}$  and has the same positive  $tc$  (temp. coefficient) as  $V_t$ . So also the voltage  $V_{R2}$  has the same  $tc$ , the absolute value of  $V_{R2}$  is chosen to a value similar to  $V_{BE}$ .

This leads to a compensation of the negative  $tc$  of  $V_{BE}$  over full temperature range. The resulting temperature error is of 2nd order and is in practice lower than 1%. The best temperature compensation will be achieved if the voltage  $V_{ref}$  is adjusted to 1.2 - 1.25 V. The absolute value of this reference voltage is better than  $\pm 5\%$  assuming all practical manufacturing tolerances.



# Bandgap-Reference Circuit

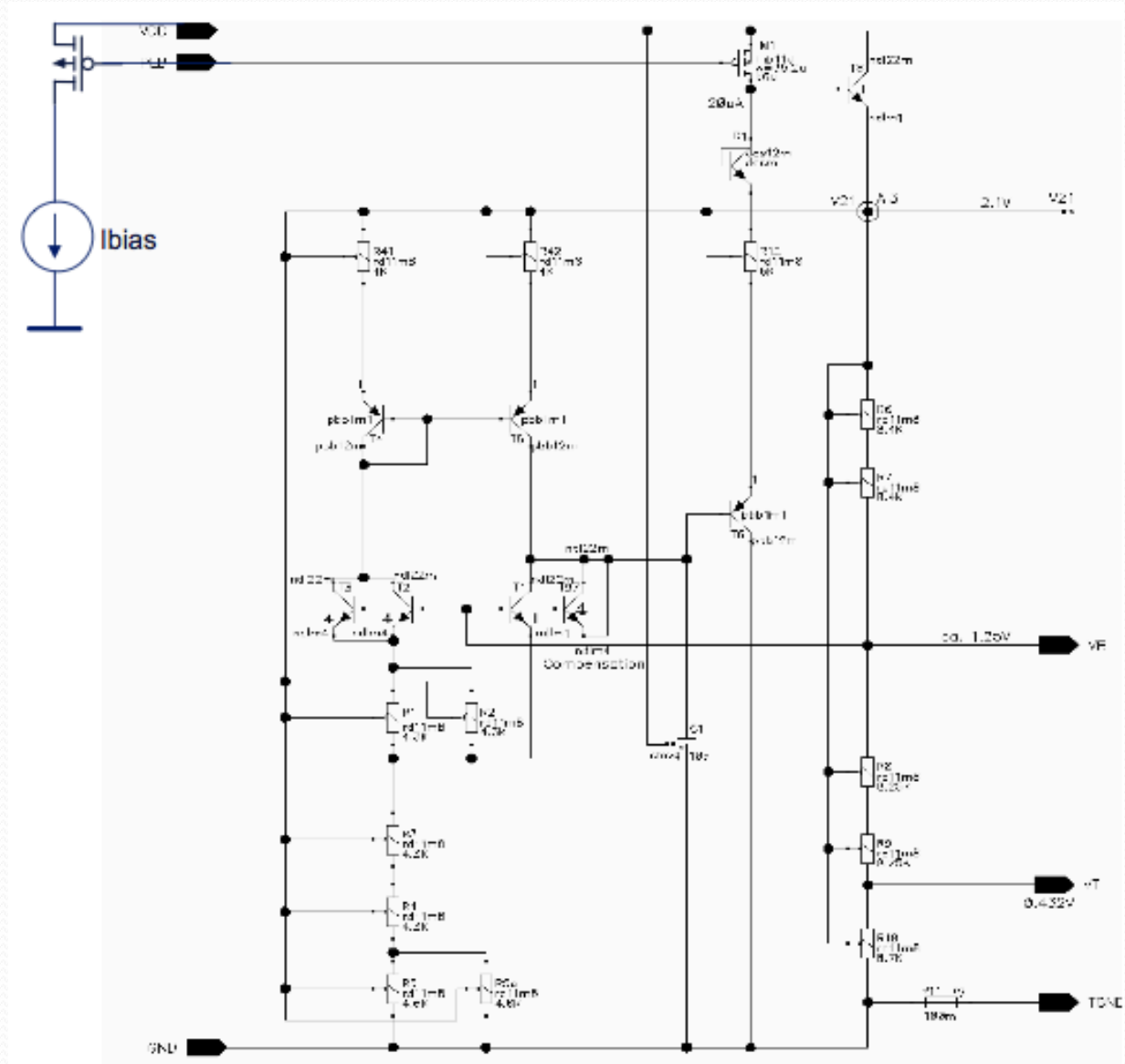

# Gummel plot of BJT

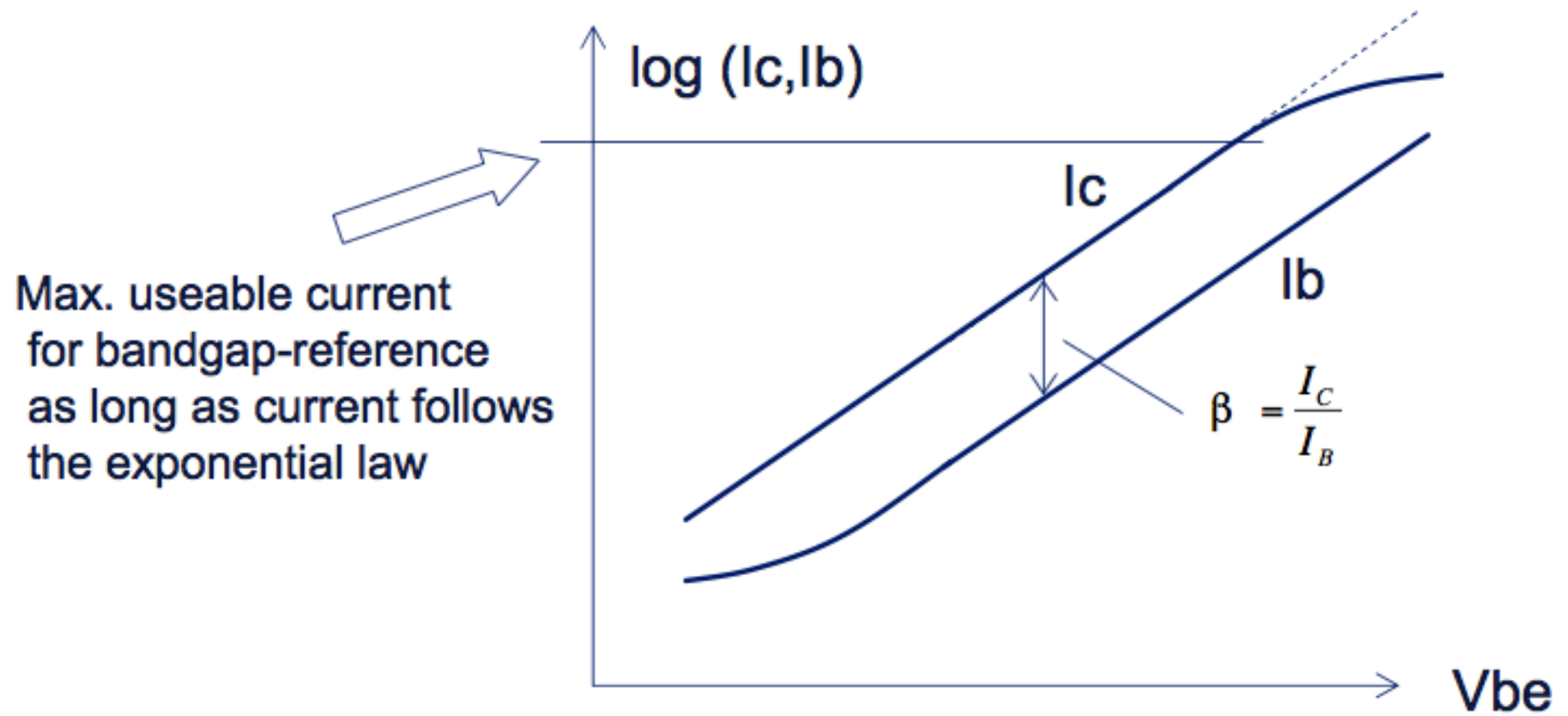
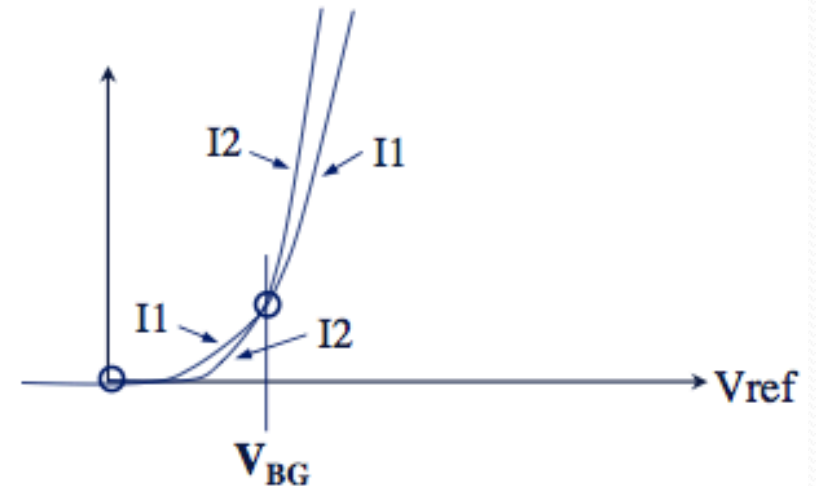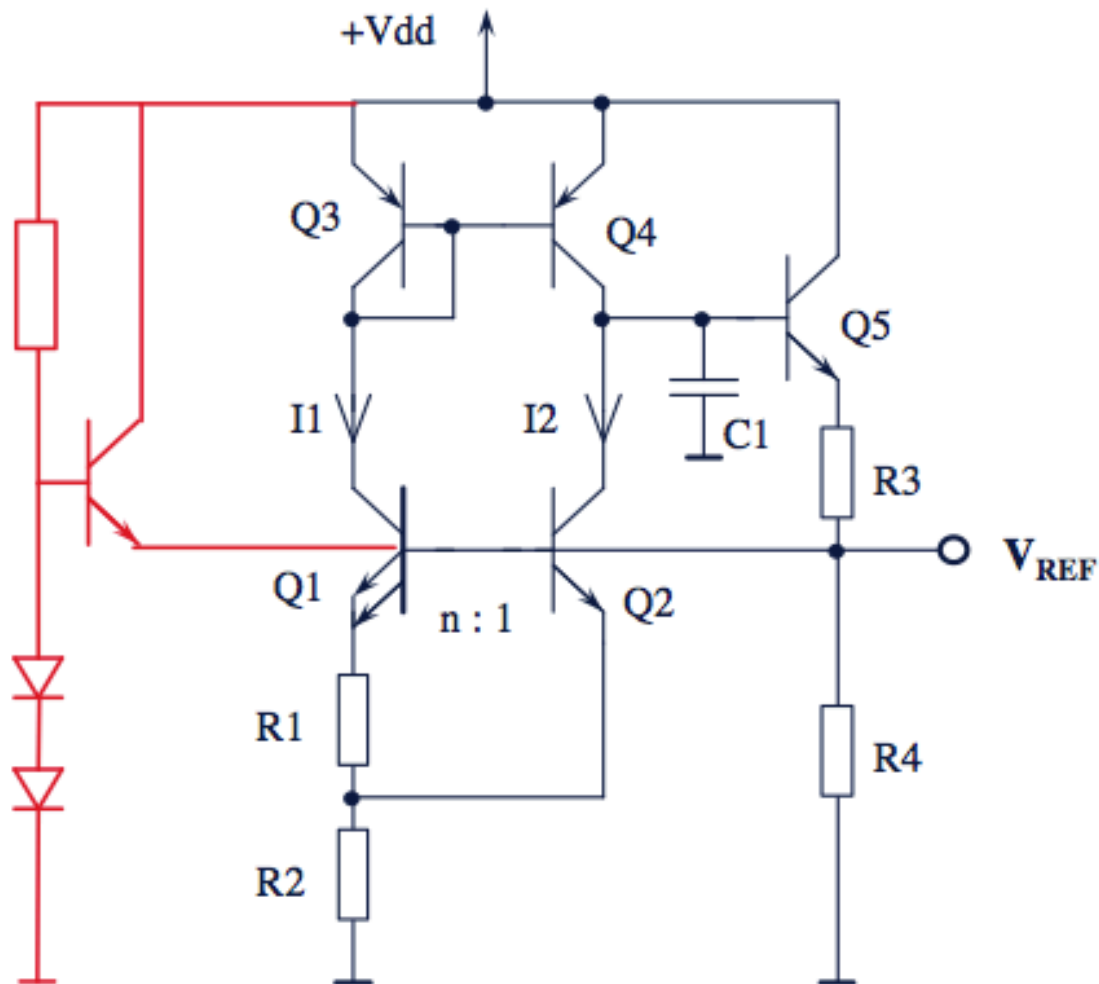
# Startup-Problem of Bandgap-Reference Circuit




Current Mirror Q3/Q4 forces  $I_1=I_2$ , this defines the operating point.

But there exists a second stable operating point:  $I_1=I_2=0$

A startup-circuit is required
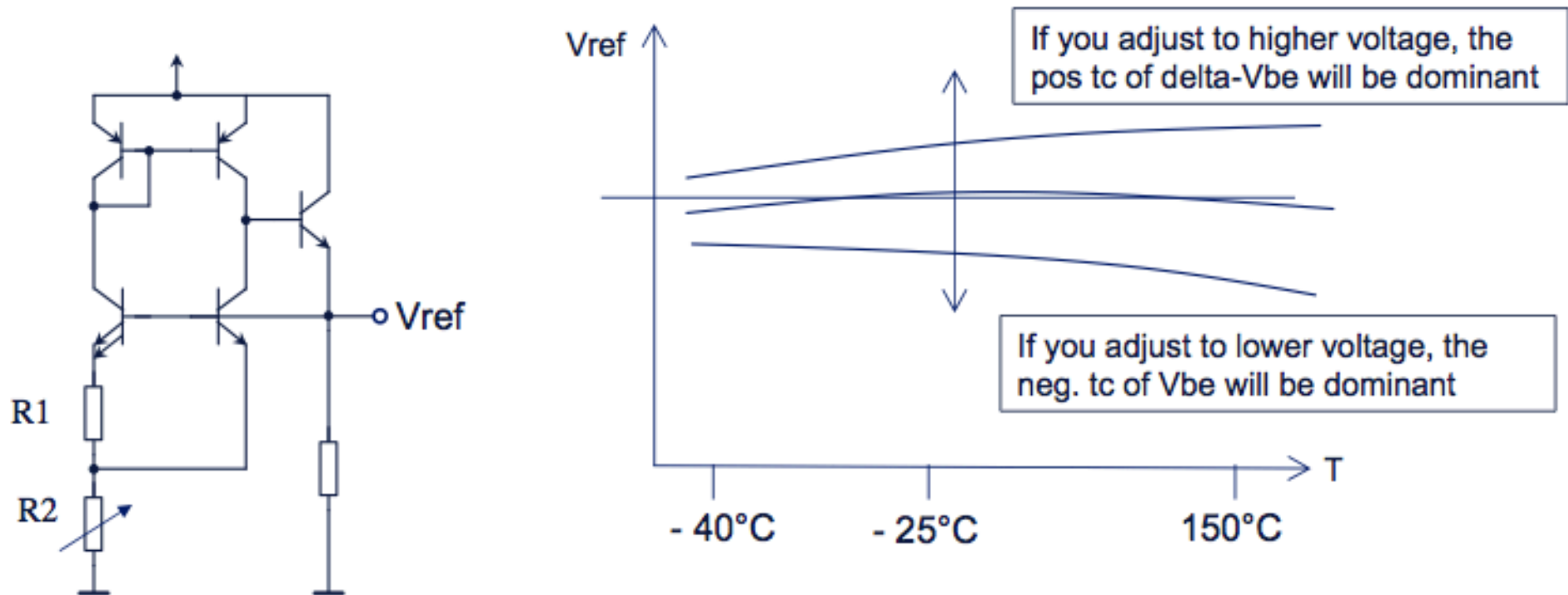
# Adjustment of bandgap reference voltage




Adjusting the Vref by changing the value of the resistor ratio  $R1/R2$  changes not only the output voltage but also the temperature behaviour.

There exists one point with minimal temperature dependence (in practice  $< 1\%$ )

For bipolar technologies this optimal voltage is around 1,25V


Adjustment can be done during wafer measurement, using „zener-zapping“ or laser trimming.
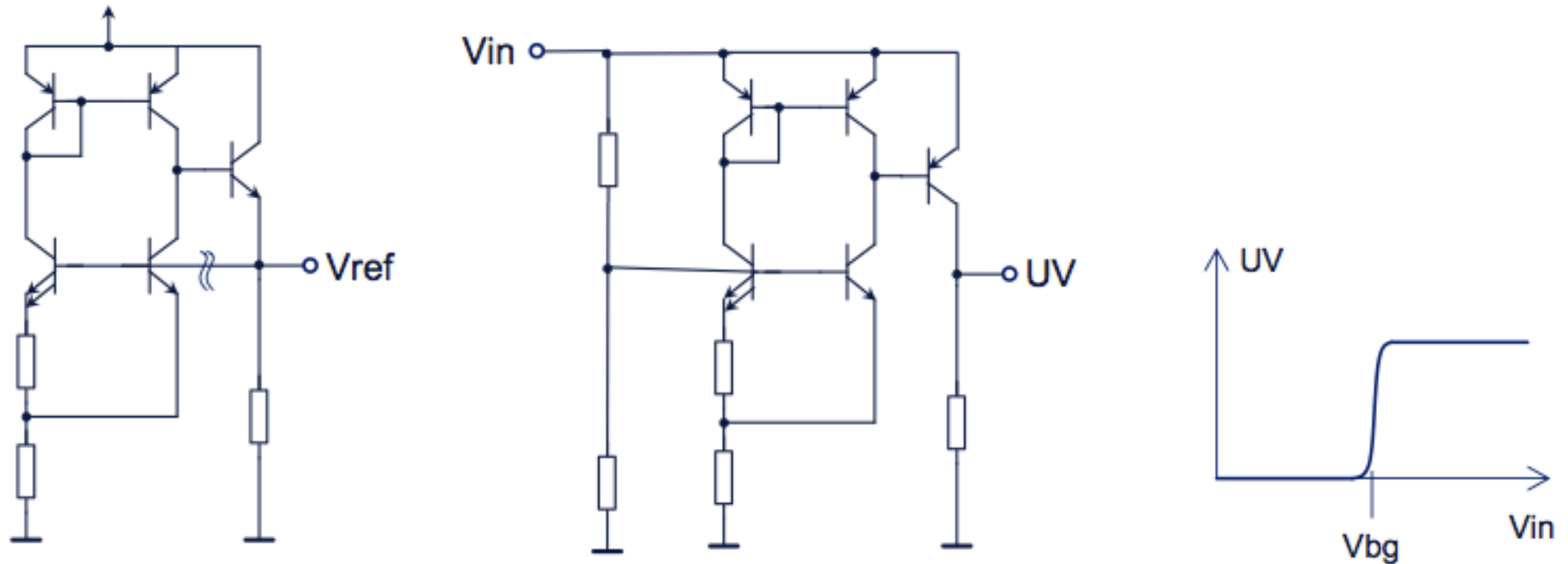
# Undervoltage detection circuit based on the bandgap reference principle



By opening the feedback of the bandgap reference circuit, similar circuit can be used for accurate switching at a given voltage threshold, e.g. for undervoltage detection

# Undervoltage detection circuit

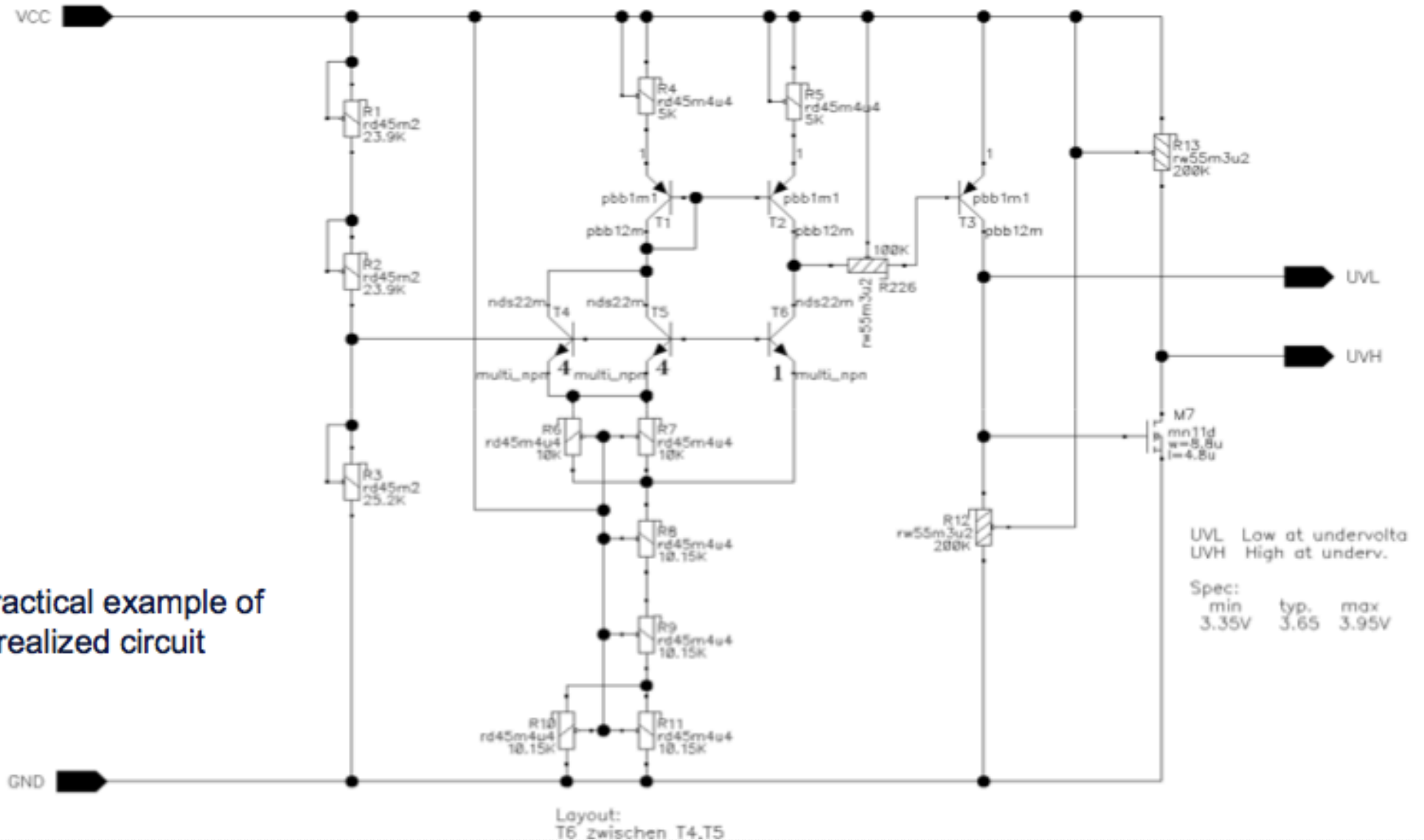


Practical example of  
a realized circuit

# CMOS Compatible Bandgap Reference


If in a CMOS process no real npn is available, use the „substrat-npn“, which always is available in a p-well CMOS technology, as bipolar reference.  
e.g. in the Smart technology this substrat-npn exists.

The collector is fixed to + Vbat (=substrat in that technologies), so you cannot use the npn as amplifier. You have only free access to base and emitter, which is enough to use the emitter-scaling for the Delta-Vbe principle.

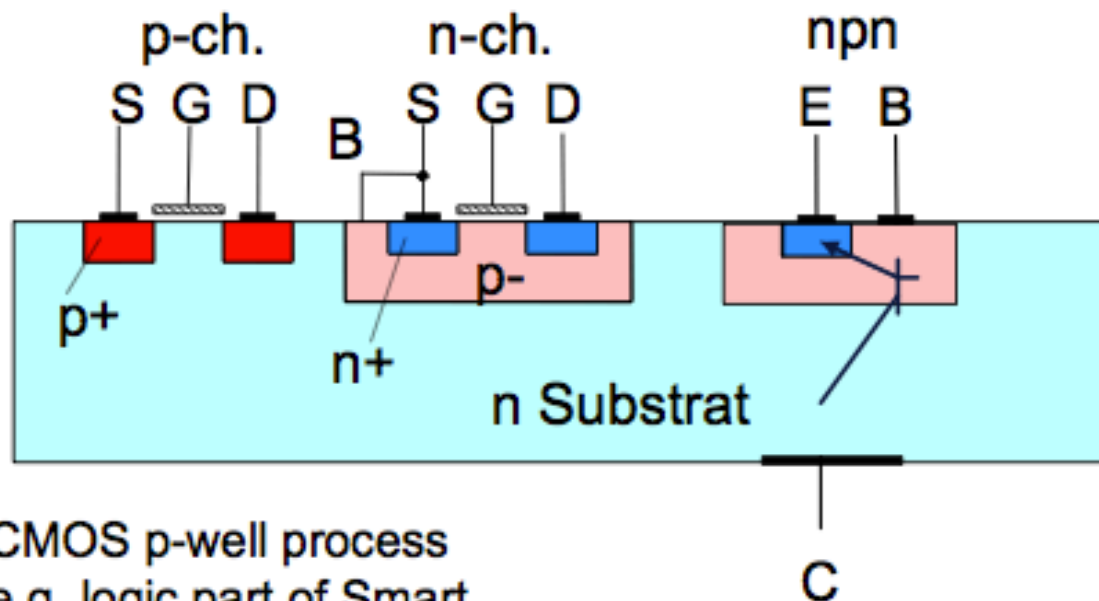
Amplifier has to be done in MOS which will cause more offset as a pure bipolar solution.



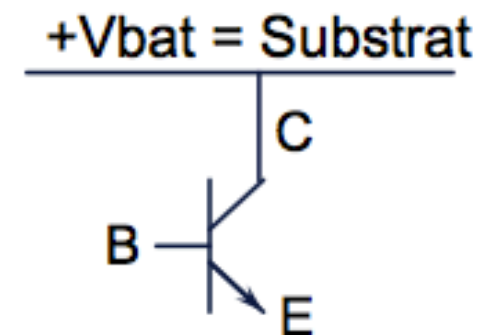CMOS p-well process  
e.g. logic part of Smart



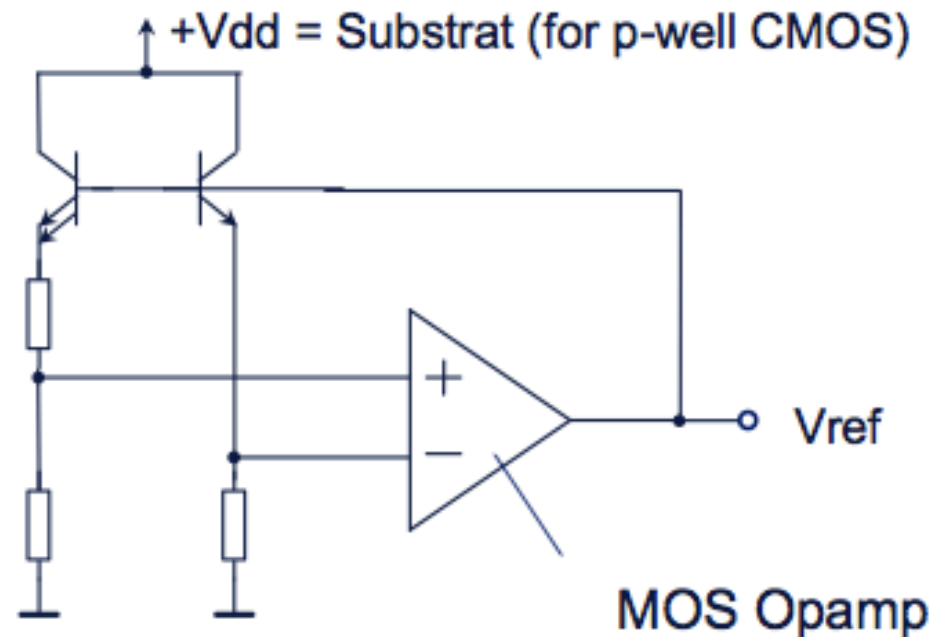
# Bandgap reference with all npn-collectors connected to $V_{DD}$




- 1) This is a possible solution to realise a bandgap reference in a CMOS technology. Take care of opamp offset
- 2) This circuit is robust against leakage currents and other parasitic currents at the bipolar collectors. So it can also be used with bipolars in the BCD process to improve robustness.
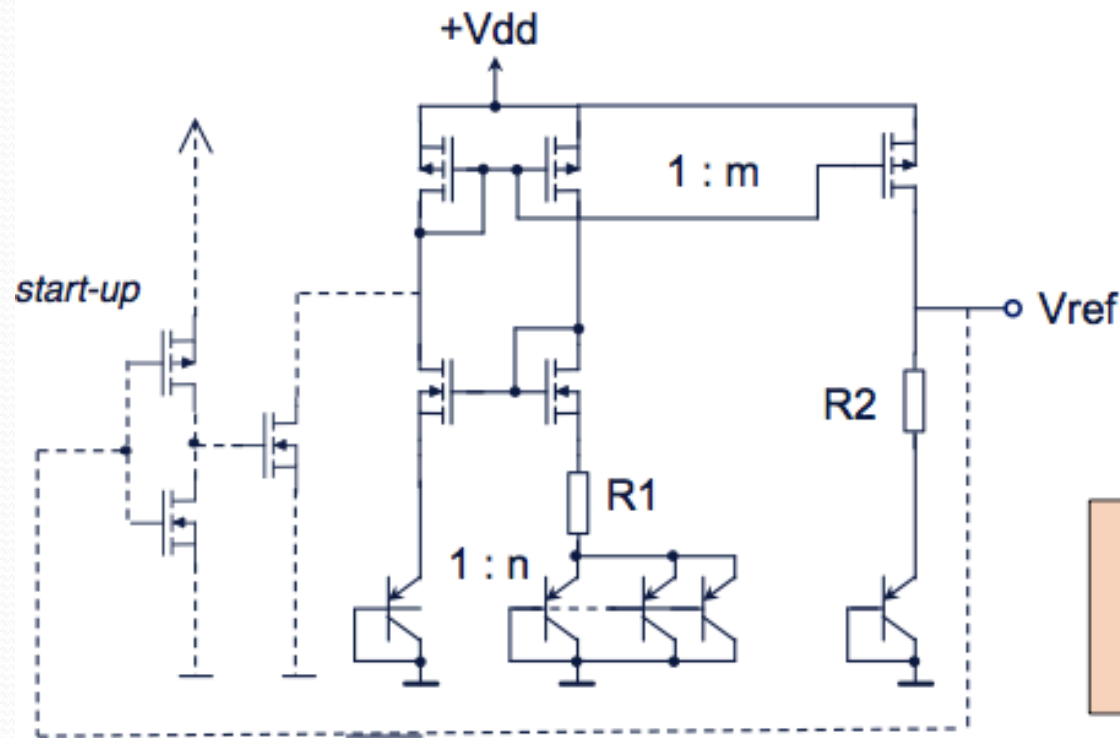
# Bandgap reference in a n-well CMOS technology




$$V_{R1} = \Delta V_{BE} = V_t \cdot \ln(n)$$
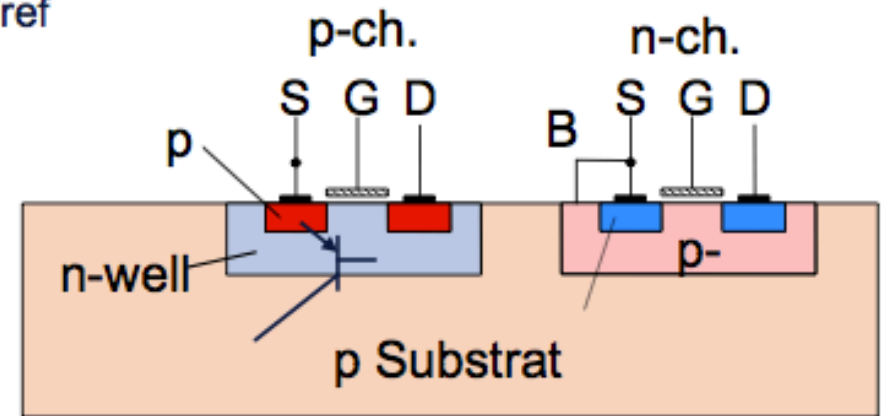
$$V_{ref} = V_{R1} \cdot m \cdot \frac{R2}{R1} + V_{BE}$$



parasitic pnp can be used as bipolar diode

# „Widlar“ Bandgap – Reference

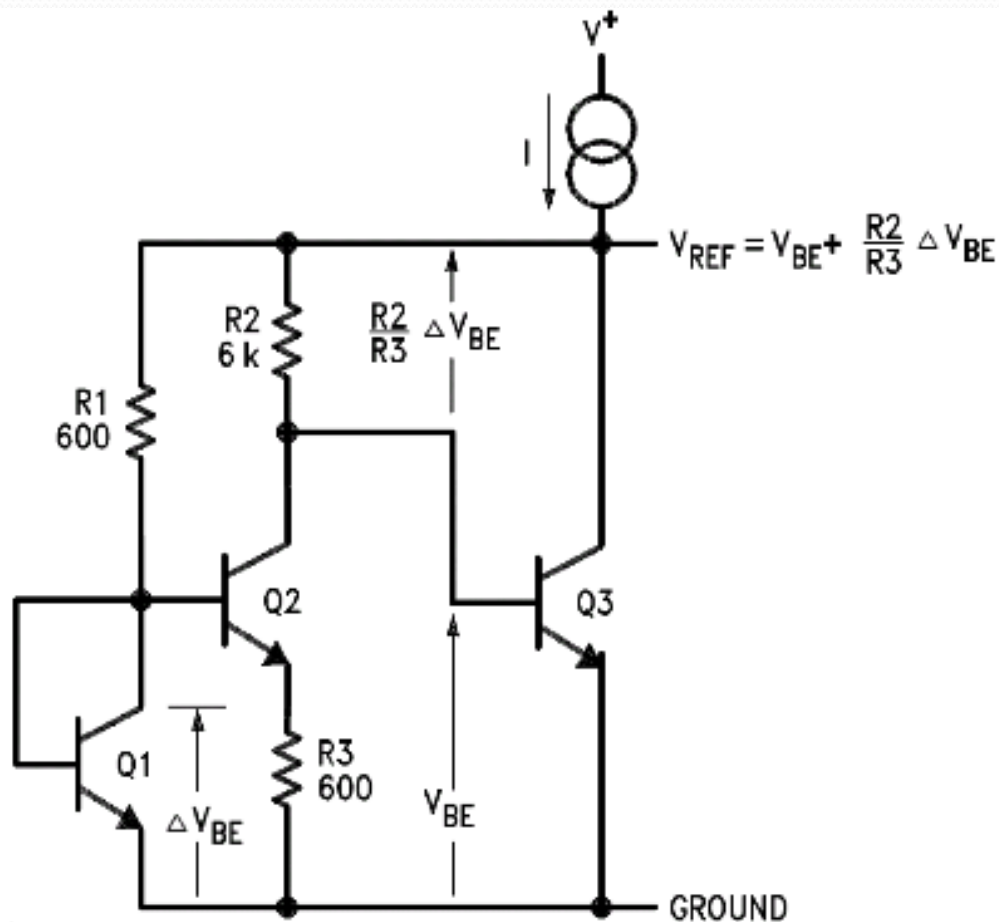


One of the first published bandgap circuits, using this idea to sum up a  $V_{be}$  (neg.temp-coeff) with a  $\Delta V_{be}$  (pos.Temp-coeff.)

Here the current difference in the transistors is set by resistors  $R_1$ ,  $R_2$  to the ratio 10, not by the size of the transistors.

If you would additional set  $Q_2$ ,  $Q_1$  to different size this result to:

$$V_{REF} = V_{BE} + \frac{R_2}{R_3} \cdot V_t \cdot \ln\left(\frac{\text{area}(Q2)}{\text{area}(Q1)} \cdot \frac{R_2}{R_1}\right)$$
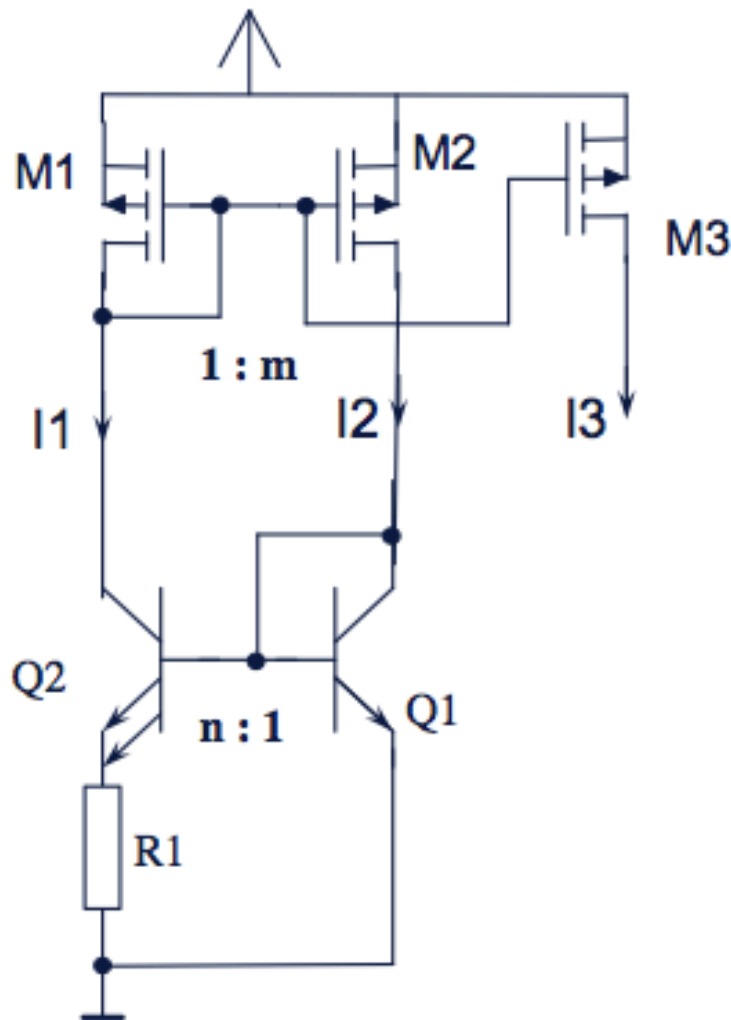
## Current - Reference based on $\Delta V_{BE}$



If  $M1 = M2 \rightarrow I1 = I2$

:

$$I_1 = \frac{\Delta V_{BE}}{R_1} = \frac{V_t \cdot \ln(n)}{R1}$$


If  $M1, M2$  not equal:  $M2/M1 = m$

Ratio  $m$  acts as multiplication-factor:

$$I_1 = \frac{\Delta V_{BE}}{R_1} = \frac{V_t \cdot \ln(n \cdot m)}{R1}$$

*Similar to bandgap reference, this circuit could need a startup-circuit*
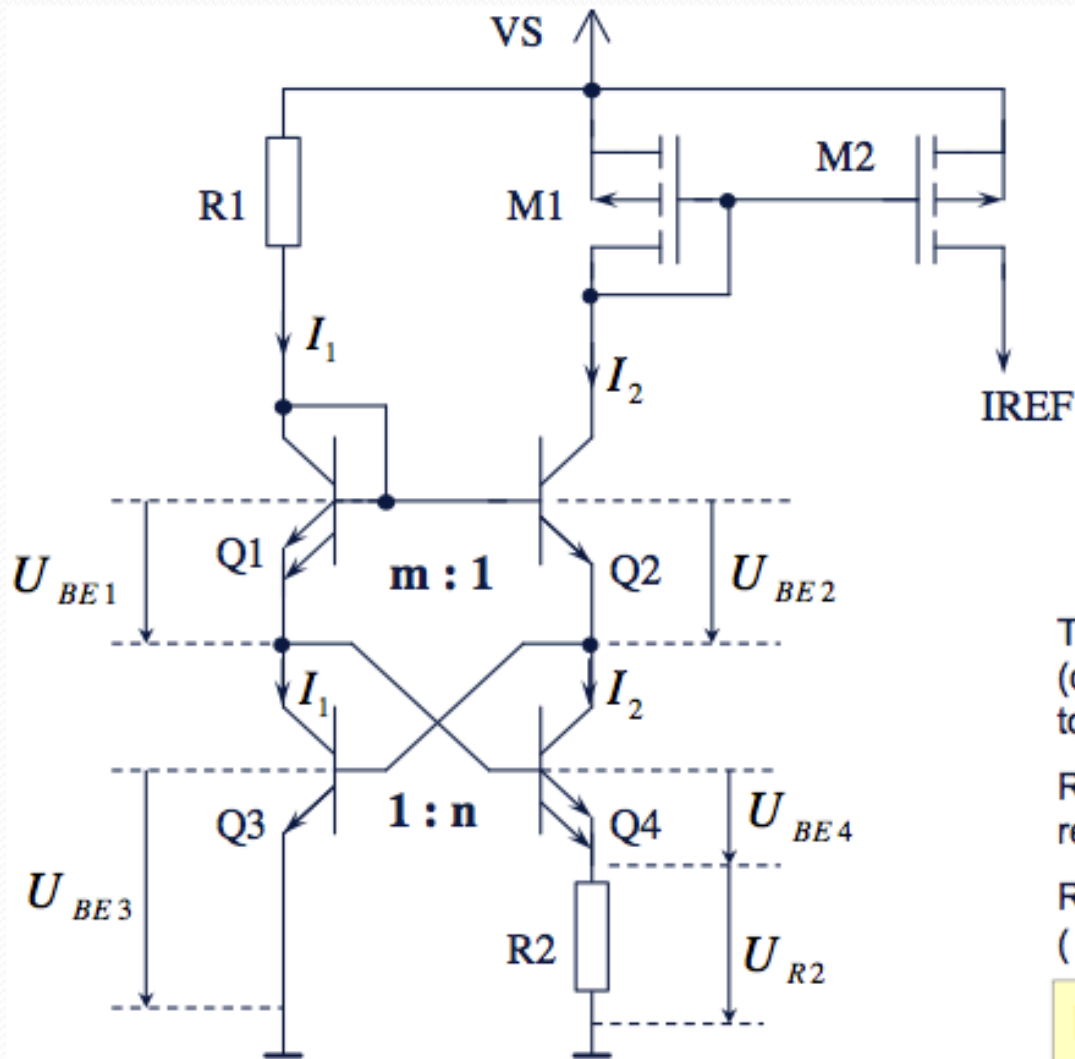
# Cross-coupled current source based on $\Delta V_{BE}$



$$\begin{aligned}
 U_{BE1} + U_{BE4} + U_{R2} &= U_{BE2} + U_{BE3} \\
 V_T \ln \frac{I_1}{mI_s} + V_T \ln \frac{I_2}{nI_s} + I_2 R &= V_T \ln \frac{I_2}{I_s} + V_T \ln \frac{I_1}{I_s} \\
 I_2 R &= V_T \left( \ln \frac{I_2}{I_s} - \ln \frac{I_2}{nI_s} + \ln \frac{I_1}{I_s} - \ln \frac{I_1}{mI_s} \right) \\
 I_2 R &= V_T \left( \ln \frac{I_2}{I_s} \cdot \frac{nI_s}{I_2} + \ln \frac{I_1}{I_s} \cdot \frac{mI_s}{I_1} \right) = V_T \ln(n + m)
 \end{aligned}$$

$$I_2 = \frac{V_t \cdot \ln(n \cdot m)}{R_2} = I_{REF}$$


The effect of cross-coupling is that the current  $I_1$  (defined by resistor  $R_1$  and  $V_s$ ) has no influence to the resulting current  $I_2$ .

R1 could be an inaccurate devices e.g. p-well resistor or junction-fet

R2 defines the accurate reference-current  
(I<sub>ref</sub> always depends on a resistor accuracy)

Easy temp.compensation, if R2 is a diffusion resistor (with pos. tc)

# Adjustable Z-diode

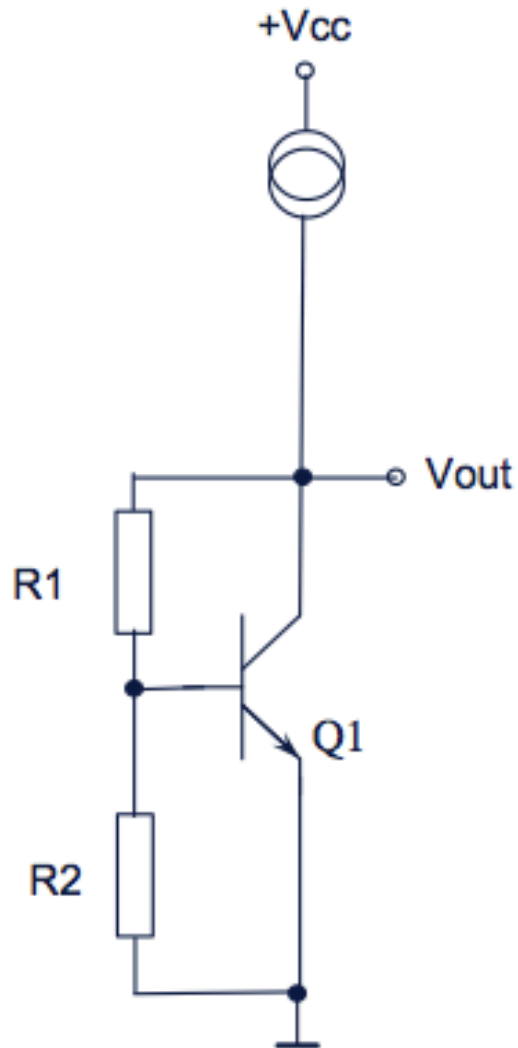


If the temperatur-dependence of  $V_{be}$  can be accepted, this is an easy solution to simulate a z-diode with a bipolar transistor.

Inside integrated circuits z-diodes are not available in each wanted voltage range, so this could be a solution.

$$V_{OUT} = \frac{R_1 + R_2}{R_2} \cdot V_{BE}$$

# Z-diode voltage multiplier

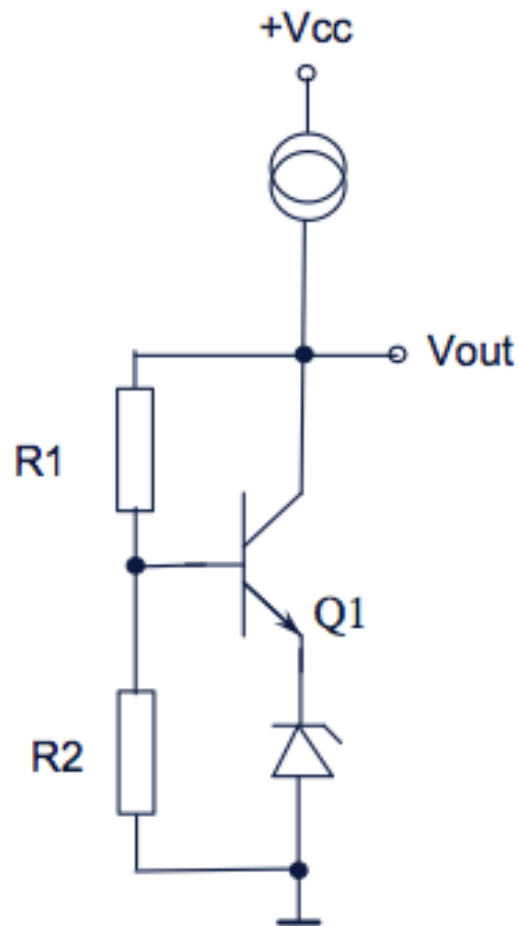

This circuit replaces a  
high-voltage Z-diode

Combination of bipolar-Vbe and Z-diode could  
lead to a first order temp.-compensation  
(depend on temp-dependence of Z-diode)

$$V_{OUT} = \frac{R_1 + R_2}{R_2} \cdot (V_{BE} + V_Z)$$