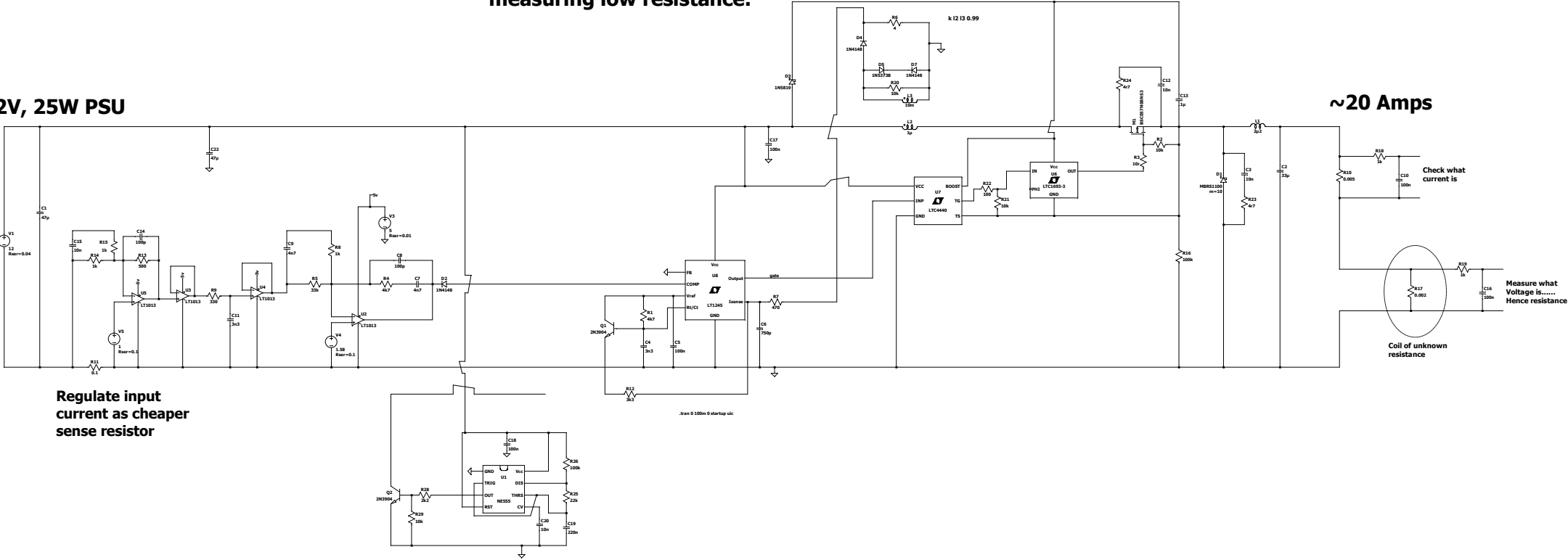


12V, 25W PSU

~20 Amp current source for  
measuring low resistance.

~20 Amps



Regulate input  
current as cheaper  
sense resistor

Check what  
current is

Measure what  
Voltage is.....  
Hence resistance