

COMPLEX POWER

Note Title

4/14/2011

Suppose we have V & I as follows:

$$V = V_0 \cos(\omega t + \chi) = \operatorname{Re}[V_0 e^{j\chi} e^{j\omega t}] \Rightarrow V_p = V_0 e^{j\chi}$$

$$I = I_0 \cos(\omega t + \beta) = \operatorname{Re}[I_0 e^{j\beta} e^{j\omega t}] \Rightarrow I_p = I_0 e^{j\beta}$$

$$P = \frac{\omega}{2\pi} \int_0^{2\pi/\omega} V_0 I_0 \cos(\omega t + \chi) \cos(\omega t + \beta) dt$$

$$= \frac{\omega}{2\pi} \frac{V_0 I_0}{2} \int_0^{2\pi/\omega} [\cos(2\omega t + \chi + \beta) + \cos(\chi - \beta)] dt$$

$$= \frac{\omega}{2\pi} \frac{V_0 I_0}{2} \left[\sin\left(2\pi \frac{1}{\omega} + \chi + \beta\right) - \sin(\chi + \beta) + \left(\frac{2\pi}{\omega} - 1\right) \cos(\chi - \beta) \right]$$

$$= \frac{\omega}{2\pi} \frac{V_0 I_0}{2} \frac{2\pi}{\omega} \cos(\chi - \beta)$$

$$P = \frac{V_0 I_0}{2} \cos(\chi - \beta)$$

To get the same thing in phasor arithmetic

$$\text{Say we do } \operatorname{Re}[V_p I_p] = V_0 I_0 \cos(\chi + \beta)$$

But that is not what we need. We need χ & β to have opposite signs \therefore we need to take the conjugate of 1 phasor

$$\text{Hence } P = \frac{1}{2} \operatorname{Re}[V_p \bar{I}_p^*]$$