

## Common Mode Range

- Parametric DC + AC analysis, vary Vcm from 0 to 2
- Find Vcm min & max where gain is  $\frac{1}{2}$  of Max (-3db)

