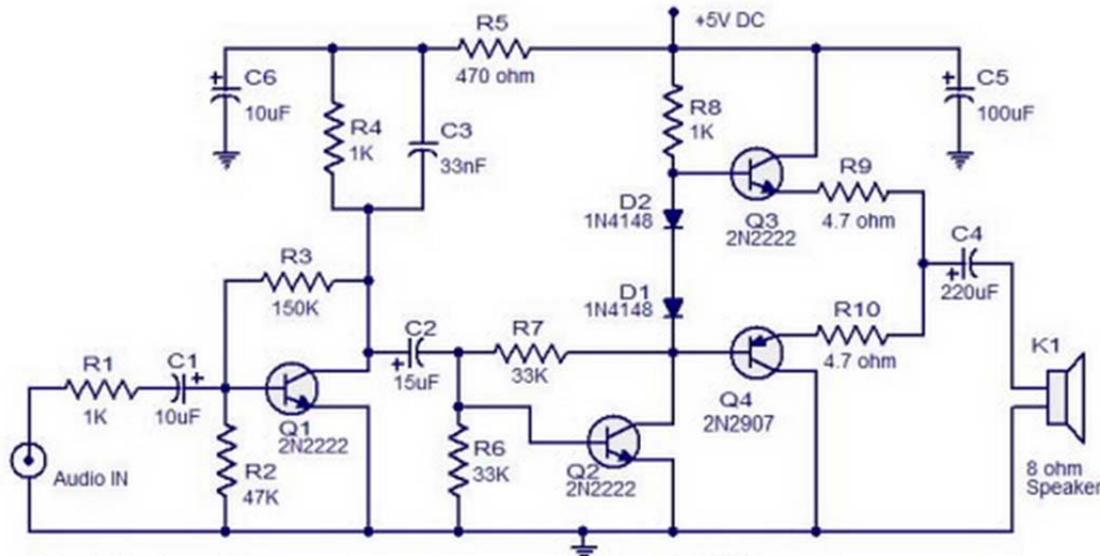



Q1. Consider the circuit shown in Figure 1. Take $V_{BE}=0.7V$, $\beta=100$, $V_T=25mV$, $C_\pi=C_\mu=2\text{ pF}$. Ignore the early effect.

1. Calculate the DC bias for the circuit
2. Derive the expression for the overall voltage gain
3. Derive the expression for the 3dB high cutoff frequency (f_H).




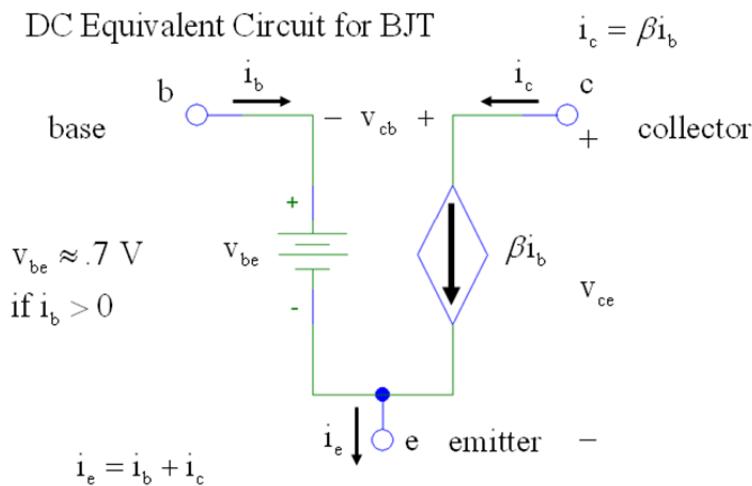1. Use DC equivalent circuit for each BJT

Read here: <http://www.fke.utm.my/mine/SEE2063/Chapter4%20BJTs%20Biasing.pdf>



Ignore capacitors at this moment

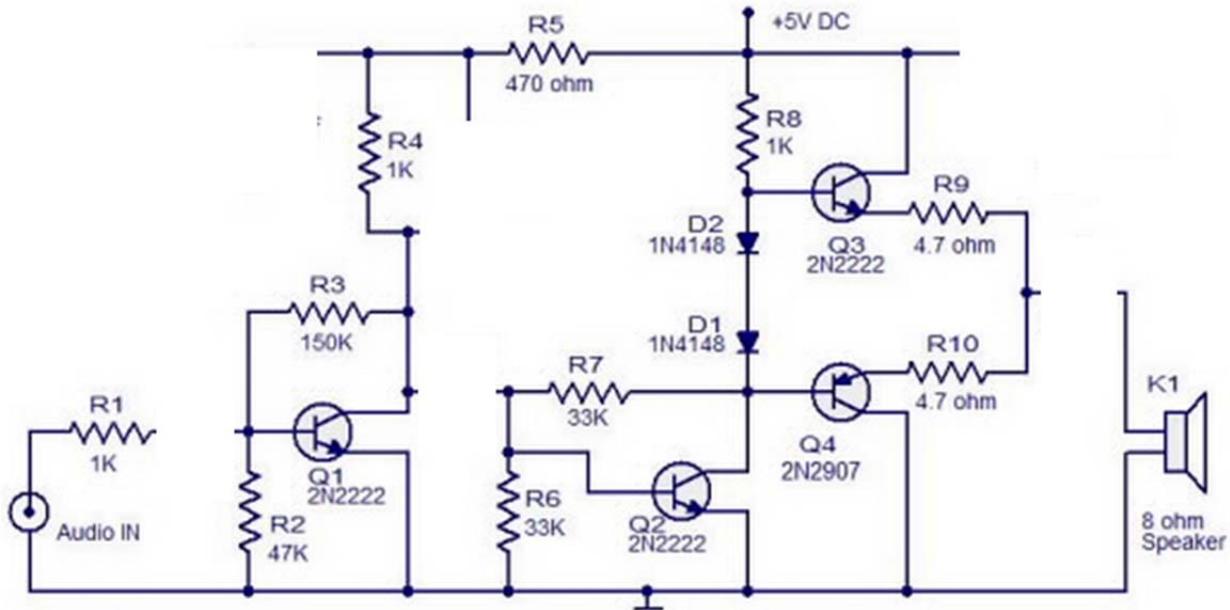


Use KVL\KCL in circuit to find all currents and voltages needed.

$$I_C = \beta I_B$$

$$I_E = (\beta + 1)I_B$$

$$V_{BE} = 0.7V$$

$$\beta = 100$$

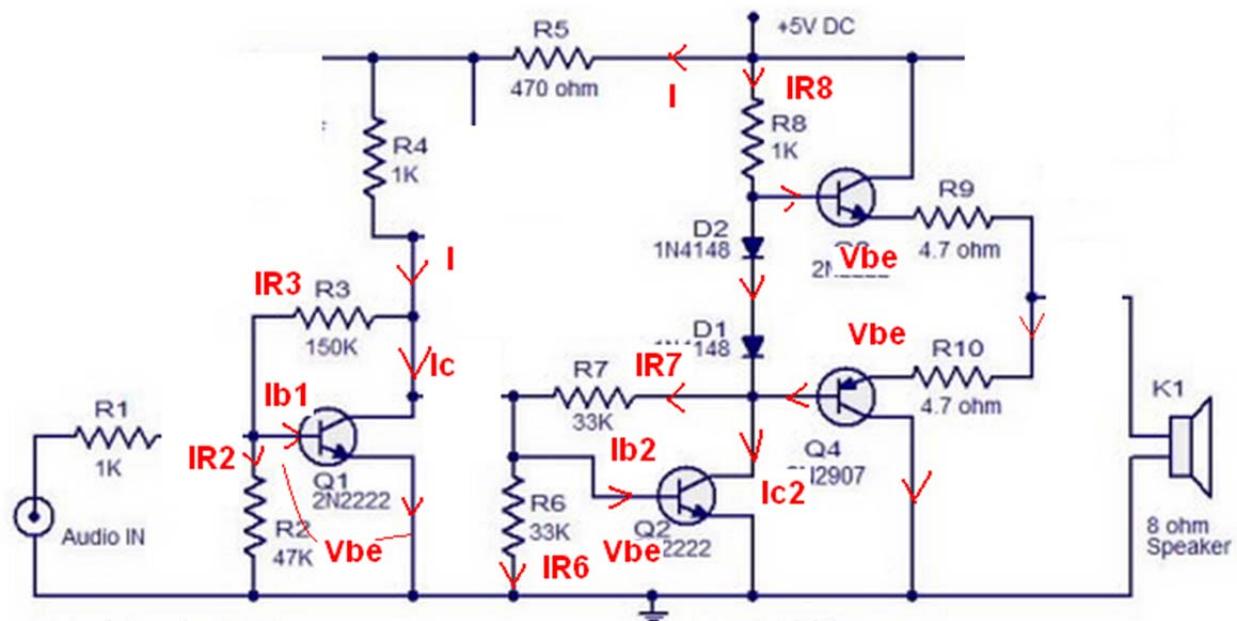

Example for Q1

$$I_{R3} = I_{R2} + I_{B1}, \quad U_{R2} = U_{BE} = 0.7V \Rightarrow I_{R2} = 0.7 / 47k = 0.01489 \text{ mA} \quad [\text{similar for } U_{R6} = U_{BE} = 0.7V \quad I_{R6} = 0.7V / 33k = 0.02121 \text{ mA}]$$

$$I = I_C + I_{R3} = \beta * I_{B1} + I_{B1} + I_{R2} = I_{B1} * 101 + 0.01489 \text{ mA}$$

$$V_{CC} = 5V = I (R_4 + R_5) + I_{R3} R_3 + 0.7 = (I_{B1} * 101 + 0.01489 \text{ mA}) (1k + 0.47k) + (I_{B1} + 0.01489) 150k + 0.7$$

$$I_{B1} (101 * 1.47k + 150k) = 5 - 0.7 - 0.01489 * (1.47k + 150k)$$

$$I_{B1} = 2.0456 / 298.47 = 0.00685 \text{ mA} = 6.85 \mu\text{A}$$

Ic=0.685mA

I= 0.7067mA

Uce(Q1)= Vcc- I(R4+R5)= 5-0.7067mA(1.47k)= 3.96V

.....
IcQ3=0 and IcQ4 =0

KVL

Ud2 + Ud1= UbeQ3 + IeQ3*R9 + IeQ4*R10 + UbeQ4, but

Ud2=Ud1=Ube=UbeQ3=UbeQ4=Ube= 0.7V

IeQ3=IeQ4

So IeQ3(R9+R10)=0 => IeQ3=0, IeQ4=0

And in this way we can ignore IbQ3=beta*IcQ3 =0 and also IbQ4 = beta* IcQ4= 0

.....