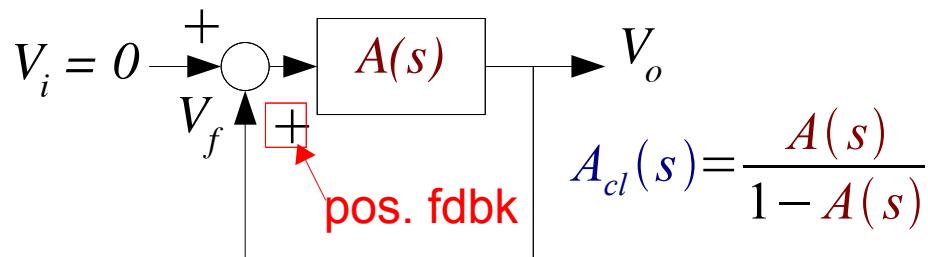


Colpitts Oscillator

- Basic positive feedback oscillator
- The Colpitts LC Oscillator circuit
- Open-loop analysis
- Closed-loop analysis
- Root locus
- Oscillation Conditions
- Colpitts design

Basic Positive Feedback Oscillator

closed-loop oscillator




$$V_o = A(s)(V_i + V_f) = A(s)(0 + V_o) \Rightarrow$$

$$V_o(1 - A(s)) = 0$$

Since: $V_o \neq 0 \Rightarrow 1 - A(s) = 0 \Rightarrow A(s) = 1 \Rightarrow$

open-loop: determine loop-gain

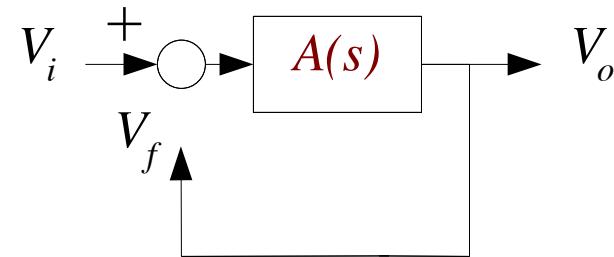

$$\frac{V_f}{V_i} = \frac{V_o}{V_i} = A(s) = \frac{K N(s)}{D(s)}$$

$$A_{cl}(s) = \frac{A(s)}{1 - A(s)} = \frac{K N(s)}{D(s) - K N(s)}$$

$$D(s) - K N(s) = 0$$


Condition for oscillation at $s = j\omega_0$:

$$A(s) = 1 e^{j \pm 2k\pi}$$


for $k = 0, 1, 2 ..$

Barkhausen criterion

Colpitts Oscillator Basic Schematic

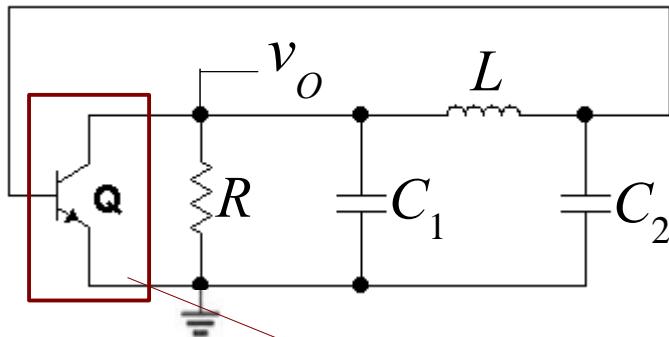


Closed-loop

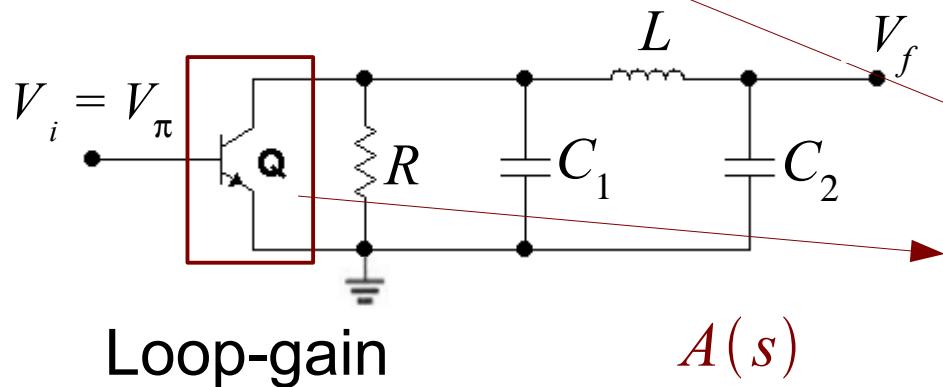


Assumptions:

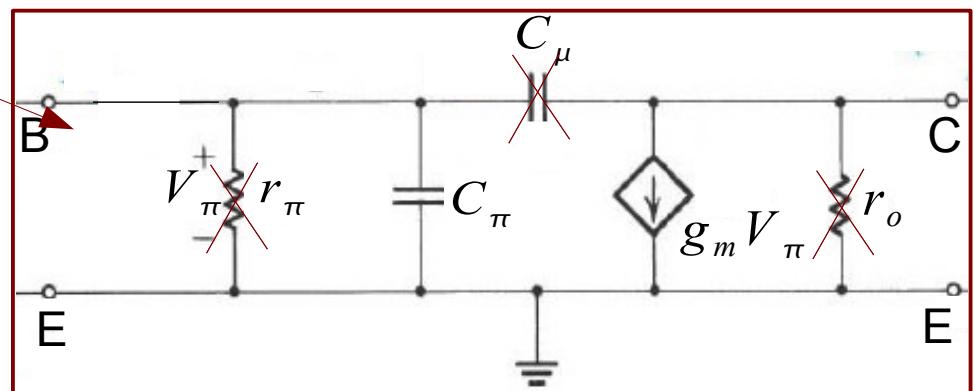1. r_π large (compared to $1/\omega C_2$).
2. C_μ negligible (compared to C_I , C_2)
3. C_π part of C_2 (*in closed loop*)
4. R represents total resistance in collector circuit, i.e. $R \parallel r_o \approx R$



Loop-Gain Analysis

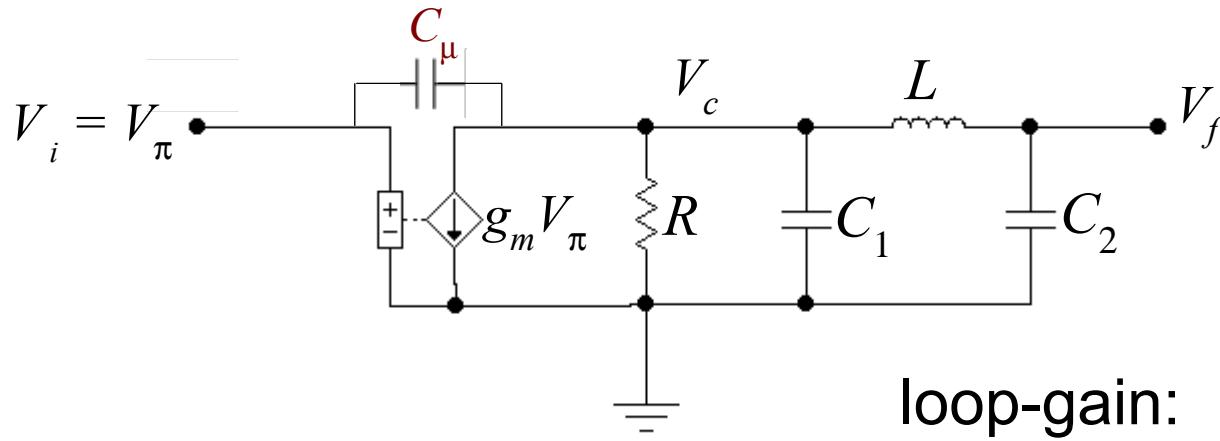

loop-gain: $A(s) = \frac{V_f}{V_i}$

Node equation at V_c :

$$(sC_1 + \frac{1}{sL} + \frac{1}{R})V_c - \frac{1}{sL}V_f + (g_m - s\cancel{C}_\mu)V_i = 0$$

$$(sC_1 + \frac{1}{sL} + \frac{1}{R})V_c - \frac{1}{sL}V_f + g_m V_i = 0 \quad (1)$$

Node equation at V_f : $\frac{-1}{sL}V_c + (\frac{1}{sL} + sC_2)V_f = 0 \quad (2)$

$$|j\omega C_\mu| \ll g_m$$

Note that

$$V_f = V_f(s)$$

$$V_c = V_c(s)$$

$$V_\pi = V_\pi(s)$$

$$V_i = V_i(s)$$

Open Loop Analysis - cont.

Rearranging (1) and (2):

$$\left(sC_1 + \frac{1}{sL} + \frac{1}{R}\right)V_c - \frac{1}{sL}V_f = -g_m V_i \quad (3)$$

$$-\frac{1}{sL}V_c + \left(\frac{1}{sL} + sC_2\right)V_f = 0 \quad (4)$$

from previous slide

$$(sC_1 + \frac{1}{sL} + \frac{1}{R})V_c - \frac{1}{sL}V_f + g_m V_i = 0 \quad (1)$$

$$-\frac{1}{sL}V_c + \left(\frac{1}{sL} + sC_2\right)V_f = 0 \quad (2)$$

Eq. (1) $- g_m V_i$
 Eq. (2)

Further rearrangement of (3) and (4):

$$\left(\frac{s^2LC_1 + 1}{sL} + \frac{1}{R}\right)V_c - \frac{1}{sL}V_f = -g_m V_i \quad (5)$$

$$-\frac{1}{sL}V_c + \left(\frac{s^2LC_2 + 1}{sL}\right)V_f = 0 \quad (6)$$

Open Loop Analysis - cont.

from previous slide

$$\left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) V_c - \frac{1}{sL} V_f = -g_m V_i \quad (5)$$

Prepare to add the two equations:

$$-\frac{1}{sL} V_c + \left(\frac{s^2 LC_2 + 1}{sL} \right) V_f = 0 \quad (6)$$

$$\frac{1}{sL} \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) V_c - \left(\frac{1}{sL} \right)^2 V_f = \frac{-g_m}{sL} V_i$$

*Eq (5)** $\frac{1}{sL}$

$$-\frac{1}{sL} \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) V_c + \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) \left(\frac{s^2 LC_2 + 1}{sL} \right) V_f = 0$$

*Eq (6)** $\left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right)$

Adding (to eliminate V_c terms):

$$\left(-\left(\frac{1}{sL} \right)^2 + \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) \left(\frac{s^2 LC_2 + 1}{sL} \right) \right) V_f = \frac{-g_m}{sL} V_i \quad (7)$$

Open Loop Analysis – cont.

From previous slide

$$\left(-\left(\frac{1}{sL} \right)^2 + \left(\frac{s^2 LC_1 + 1}{sL} + \frac{1}{R} \right) \left(\frac{s^2 LC_2 + 1}{sL} \right) \right) V_f = \frac{-g_m}{sL} V_i \quad (7)$$

Multiply (7) by $(sL)^2$:

$$\left(-1 + \left(s^2 LC_1 + 1 + \frac{sL}{R} \right) \left(s^2 LC_2 + 1 \right) \right) V_f = -g_m sL V_i$$

Expand and collect terms according to s^n :

$$\left(-1 + s^4 C_1 C_2 L^2 + s^2 (LC_1 + LC_2) + s^3 \frac{L^2 C_2}{R} + s \frac{L}{R} + 1 \right) V_f = -g_m sL V_i \quad (8)$$

Open Loop Analysis - cont.

From previous slide

$$\left(-\cancel{1} + s^4 C_1 C_2 L^2 + s^2 (LC_1 + LC_2) + \frac{s^3 L^2 C_2}{R} + \frac{s L}{R} + \cancel{1} \right) V_f = -g_m s L V_i \quad (8)$$

Cancelling (-1 by 1) in (8) and dividing by sL :

$$\left(s^3 C_1 C_2 L + s (C_1 + C_2) + \frac{s^2 L C_2}{R} + \frac{1}{R} \right) V_f = -g_m V_i$$

Multiply by R :

$$\left(s^3 R C_1 C_2 L + s R (C_1 + C_2) + s^2 L C_2 + 1 \right) V_f = -g_m R V_i \quad (9)$$

Open Loop Analysis - cont.

From previous slide

$$\left(s^3 R C_1 C_2 L + s R (C_1 + C_2) + s^2 L C_2 + 1 \right) V_f = -g_m R V_i \quad (9)$$

Divide (9) by RC_1C_2L :

$$\left(s^3 + s \frac{(C_1 + C_2)}{C_1 C_2 L} + s^2 \frac{1}{R C_1} + \frac{1}{R C_1 C_2 L} \right) V_f = \frac{-g_m R}{R C_1 C_2 L} V_i$$

The loop-gain transfer function:

$$\frac{V_f}{V_i} = A(s) = \frac{\frac{-g_m}{C_1 C_2 L}}{s^3 + s^2 \frac{1}{R C_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{R C_1 C_2 L}} = \frac{K N(s)}{D(s)} \quad (10)$$

Closed Loop Analysis

The closed loop equation:

$$A_{cl}(s) = \frac{A(s)}{1 - A(s)} = \frac{K N(s)}{D(s) - K N(s)} = \frac{K N(s)}{D'(s)}$$

$$\frac{V_f}{V_i} = A(s) = \frac{\frac{-g_m}{C_1 C_2 L}}{s^3 + s^2 \frac{1}{R C_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{R C_1 C_2 L}} = \frac{K N(s)}{D(s)} \quad (10)$$

where:

$$A(s) = \frac{K N(s)}{D(s)} \quad K = \frac{-g_m}{C_1 C_2 L} \quad N(s) = 1$$

$$D(s) = s^3 + s^2 \frac{1}{R C_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{R C_1 C_2 L} \quad (11)$$

then:

$$D'(s) = D(s) - \frac{-g_m}{C_1 C_2 L} = s^3 + s^2 \frac{1}{R C_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1 + g_m R}{R C_1 C_2 L} \quad (12)$$

Closed Loop Analysis - cont.


We know that the open loop system $A(s)$ is stable. It has poles in the left half plane, since it is a passive RLC circuit. We also know that it has 3 poles. One is negative-real, the other 2 can be negative-real or LHP complex conjugates.

$$D(s) = s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{RC_1 C_2 L} \quad (11)$$


So, let's do a rough sketch of the root locus for a feedback system with a 3 pole $A(s)$.

Root Locus Characteristic

Open loop
poles somewhere
in here

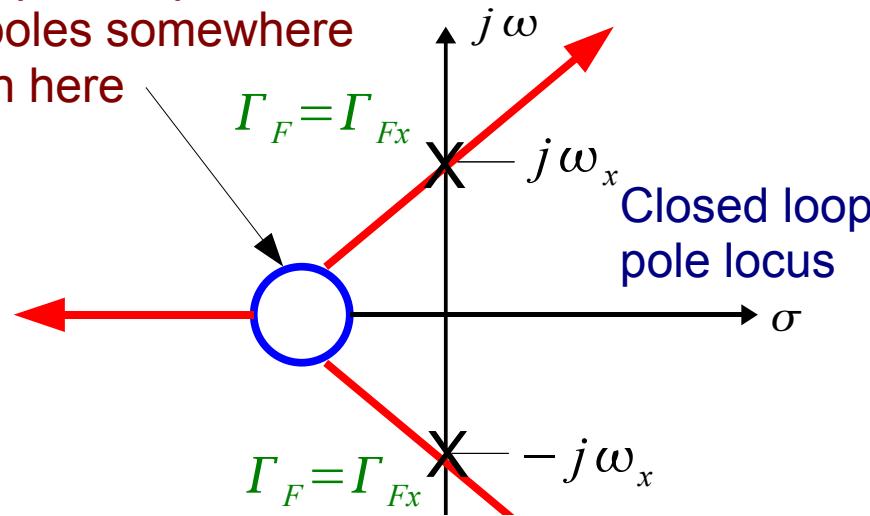

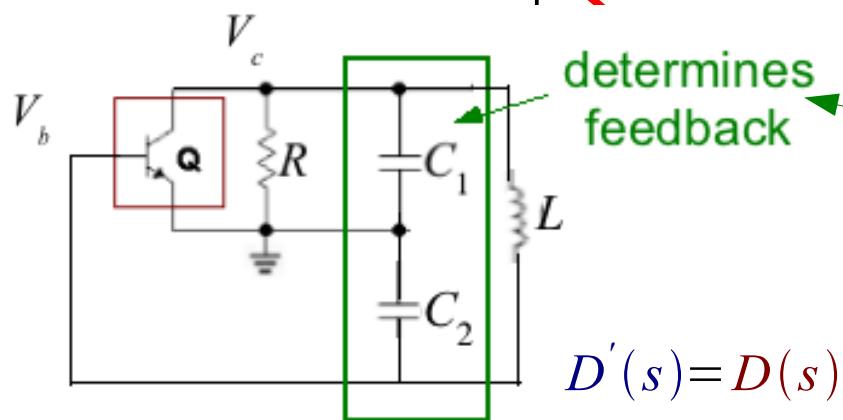- The loop will become unstable for any value of $\Gamma_F > \Gamma_{Fx}$.
- Rather than sketch the root locus in more exacting detail – it has served its purpose by verifying that oscillation is possible.
- Let's solve for the required Γ_{Fx} .



determines
feedback

$$D(s) = s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1}{RC_1 C_2 L} \quad (11)$$

$$D'(s) = D(s) - K_N(s) = s^3 + s^2 \frac{1}{RC_1} + s \frac{(C_1 + C_2)}{C_1 C_2 L} + \frac{1 + g_m R}{RC_1 C_2 L} \quad (12)$$

Closed Loop Oscillation Conditions

If the closed loop system is at the stability limit, the complex conjugate are poles on $j\omega$ axis:

$$D'(s) = D(s) + K_N(s) = (s+a)(s^2 + \omega_x^2) = 0$$

Multiplying terms:

$$D'(s) = s^3 + as^2 + \omega_x^2 s + a\omega_x^2 = 0 \Rightarrow D'(j\omega) = (a\omega_x^2 - a\omega^2) + j(\omega_x^2\omega - \omega^3) = 0$$

to oscillate at $\omega = \omega_x$

Match term by term with symbolic circuit equation:

$$D'(s) = s^3 + s^2 \frac{a}{RC_1} + s \frac{\omega_x^2}{C_1 C_2 L} + \frac{a\omega_x^2}{RC_1 C_2 L}$$

$$a = \frac{1}{RC_1} \quad \omega_x^2 = \frac{(C_1 + C_2)}{C_1 C_2 L} \quad a\omega_x^2 = \frac{1 + g_m R}{RC_1 C_2 L} \quad \text{s.t.} \quad a * \omega_x^2 = a\omega_x^2$$

Closed Loop Oscillation Conditions cont.

$$a = \frac{1}{RC_1}$$

$$\omega_x^2 = \frac{C_1 + C_2}{C_1 C_2 L}$$

$$a \omega_x^2 = \frac{1 + g_m R}{RC_1 C_2 L}$$

$$a * \omega_x^2 = a \omega_x^2$$

To find the “gain” requirement for oscillation, equate $a * \omega_x^2 = a \omega_x^2$

$$\frac{\frac{1}{RC_1}}{a} \frac{\frac{C_1 + C_2}{C_1 C_2 L}}{\omega_x^2} = \frac{C_1 + C_2}{RC_1^2 C_2 L} = \frac{\frac{1 + g_m R}{RC_1 C_2 L}}{a \omega_x^2}$$

$$\frac{C_1 + C_2}{RC_1^2 C_2 L} = \frac{1 + g_m R}{RC_1 C_2 L} \Rightarrow \cancel{1} + g_m R = \frac{C_1 + C_2}{C_1} = \cancel{1} + \frac{C_2}{C_1}$$

$$g_m R = \frac{C_2}{C_1}$$

$$\omega_x = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}$$

Oscillator Design Summary

The oscillation frequency:

$$\omega_x = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}$$

The required feedback gain $\Gamma_F = g_m R$: $\Gamma_{Fx} = (g_m)_x R = \frac{C_2}{C_1}$ poles at $\pm j\omega_x$

To insure the start-up of oscillation:

$$(g_m)_x R > \frac{C_2}{C_1}$$

Comments:

1. Unfortunately we don't control "R".
2. Set C_2 & C_1 to convenient values, say $C_2 = C_1 = C$, and adjust g_m using I_C s.t. $g_m R > C_2/C_1$; then adjust "L" to maintain ω_x at the desired oscillation frequency.

Practical Colpitts Oscillator Circuit

