


Lecture 20: BJT/FET Mixers/Mixer Noise

Prof. Ali M. Niknejad

University of California, Berkeley


Copyright © 2008 by Ali M. Niknejad

A BJT Mixer

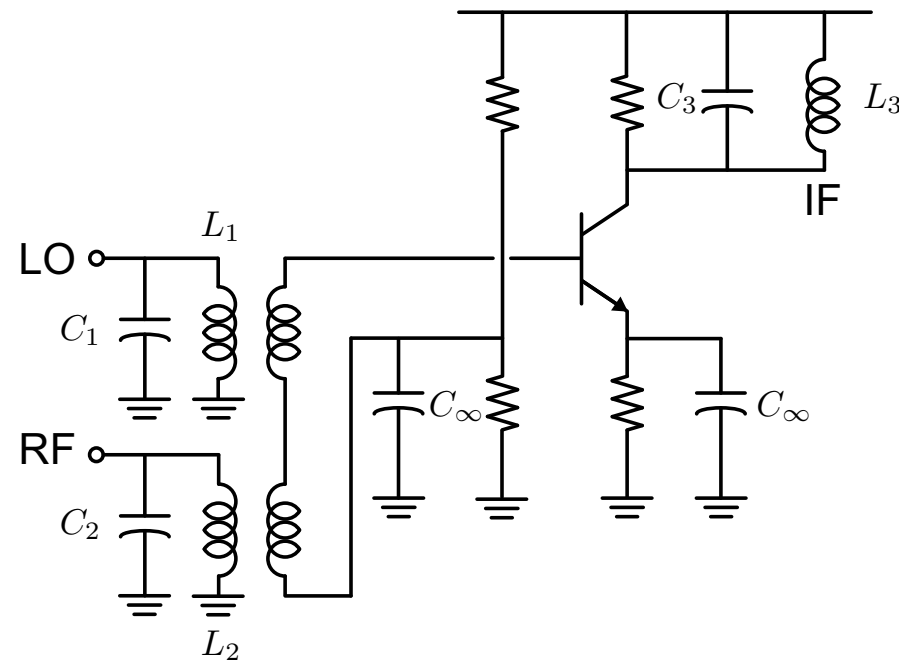

- The transformer is used to sum the LO and RF signals at the input. The winding inductance is used to form resonant tanks at the LO and RF frequencies.
- The output tank is tuned to the IF frequency.
- Large capacitors are used to form AC grounds.

AC Eq. Circuit

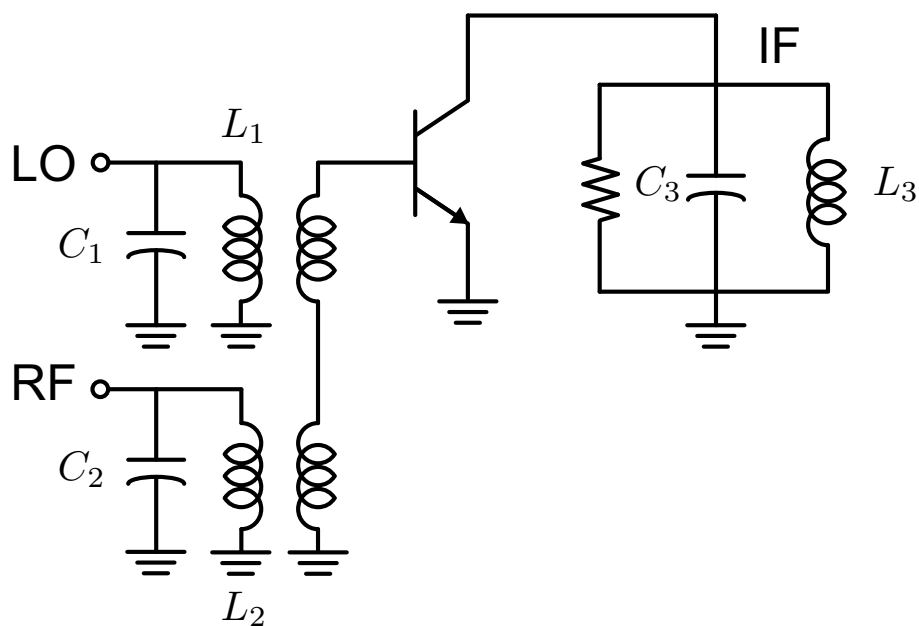

- The AC equivalent circuit is shown above.

BJT Mixer Analysis

- When we apply the LO alone, the collector current of the mixer is given by

$$I_C = I_Q \left(1 + \frac{2I_1(b)}{I_0(b)} \cos \omega t + \frac{2I_2(b)}{I_0(b)} \cos 2\omega t + \dots \right)$$

- We can therefore define a time-varying $g_m(t)$ by

$$g_m(t) = \frac{I_C(t)}{V_t} = \frac{qI_C(t)}{kT}$$

- The output current when the RF is also applied is therefore given by $i_C(t) = g_m(t)v_s$

$$i_C = \frac{qI_Q}{kT} \left(1 + \frac{2I_1(b)}{I_0(b)} \cos \omega t + \frac{2I_2(b)}{I_0(b)} \cos 2\omega t + \dots \right) \times \hat{V}_s \cos \omega_s t$$


BJT Mixer Analysis (cont)

- The output at the IF is therefore given by

$$i_C|_{\omega_{IF}} = \underbrace{\hat{V}_s \frac{qI_Q}{kT}}_{g_{mQ}} \underbrace{\frac{I_1(b)}{I_0(b)}}_{\omega_{IF}} \cos(\omega_0 - \omega_s)t$$

- The conversion gain is given by
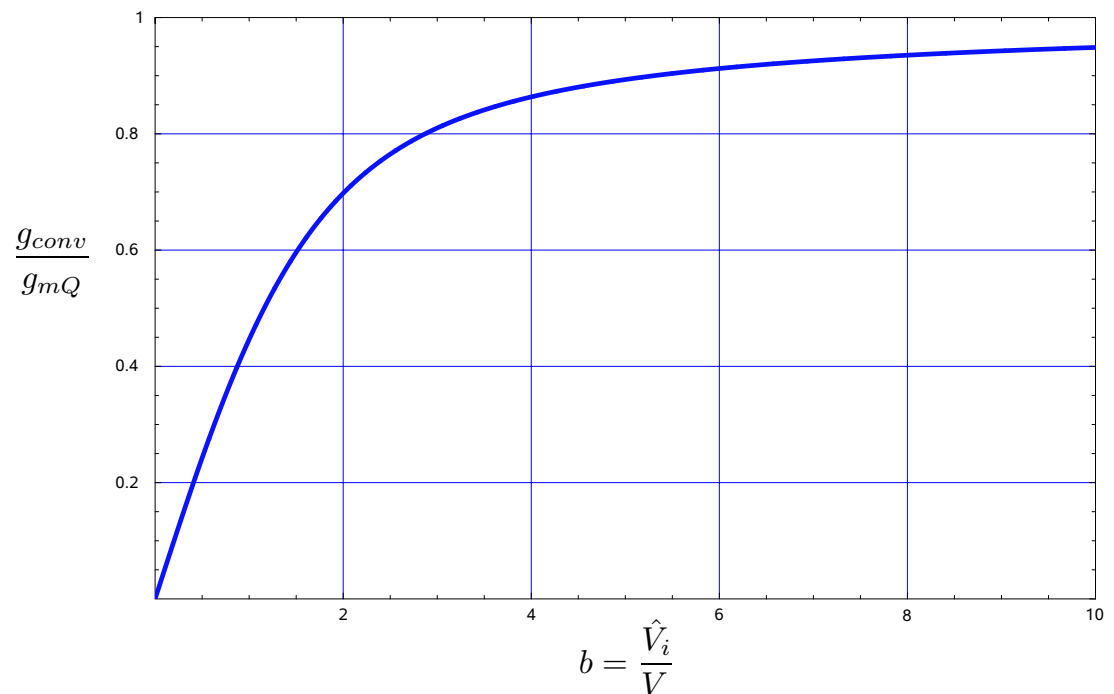
$$g_{conv} = g_{mQ} \frac{I_1(b)}{I_0(b)}$$



LO Signal Drive

- For now, let's ignore the small-signal input and determine the impedance seen by the LO drive. If we examine the collector current

$$I_C = I_Q \left(1 + \frac{2I_1(b)}{I_0(b)} \cos \omega t + \frac{2I_2(b)}{I_0(b)} \cos 2\omega t + \dots \right)$$

- The base current is simply I_C/β , and so the input impedance seen by the LO is given by

$$\begin{aligned} Z_i|_{\omega_0} &= \frac{\hat{V}_o}{i_{B,\omega_0}} = \frac{\beta \hat{V}_o}{i_{C,\omega_0}} = \frac{\beta \hat{V}_o}{I_Q \frac{2I_1(b)}{I_0(b)}} = \frac{\beta b V_t}{I_Q \frac{2I_1(b)}{I_0(b)}} \\ &= \frac{b}{2} \frac{\beta}{g_{mQ}} \frac{I_0(b)}{I_1(b)} = \frac{\beta}{G_m} \end{aligned}$$

RF Signal Drive

- The impedance seen by the RF signal source is also the base current at the ω_s components. Typically, we have a high-Q circuit at the input that resonates at RF.

$$i_B(t) = \frac{i_C(t)}{\beta}$$

$$= \frac{1}{\beta} \frac{qI_Q}{kT} \left(\hat{V}_s \cos \omega_s t + \frac{2I_1(b)}{I_0(b)} \cos(\omega_0 \pm \omega_s)t + \dots \right)$$

- The input impedance is thus the same as an amplifier

$$R_{in} = \frac{\hat{V}_s}{|\text{component in } i_B \text{ at } \omega_s|} = \beta \frac{kT}{qI_Q} = \frac{\beta}{g_{mQ}}$$

Mixer Analysis: General Approach

- If we go back to our original equations, our major assumption was that the mixer is a linear time-varying function relative to the RF input. Let's see how that comes about

$$I_C = I_S e^{v_{BE}/V_t}$$

where

$$v_{BE} = v_{in} + v_o + V_A$$

or

$$I_C = I_S e^{V_A/V_t} \times e^{b \cos \omega_0 t} \times e^{\frac{\hat{V}_s}{V_t} \cos \omega_s t}$$

- If we assume that the RF signal is weak, then we can approximate $e^x \approx 1 + x$

General Approach (cont)

- Now the output current can be expanded into

$$I_C = I_Q \left(1 + \frac{2I_1(b)}{I_0(b)} \cos \omega t + \frac{2I_2(b)}{I_0(b)} \cos 2\omega t + \dots \right) \\ \times \left(1 + \frac{\hat{V}_s}{V_t} \cos \omega_s t \right)$$

- In other words, the output can be written as

$$= \text{BIAS} + \text{LO} + \text{Conversion Products}$$

- In general we would filter the output of the mixer and so the *LO* terms can be minimized. Likewise, the RF terms are undesired and filtered from the output.

Distortion in Mixers

- Using the same formulation, we can now insert a signal with two tones

$$v_{in} = \hat{V}_{s1} \cos \omega_{s1} t + \hat{V}_{s2} \cos \omega_{s2} t$$

$$I_C = I_S e^{V_A/V_t} \times e^{b \cos \omega_0 t} \times e^{\frac{\hat{V}_{s1}}{V_t} \cos \omega_{s1} t + \frac{\hat{V}_{s2}}{V_t} \cos \omega_{s2} t}$$


- The final term can be expanded into a Taylor series

$$I_C = I_S e^{V_A/V_t} \times e^{b \cos \omega_0 t} \times$$

$$\left(1 + \frac{\hat{V}_{s1}}{V_t} \cos \omega_{s1} t + \frac{\hat{V}_{s2}}{V_t} \cos \omega_{s2} t + \left(\frac{\hat{V}_{s1}}{V_t} \cos \omega_{s1} t \right)^2 + \left(\frac{\hat{V}_{s2}}{V_t} \cos \omega_{s2} t \right)^2 + \dots \right)$$


- The square and cubic terms produce IM products as before, but now these products are frequency translated to the IF frequency

Another BJT Mixer

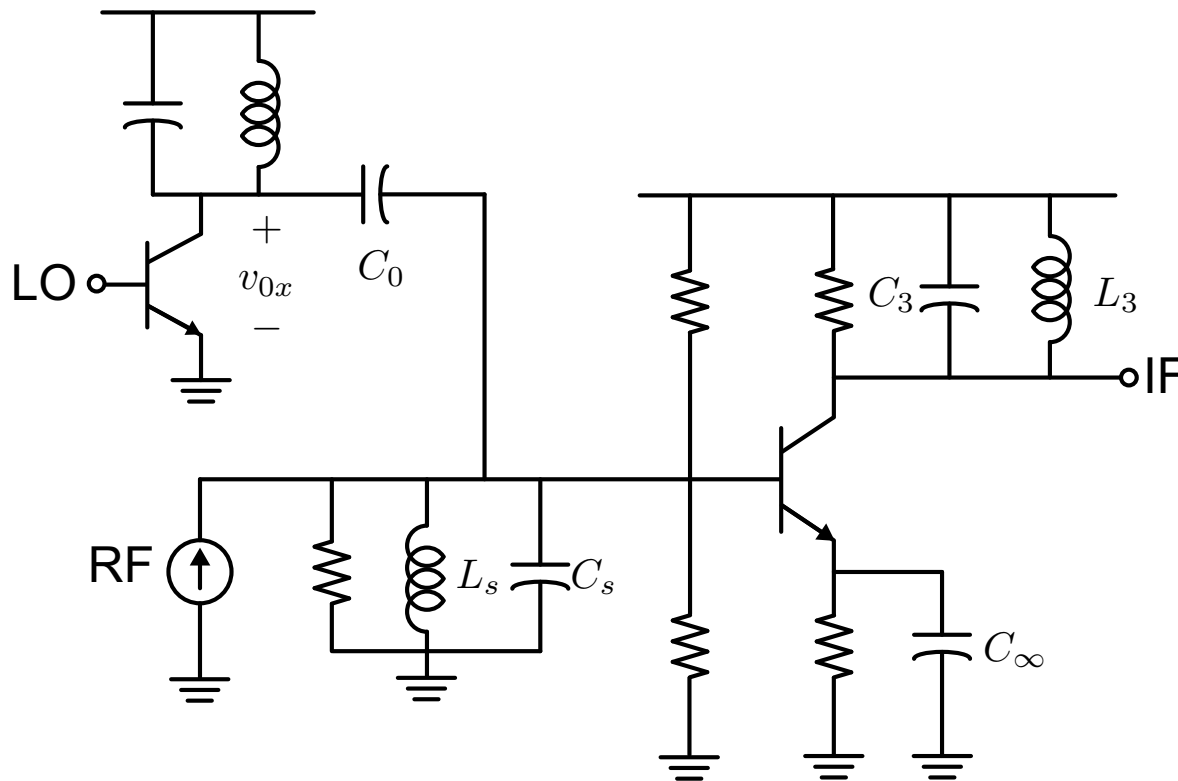

- The signal from the LO driver is capacitively coupled to the BJT mixer


LO Capacitive Divider

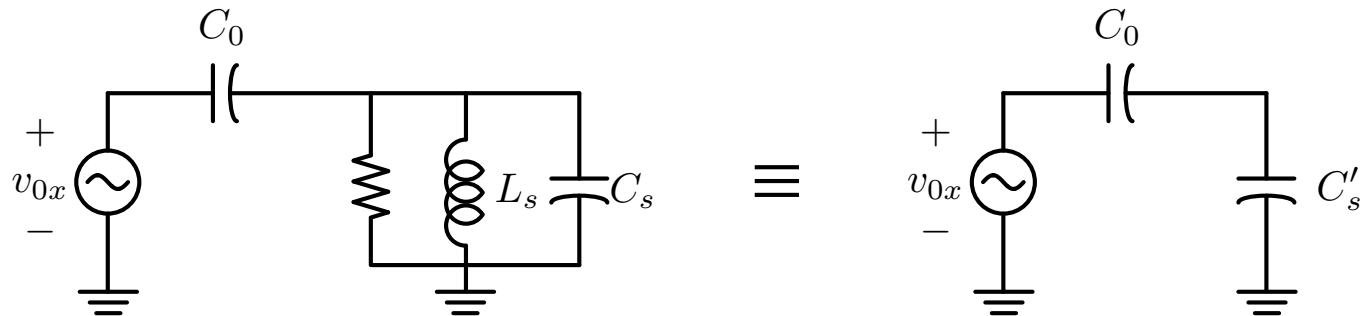

- Assume that $\omega_{LO} > \omega_{RF}$, or a high side injection
- Note beyond resonance, the input impedance of the tank appears capacitive. Thus C'_s is the effective capacitance of the tank. The equivalent circuit for the LO drive is therefore a capacitive divider

$$v_o = \frac{C_o}{C_o + C'_s} v_{ox}$$

Harmonic Mixer

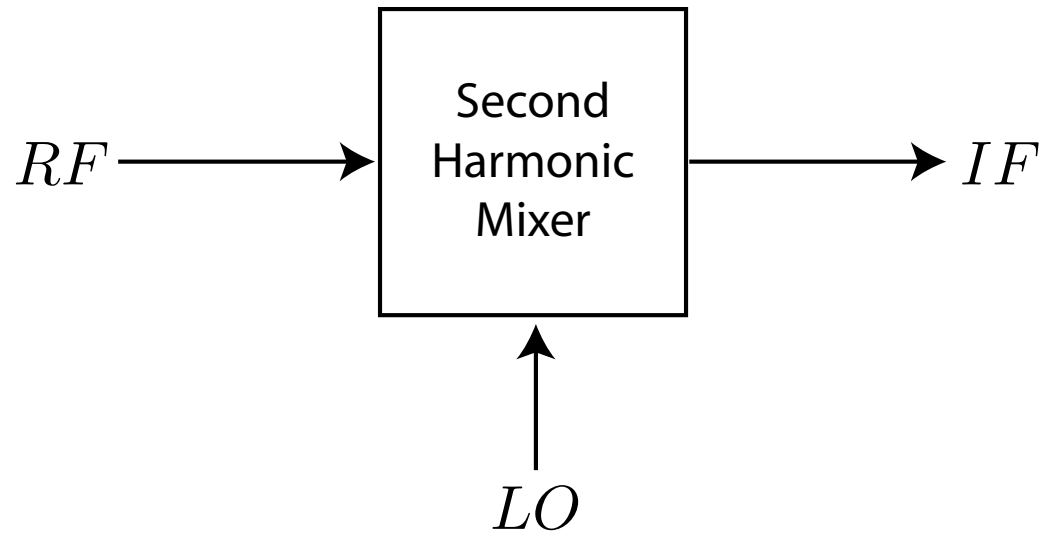

- We can use a harmonic of the LO to build a mixer.
- Example, let $LO = 500\text{MHz}$, $RF = 900\text{MHz}$, and $IF = 100\text{MHz}$.
- Note that $IF = 2LO - RF = 1000 - 900 = 100$

Harmonic Mixer Analysis

- The n th harmonic conversion transconductance is given by


$$g_{conv,n} = \frac{|\text{IF current out}|}{|\text{input signal voltage}|} = \frac{g_n}{2}$$

- For a BJT, we have

$$g_{conv,n} = g_{mQ} \frac{I_n(b)}{I_0(b)}$$

- The advantage of a harmonic mixer is the use of a lower frequency LO and the separation between LO and RF.
- The disadvantage is the lower conversion gain and higher noise.

FET Large Signal Drive

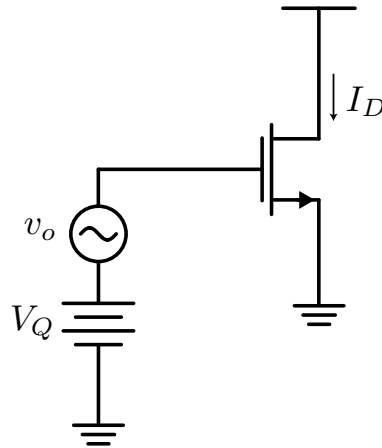


- Consider the output current of a FET driven by a large LO signal

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

- where $V_{GS} = V_A + v_{LO} = V_A + V_o \cos \omega_0 t$. Here we implicitly assume that V_o is small enough such that it does not take the device into cutoff.

FET Large Signal Drive (cont)

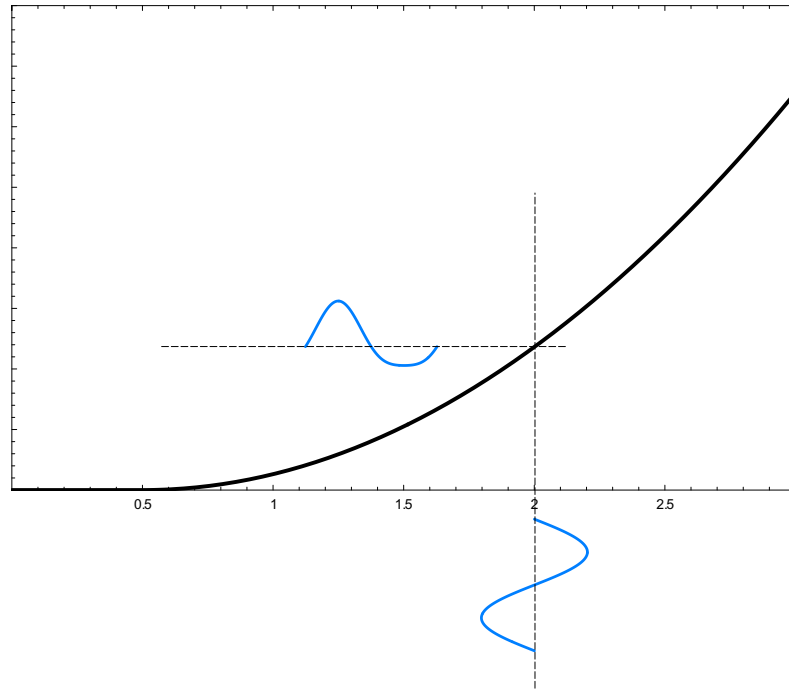

- That means that $V_A + V_0 \cos \omega_0 t > V_T$, or $V_A - V_0 > V_T$, or equivalently $V_0 < V_A - V_T$. Under such a case we expand the current

$$I_D \propto ((V_A - V_T)^2 + V_0^2 \cos^2 \omega_0 t + 2(V_A - V_T)V_0 \cos \omega_0 t)$$

FET Current Components

- The \cos^2 term can be further expanded into a DC and second harmonic term.
- Identifying the quiescent operating point

$$I_Q = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_A - V_T)^2 (1 + \lambda V_{DS})$$

$$I_D = I_{DQ} + \mu C_{ox} \frac{W}{L} \left(\underbrace{\frac{1}{4} V_0^2}_{\text{bias point shift}} + \underbrace{(V_A - V_T) V_o \cos \omega_0 t}_{\text{LO modulation}} + \underbrace{\frac{V_0^2}{4} \cos(2\omega_0 t)}_{\text{LO 2nd harmonic}} \right) (1 + \lambda V_{DS})$$

FET Time-Varying Transconductance

- The transconductance of a FET is given by (assuming strong inversion operation)

$$g(t) = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)(1 + \lambda V_{DS})$$


$$V_{GS}(t) = V_A + V_0 \cos \omega_0 t$$

$$g(t) = \mu C_{ox} \frac{W}{L} (V_A - V_T + V_0 \cos \omega_0 t)(1 + \lambda V_{DS})$$

$$g(t) = g_{mQ} \left(1 + \frac{V_0}{V_A - V_T} \cos \omega_0 t \right) (1 + \lambda V_{DS})$$

- This is an almost ideal mixer in that there is no harmonic components in the transconductance.

MOS Mixer

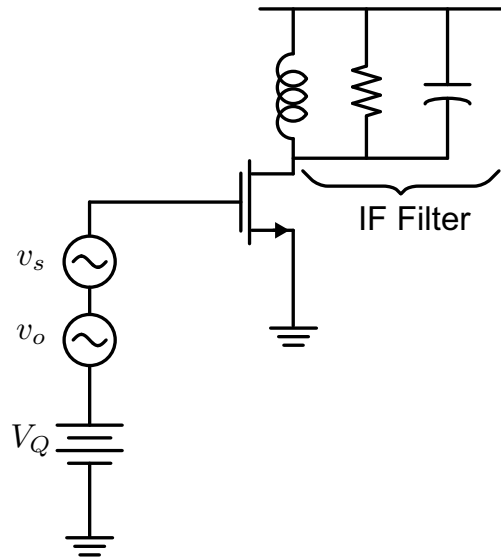

- We see that we can build a mixer by simply injecting an $LO + RF$ signal at the gate of the FET (ignore output resistance)

$$i_0 = g(t)v_s = g_{mQ} \left(1 + \frac{V_0}{V_A - V_T} \cos \omega_0 t \right) V_s \cos \omega_s t$$

$$i_0|_{IF} = \frac{g_{mQ}}{2} \frac{V_0}{V_A - V_T} \cos(\omega_0 \pm \omega_s)t V_s$$

$$g_c = \frac{i_0|_{IF}}{V_s} = \frac{g_{mQ}}{2} \frac{V_0}{V_A - V_T}$$


MOS Mixer Summary

- But $g_{mQ} = \mu C_{ox} \frac{W}{L} (V_A - V_T)$

$$g_c = \frac{\mu C_{ox}}{2} \frac{W}{L} V_0$$


- which means that g_c is independent of bias V_A . The gain is controlled by the LO amplitude V_0 and by the device aspect ratio.
- Keep in mind, though, that the transistor must remain in forward active region in the entire cycle for the above assumptions to hold.
- In practice, a real FET is not square law and the above analysis should be verified with extensive simulation. Sub-threshold conduction and output conductance complicate the picture.

“Dual Gate” Mixer

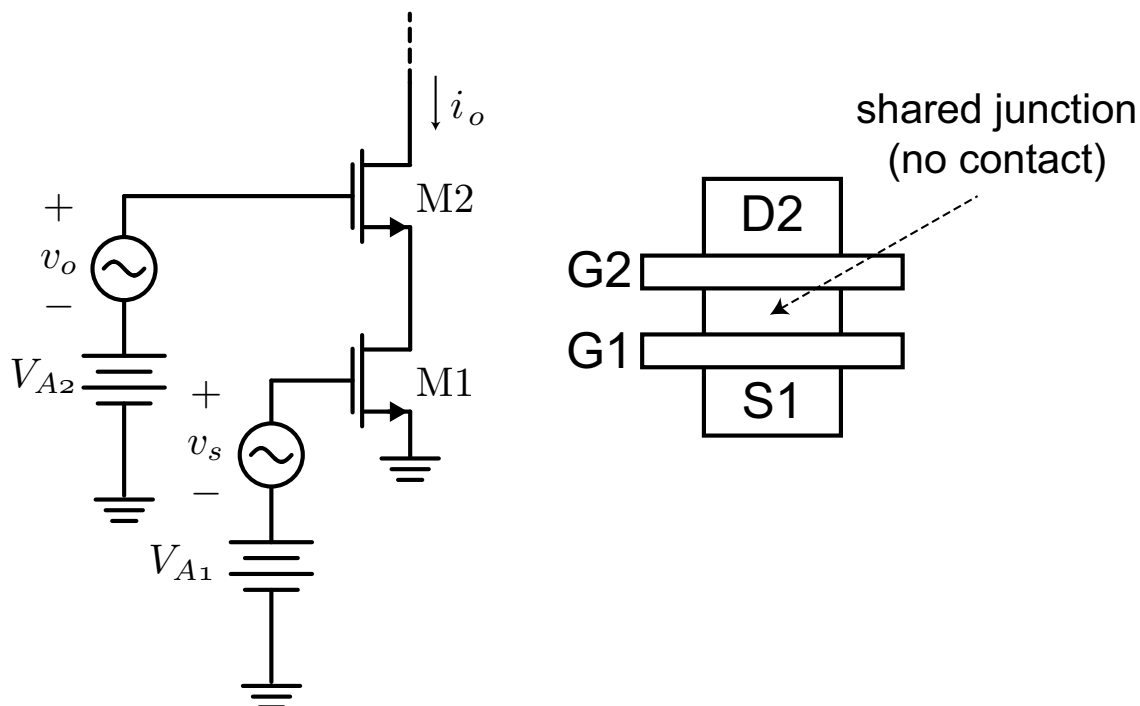

- The “dual gate” mixer, or more commonly a cascode amplifier, can be turned into a mixer by applying the LO at the gate of $M2$ and the RF signal at the gate of $M1$. Using two transistors in place of one transistor results in area savings since the signals do not need to be combined with a transformer or capacitively .

Dual Gate Mixer Operation

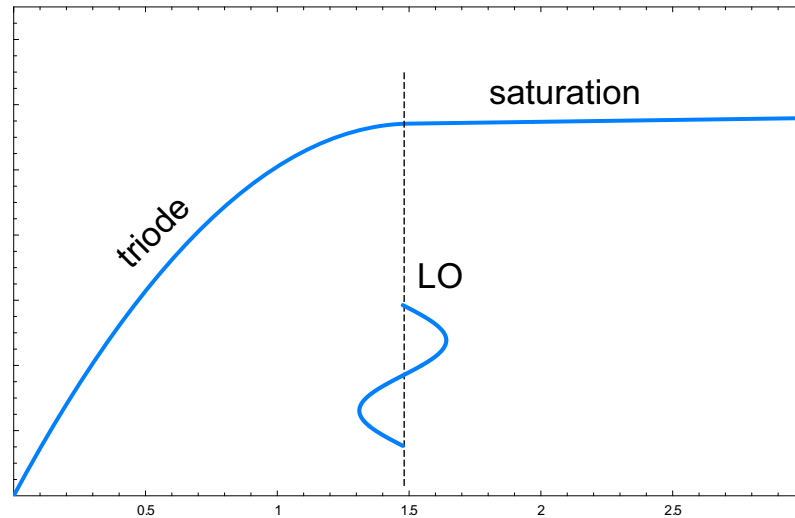


- Without the LO signal, this is simply a cascode amplifier. But the LO signal is large enough to push $M1$ into triode during part of the operating cycle.
- The transconductance of $M1$ is therefore modulated periodically

$$g_m|_{\text{sat}} = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

$$g_m|_{\text{triode}} = \mu C_{ox} \frac{W}{L} V_{DS}$$

Dual Gate Waveforms

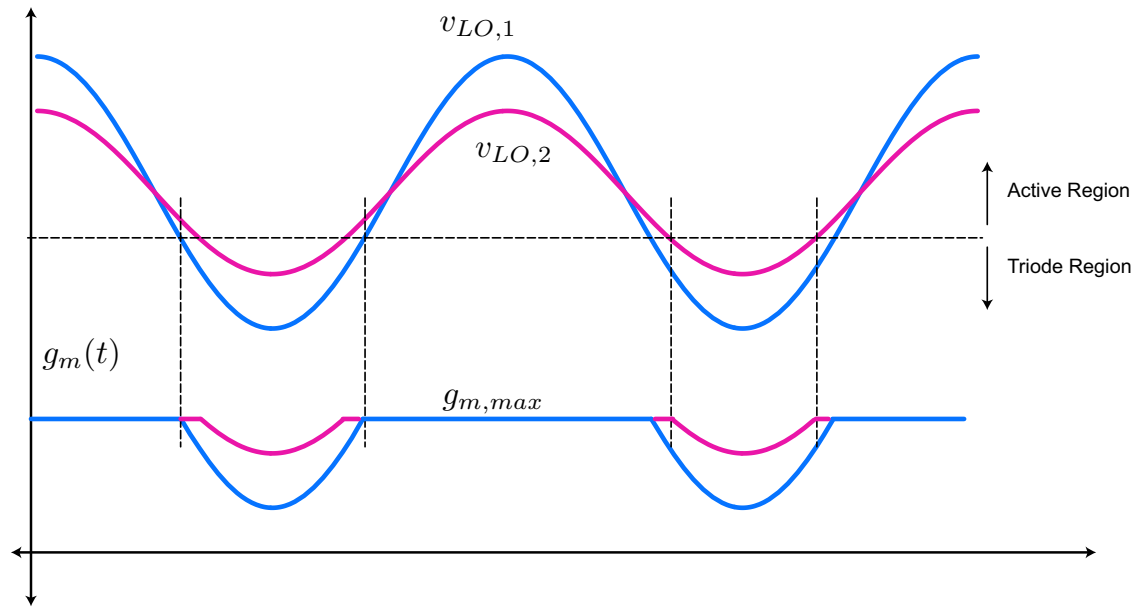

- V_{GS2} is roughly constant since $M1$ acts like a current source.

$$V_{D1} = v_{LO} - V_{GS2} = V_{A2} + V_0 \cos \omega_0 t - V_{GS2}$$

$$g(t) = \begin{cases} \mu C_{ox} \frac{W}{L} (V_{GS1} - V_T) & V_{D1} > V_{GS} - V_T \\ \mu C_{ox} (V_{A2} - V_{GS2} - |V_0 \cos \omega_0 t|) & V_{D1} < V_{GS} - V_T \end{cases}$$

Realistic Waveforms

- A more sophisticated analysis would take sub-threshold operation into account and the resulting $g(t)$ curve would be smoother. A Fourier decomposition of the waveform would yield the conversion gain coefficient as the first harmonic amplitude.

Mixer Analysis: Time Domain

- A generic mixer operates with a periodic transfer function $h(t + T) = h(t)$, where $T = 1/\omega_0$, or T is the LO period. We can thus expand $h(t)$ into a Fourier series

$$y(t) = h(t)x(t) = \sum_{-\infty}^{\infty} c_n e^{j\omega_0 n t} x(t)$$

- For a sinusoidal input, $x(t) = A(t) \cos \omega_1 t$, we have

$$y(t) = \sum_{-\infty}^{\infty} \frac{c_n}{2} A(t) \left(e^{j(\omega_1 + \omega_0 n)t} + e^{j(-\omega_1 + \omega_0 n)t} \right)$$

- Since $h(t)$ is a real function, the coefficients $c_{-k} = c_k^*$ are even. That means that we can pair positive and negative frequency components.

Time Domain Analysis (cont)

- Take c_1 and c_{-1} as an example

$$\begin{aligned} &= c_1 \frac{e^{j(\omega_1 + \omega_0)t} + e^{j(-\omega_1 + \omega_0)t}}{2} A(t) + c_1 \frac{e^{j(\omega_1 - \omega_0)t} + e^{j(-\omega_1 - \omega_0)t}}{2} A(t) + \dots \\ &= c_1 A(t) \cos(\omega_1 + \omega_0)t + c_1 A(t) \cos(\omega_1 - \omega_0)t + \dots \end{aligned}$$

- Summing together all the components, we have

$$y(t) = \sum_{-\infty}^{\infty} c_n \cos(\omega_1 + n\omega_0)t$$

- Unlike a perfect multiplier, we get an infinite number of frequency translations up and down by harmonics of ω_0 .

Frequency Domain Analysis


- Since multiplication in time, $y(t) = h(t)x(t)$, is convolution in the frequency domain, we have

$$Y(f) = H(f) * X(f)$$

- The transfer function $H(f) = \sum_{-\infty}^{\infty} c_n \delta(f - nf_0)$ has a discrete spectrum. So the output is given by

$$\begin{aligned} Y(f) &= \int_{-\infty}^{\infty} \sum_{-\infty}^{\infty} c_n \delta(\sigma - nf_0) X(f - \sigma) d\sigma \\ &= \sum_{-\infty}^{\infty} c_n \int_{-\infty}^{\infty} \delta(\sigma - nf_0) X(f - \sigma) d\sigma \end{aligned}$$

Frequency Domain (cont)

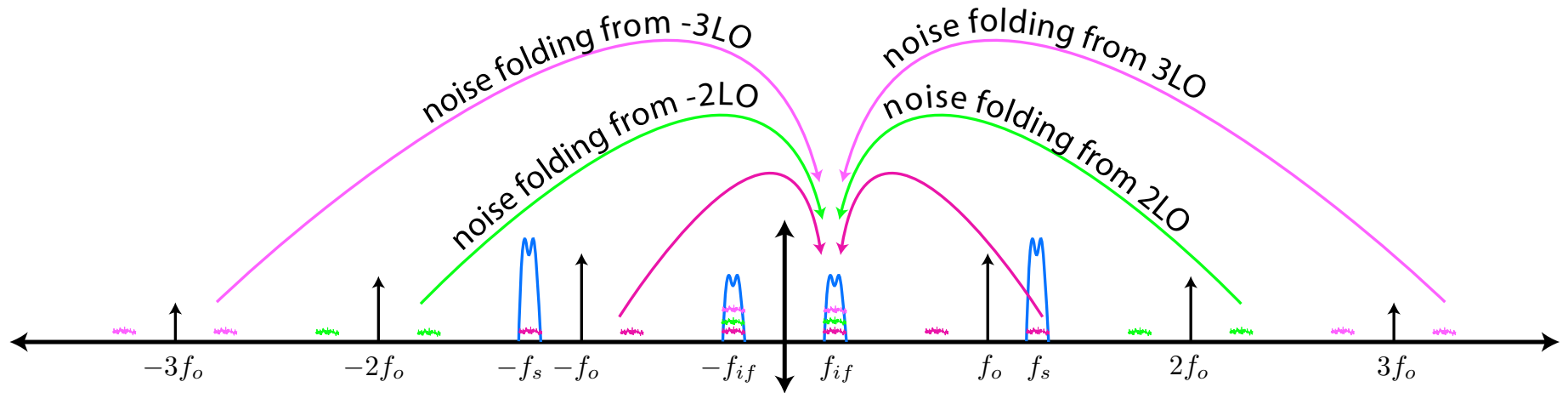

- By the frequency sifting property of the $\delta(f - \sigma)$ function, we have



$$Y(f) = \sum_{n=-\infty}^{\infty} c_n X(f - n f_0)$$

- Thus, the input spectrum is shifted by all harmonics of the LO up and down in frequency.


Noise/Image Problem

- Previously we examined the “image” problem. Any signal energy a distance of IF from the LO gets downconverted in a perfect multiplier. But now we see that for a general mixer, any signal energy with an IF of any harmonic of the LO will be downconverted !
- These other images are easy to reject because they are distant from the desired signal and a image reject filter will be able to attenuate them significantly.
- The noise power, though, in all image bands will fold onto the IF frequency. Note that the noise is generated by the mixer source resistance itself and has a white spectrum. Even though the noise of the antenna is filtered, new noise is generated by the filter itself!

Current Commutating Mixers

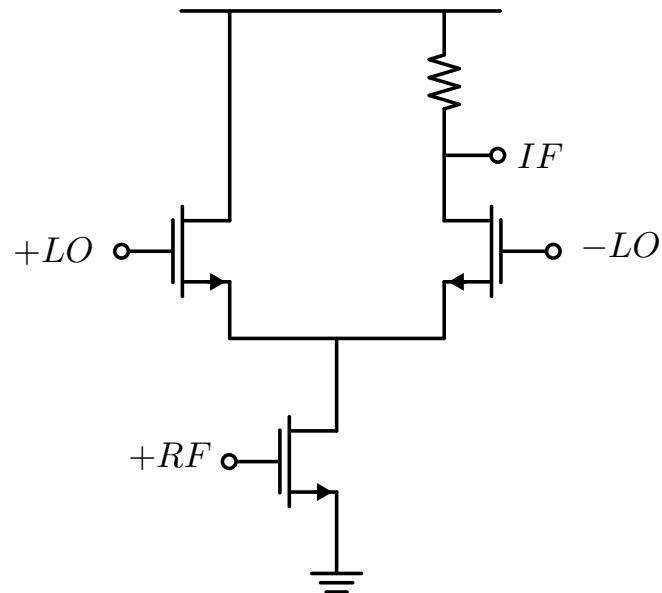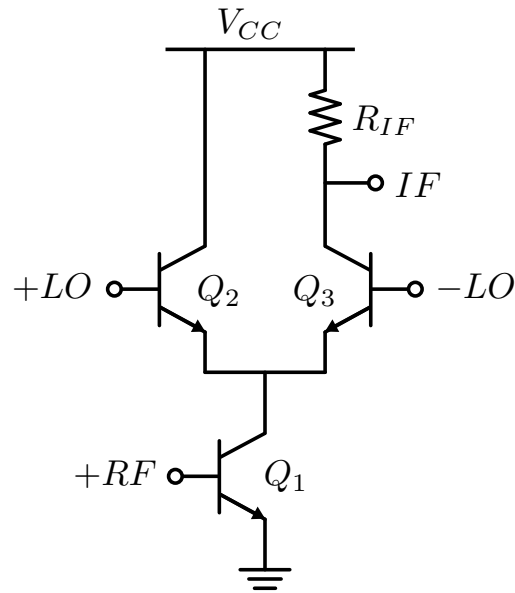


Current Commutating Mixer Model

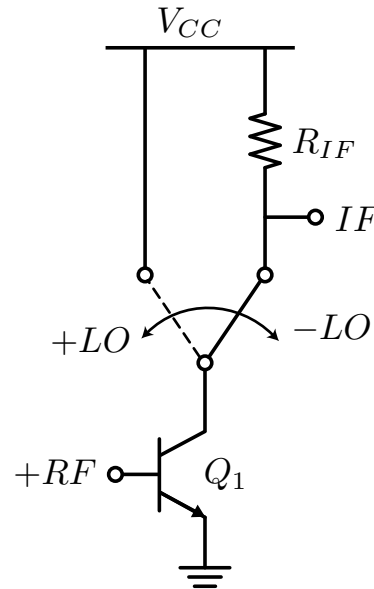

- If we model the circuit with ideal elements, we see that the current I_{C1} is either switched to the output or to supply at the rate of the LO signal.
- When the LO signal is positive, we have a cascode dumping its current into the supply. When the LO signal is negative, though, we have a cascode amplifier driving the output.

Conversion Gain

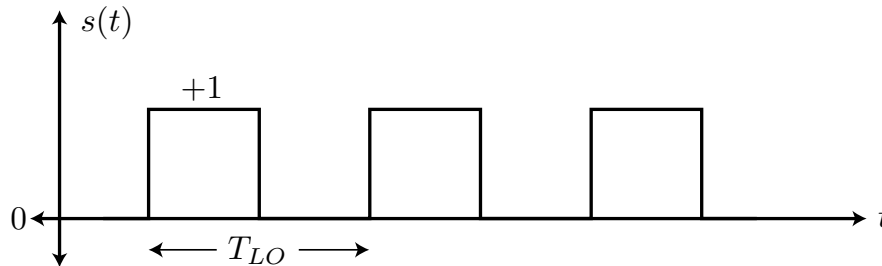

- We can now see that the output current is given by a periodic time varying transconductance

$$i_o = g_m(t)v_s = g_{mQ}s(t)v_s$$

- where $s(t)$ is a square pulse waveform (ideally) switching between 1 and 0 at the rate of the LO signal. A Fourier decomposition yields

$$i_o = g_{mQ}v_s \left(0.5 + \frac{2}{\pi} \cos \omega_0 t - \frac{2}{\pi} \frac{1}{3} \cos 3\omega_0 t + \dots \right)$$


Conversion Gain (cont)

- So the RF signal v_s is amplified (feed-thru) by the DC term and mixed by all the harmonics

$$\frac{i_o}{V_s} = \frac{g_m Q}{2} \left(\frac{1}{2} \cos \omega_s t + \frac{2}{\pi} \cos(\omega_0 \pm \omega_s) t - \frac{2}{3\pi} \cos(3\omega_0 \pm \omega_s) t + \dots \right)$$

- The primary conversion gain is $g_c = \frac{1}{\pi} g_m Q$.
- Since the role of $Q1$ (or $M1$) is to simply create an RF current, it can be degenerated to improve the linearity of the mixer. Inductance degeneration can be employed to also achieve an impedance match.
- MOS version acts in a similar way but the conversion gain is lower (lower g_m) and it requires a larger LO drive.


Differential Output

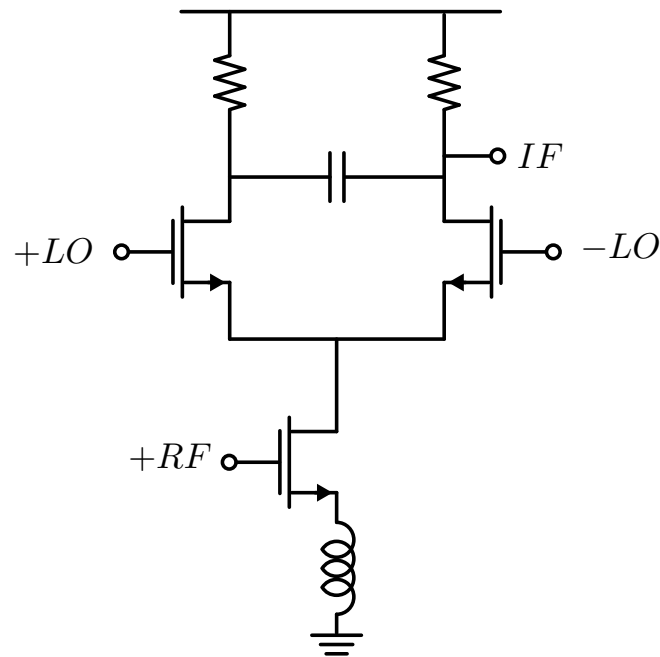

- This block is commonly known as the Gilbert Cell
- If we take the output signal differentially, then the output current is given by

$$i_o = g_m(t)v_s = g_{mQ}s_2(t)v_s$$

Differential Output Gain

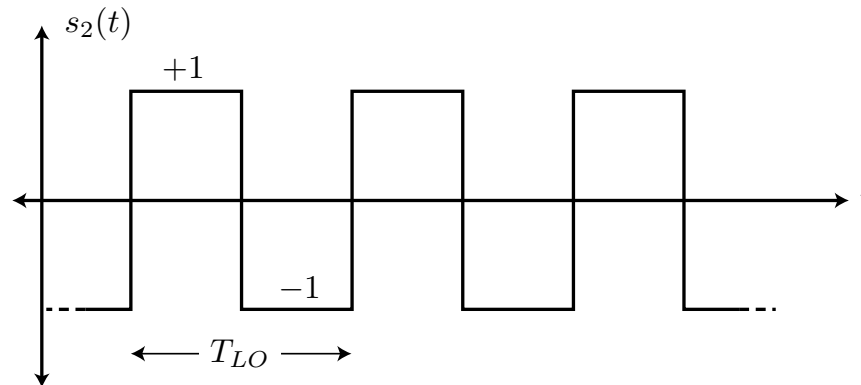

- The pulse waveform $s_2(t)$ now switches between ± 1 , and thus has a zero DC value

$$s_2(t) = \frac{4}{\pi} \cos \omega_0 t - \frac{1}{3} \frac{4}{\pi} \cos 3\omega_0 t + \dots$$

- The lack of the DC term means that there is ideally no RF feedthrough to the IF port. The conversion gain is doubled since we take a differential output $g_c/g_{mQ} = \frac{2}{\pi}$