



Assuming ideal OpAmp (No currents in, and voltage at both input ports are the same):

$$I = \frac{V_{in} - V_o}{Z_c} = \frac{V_o - V_{in}}{R_2} = \frac{V_{in}}{R_1}$$

Using the last two terms:

$$V_o = V_{in} \frac{R_1 + R_2}{R_1}$$

Combining this with the first term:

$$I = \frac{V_{in} - V_{in} \left(\frac{R_1 + R_2}{R_1} \right)}{Z_c} = -V_{in} \left(\frac{R_2}{R_1 * Z_c} \right)$$

Thus:

$$\frac{V_{in}}{I} = Z_{in} = -\frac{R_1 * Z_c}{R_2}$$

So, when $R_1 = R_2$,

$$Z_{in} = -Z_c$$