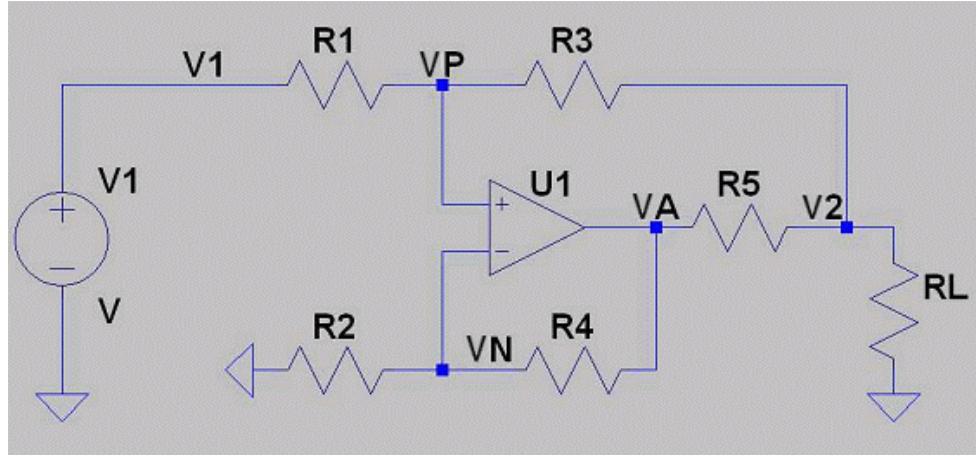


Dimensioning of an OP Current Source



$$\frac{V_A - V_N}{R_4} - \frac{V_N}{R_2} = 0 \quad (1)$$

$$\frac{V_1 - V_P}{R_1} + \frac{V_2 - V_P}{R_3} = 0 \quad (2)$$

$$\frac{V_A - V_2}{R_5} + \frac{V_P - V_2}{R_3} = I_2 \quad (3)$$

$$V_A = V_N \frac{R_2 + R_4}{R_2} \quad (1a)$$

$$V_P = V_1 \frac{R_3}{R_1 + R_3} + V_2 \frac{R_1}{R_1 + R_3} \quad (2a)$$

$$V_N = V_P$$

$$V_A = V_1 \frac{R_3(R_2 + R_4)}{(R_1 + R_3)R_2} + V_2 \frac{R_1(R_2 + R_4)}{(R_1 + R_3)R_2} \quad (1a+2a)$$

$$I_2 R_3 R_5 = V_1 \left(\frac{R_3^2 (R_2 + R_4)}{(R_1 + R_3)R_2} + \frac{R_3 R_5}{R_1 + R_3} \right) + \\ V_2 \left(\frac{R_1 R_3 (R_2 + R_4)}{(R_1 + R_3)R_2} - R_3 + \frac{R_1 R_5}{R_1 + R_3} - R_5 \right) \quad (1-3)$$

Condition for Infinite Output Resistance:

$$R_1 R_3 (R_2 + R_4) - R_3 (R_1 + R_3) R_2 + R_1 R_5 R_2 - R_5 (R_1 + R_3) R_2 = 0 \quad I_2 \neq f(V_2)$$

$$R_1 R_4 = R_2 (R_3 + R_5) \quad (4)$$

Case 1: $R_l = R_2$

$$R_4 = R_3 + R_5 \quad (4a)$$

$$I_2 = V_1 \frac{R_3 + R_5}{R_l R_5} \quad (5a)$$

Case 2: $R_3 = R_4$

$$R_l = R_2 \frac{R_3 + R_5}{R_3} \quad (4b)$$

$$I_2 = V_1 \frac{R_3}{R_2 R_5} \quad (5b)$$