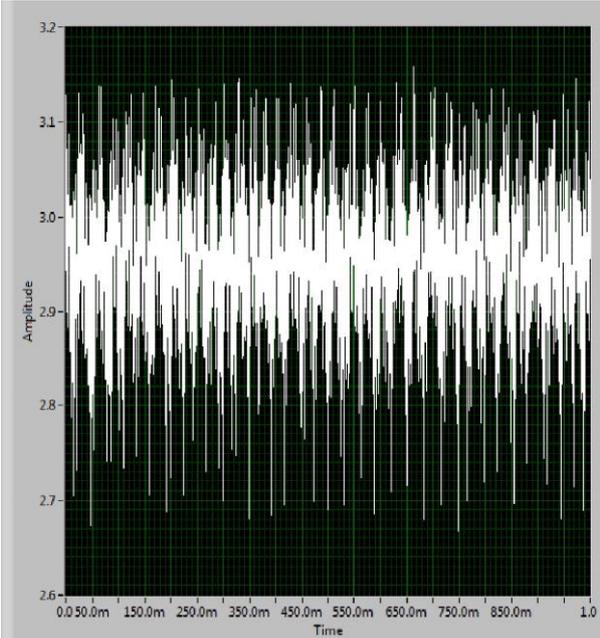


PhotoTransistor *Collector* Output with supply= 3V



with supply=0V


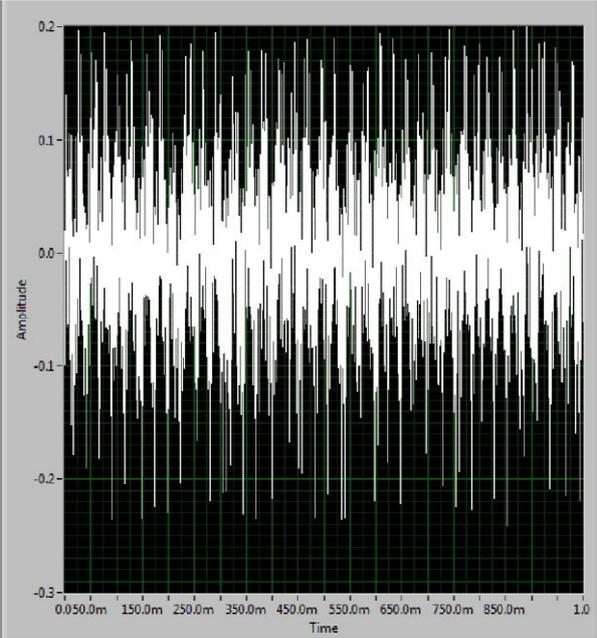


Photo Transistor *Emitter* output when supply=0V

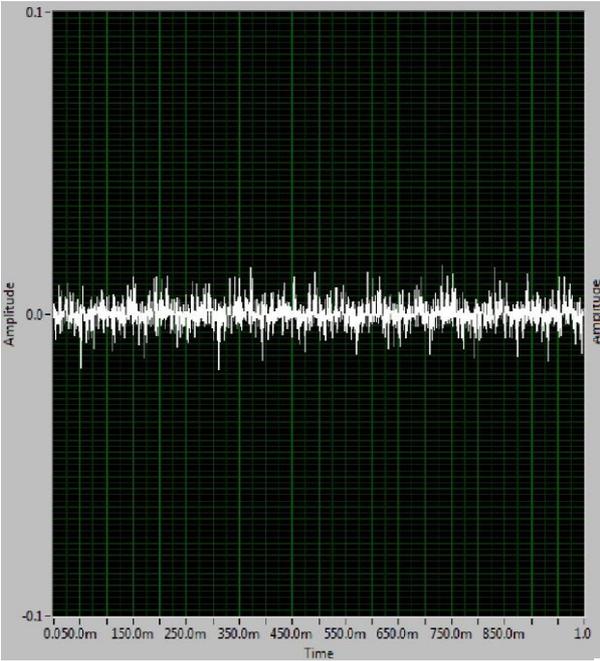

when supply(ON)=3V

