

Solving for I_A :

$$= \frac{635202000}{(12)(1690)(-300) - (12)(-1000)(-1000) - (12)(1690)(1690)} = 0.0351 \text{ A} = 35.1 \text{ mA}$$

12	-300	-1000	1690
0	1690	-1000	0
0	-1000	0	1690

Solving for I_B :

$$= \frac{635202000}{(12)(-300)(-1000) - (-300)(12)(1690) - (12)(-1000)(-1000)} = 0.0162 \text{ A} = 16.2 \text{ mA}$$

630	12	-300	0
-330	0	-1000	1690
-300	1690	0	0

Solving for I_C :

$$= \frac{635202000}{(12)(-330)(-1000) - (-330)(12)(1690) - (12)(-1000)(-1000)} = 0.0158 \text{ A} = 15.8 \text{ mA}$$

630	-330	12	0
-330	1690	0	0
-300	-1000	0	1690

The current in R_1 is the difference between I_A and I_B :

$$I_1 = (I_A - I_B) = 35.1 \text{ mA} - 16.2 \text{ mA} = 18.9 \text{ mA}$$

The current in R_2 is the difference between I_A and I_C :

$$I_2 = (I_A - I_C) = 35.1 \text{ mA} - 15.8 \text{ mA} = 19.3 \text{ mA}$$

The current in R_3 is I_B :

$$I_3 = I_B = 16.2 \text{ mA}$$

The current in R_4 is I_C :

$$I_4 = I_C = 15.8 \text{ mA}$$

The current in R_L is the difference between I_B and I_C :

$$I_L = (I_B - I_C) = 16.2 \text{ mA} - 15.8 \text{ mA} = 0.4 \text{ mA}$$

Use a calculator to verify the loop currents in this example.

Use Multisim file E09-09 to verify the calculated results in this example and to confirm your calculations for the related problem.

Related Problem



While the circuit is primarily a three-loop circuit using reactive components, it is introduced here to illustrate the solution. A loaded resistive bridged-T is shown in Figure 9-13. The coefficients for simultaneous equations will often be in $k\Omega$ (or even $M\Omega$) so the coefficients for simultaneous equations will be quite large if they are shown explicitly in solving equations. To simplify solving equations with $k\Omega$, it is common practice to drop the $k\Omega$ in the equations that the unit for current is the mA if the voltage is volts. The following bridged-T circuit illustrates this idea.