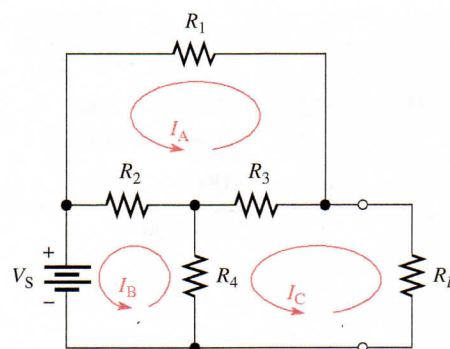



► FIGURE 9-13



## EXAMPLE 9-10

Figure 9-14 shows a bridged-T circuit with three loops. Set up the standard form equations for the loop currents. Solve the equations with a calculator and find the current in each resistor.

► FIGURE 9-14

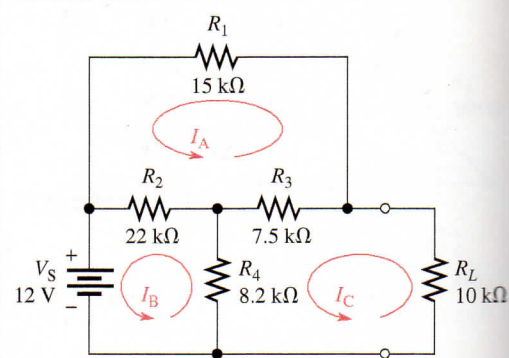

**Solution** Assign three counterclockwise loop currents ( $I_A$ ,  $I_B$ , and  $I_C$ ) as shown in Figure 9-14. Write the loop equations, but drop the k prefix from the resistances. Current will be in mA.

$$\text{Loop A: } 22(I_A - I_B) + 15I_A + 7.5(I_A - I_C) = 0$$

$$\text{Loop B: } -12 + 22(I_B - I_A) + 8.2(I_B - I_C) = 0$$

$$\text{Loop C: } 8.2(I_C - I_B) + 7.5(I_C - I_A) + 10I_C = 0$$

Rearrange the equations into standard form:

$$\text{Loop A: } 44.5I_A - 22I_B - 7.5I_C = 0$$

$$\text{Loop B: } -22I_A + 30.2I_B - 8.2I_C = 12$$

$$\text{Loop C: } -7.5I_A - 8.2I_B + 25.7I_C = 0$$

**Calculator Solution:** A calculator solution requires entry of the number of equations (3), the coefficients, and the constants. The calculator SOLVE function produces the results as shown in Figure 9-15. Because the resistors were in kΩ, the unit for the loop currents is mA. Solve for the current in each resistor. The current in  $R_1 = I_A$ .

$$I_1 = 0.512 \text{ mA}$$

► FIGURE 9-15

