 


Digital CMOS Logic Circuits


Sedra & Smith, Chapter 10



Inverter Circuit

CMOS Logic Gate Circuit

Similar structure to inverter:


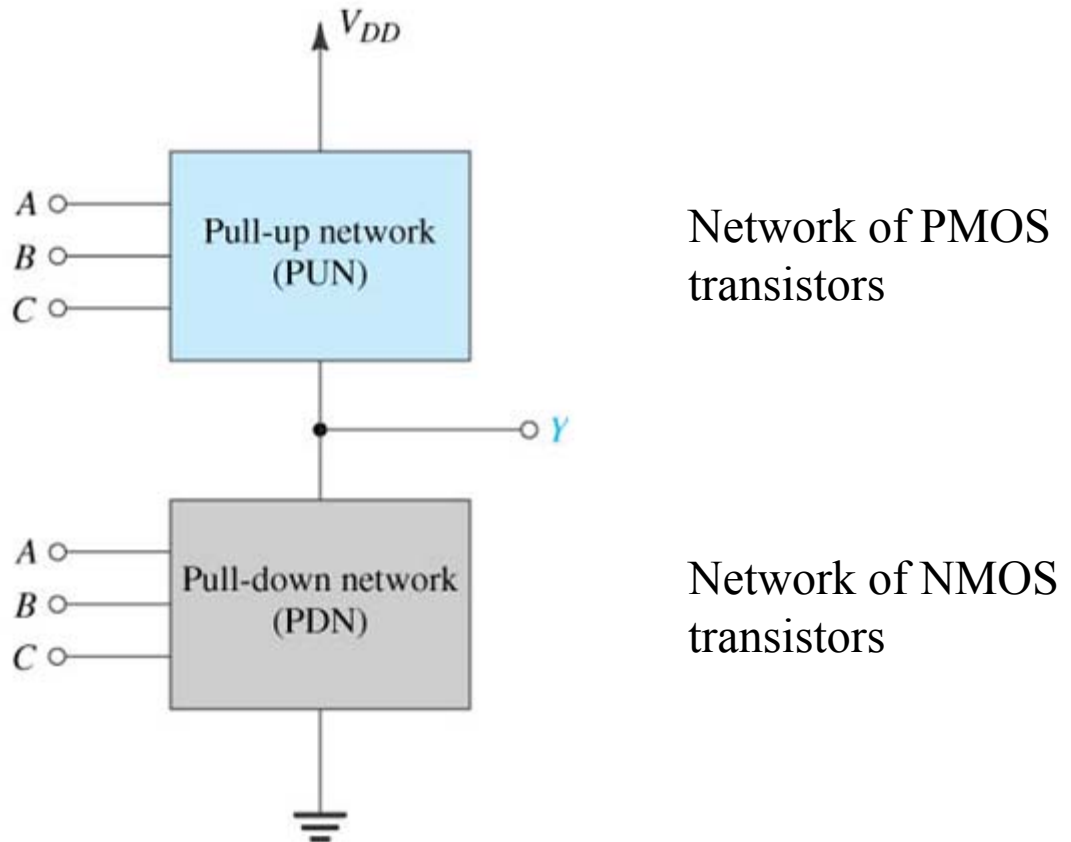


PUN & PDN Basic Structure



Parallel \rightarrow OR

Series \rightarrow AND

PUN

 
 


PDN

  

Combinations of Basic Structures


PUN

  


PDN

Alternative (Digital) Symbols

NMOS

 

PMOS

 

PMOS Active Low: Transistor is conducting (activated) when input is low.

2-input NOR


$$Y = \overline{A + B} = \bar{A}\bar{B}$$

$$Y = \bar{A}\bar{B}$$

Y is high (PUN conducting) when A **AND** B are Low.

$$\bar{Y} = A + B$$

 Y is low (PDN conducting) when A **OR** B is High.



2-input NAND


$$Y = \overline{AB} = \bar{A} + \bar{B}$$

$$Y = \bar{A} + \bar{B}$$

Y is high (PUN conducting) when A **OR** B are Low.

$$\bar{Y} = AB$$

 Y is low (PDN conducting) when A **AND** B are High.




A Complex Gate

$$Y = \overline{A(B + CD)}$$

For PUN expression must be of Y in terms of the variables complements:

By DeMorgan's Law:
 
$$Y = \overline{A(B + CD)} = \bar{A} + \overline{(B + CD)} = \bar{A} + \bar{B}\bar{C}\bar{D}$$
$$= \bar{A} + \bar{B}(\bar{C} + \bar{D})$$




A Complex Gate

$$Y = \overline{A(B + CD)}$$

For PDN expression must be of \bar{Y} in terms of the variables:

$$\bar{Y} = A(B + CD)$$

 


Complete Complex Gate

$$Y = \overline{A(B + CD)}$$



$$Y = \overline{A(B + CD)} = \bar{A} + \bar{B}(\bar{C} + \bar{D})$$

$$\bar{Y} = A(B + CD)$$

Note: Two transistors per variable.

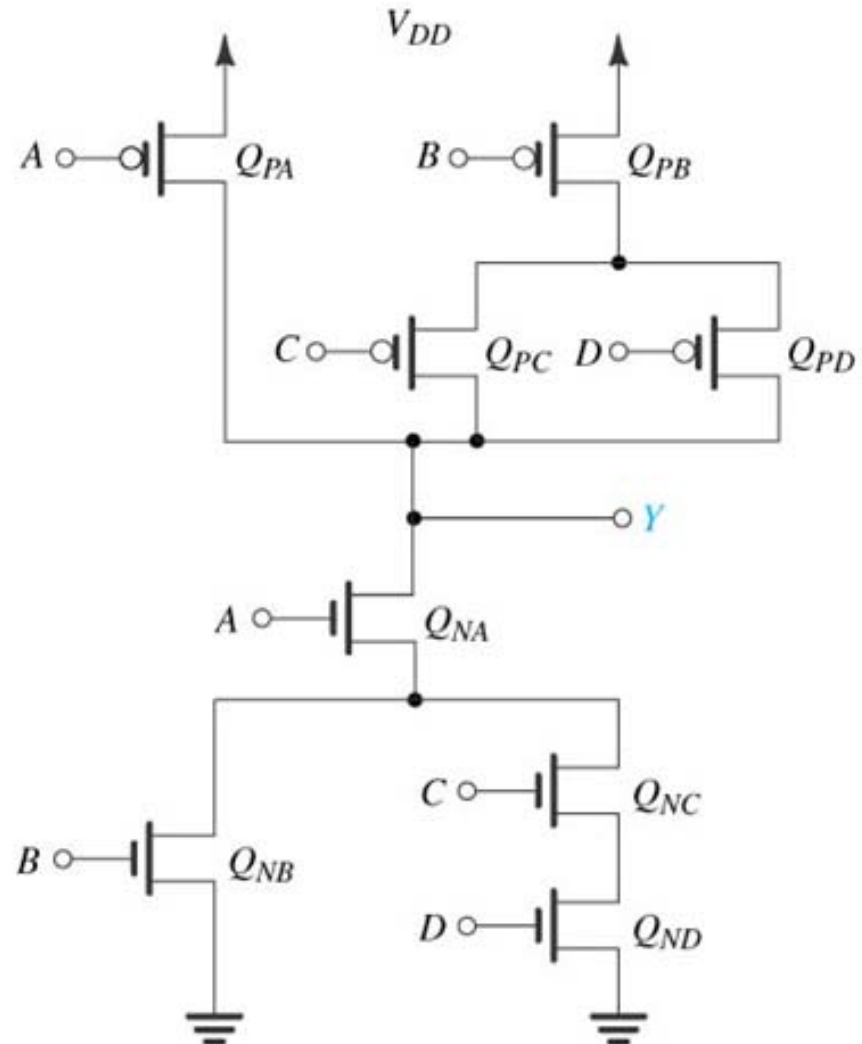


PUN/PDN Duality

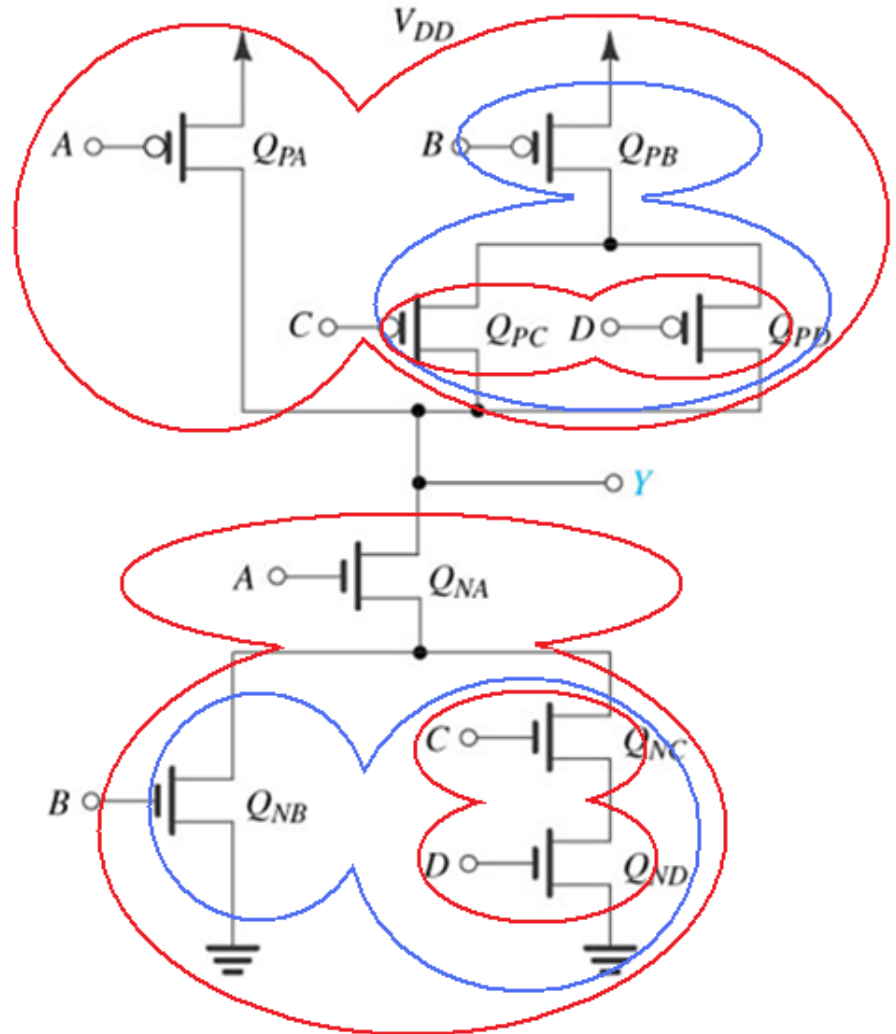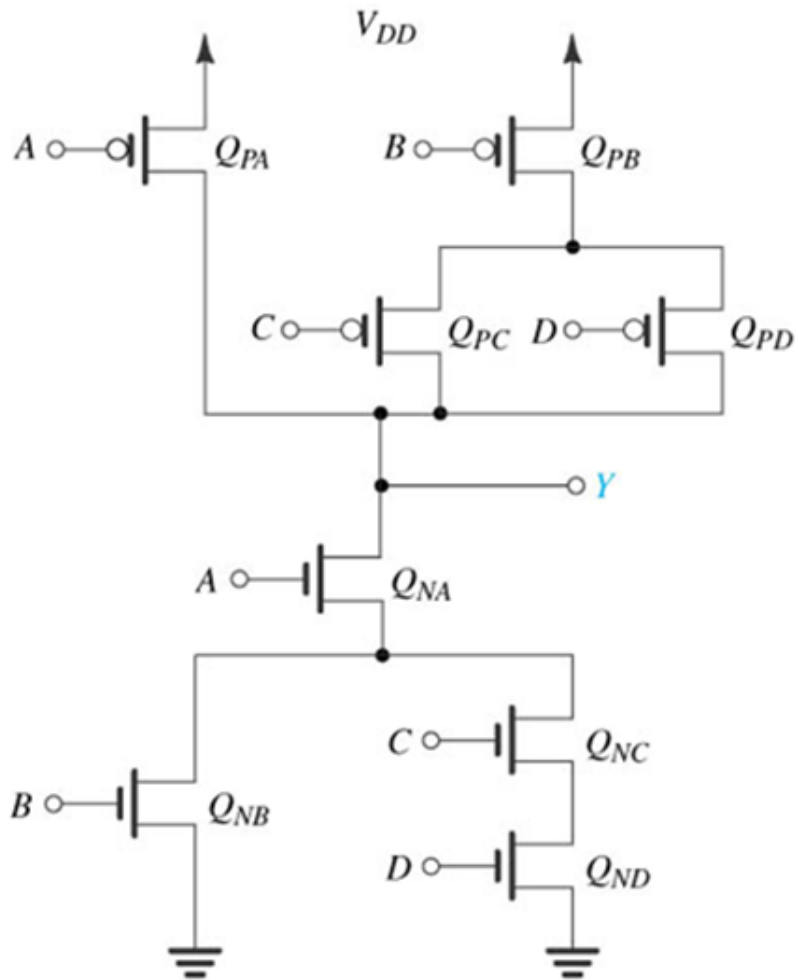

Design by Duality

$$Y = \overline{A + B + C(D + E)}$$

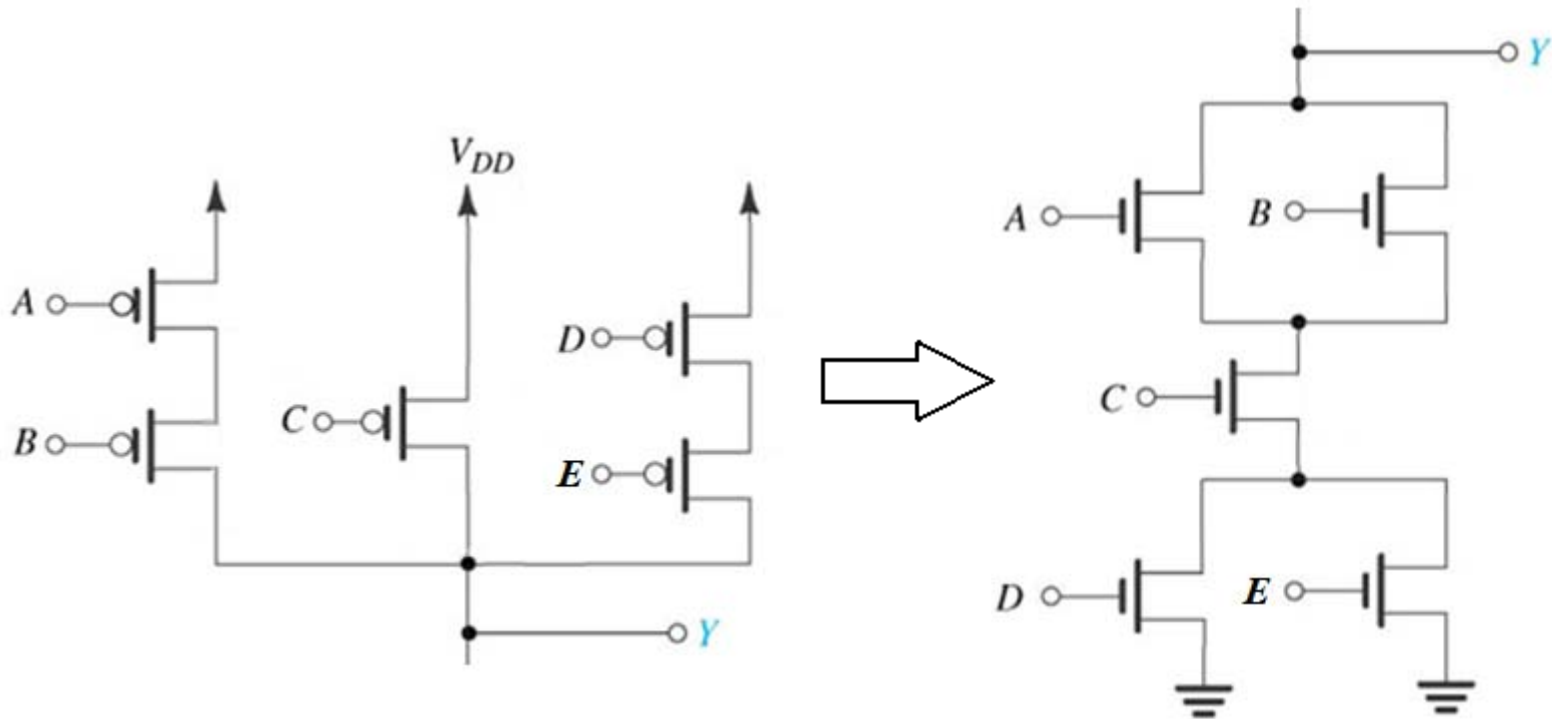
$$Y = \overline{A + B + C(D + E)} = \bar{A}\bar{B} + \bar{C} + \overline{D + E} = \bar{A}\bar{B} + \bar{C} + \bar{D}\bar{E}$$




XOR PUN

$$Y = A\bar{B} + \bar{A}B$$

PUN

 

 
$$Y = \bar{\bar{A}}\bar{B} + \bar{A}\bar{\bar{B}}$$




XOR PDN
 
$$\begin{aligned}\bar{Y} &= \overline{A\bar{B} + \bar{A}B} = \overline{(A\bar{B})} \overline{(\bar{A}B)} = (\bar{A} + B)(A + \bar{B}) \\ &= A\bar{A} + AB + \bar{A}\bar{B} + B\bar{B} = AB + \bar{A}\bar{B}\end{aligned}$$



Complete XOR

$$Y = A\bar{B} + \bar{A}B$$

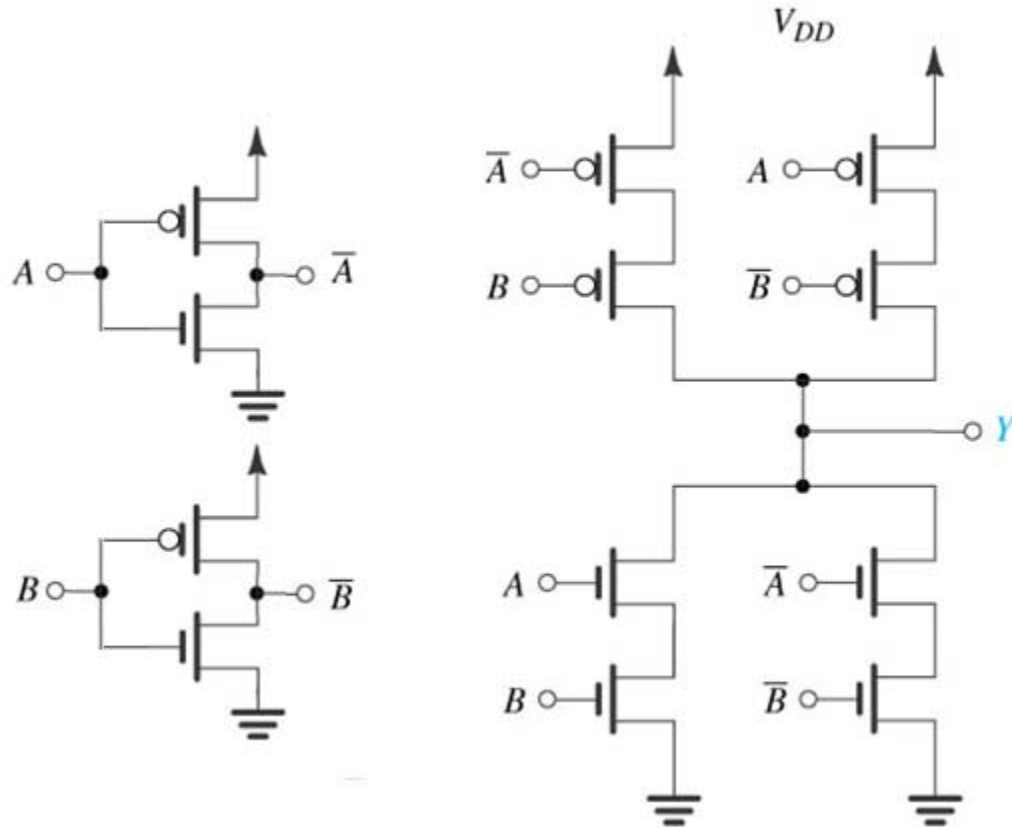

Number of transistors is 12!

Transistor Sizing

$$I_{PUN} = I_{PDN} = I_{Inverter}$$

Define: $n = \frac{W_n}{L_n} \approx 1.5 \text{ to } 2$ and $p = \frac{W_p}{L_p} = n \frac{\mu_n}{\mu_p}$ recall $\frac{\mu_n}{\mu_p} \approx 2 \text{ to } 3$

$$r_{DS} \propto \frac{L}{W} \quad R_{series} = r_{DS1} + r_{DS1} + \dots = b \left(\frac{L}{W} \right)_1 + b \left(\frac{L}{W} \right)_2 + \dots = b \left(\frac{L}{W} \right)_{eq}$$

$$\left(\frac{W}{L} \right)_{series,eq} = \frac{1}{\frac{1}{(W/L)_1} + \frac{1}{(W/L)_2} + \dots}$$


Similarly $\left(\frac{W}{L} \right)_{parallel,eq} = (W/L)_1 + (W/L)_2 + \dots$

If $\frac{W}{L} = 4$ then for two transistors $\left(\frac{W}{L} \right)_{series} = 2$ and $\left(\frac{W}{L} \right)_{parallel} = 8$

Transistor Sizing Example-1

$$\left(\frac{W}{L}\right)_{series} = \frac{1}{4 \frac{1}{(W/L)}} = \frac{1}{4} \left(\frac{W}{L}\right)$$
 
$$\left(\frac{W}{L}\right)_{parallel} = 4 \left(\frac{W}{L}\right)$$



Design

4p

4p

4p

4p

n n n n

Design with worst case in mind.

Transistor Sizing Example-2

Let $n = 1.5, p = 5, L = 0.25\mu m$.


Calculate W/L for all transistors.

PDN **worst** case:

Q_{NB} and (Q_{NC} or Q_{ND}) ON. \rightarrow 2 transistors in series.

$$\left(\frac{W}{L}\right)_{Q_{NB}} = \left(\frac{W}{L}\right)_{Q_{NC}} = \left(\frac{W}{L}\right)_{Q_{ND}} = 2n = 3 = \frac{0.75\mu m}{0.25\mu m}$$
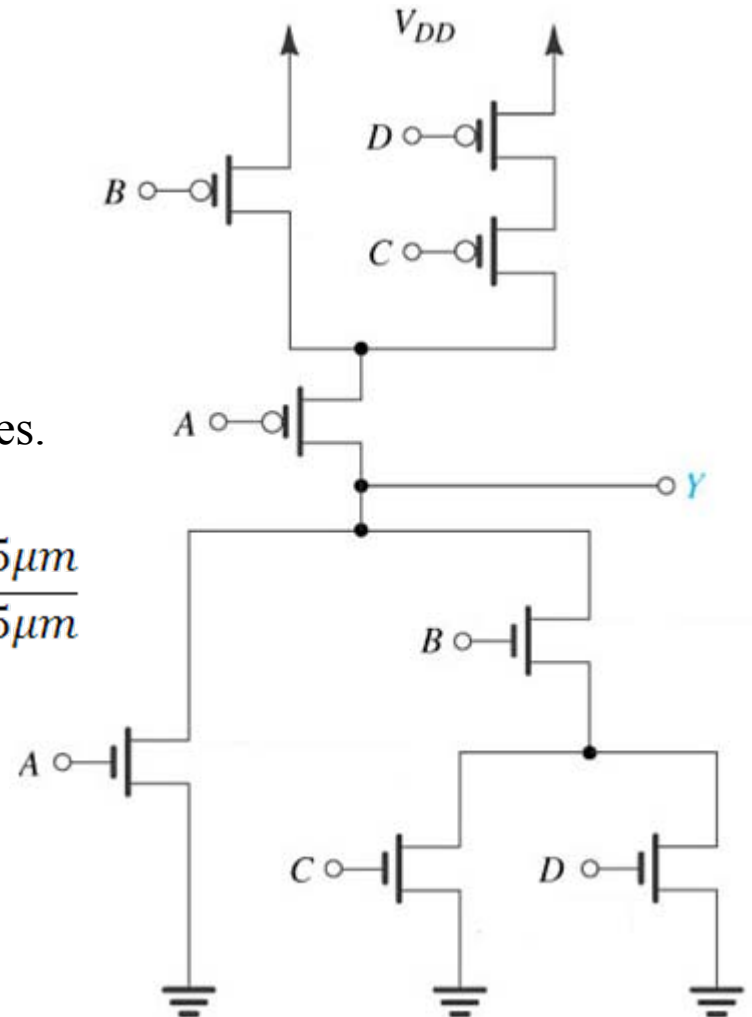
$$\left(\frac{W}{L}\right)_{Q_{NA}} = n = 1.5 = \frac{0.375\mu m}{0.25\mu m}$$



Transistor Sizing Example-2

PUN **worst** case:

Q_{PA} and Q_{PC} and Q_{PD} ON. \rightarrow 3 transistors in series.

$$\left(\frac{W}{L}\right)_{Q_{PA}} = \left(\frac{W}{L}\right)_{Q_{PC}} = \left(\frac{W}{L}\right)_{Q_{PD}} = 3p = 15 = \frac{3.75\mu m}{0.25\mu m}$$


Q_{PA} and Q_{PB} ON. \rightarrow 2 transistors in series.

Q_{PA} fixed:

$$\left(\frac{W}{L}\right)_{Q_P} = \frac{1}{\frac{1}{(W/L)_{Q_{PA}}} + \frac{1}{(W/L)_{Q_{PB}}}}$$

$$p = \frac{1}{\frac{1}{3p} + \frac{1}{xp}} = \frac{3p}{1 + \frac{3}{x}} \rightarrow 1 + \frac{3}{x} = 3 \rightarrow x = 1.5$$
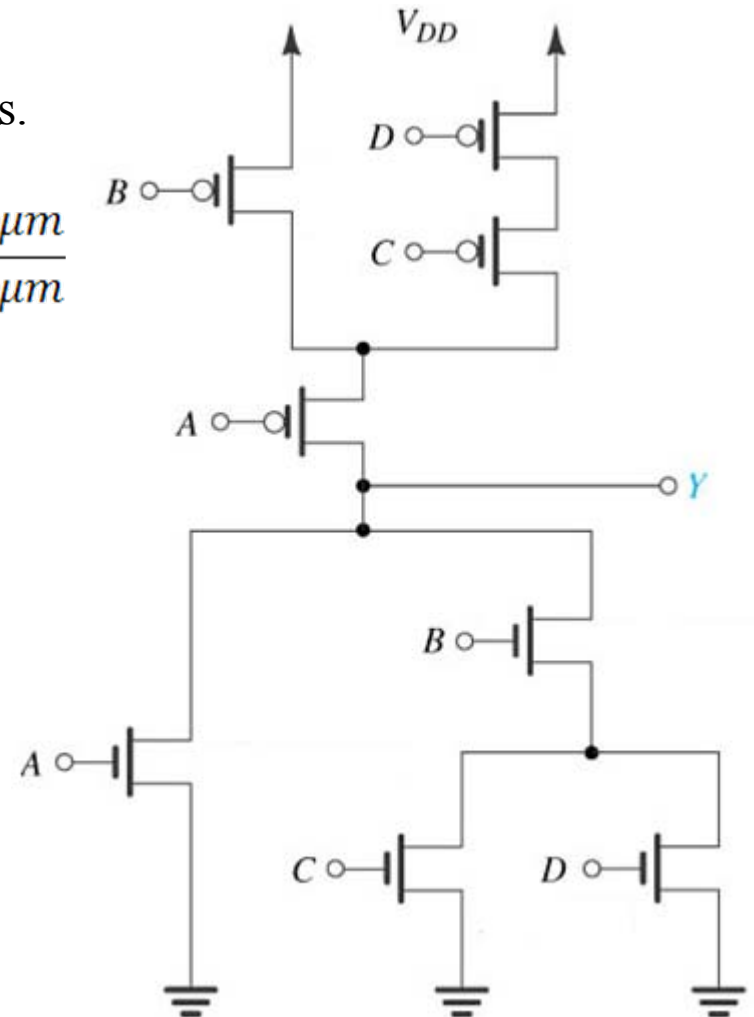
$$\left(\frac{W}{L}\right)_{Q_{PB}} = 1.5p = 7.5 = \frac{1.875\mu m}{0.25\mu m}$$



Fan-in & Fan-out VS. Propagation Delay

Fan-in \uparrow


additional input \rightarrow 2 extra transistors $\left\{ \begin{array}{l} \rightarrow \text{chip area } \uparrow \\ \rightarrow C_{EQ} \uparrow \rightarrow t_P \uparrow \end{array} \right.$

Fan-out \uparrow

additional output $\rightarrow C_{load} \uparrow \rightarrow C_{EQ} \uparrow \rightarrow t_P \uparrow$


Also more complex circuits for both cases.

Pseudo-NMOS Inverter

 

Advantages:

 - One gate per input.
- Less loading capacitance.
- Smaller Area.



Pseudo-NMOS Logic Static Characteristics


Point E

Q_P saturation:

$$i_{DP} = \frac{1}{2} k_p (V_{DD} - V_t)^2$$

 Q_N triode:
 
$$i_{DN} = k_n \left[(v_I - V_t)v_O - \frac{1}{2}v_O^2 \right]$$



Point A

Q_p triode:

$$i_{DP} = k_p \left[(V_{DD} - V_t)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right]$$

Ratioed Type

Q_N saturation (cutoff):

$$i_{DN} = \frac{1}{2} k_n (v_I - V_t)^2$$

$$k_n = k'_n \left(\frac{W}{L} \right)_n \quad k_p = k'_p \left(\frac{W}{L} \right)_p \quad r \equiv \frac{k_n}{k_p}$$

Pseudo-NMOS Logic V_{OH} and V_{OL}

For $v_I=0$ (point A)

Q_P triode, Q_N cutoff

$$i_P = 0, v_{DSP} = 0$$

$$v_O = V_{OH} = V_{DD}$$


For $v_I=V_{DD}$ (point E)

Q_P saturation, Q_N triode

$$v_O = V_{OL} \neq 0$$

Gate conducts (static) current I_{stat} !

$$P_D = I_{stat} \times V_{DD}$$

 


Pseudo-NMOS Logic VTC

Region I (AB)
 Q_P triode, Q_N cutoff

Region II (BC)
 Q_P triode, Q_N saturation

Region III (CD)
 Q_P triode, Q_N triode

 Region IV (DE)
 Q_P saturation, Q_N triode



Pseudo-NMOS Logic VTC Regions I & II

Region I $v_I < V_t$

Q_P triode, Q_N cutoff

$$v_O = V_{OH} = V_{DD}$$

Region II $v_O \geq v_I - V_t$


Q_P triode, Q_N saturation

$$v_O = V_t + \sqrt{(V_{DD} - V_t)^2 - r(v_I - V_t)^2}$$

Setting $\frac{dv_O}{dv_I} = -1$ and $v_I = V_{IL}$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{r(r+1)}}$$

$$V_M|_{v_O=v_I} = V_t + \frac{V_{DD} - V_t}{\sqrt{r+1}}$$

 

Pseudo-NMOS Logic VTC Regions III & IV

Region III

Q_P triode, Q_N triode

Not significant.

Point **C**: Set $v_O = v_I - V_t$ in region II
 v_O formula.

Point **D**: $v_O = V_t$


Region IV

Q_P saturation, Q_N triode

$$v_O = v_I - V_t - \sqrt{(v_I - V_t)^2 - \frac{1}{r}(V_{DD} - V_t)^2}$$

Setting $\frac{dv_O}{dv_I} = -1$ and $v_I = V_{IH}$
 
$$V_{IH} = V_t + \frac{2}{\sqrt{3}r}(V_{DD} - V_t)$$




Pseudo-NMOS Logic V_{OL} & I_{stat}

Set $v_I = V_{DD}$ in region IV v_O formula:

$$V_{OL} = (V_{DD} - V_t) \left(1 - \sqrt{1 - \frac{1}{r}} \right)$$

Static current is Q_P current in saturation
 
$$I_{stat} = \frac{1}{2} k_p (V_{DD} - V_t)^2$$




Noise Margins for Pseudo-NMOS Logic

$$NML = V_t - (V_{DD} - V_t) \left(1 - \sqrt{1 - \frac{1}{r}} - \frac{1}{\sqrt{r(r+1)}} \right)$$

$$NMH = (V_{DD} - V_t) \left(1 - \frac{2}{\sqrt{3r}} \right)$$

 
By controlling the ratio $r = k_n/k_p$ we can adjust the noise margins and V_{OL} .



Pseudo-NMOS Dynamic Operation

t_{PLH}


Similar to CMOS.

 

$$t_{PLH} = \frac{1.7C_{EQ}}{k_p V_{DD}}$$

t_{PHL}

Not so similar to CMOS.

 

Must subtract i_{DP}
from i_{DN} .

$$t_{PHL} = \frac{1.7C_{EQ}}{k_n \left(1 - \frac{0.46}{r}\right) V_{DD}}$$


If r is large the formulas will look identical **but**:

$$r \equiv \frac{k_n}{k_p}$$

So t_{PLH} will be r times t_{PHL} . \rightarrow Asymmetrical delay.



Pseudo-NMOS Logic Design Considerations

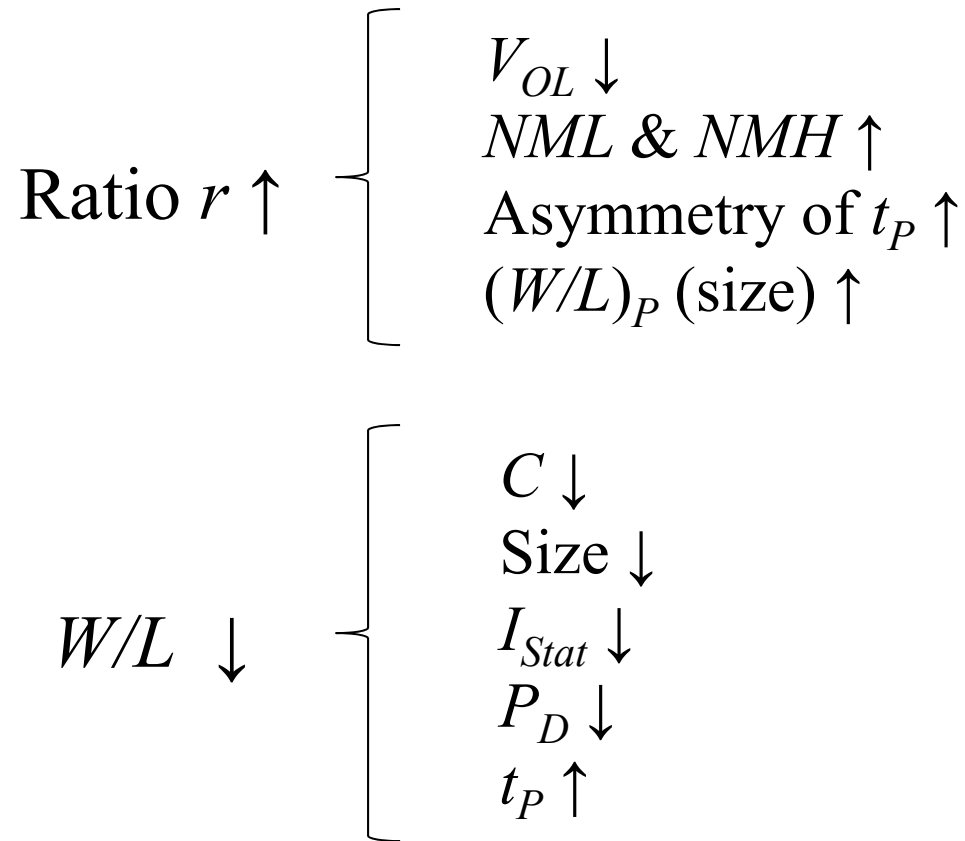Design of either P or N MOSFET ratio r and W/L is chosen. The design of the counterpart is determined by the ratio r .



Pseudo-NMOS Logic Circuit

PDN same as for CMOS.

  

Less transistors than CMOS.


Most used in RAMs, memory decoders, and when output is mostly high.

Pass-Transistor Logic (PTL)


Transmission-Gate Logic

Use logic variables to connect another input variable to output.

$$Y = ABC$$

 


Used with CMOS gates.

 


$$Y = A(B+C)$$

PTL Switch Types

 


Single NMOS
Transistor

 

Two complimentary CMOS
Transistors.
CMOS Transmission Gate


PTL Needs Path to V_{DD} /Ground

 

B	S_1		A	Y
High	Closed	$Y=A$	Low	Low
			High	High
Low	Open	$Y=?$	Was Low	Low
			Was High	Slow Discharge!

Not a static combinational logic circuit!


PTL Path to V_{DD} /Ground Solved

 

S_2 low resistance path to ground.

Every node must always have a low resistance path to V_{DD} or ground.

Single NMOS & Body Effect

 

When v_I goes high Q will be in saturation.

$$i_D = \frac{1}{2} k_n (V_{DD} - v_O - V_t)^2$$

Body Effect: $V_t = V_{t0} + \gamma \left(\sqrt{v_O - 2\phi_f} - \sqrt{2\phi_f} \right)$ Body connected to source at v_O .


- 1- As $v_O \uparrow \rightarrow V_t \uparrow$ and $i_D \downarrow \rightarrow$ Charging will be slowed.
- 2- When $v_O = V_{DD} - V_t$ the current $i_D = 0 \rightarrow V_{OH} = V_{DD} - V_t$ (poor 1).
- 3- Because $V_{OH} = V_{DD} - V_t$ load Q_P will conduct $\rightarrow P_D \neq 0$.

Restoration of V_{DD}

v_{OI}	v_{OI}	Q_R
Low	High	Off
Poor High	Low	On


When Q_R is on it will charge C up to V_{DD} (good High).

Warning: Positive feedback!

 

Or use special transistors with small V_t preferably $V_t=0V$.

CMOS Transmission Gates

 

Switch=On

$V_{DSN}=V_{DD}$ & $V_{GSN}=V_{DD}$ Q_N in saturation.

$$i_{DN} = \frac{1}{2} k_n (V_{DD} - v_O - V_{tn})^2 \quad \& \quad V_{tn} = V_{t0} + \gamma \left(\sqrt{v_O - 2\phi_f} - \sqrt{2\phi_f} \right)$$

i_{DN} is going down again!

What about Q_P ?

$V_{DSP}=-V_{DD}$ & $V_{GSP}=-V_{DD}$ Q_P also in saturation.

$$i_{DP} = \frac{1}{2} k_p (V_{DD} - |V_{tp}|)^2 \quad \text{No body effect. Why?}$$

Q_P will continue to conduct after $v_O=|V_{tp}|$ until $v_O=V_{DD}=V_{OH}$.

Transmission Gate Vs. Single Transistor


Pros:

- Improved t_p because two transistors conduct giving higher current.
- Good V_{OH} .

Cons:

- Increased capacitance C because of two transistors.
- More complex circuit.
- More area.


PTL Example 1

 


$$Y = CA + \bar{C}B$$

2 to 1 MUX

PTL Example 2

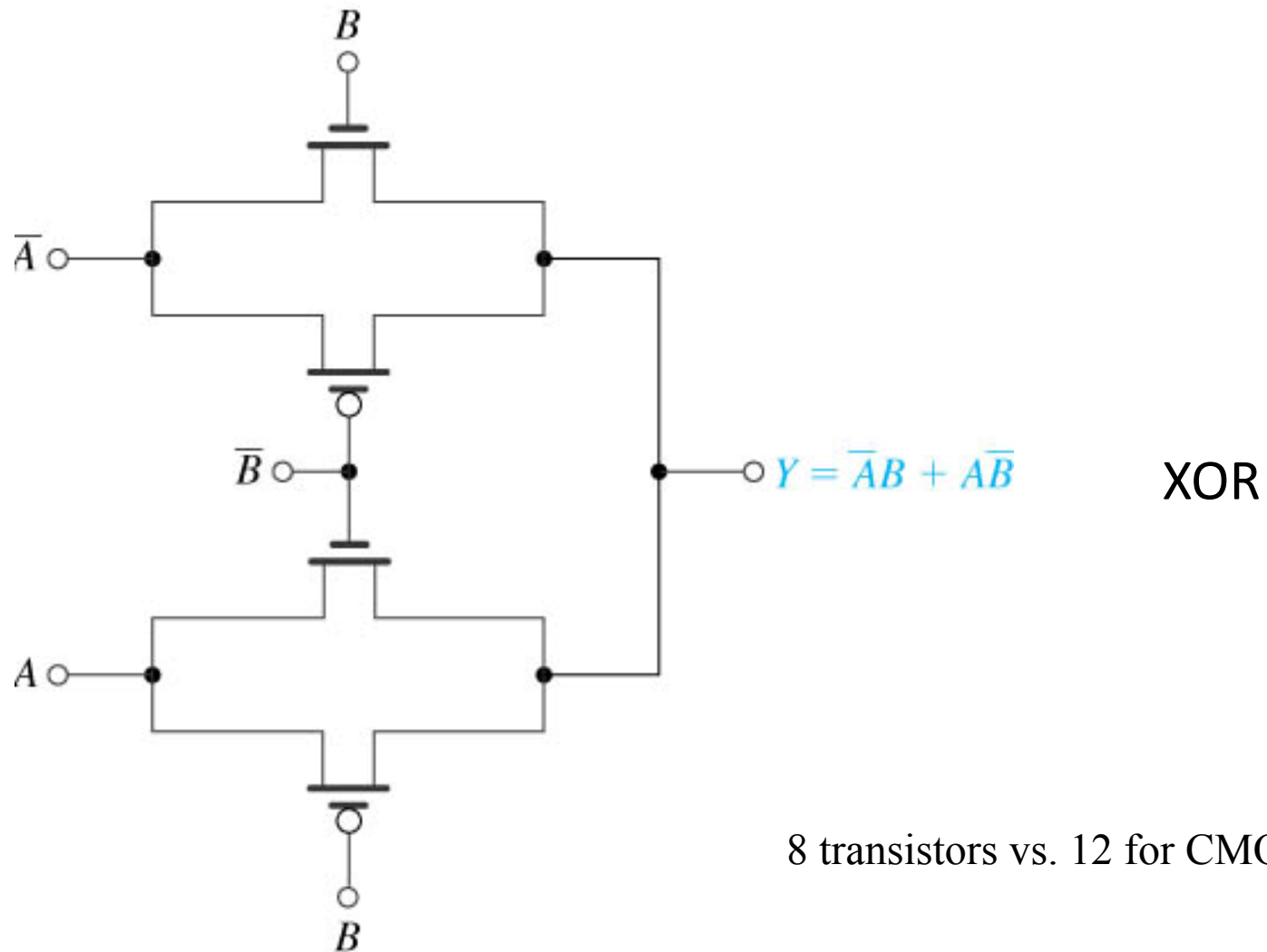

Complementary PTL Example

 

Use small V_t or $V_t = 0V$.


Dynamic Logic Circuits

Basic principle: Storage of voltages on capacitors.
Capacitors lose charge over time. Need **refresh** (clock).

Why dynamic logic?

- 1- Small number of transistors.
- 2- Static power dissipation is zero.

Dynamic Logic Operation Principle

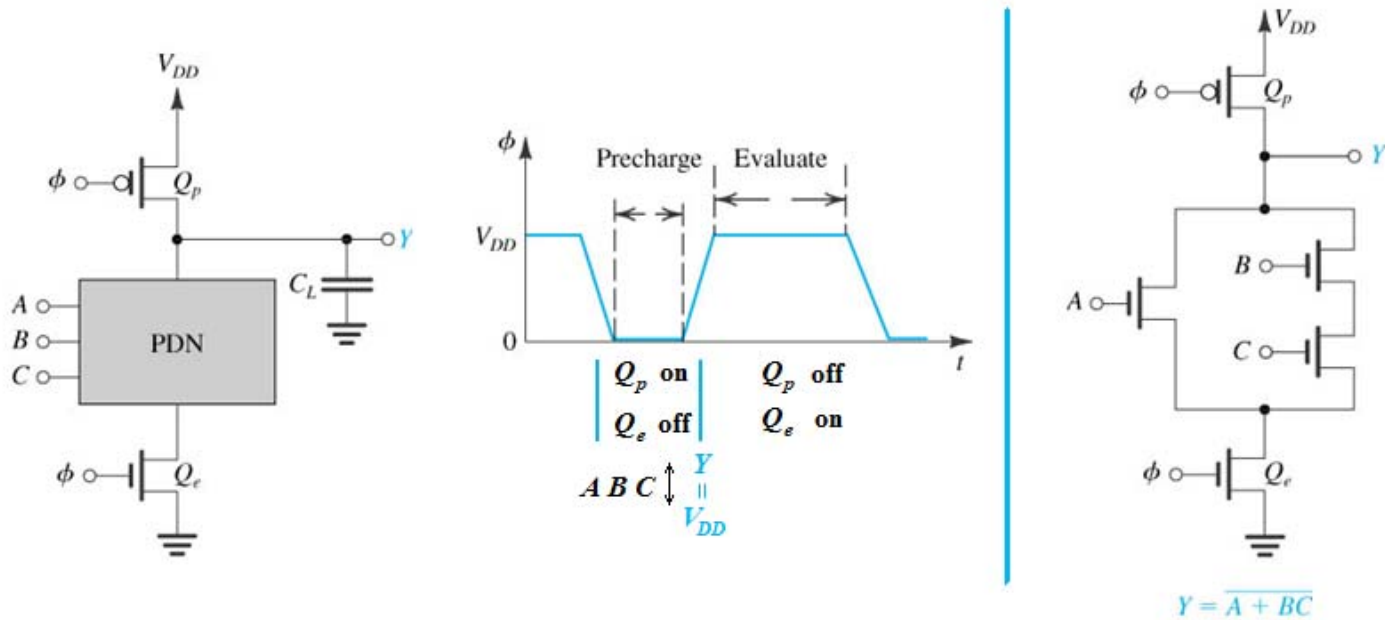

Precharge: Q_p on, Q_e off $\rightarrow C_L$ charged to $V_{DD} = Y = V_{OH}$.
Inputs settle.

Evaluate: Q_p off, Q_e on $\left\{ \begin{array}{l} F(A,B,C) \text{ high} \rightarrow \text{PDN off} \rightarrow Y \text{ high, } t_{PLH}=0 \\ F(A,B,C) \text{ low} \rightarrow \text{PDN on} \rightarrow Y \text{ low, } V_{OL}=0, t_{PHL} \neq 0 \end{array} \right.$

Q_p W/L to fully charge C_L during $T_{Precharge}$

Dynamic Logic Characteristics 1


$$V_{IL} \approx V_{IH} \approx V_{tn}$$

Noise Margins: $NML = V_{tn}$ $NMH = V_{DD} - V_{tn}$


NML ≠ NMH *NML small*

C_L will discharge into the load gate.

 Clock cycle must be small to limit discharge.




Dynamic Logic Characteristics 2

 

Charge Sharing

Evaluation phase

 If Q_1 on and Q_2 off. C_L loses some charge to $C_1 \rightarrow v_O$ decay.



Solution

Dynamic Logic Characteristics 3

Dynamic Logic Circuits in Cascade

Evaluation phase

In theory: A high $\rightarrow Y_1$ low $\rightarrow Y_2$ high


In reality: Y_1 at V_{DD} and discharging

Q_2 will stay on until Y_1 drops to V_t

In the mean time Y_2 is discharging!

$v_O < V_{DD}$ (Poor One)

It doesn't work properly!

 


Domino CMOS Logic Circuits

(Dynamic Logic Circuits In Cascade)

Precharge Phase: Y low

Evaluation Phase: $\left\{ \begin{array}{l} X \text{ high} \rightarrow Y \text{ low}, \quad t_{PHL}=0 \\ X \text{ low} \rightarrow Y \text{ high}, \quad t_{PLH} \neq 0 \end{array} \right.$

Will it work?

 

Domino CMOS Logic Circuits 2

Precharge Phase:

X_1 high(V_{DD}) \rightarrow Y_1 low(0V)

X_2 high(V_{DD}) \rightarrow Y_2 low(0V)

Evaluation Phase:



A high, $\phi \uparrow$

C_{L1} discharges pulling X_1 down

Wait until $v_{X1} \leq V_t$ then Y_1 high(V_{DD})

C_{L2} discharges pulling X_2 down

  Wait until $v_{X2} \leq V_t$ then Y_2 high(V_{DD})



Delay

Small size + high speed + zero static power dissipation

Difficult in design