

PUSH PULL CONVERTER DESIGN AND CIRCUIT


Written by

GEORGE LEON

Nagercoil, India.

george_leon@rediffmail.com

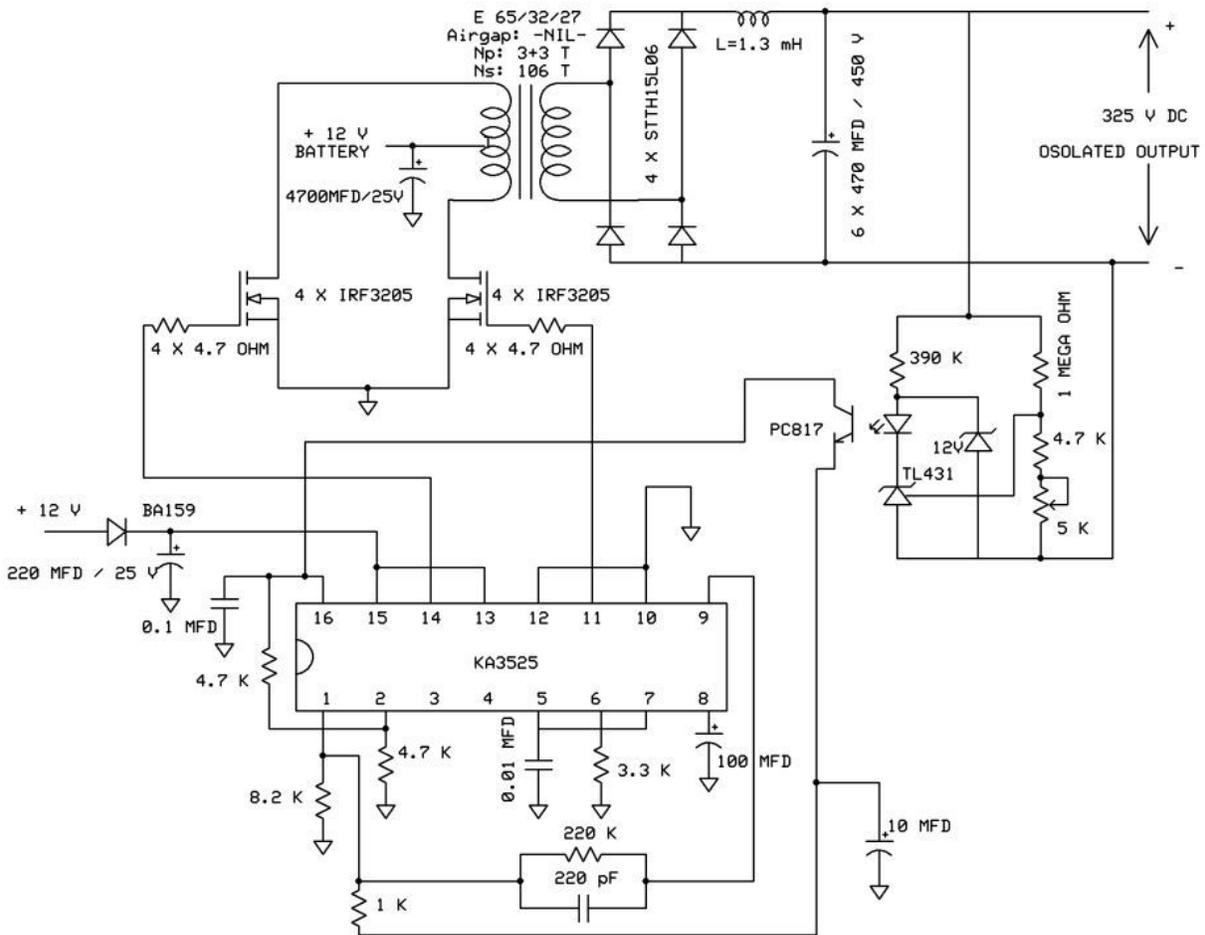The circuit and calculation given are to step up 12V DC supply to 325V DC to deliver 1KW Power. KA3525 push-pull SMPS controller is used. If the output is used for pure sine wave inverter then output filter capacitor should be 2.5 times output power. Use 16 Sq mm copper cable of length less than 1m each to connect battery with converter.



Ferrite core selected for Transformer: **E 65/32/27**

Area of ferrite core $A_e = 540 \text{ mm}^2$

Max flux density $B_m = 0.1 \text{ Wb/m}^2$ (for push-pull configuration)

Air gap = 0

Timing resistor $R_T = 3.3 \text{ K}\Omega$

Timing capacitor $C_T = 0.01 \mu\text{F}$

Dead time resistor $R_D = 0 \Omega$

Maximum duty cycle $D_{\text{max}} = 49 \%$


$$\begin{aligned} \text{Frequency of oscillator } F_{\text{OSC}} &= 1 / (C_T (0.7 \times R_T + 3 \times R_D)) \\ &= 1 / (0.01 \times 10^{-6} \times (0.7 \times 3.3 \times 10^3 + 3 \times 0)) \\ &= 43.2 \text{ KHz} \end{aligned}$$

$$\begin{aligned} \text{Switching frequency } F_s &= F_{\text{OSC}} / 2 \\ &= 43.2 / 2 \\ &= 21.6 \text{ KHz} \end{aligned}$$

$$\begin{aligned} \text{Switching time period } T &= 1 / F_s \\ &= 1 / 21.6 \times 10^3 \\ &= 46.2 \mu\text{s} \\ T/2 &= 23.1 \mu\text{s} \end{aligned}$$

Minimum input voltage $V_{\text{min}} = 10.5\text{V}$

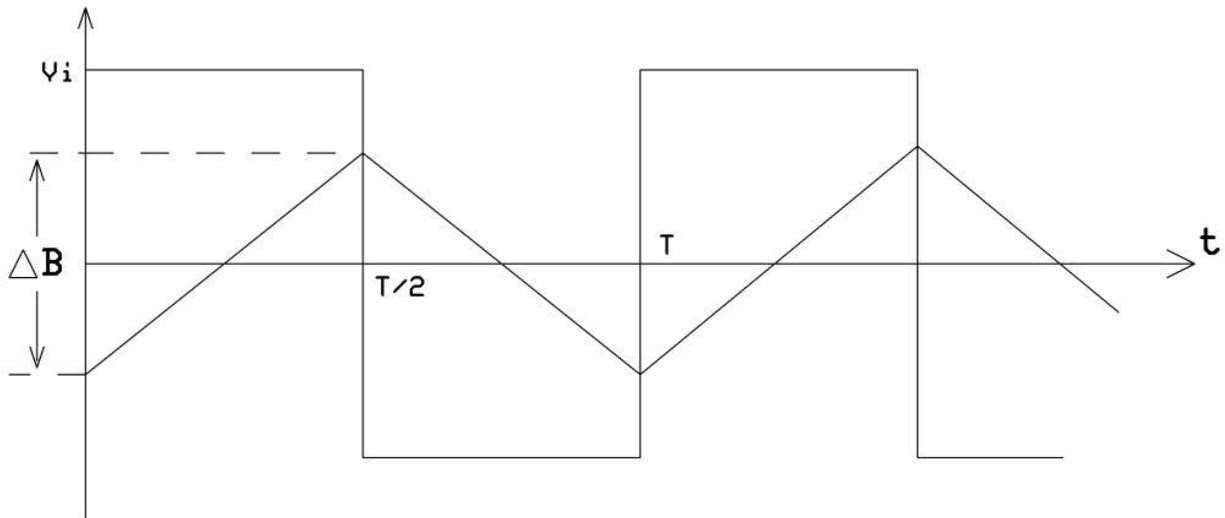Drain source on voltage $V_{\text{DS}}(\text{on}) = 1\text{V}$



Secondary
Primary
Secondary
Core
Secondary
Primary
Secondary

Placing Winding
For better coupling

$$\text{Primary turns } N_p(\text{min}) = \frac{V_i \times T/2}{\Delta B \times A_e}$$

$$N_p(\text{min}) = \frac{(10.5-1) \times 23.1 \times 10^{-6}}{2 \times 0.1 \times 540 \times 10^{-6}}$$

$$N_p(\text{min}) = 2.03 \text{ T}$$

Take primary turns N_p as 3 Turns per limb.

$$\text{Output Voltage } V_o = 325 \text{ V}$$

$$\text{Diode voltage drop } V_f = 1 \text{ V}$$

$$\text{Secondary Voltage } V_s = (V_o + 2 \times V_f) / (2 \times D_{\text{max}})$$

$$= (325 + 2 \times 1) / (2 \times 0.49)$$

$$= 334 \text{ V}$$

$$\text{Secondary Turns } N_s = N_p \times V_s / V_i$$

$$= 3 \times 334 / 9.5$$

Secondary Turns N_s = 106 Turns

Selection of wire gauge

$$\text{Output Power} = 1000 \text{ W}$$

$$\text{Output Current } I_o = 1000 / 325$$

$$= 3.1 \text{ A}$$

Take current density of 5 A/mm^2

$$\text{Secondary wire cross section area} = 3.1 / 5 = 0.62 \text{ mm}^2$$

So 20 SWG wire selected for secondary winding.

Assume efficiency = 85%

$$\text{Input power} = 1000 / 0.85 = 1176 \text{ W}$$

$$\text{Input current} = P_i / (V_{\text{min}} \times 2 \times D_{\text{max}}) = 114 \text{ A}$$

$$\text{Per limb Input Current} = 114 / 2 = 57 \text{ A}$$

As primary turns are only 3, higher current density may be allowed (9 A/mm^2).

$$\text{Primary wire cross section area} = 57 / 9 = 6.3 \text{ mm}^2$$

So 2 x 14 SWG wire selected for primary winding / Limb.

Design of Output Inductor L

Assume the maximum input voltage of 12 V under fully loaded condition

$$\text{Secondary voltage } V_s = N_s \times V_i / N_p$$

$$= 106 \times (12-1) / 3$$

$$= 389 \text{ V}$$

$$\text{MOSFET on Time } T_{\text{on}} = 23.1 \times 325 / (389 - 2)$$

$$= 19.7 \text{ } \mu\text{S}$$

$$\text{Voltage applied across Output inductor } V_L = V_s - 2 \times V_f - V_o$$

$$V_L = 389 - 2 - 325$$

$$V_L = 62 \text{ V}$$

Assume Maximum allowed current ripple $\Delta I_o = 0.3 \times I_o$
 $= 0.93 \text{ A}$

Inductance $L = e \times dt / di$

$$\text{Output Inductor } L = 62 \times 19.7 \times 10^{-6} / 0.93$$

Output Inductor L = 1.3 milli Henry

$$\begin{aligned} \text{Peak Inductor current } I_{\text{peak}} &= I_o + \Delta I_o / 2 \\ &= 3.1 + 0.93 / 2 \\ I_{\text{peak}} &= 3.6 \text{ A} \end{aligned}$$

Ferrite core selected for Output Inductor: **E 42/21/15**

Cross section area $A_e = 178 \text{ mm}^2$

Saturation flux density $B_{\text{sat}} = 0.35 \text{ Wb/m}^2$

From datasheet of core $A_L = 3600 \text{ nH/T}^2$

$$\begin{aligned} \text{Minimum Inductor Turns } N &= L \times I_{\text{peak}} / (B_{\text{sat}} \times A_e) \\ &= 1.3 \times 10^{-3} \times 3.6 / (0.35 \times 178 \times 10^{-6}) \end{aligned}$$

Inductor Turns N = 76 Turns

$$\begin{aligned} \text{Air gap required} &= \mu_o \times A_e \times ((N^2/L) - (1/A_L)) \\ &= 4 \times \pi \times 10^{-7} \times 178 \times 10^{-6} \times ((76^2 / 1.3 \times 10^{-3}) - (1/3600 \times 10^{-9})) \\ &= 0.93 \text{ mm} \end{aligned}$$

Per limb Air gap = 0.93 / 2 = 0.465 mm

Same secondary current flows through this inductor also, so the same 20 SWG wire may be used.