

RCD Clamp Design

- Step 1: Select maximum voltage, V_{max} that we are going to allow on our FET
 - The higher this voltage the lower the losses in the snubber, we would like the maximum spike possible without damaging the FET
 - Typically 66% of the FET's maximum allowable voltage or 85% of FETs maximum allowable voltage minus 20V to allow for overshoot is a good compromise
 - As an alternative you can calculate exactly how much power loss you are willing to tolerate in the clamp and make sure and then reverse calculate the maximum clamp voltage
 - Please see Basso's book for exact equations
- Step 2: Calculate V_{clamp}
 - From previous slides: $V_{clamp} = V_{max} - V_{in}$
- Step 3: Calculate R_{clamp} from this*:

$$R_{clamp} = \frac{2 V_{clamp} (V_{clamp} - N V_{out})}{F_s L_{leakage} I_{peak}^2}$$

Diagram illustrating the equation for R_{clamp} with source annotations:

- From Step 2**: Points to V_{clamp} in the numerator.
- Vout reflected to input**: Points to $N V_{out}$ in the numerator.
- From WDS**: Points to I_{peak}^2 in the denominator.
- From our transformer measurement test**: Points to $L_{leakage}$ in the denominator.

* See Basso "Switch-Mode Power Supplies Spice Simulations and Practical Designs" for full proofs of equations

RCD Clamp Design

- Step 4: Calculate Cclamp
 - Unlike the RC snubber, the value of RCD capacitor does not impact the losses
 - Its value therefore is not crucial; it just needs to be large enough such that voltage remains constant during the snubber operation
 - It is essentially an RC circuit so a good compromise would be to allow 2.5 to 5 time constants*:

$$C_{clamp} = \frac{5}{R_{clamp} F_s}$$

- Step 5: Calculate total power loss in the snubber*

$$P_{loss_clamp} = \frac{1}{2} L_{leakage} I_{peak}^2 F_s \left(\frac{V_{clamp}}{V_{clamp} - N V_{out}} \right)$$

- If power loss is too much then you need to increase the clamping voltage which could mean buying a bigger FET