
Chapter 2-1

Resonators and Impedance Matching with Lumped Elements

Chien-Jung Li

**Department of Electronics Engineering
National Taipei University of Technology**

Resonators

- Lump Resonators

- Series resonant circuit

$$Z_{in}(\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$P_R = \frac{1}{2} |I|^2 R$$


$$W_m = \frac{1}{4} |I|^2 L$$

$$W_e = \frac{1}{4} |V_C|^2 C = \frac{1}{4} |I|^2 \frac{C}{\omega^2 C^2} = \frac{1}{4} |I|^2 \frac{1}{\omega^2 C}$$

At resonant frequency $\omega_0 = 2\pi f_0$

$$W_m = W_e \quad \rightarrow \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$Z_{in}(\omega_0) = R$$

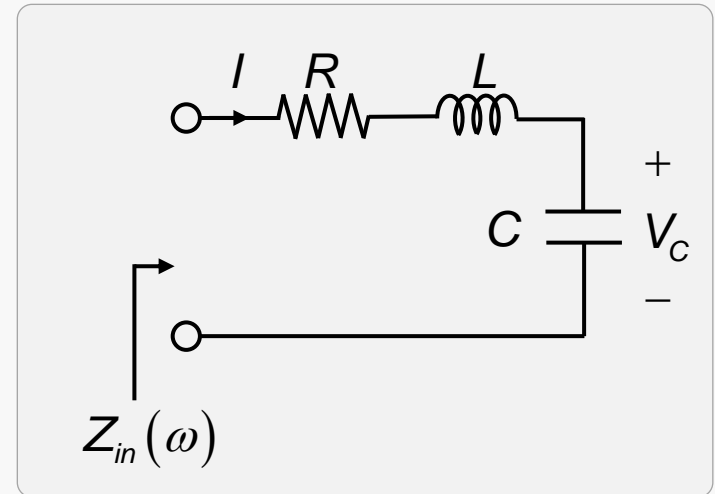

Resonance occurs when the average stored magnetic and electric energies are equal, and the input impedance is a purely real impedance.

Series Resonant Circuit

- Quality Factor:

$$Q \triangleq \omega \frac{W_m + W_e}{P_R} = \omega \frac{\text{average energy stored}}{\text{energy loss/sec}}$$

Q is a measure of the loss of a resonance circuit, and lower loss implies higher Q.

At resonance $\omega = \omega_0$


$$Q = \omega_0 \frac{2W_m}{P_R} = \omega_0 \frac{2 \cdot \frac{1}{4} |I|^2 L}{\frac{1}{2} |I|^2 R} = \frac{\omega_0 L}{R}$$

$$Q = \omega_0 \frac{2W_e}{P_R} = \omega_0 \frac{2 \cdot \frac{1}{4} |I|^2 \frac{1}{\omega_0^2 C}}{\frac{1}{2} |I|^2 R} = \frac{1}{\omega_0 CR}$$

$$Q = \frac{|X|}{R} \quad \text{where} \quad |X| = \omega_0 L \text{ or } \frac{1}{\omega_0 C}$$


Comparisons

- For series RL and series RC Circuits

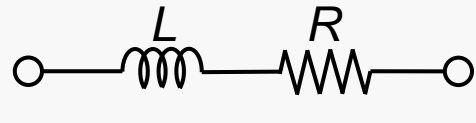

A circuit diagram of a series RL circuit. It consists of an inductor with inductance L and a resistor with resistance R connected in series between two terminals. The inductor is represented by a coiled line, and the resistor is represented by a zigzag line.

$$Q \triangleq \frac{|X|}{R} = \frac{\omega L}{R}$$

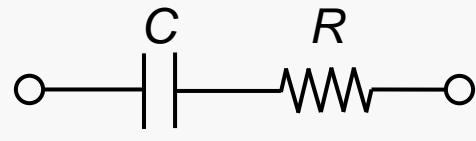

A circuit diagram of a series RC circuit. It consists of a capacitor with capacitance C and a resistor with resistance R connected in series between two terminals. The capacitor is represented by two parallel vertical lines, and the resistor is represented by a zigzag line.

$$Q \triangleq \frac{|X|}{R} = \frac{1}{\omega CR}$$


Although the Q is defined, but the resonant frequency can't be defined (they are not resonators).

Define the Bandwidth

- For series resonant circuits, as $\omega \rightarrow \omega_0$

$$Z_{in}(\omega) = R + j\omega L + \frac{1}{j\omega C}$$

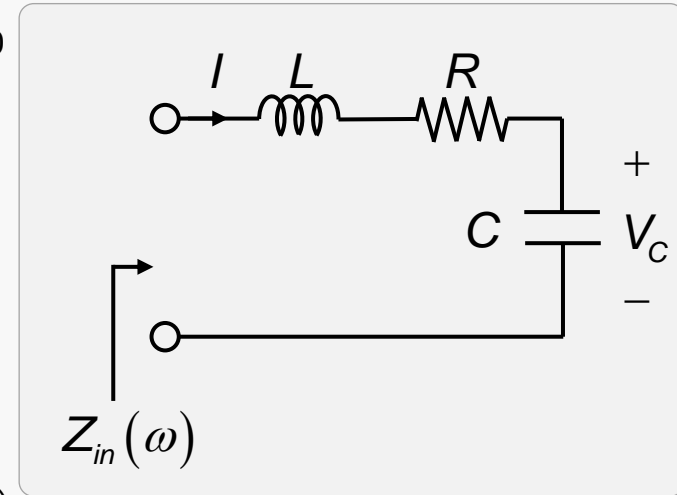Let $\omega = \omega_0 + \Delta\omega$ $\Delta\omega \rightarrow 0$ $\omega_0 = \frac{1}{\sqrt{LC}}$



$$Z_{in}(\omega) = R + j\omega L \left(1 - \frac{1}{\omega^2 LC} \right) = R + j\omega L \left(1 - \frac{1}{\omega^2 / \omega_0^2} \right) = R + j\omega L \left(\frac{\omega^2 - \omega_0^2}{\omega^2} \right)$$

$$= R + j\omega L \frac{(\omega + \omega_0)(\omega - \omega_0)}{\omega^2} \simeq R + jL \frac{2\omega_0 \cdot \Delta\omega}{\omega_0}$$

$$= R + 2j\Delta\omega L = R + 2j\Delta\omega \left(\frac{QR}{\omega_0} \right) \quad \text{where} \quad Q = \frac{\omega_0 L}{R}$$

3-dB Bandwidth

- Define the bandwidth $BW \triangleq \frac{2\Delta\omega}{\omega_0}$


$$Z_{in} = R + 2j \frac{BW \cdot \omega_0}{2} \left(\frac{QR}{\omega_0} \right) = R + jBW \cdot QR$$

when $BW = \frac{1}{Q}$

$$|Z_{in}| = |R + jR| = \sqrt{2}R$$

$$\text{3-dB Bandwidth} = BW \cdot \omega_0 = \frac{\omega_0}{Q}$$
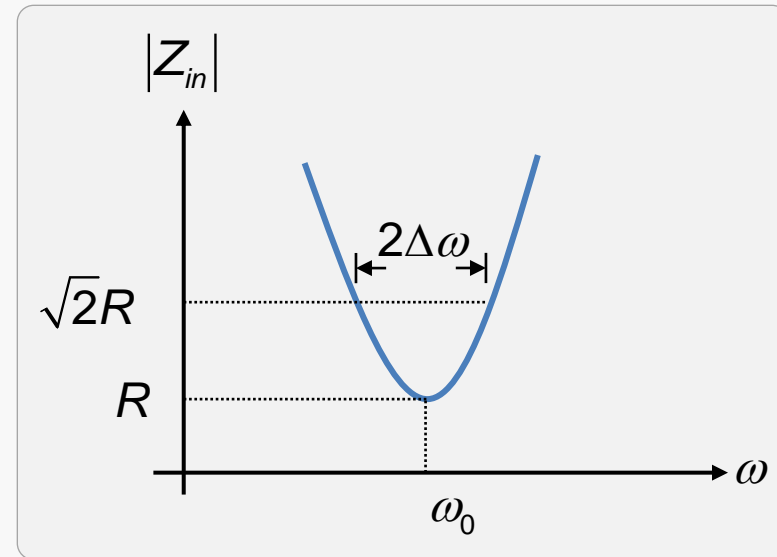
$$\text{3-dB Bandwidth in \%} = BW = \frac{1}{Q}$$



When resonance occurs, the absolute value of impedance is minimum in the series resonant circuit.

Parallel Resonant Circuit

➤ Parallel resonant circuit

$$Y_{in}(\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$


$$P_R = \frac{|V|^2}{2R}$$

$$W_e = \frac{1}{4} |V|^2 C$$

$$W_m = \frac{1}{4} |I_L|^2 L = \frac{1}{4} \frac{|V|^2}{\omega^2 L^2} L = \frac{1}{4} \frac{|V|^2}{\omega^2 L}$$

At resonance, the angular resonant frequency $\omega_0 = 2\pi f_0$
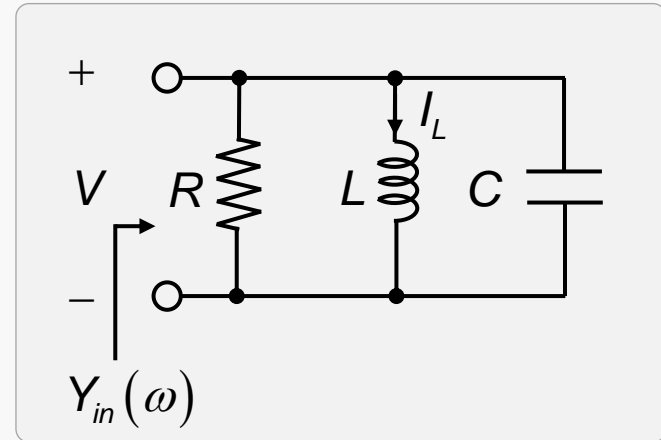
$$W_m = W_e \quad \omega_0 = \frac{1}{\sqrt{LC}}$$
$$Y_{in}(\omega_0) = \frac{1}{R}$$



Parallel Resonant Circuit


- Quality Factor:

$$Q \triangleq \omega \frac{W_m + W_e}{P_R} = \omega \frac{\text{average energy stored}}{\text{energy loss/sec}}$$


At resonance $\omega = \omega_0$

$$Q = \frac{|B|}{G} \quad \text{where} \quad G = \frac{1}{R} \quad \text{and} \quad |B| = \omega_0 C \text{ or } \frac{1}{\omega_0 L}$$

Comparisons:

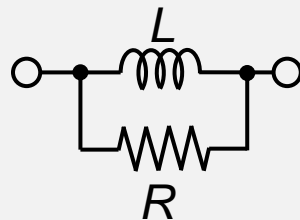

$$Q \triangleq \frac{|B|}{G} = \frac{R}{\omega L}$$

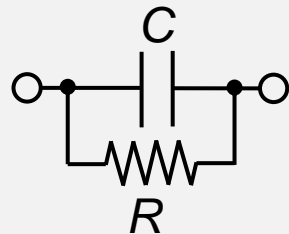

$$Q \triangleq \frac{|B|}{G} = \omega CR$$

3dB Bandwidth

- For parallel resonant circuits, as $\omega \rightarrow \omega_0$

$$Y_{in}(\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C \approx \frac{1}{R} + 2jC\Delta\omega$$

Define $BW \triangleq \frac{2\Delta\omega}{\omega_0}$


$$Y_{in}(\omega) = \frac{1}{R} + 2j \frac{BW \cdot \omega_0}{2} \frac{Q}{\omega_0 R} = \frac{1}{R} + jBW \frac{Q}{R}$$

when $BW = \frac{1}{Q}$

$$|Y_{in}| = \left| \frac{1}{R} + j \frac{1}{R} \right| = \frac{\sqrt{2}}{R}$$

$$\text{3-dB Bandwidth} = BW \cdot \omega_0 = \frac{\omega_0}{Q}$$
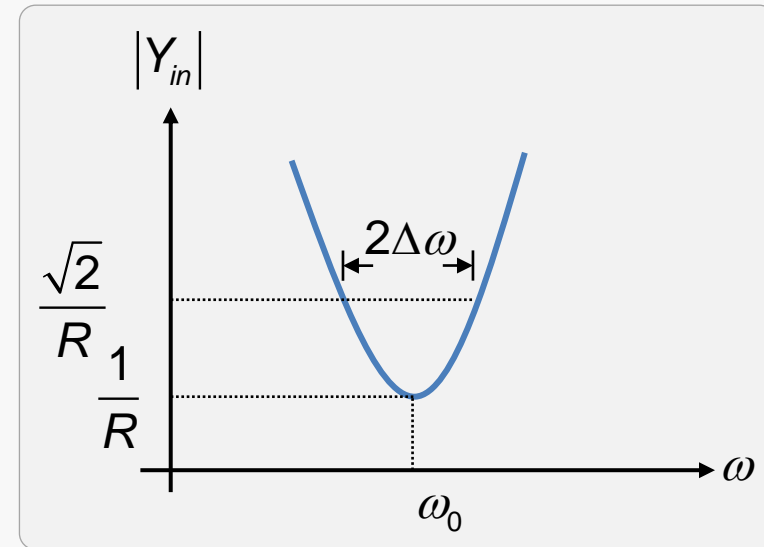
$$\text{3-dB Bandwidth in \%} = BW = \frac{1}{Q}$$



When resonance occurs, the absolute value of admittance is minimum (maximum impedance) in the parallel resonant circuit.

Loaded and Unloaded Q

- For series RLC circuit

$$Q_L = \frac{\omega_0 L}{R + R_L} = \frac{1}{\omega_0 C(R + R_L)}$$

- For parallel RLC circuit


$$Q_L = \frac{R // R_L}{\omega_0 L} = \omega_0 C(R // R_L)$$

- Define the external Q (Q_e)


$$Q_e = \frac{\omega_0 L}{R_L} = \frac{1}{\omega_0 R_L C} \quad \text{for series RLC}$$

$$Q_e = \frac{R_L}{\omega_0 L} = \omega_0 R_L C \quad \text{for parallel RLC}$$
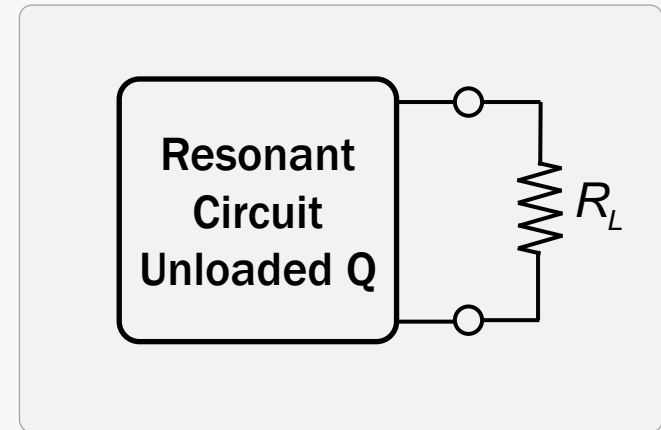
$$\frac{1}{Q_L} = \frac{1}{Q} + \frac{1}{Q_e} \quad \text{for both cases}$$











Impedance Matching

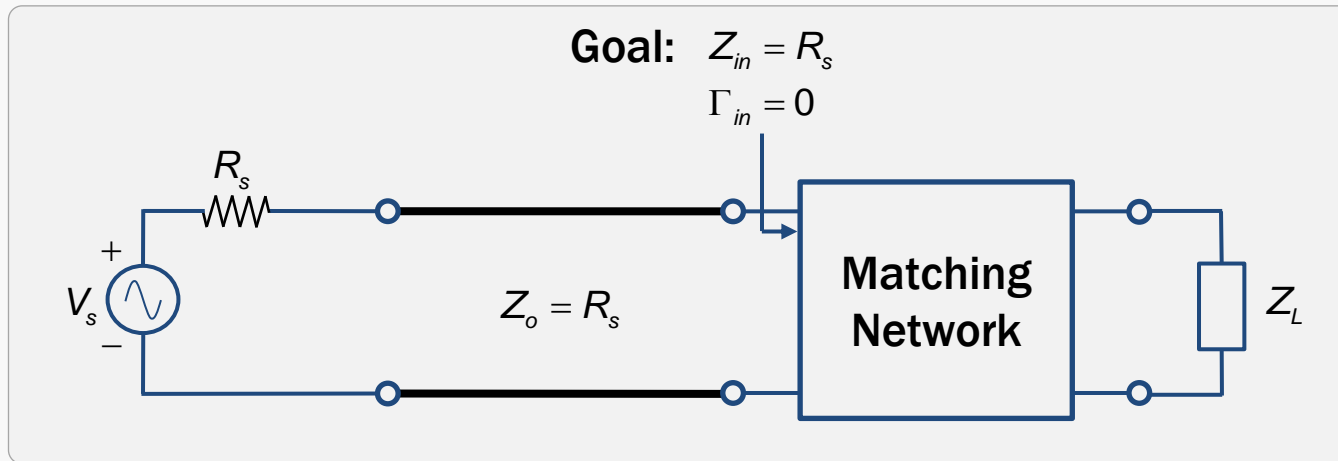

- The matching network is ideally lossless, to avoid unnecessary loss of power, and is usually designed so that the impedance seen looking into the matching network is Z_o (matched with the transmission line) or R_s (matched with the source impedance when no line connected).
- Maximum power is delivered when the load is matched to the line (assuming the generator is matched), and power loss in the feed line is minimized.
- Impedance matching may be used to improve the signal-to-noise ratio or amplitude/phase errors in some applications.


Eight EL Matching Sections (L-Shape)

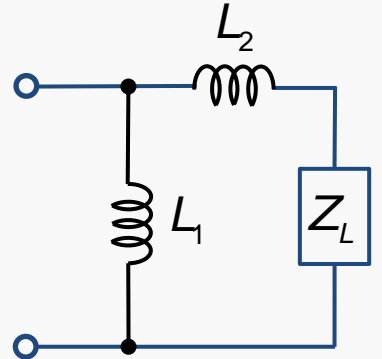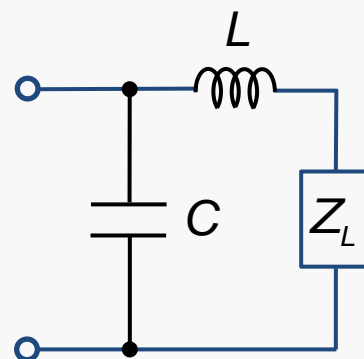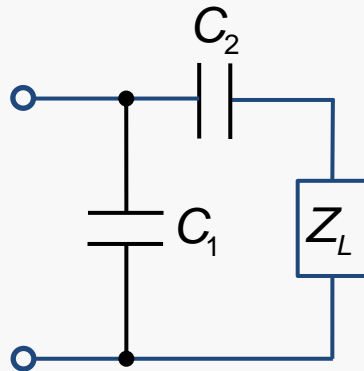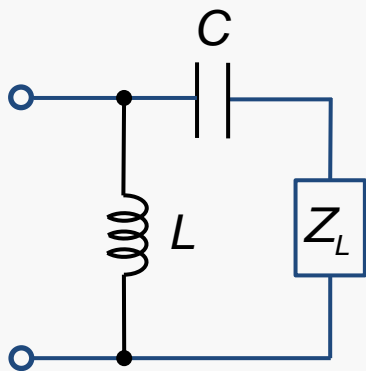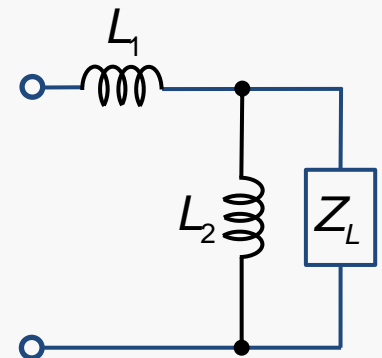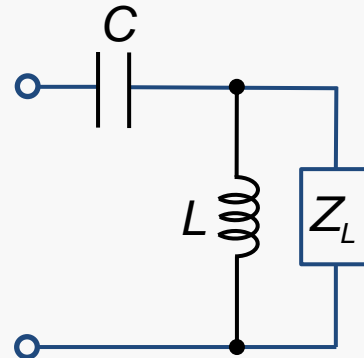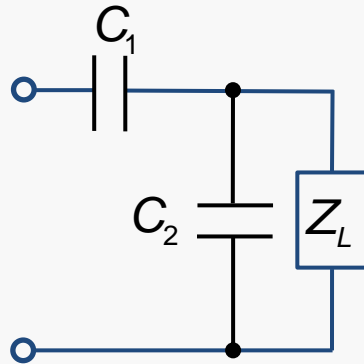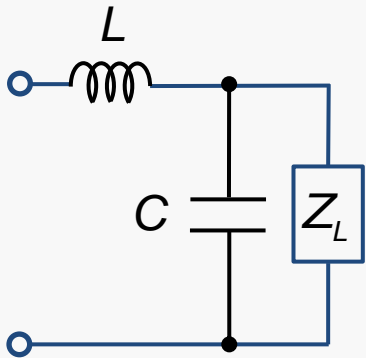

Lump Element Matching

- Two element (L-shape) matching

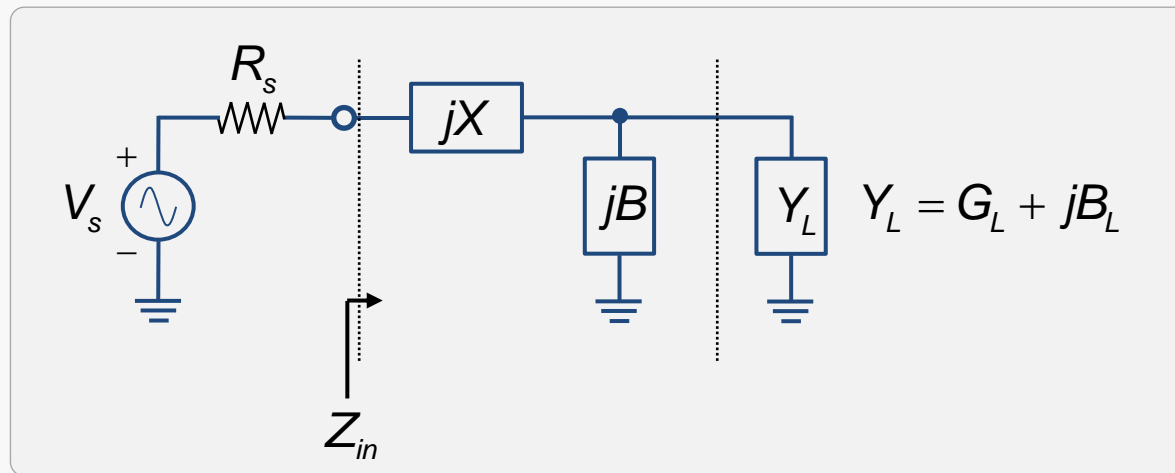➤ Case (a) $R_s < \frac{1}{G_L}$ (or $R_s < R_L$)



X : matching reactance

B : matching susceptance

We want to find X and B

Goal: $Z_{in} = R_s$

$$\Gamma = \frac{Z_{in} - R_s}{Z_{in} + R_s} = 0$$

L-Shape Matching – Case (a) $R_s < R_L$


$$Z_{in} = jX + \frac{1}{(G_L + jB_L) + jB} = R_s$$

Real part: $R_s G_L + X(B + B_L) = 1$

Imaginary part: $R_s(B + B_L) - XG_L = 0$

Use the resonator concept:

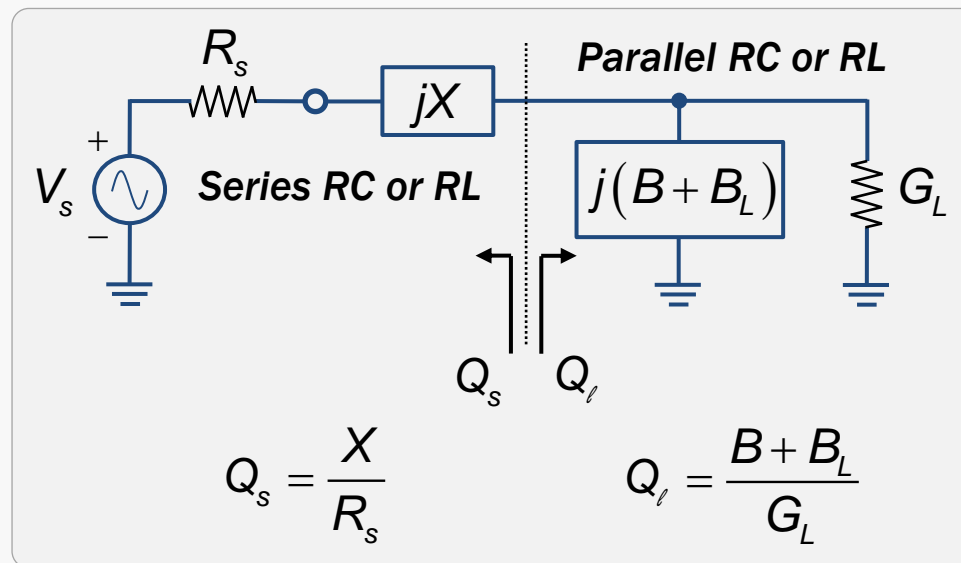When the impedances are matched, the imaginary part of the input impedance looking into the matching network is equal to zero.



L-Shape Matching – Case (a) $R_s < R_L$

Imaginary part: $R_s(B + B_L) - XG_L = 0$

Real part: $R_s G_L + X(B + B_L) = 1$ and $Q_s = \frac{X}{R_s} = Q_l = \frac{B + B_L}{G_L}$

$$\rightarrow R_s G_L (Q^2 + 1) = 1 \rightarrow Q = \pm \sqrt{\frac{1}{R_s G_L} - 1} \quad \left(\text{or } \pm \sqrt{\frac{R_L}{R_s} - 1} \right)$$

Choose $Q = Q_s = Q_l = +\sqrt{\frac{1}{R_s G_L} - 1}$


When Q is chosen, X and B are also decided.

$$X = R_s Q = R_s \sqrt{\frac{1}{R_s G_L} - 1} \quad (>0, \text{ inductance})$$

$$B = G_L Q - B_L = G_L \sqrt{\frac{1}{R_s G_L} - 1} - B_L \quad \begin{array}{l} (>0, \text{ capacitance}) \\ (<0, \text{ inductance}) \end{array}$$

L-Shape Matching – Case (b) $R_s > R_L$

➤ Case (b) $R_s > R_L$

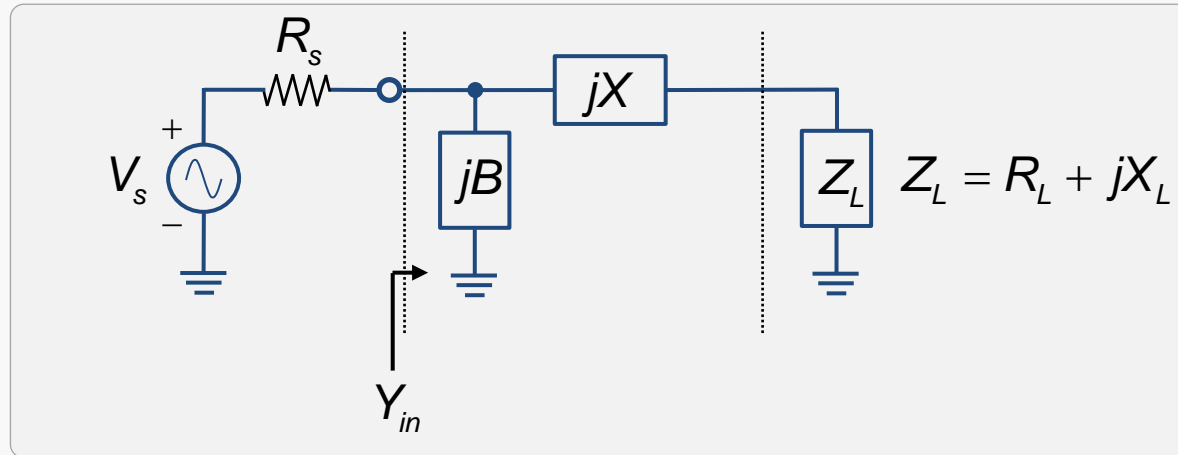

X : matching reactance

B : matching susceptance

Again, we want to find X and B

Goal:

$$Y_{in} = \frac{1}{R_s} \quad \Gamma = \frac{\frac{1}{R_s} - Y_{in}}{\frac{1}{R_s} + Y_{in}} = 0$$

L-Shape Matching – Case (b) $R_s > R_L$


$$Y_{in} = jB + \frac{1}{(R_L + jX_L) + jX} = \frac{1}{R_s}$$

Real part: $BR_s(X + X_L) = R_s - R_L$

Imaginary part: $(X + X_L) - BR_sR_L = 0$

Use resonator concept:

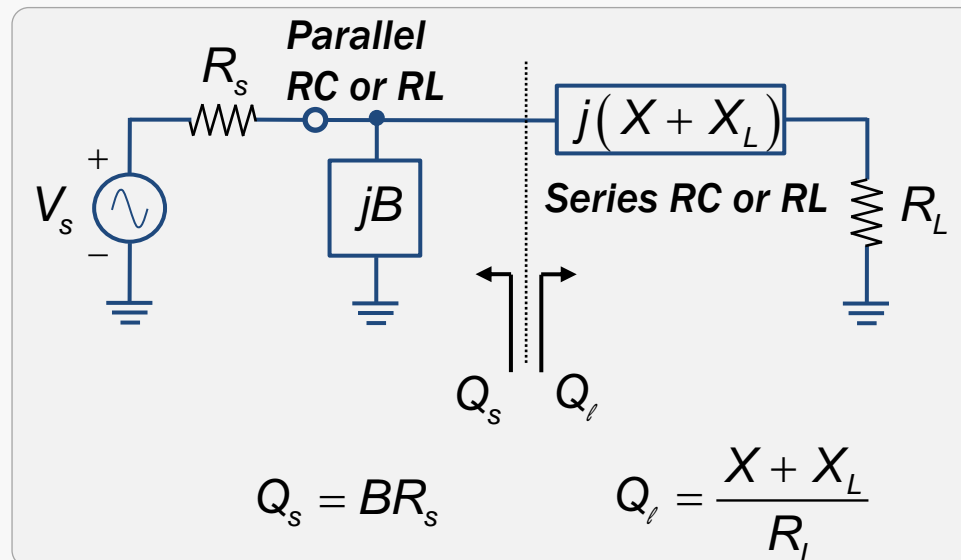When the impedances are matched, the imaginary part of the input admittance looking into the matching network is equal to zero.



L-Shape Matching – Case (b) $R_s > R_L$

Imaginary part: $(X + X_L) - BR_s R_L = 0$ $\frac{X + X_L}{R_L} = Q_\ell = BR_s = Q_s = Q$

Real part: $BR_s (X + X_L) = R_s - R_L$

→ $Q^2 R_L = R_s - R_L$ $Q = \pm \sqrt{\frac{R_s}{R_L} - 1}$

Choose $Q = Q_s = Q_\ell = +\sqrt{\frac{R_s}{R_L} - 1}$


When Q is chosen, X and B are also decided.

$$B = \frac{Q}{R_s} = \frac{1}{R_s} \sqrt{\frac{R_s}{R_L} - 1} \quad (>0, \text{ capacitance})$$

$$X = R_L Q - X_L = R_L \sqrt{\frac{R_s}{R_L} - 1} - X_L \quad \begin{array}{l} (>0, \text{ inductance}) \\ (<0, \text{ capacitance}) \end{array}$$


Series-to-Parallel Transformation

- Series-to-Parallel transformation

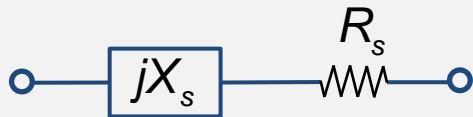

$$Q_s = \frac{X_s}{R_s}$$

$$Z_s = R_s + jX_s$$

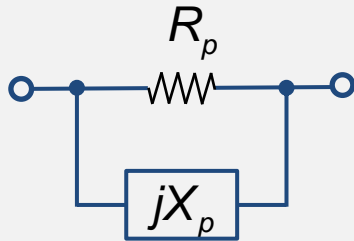

$$Q_p = \frac{R_p}{X_p}$$

$$Z_p = \frac{R_p \cdot jX_p}{R_p + jX_p}$$



$$Q_s = Q_p = Q = \frac{X_s}{R_s} = \frac{R_p}{X_p}$$

$$Z_s = Z_p = R_s + jX_s = \frac{R_p \cdot jX_p}{R_p + jX_p}$$


$$R_s (1 + Q^2) = R_p$$

Matching Bandwidth (I)

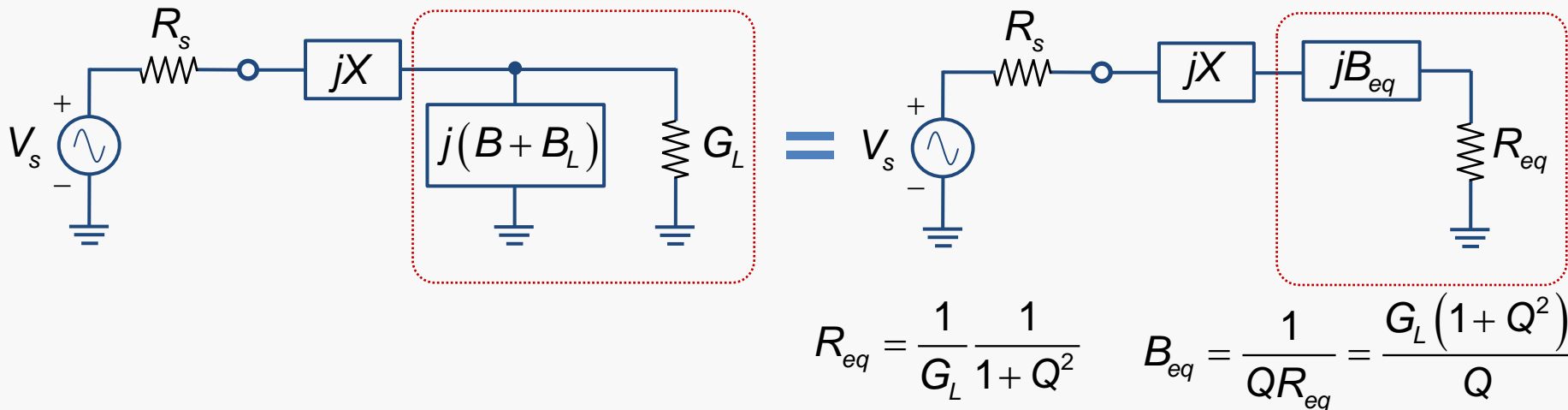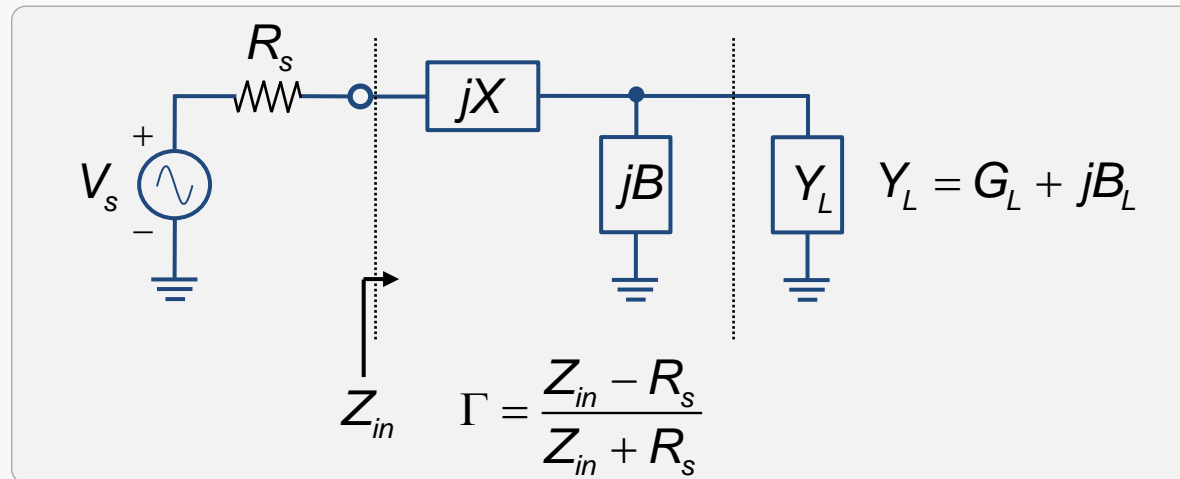➤ Case (a) $R_s < \frac{1}{G_L}$ (or $R_s < R_L$)



Matching Bandwidth (II)

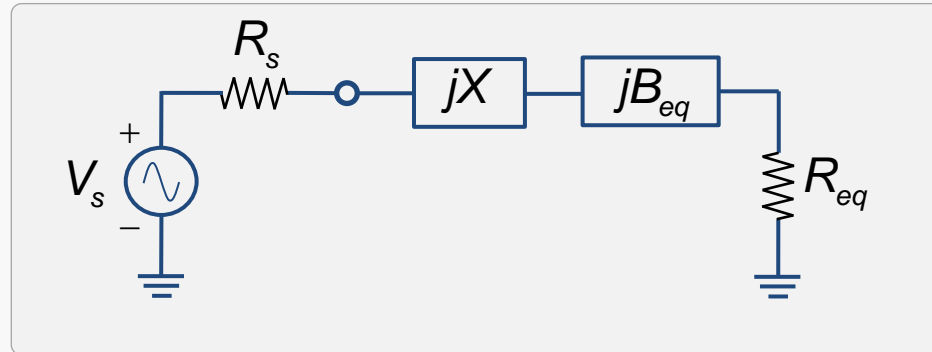

Impedance matching at $\omega = \omega_0$

Series resonant circuit

$$Z_{in}(\omega = \omega_0) = jX + \frac{1}{jB_{eq}} + R_{eq} = R_s$$


Imaginary part: $jX + \frac{1}{jB_{eq}} = 0 \quad \Rightarrow \quad XB_{eq} = 1$

Let $X = \omega_0 L$ and $B_{eq} = \omega_0 C$, where $\omega_0 = \frac{1}{\sqrt{LC}}$

Real part: $R_{eq} = R_s \quad \Rightarrow \quad \frac{1}{G_L} \frac{1}{1 + Q^2} = R_s \quad \text{and} \quad Q = \pm \sqrt{\frac{1}{G_L R_s} - 1}$

Matching Bandwidth (III)

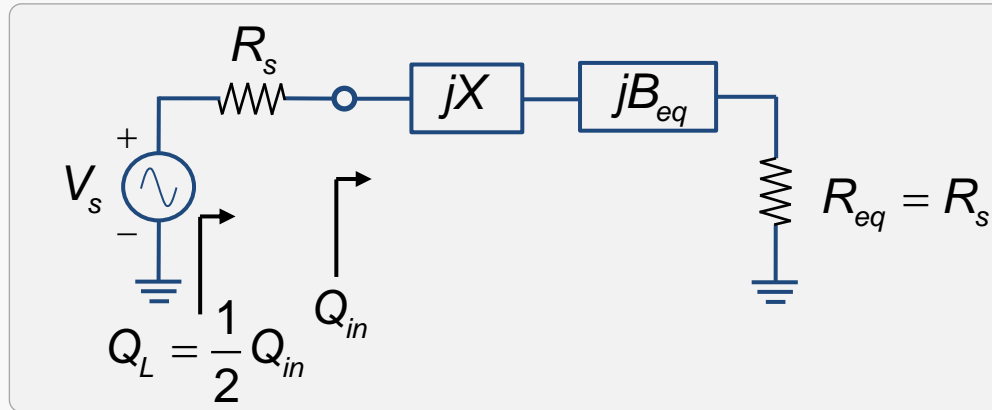- Define Q_L and Q_{in} for RLC resonator



- Find 3-dB bandwidth for $|\Gamma|$

Let $X = \omega L$ and $B_{eq} = \omega C$

as $\omega \rightarrow \omega_0$, let $\omega = \omega_0 + \Delta\omega$ where $\Delta\omega \rightarrow 0$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\Gamma = \frac{Z_{in} - R_s}{Z_{in} + R_s} = \frac{jX + \frac{1}{jB_{eq}}}{jX + \frac{1}{jB_{eq}} + 2R_s} \simeq \frac{2jL\Delta\omega}{2jL\Delta\omega + 2R_s}$$

$$Q_{in} = \frac{X}{R_{eq}} = R_s \cdot |Q| \cdot G_L (1 + Q^2) = |Q|$$

Matching Bandwidth (IV)

- 3-dB bandwidth for $|\Gamma|$ ($= 2\Delta\omega$) occurs when


$$2L\Delta\omega = 2R_s \quad \rightarrow \quad 2\Delta\omega = \frac{2R_s}{L} = \frac{2R_s\omega_0}{X}$$

3-dB Bandwidth in % = BW

$$BW = \frac{2\Delta\omega}{\omega_0} = \frac{2R_s}{X} = \frac{2}{|Q|} = \frac{1}{Q_L} = \frac{2}{\sqrt{\frac{1}{R_s G_L} - 1}}$$

- Similarly, for case (b)

$$BW = \frac{1}{Q_L} = \frac{2}{|Q|} = \frac{2}{\sqrt{\frac{1}{R_s G_L} - 1}}$$

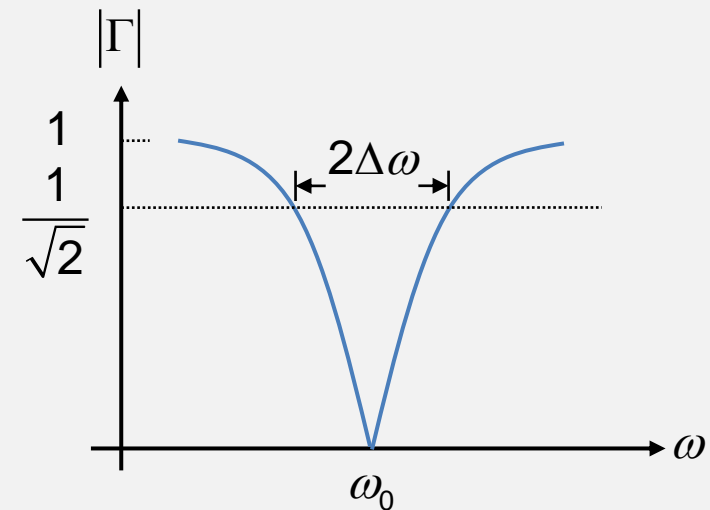

- Case (a)

$$R_s < \frac{1}{G_L}$$

$$|Q| = \sqrt{\frac{1}{R_s G_L} - 1}$$

- Case (b)

$$R_s > R_L$$

$$|Q| = \sqrt{\frac{R_s}{R_L} - 1}$$


Example – L-Shape Matching (I)

- Find element values and 3-dB fractional bandwidth of the two-element matching network.

$$R_s < \frac{1}{G_L}, \text{ choose case (a)}$$

$$Q = \pm \sqrt{\frac{1}{R_s G_L} - 1} = \pm \sqrt{\frac{2000}{50} - 1}$$


$$= \pm 6.245$$

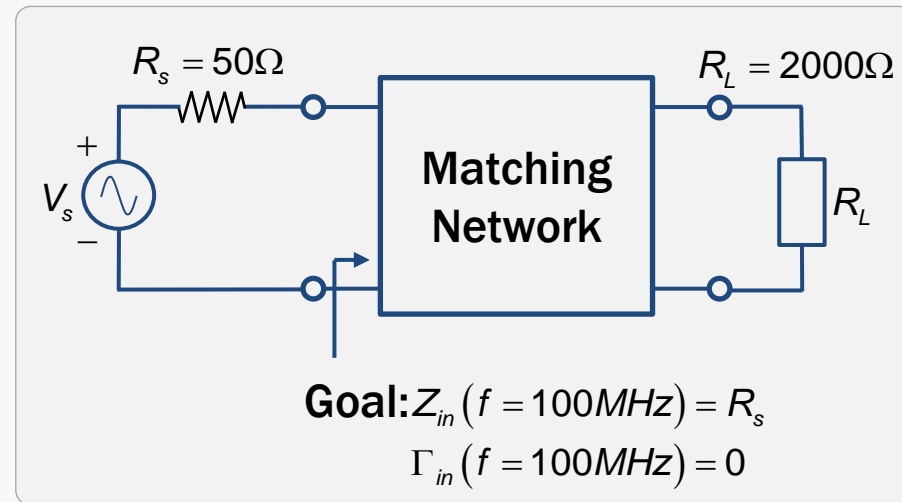

➤ **1st Solution:** choose $Q = +6.245$

$$\rightarrow \begin{cases} X = R_s Q = 50 \cdot 6.245 = 2\pi \cdot 100 \times 10^6 \cdot L \\ B = G_L Q - B_L = 6.245/2000 - 0 = 2\pi \cdot 100 \times 10^6 \cdot C \end{cases}$$
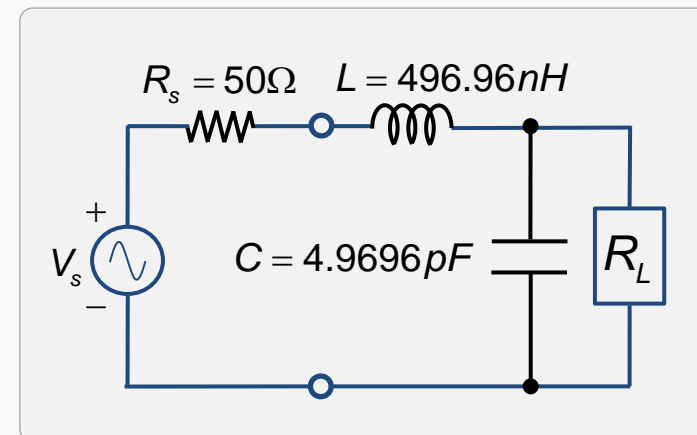
$$\rightarrow \begin{cases} L = 496.96 \times 10^{-9} (H) = 496.96 \text{ (nH)} \\ C = 4.9696 \times 10^{-12} (F) = 4.9696 \text{ (pF)} \end{cases}$$





Example – L-Shape Matching (II)

➤ **2nd Solution:** choose $Q = -6.245$

$$\rightarrow \begin{cases} X = R_s Q = 50 \cdot (-6.245) = -1/(2\pi \cdot 100 \times 10^6 \cdot C) \\ B = G_L Q - B_L = (-6.245)/2000 - 0 = -1/(2\pi \cdot 100 \times 10^6 \cdot L) \end{cases}$$


$$\rightarrow \begin{cases} C = 5.097 \times 10^{-12} (F) = 5.097 \text{ (pF)} \\ L = 509.7 \times 10^{-9} (H) = 509.7 \text{ (nH)} \end{cases}$$

$$BW_{3dB} = \frac{1}{Q_L} = \frac{2}{|Q|} = \frac{2}{6.245} = 32\% \quad \text{and} \quad BW_{9dB} \approx 16\%, \quad BW_{15dB} \approx 8\%$$

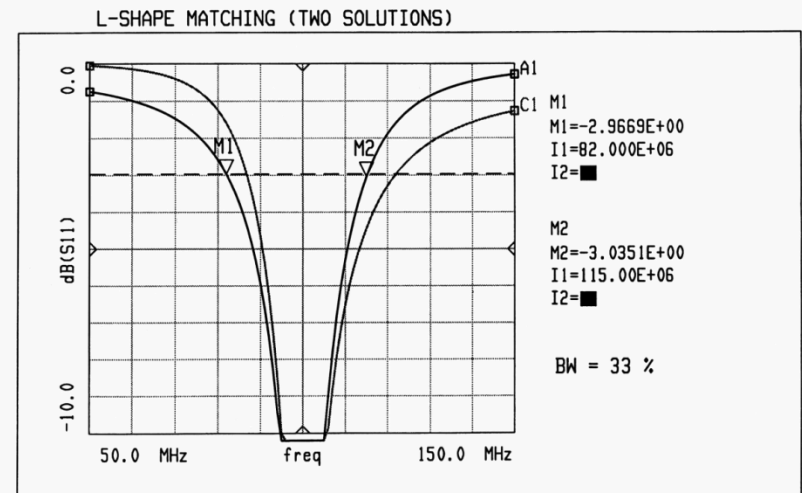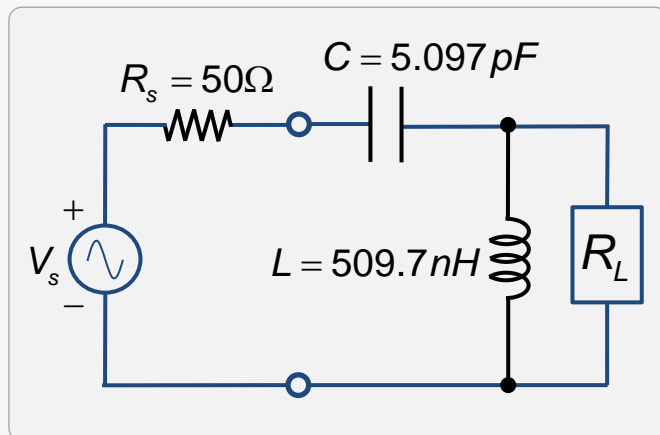


Three Elements Matching (High Q)


➤ Case (a) Pi-Shape Matching

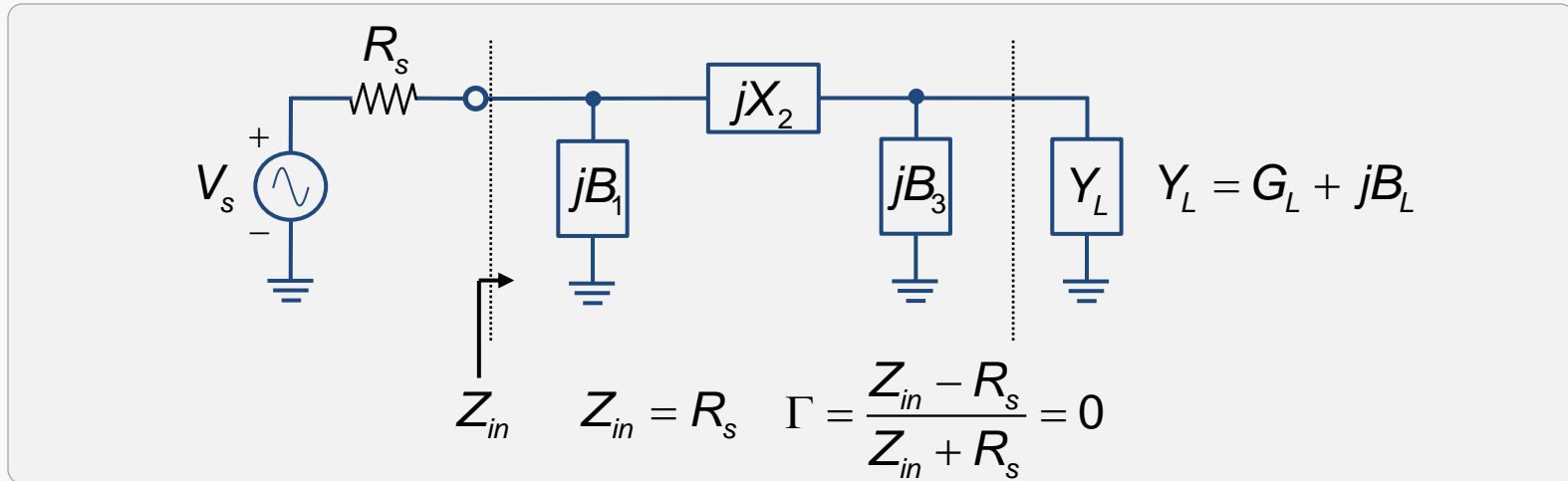

➤ Case (b) T-Shape Matching

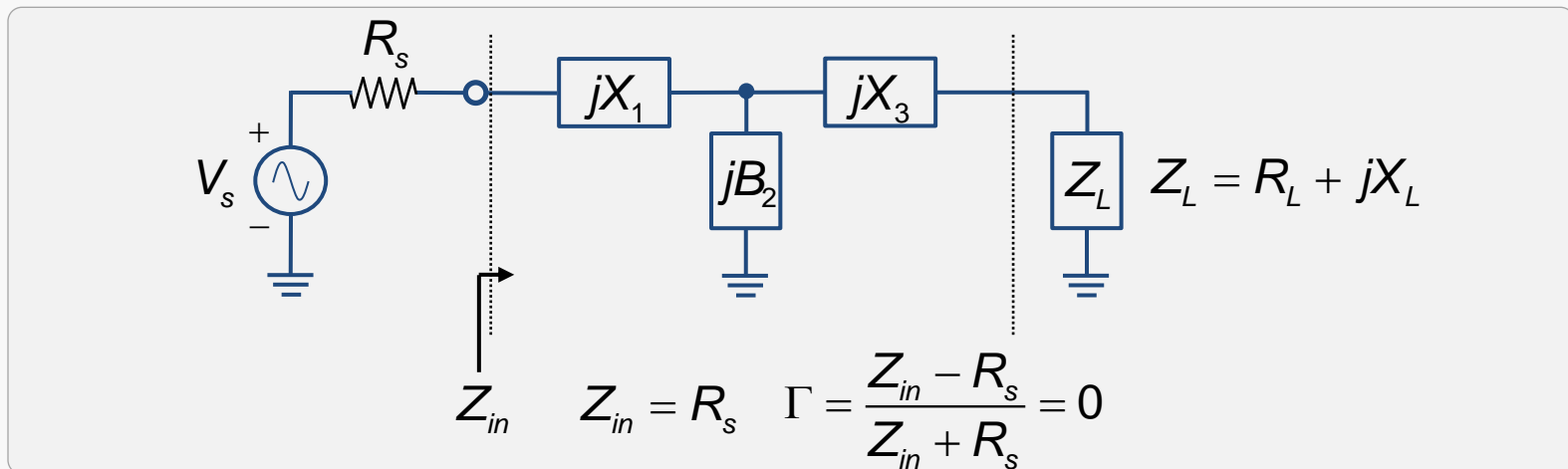


Pi-Shape Matching

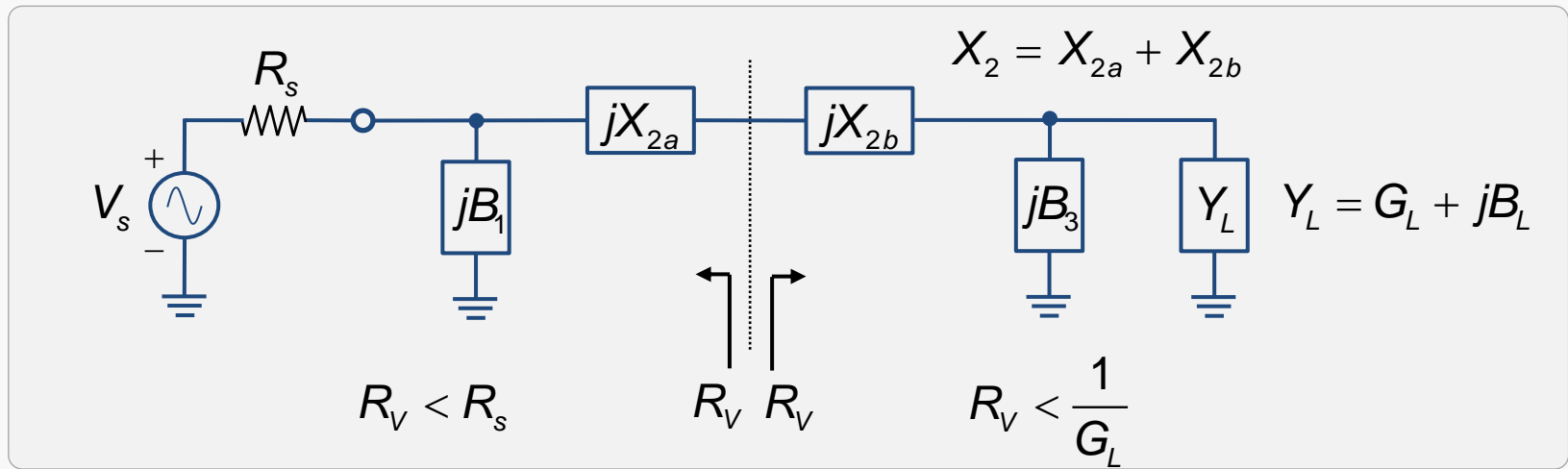


R_V : virtual resistance (designed by yourself)

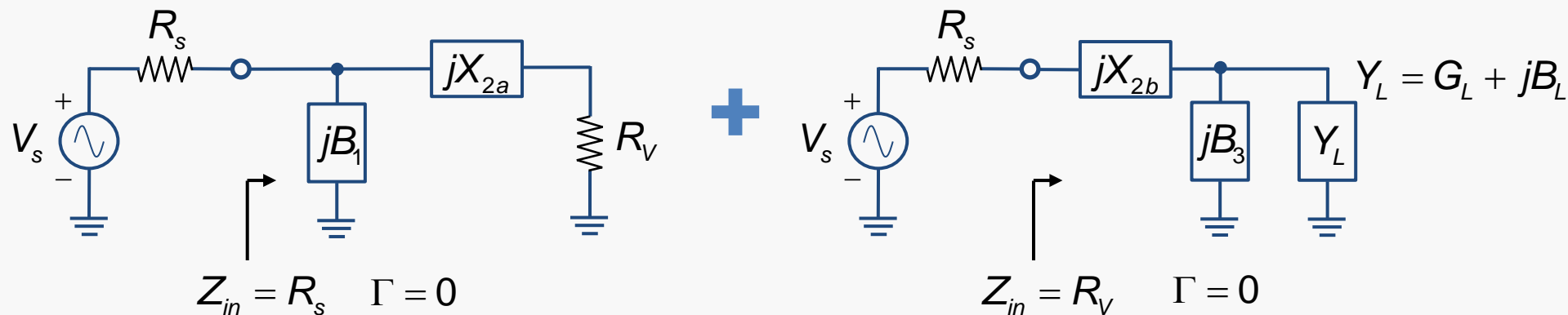
Splitting into 2 “L-shape” matching networks



Pi-Shape Matching

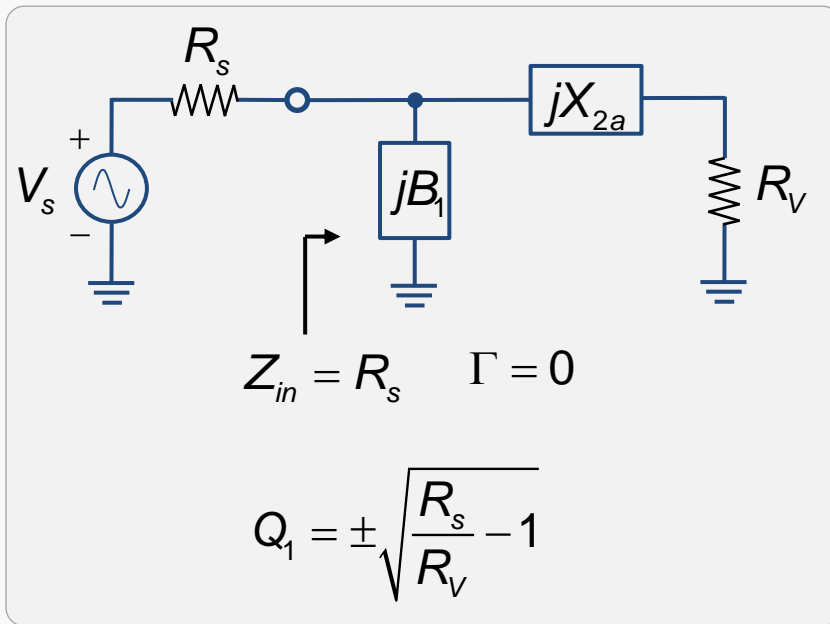

+

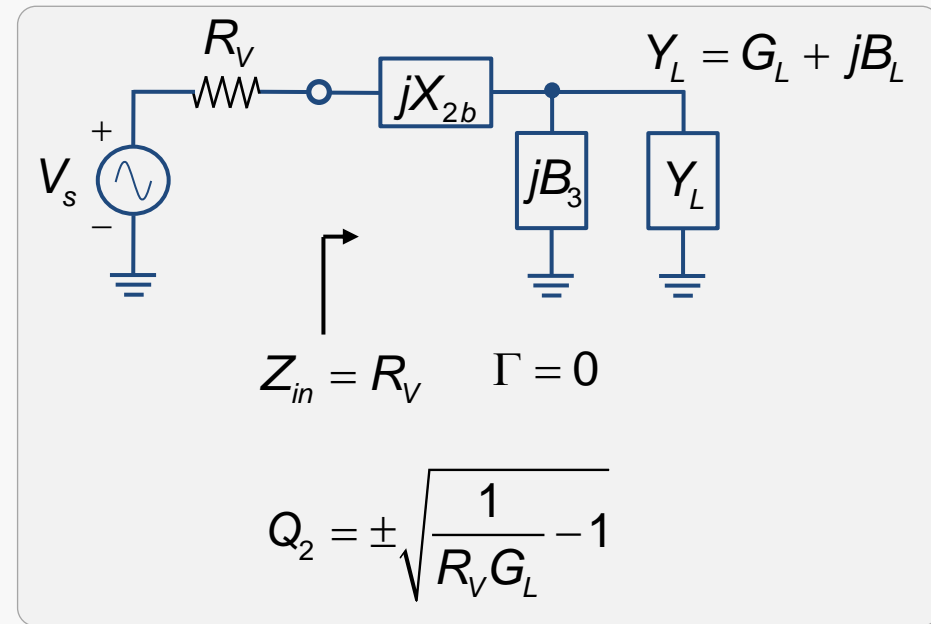


Since R_V is small, you can get a high Q

$$BW_1 = \frac{2}{|Q_1|}$$

$$BW_2 = \frac{2}{|Q_2|}$$


$$BW \simeq \min(BW_1, BW_2)$$

T-Shape Matching

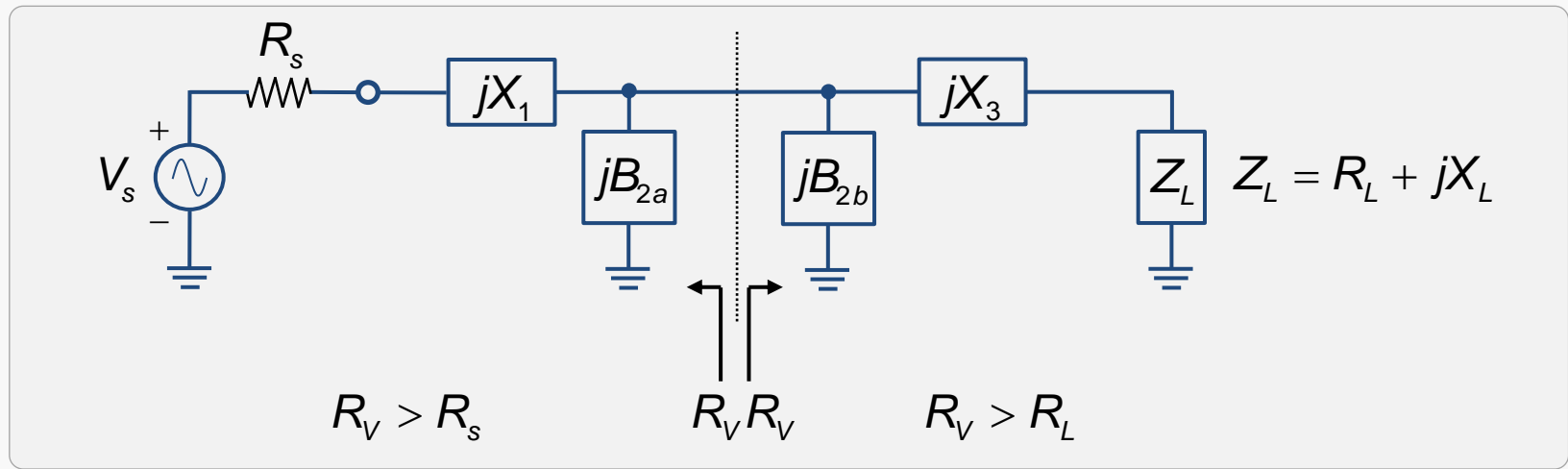


R_V : virtual resistance (designed by yourself)

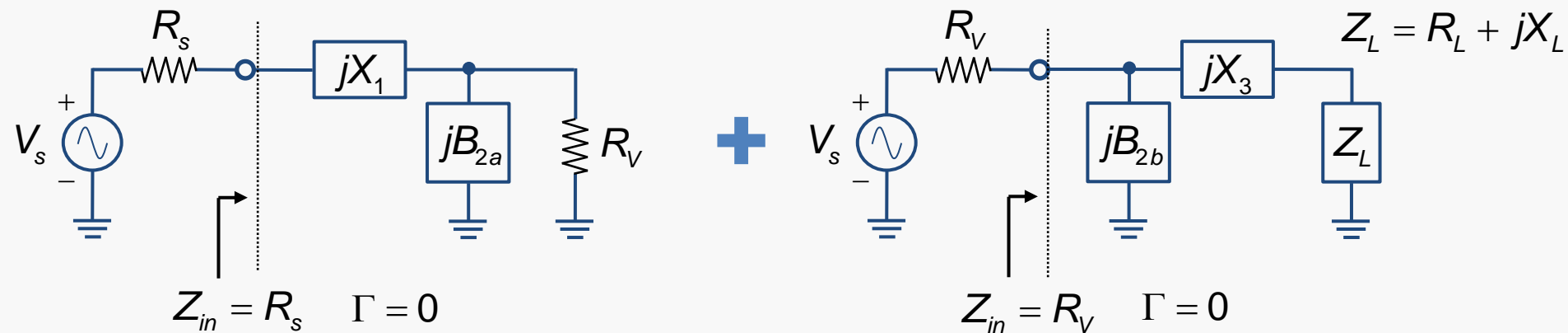Splitting into 2 “L-shape” matching networks




T-Shape Matching

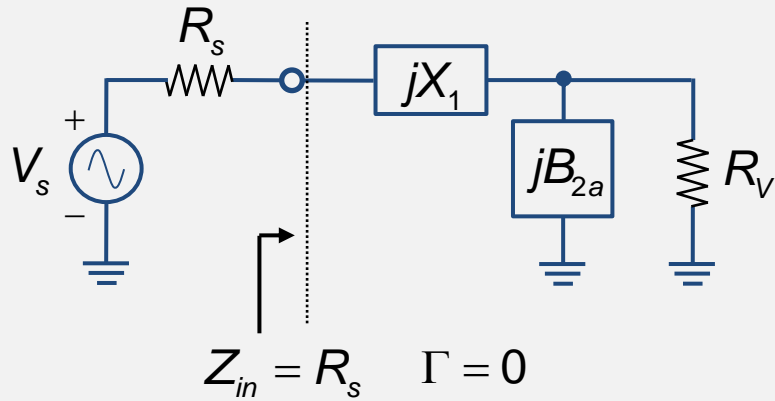

$$Q_1 = \pm \sqrt{\frac{R_V}{R_s} - 1}$$

+

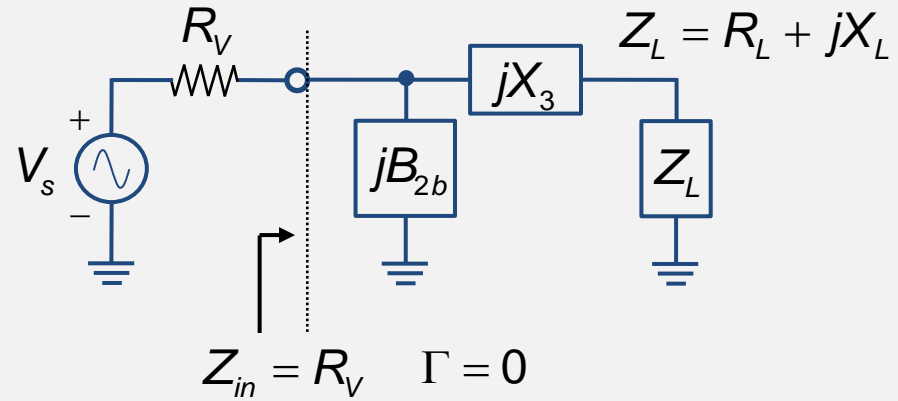

$$Q_2 = \pm \sqrt{\frac{R_V}{R_L} - 1}$$

Since R_V is large, you can get a high Q


$$BW_1 = \frac{2}{|Q_1|}$$

$$BW_2 = \frac{2}{|Q_2|}$$

$$BW \simeq \min(BW_1, BW_2)$$

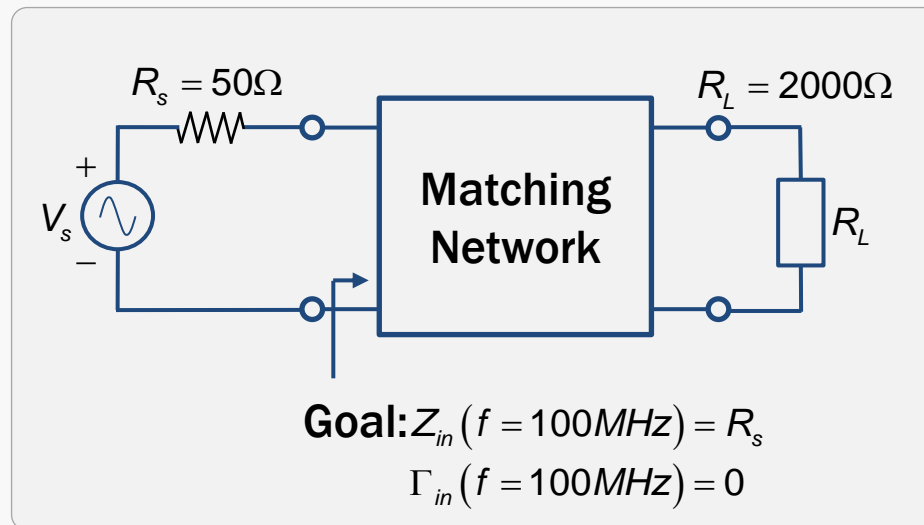Example – Pi and T Matching Networks

- Use Pi and T matching networks to achieve a matching BW<5%.




Example – Pi Matching Network (I)


➤ Pi-section matching network

$$Q = \max(|Q_1|, |Q_2|) = \max(\sqrt{50/R_v} - 1, \sqrt{2000/R_v} - 1) = \sqrt{2000/R_v} - 1$$
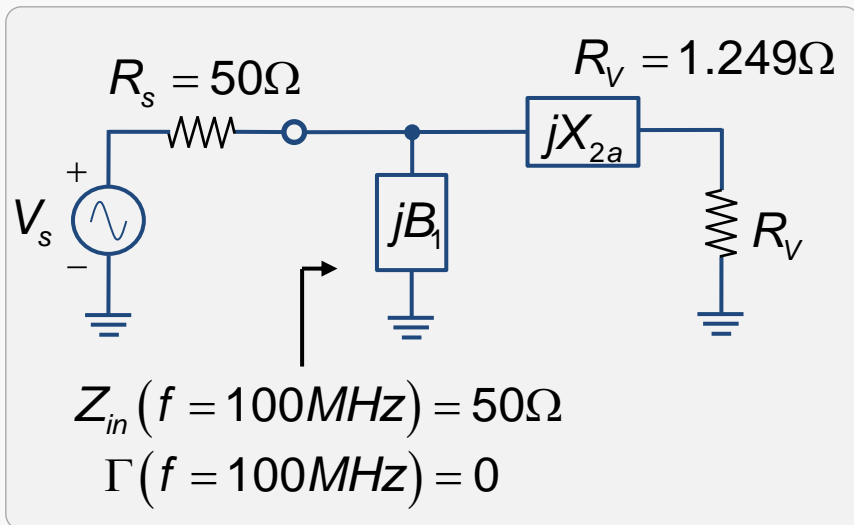
$$BW = \frac{2}{\sqrt{(2000/R_v) - 1}} \leq 5\% \Rightarrow R_v \leq 1.249 \Omega$$




+

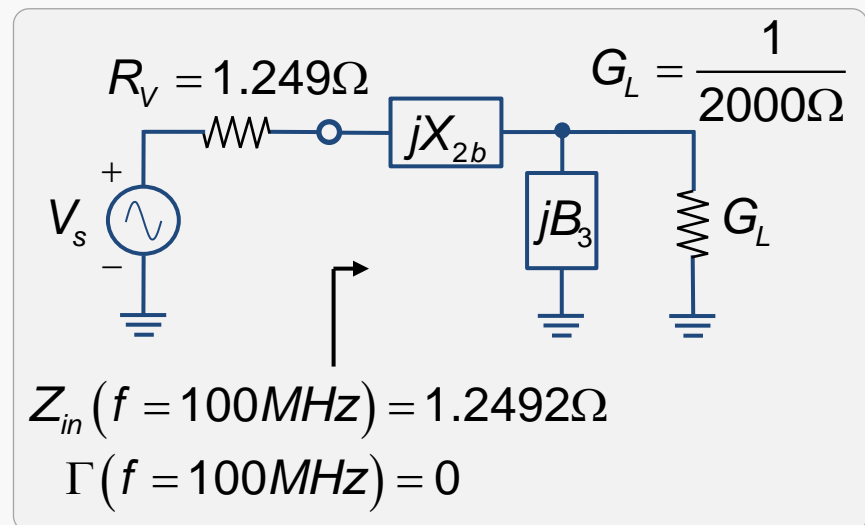

$$Q_1 = \pm \sqrt{\frac{R_s}{R_v} - 1} = \pm \sqrt{\frac{50}{1.2492} - 1} = \pm 6.247$$

$$Q_2 = \pm \sqrt{\frac{1}{R_v G_L} - 1} = \pm \sqrt{\frac{2000}{1.2492} - 1} = \pm 40$$


Example – Pi Matching Network (II)

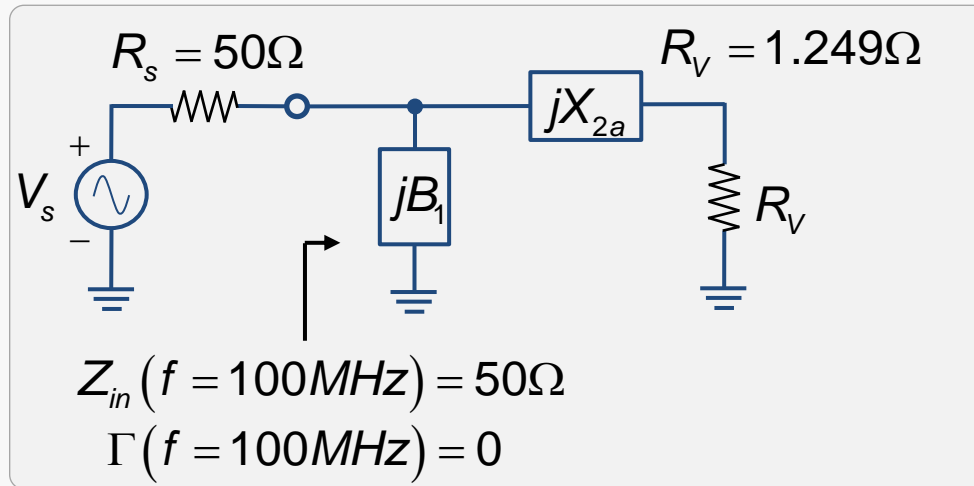

$$Q_1 = +6.247 \rightarrow \begin{cases} B_1 = \frac{Q_1}{R_s} = \omega_0 C & C = 198.85\text{pF} \\ X_{2a} = R_V Q_1 = \omega_0 L & L = 12.42\text{nH} \end{cases}$$

$$Q_1 = -6.247 \rightarrow \begin{cases} B_1 = \frac{Q_1}{R_s} = \frac{-1}{\omega_0 L} & L = 12.74\text{nH} \\ X_{2a} = R_V Q_1 = \frac{-1}{\omega_0 C} & C = 203.95\text{pF} \end{cases}$$





Example – Pi Matching Network (III)

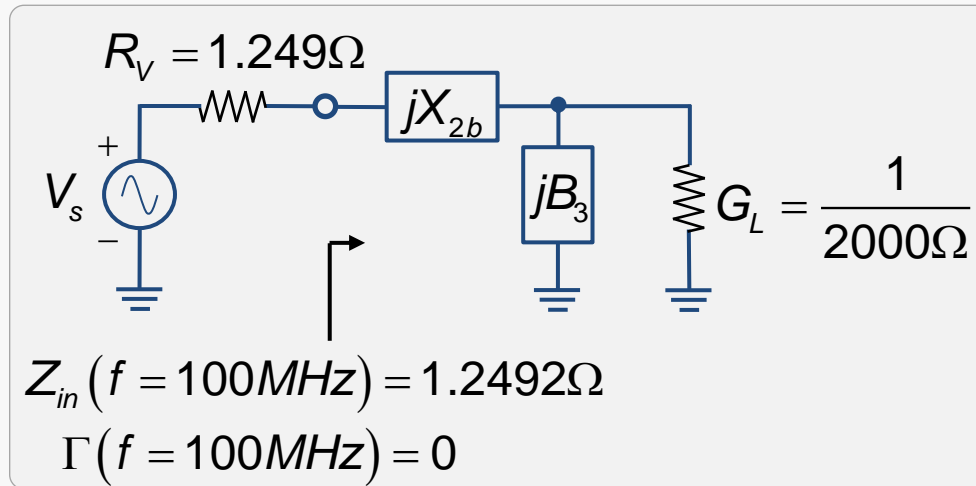

$$Q_2 = +40 \rightarrow \begin{cases} B_3 = G_L Q_2 - B_L = \omega_0 C & C = 31.83\text{pF} \\ X_{2b} = R_V Q_2 = \omega_0 L & L = 79.53\text{nH} \end{cases}$$


$$Q_2 = -40 \rightarrow \begin{cases} B_3 = G_L Q_2 - B_L = \frac{-1}{\omega_0 L} & L = 79.58\text{nH} \\ X_{2b} = R_V Q_2 = \frac{-1}{\omega_0 C} & C = 31.85\text{pF} \end{cases}$$

Example – Pi Matching Network (IV)

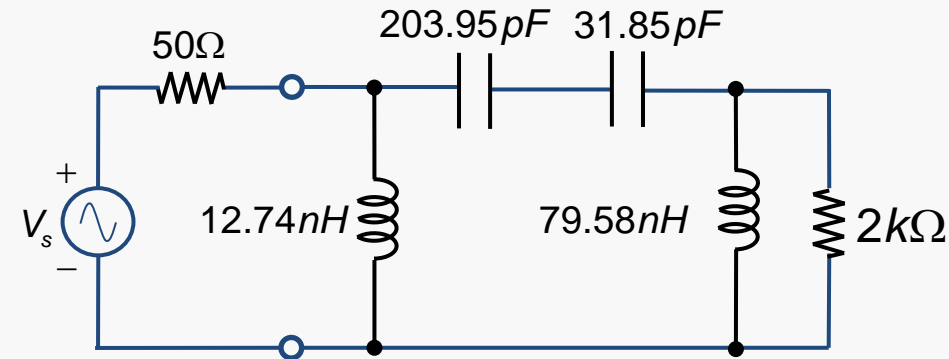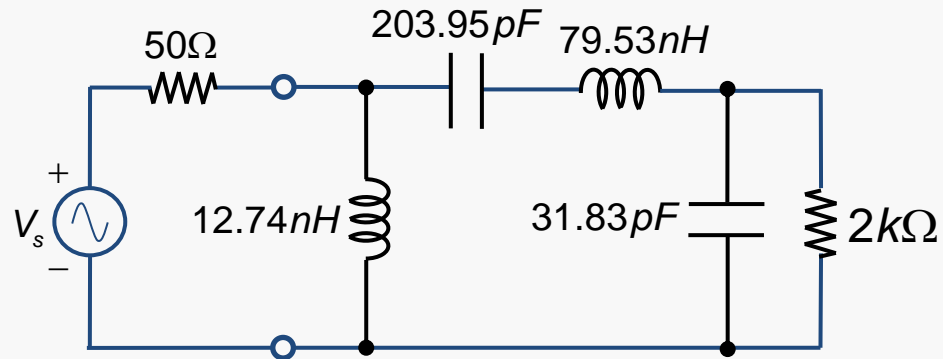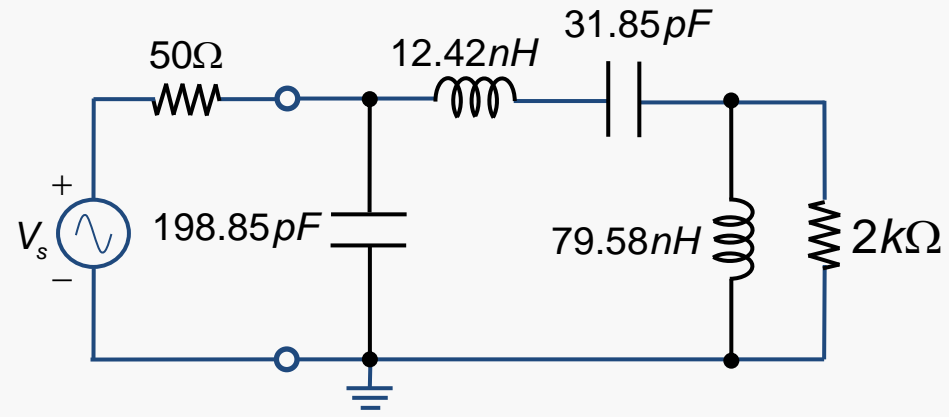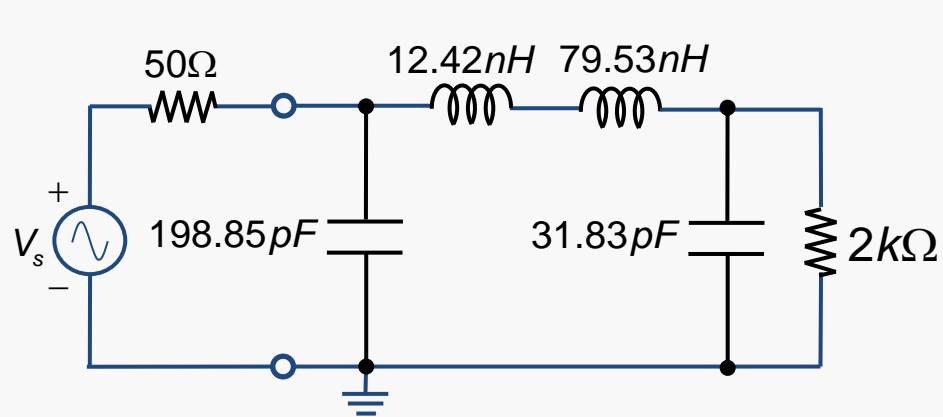

Example – Pi Matching Network (V)

PI-SHAPE MATCHING (FOUR SOLUTIONS)

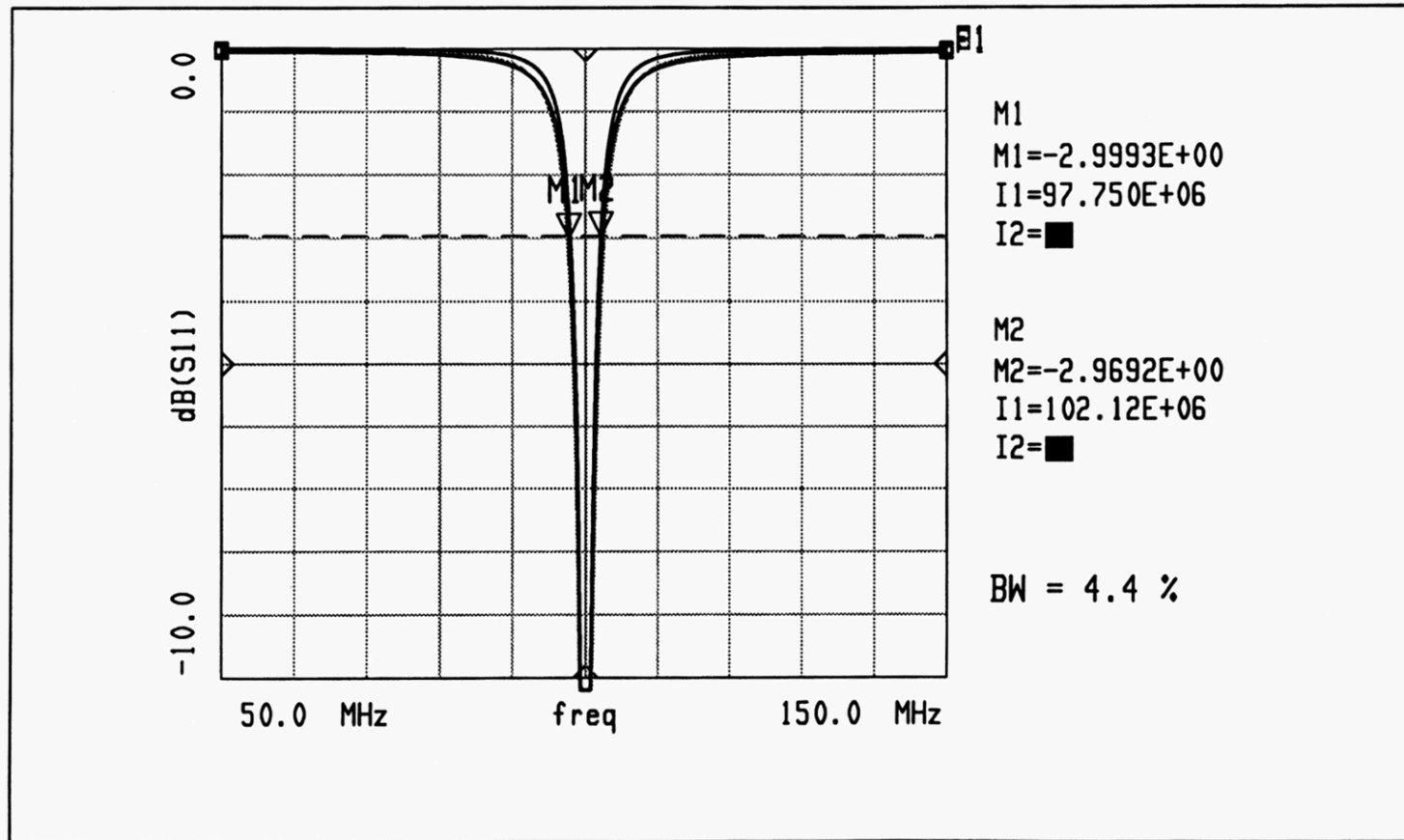


Example – T Matching Network (I)


➤ T-section matching network

$$Q = \max(|Q_1|, |Q_2|) = \max(\sqrt{(R_v/50) - 1}, \sqrt{(R_v/2000) - 1}) = \sqrt{(R_v/50) - 1}$$
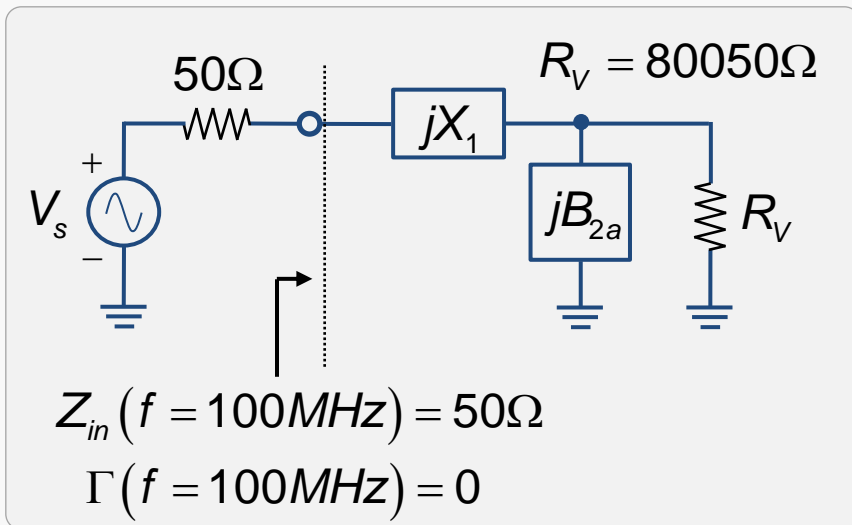
$$BW = \frac{2}{\sqrt{(R_v/50) - 1}} \leq 5\% \Rightarrow R_v \geq 80050 \Omega$$




+

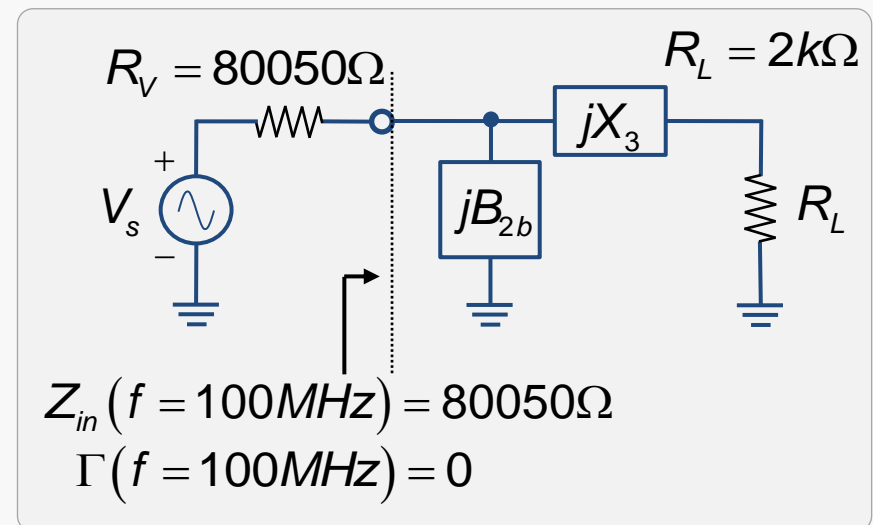

$$Q_1 = \pm \sqrt{\frac{R_v}{R_s} - 1} = \pm \sqrt{\frac{80050}{50} - 1} = \pm 40$$

$$Q_2 = \pm \sqrt{\frac{R_v}{R_L} - 1} = \pm \sqrt{\frac{80050}{2000} - 1} = \pm 6.247$$


Example – T Matching Network (II)

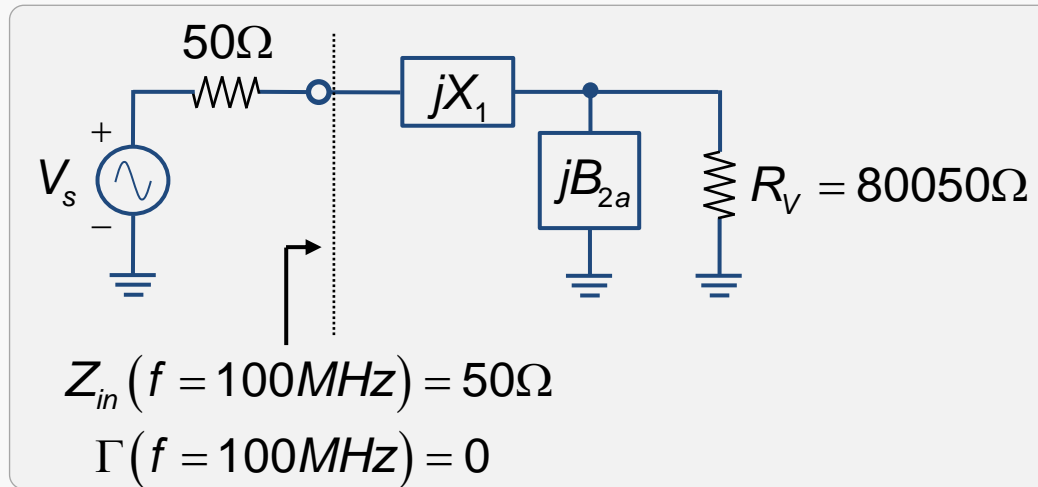

$$Q_1 = +40 \rightarrow \begin{cases} X_1 = R_s Q_1 = \omega_0 L & L = 3.183\mu\text{H} \\ B_{2a} = \frac{Q_1}{R_V} = \omega_0 C & C = 0.795\text{pF} \end{cases}$$

$$Q_1 = -40 \rightarrow \begin{cases} X_1 = R_s Q_1 = \frac{-1}{\omega_0 C} & C = 0.796\text{pF} \\ B_{2a} = \frac{Q_1}{R_V} = \frac{-1}{\omega_0 L} & L = 3.185\mu\text{H} \end{cases}$$





Example – T Matching Network (III)

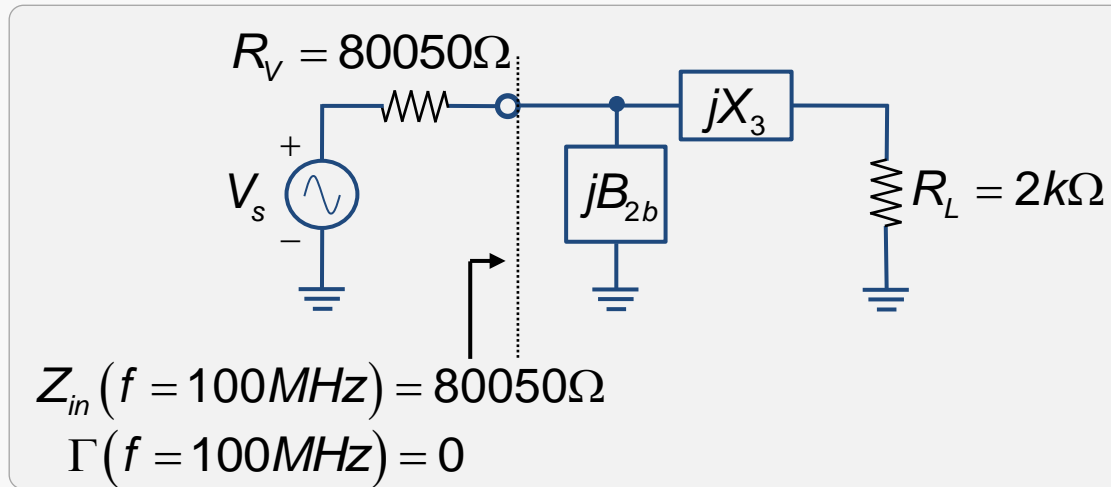

$$Q_2 = +6.247 \rightarrow \begin{cases} B_{2b} = \frac{Q_2}{R_V} = \omega_0 C & C = 0.124 pF \\ X_3 = R_L Q_2 - X_L = \omega_0 L & L = 19.884 \mu H \end{cases}$$


$$Q_2 = -6.247 \rightarrow \begin{cases} B_{2b} = \frac{Q_2}{R_V} = \frac{-1}{\omega_0 L} & L = 20.394 \mu H \\ X_3 = R_L Q_2 - X_L = \frac{-1}{\omega_0 C} & C = 0.127 pF \end{cases}$$

Example – T Matching Network (IV)

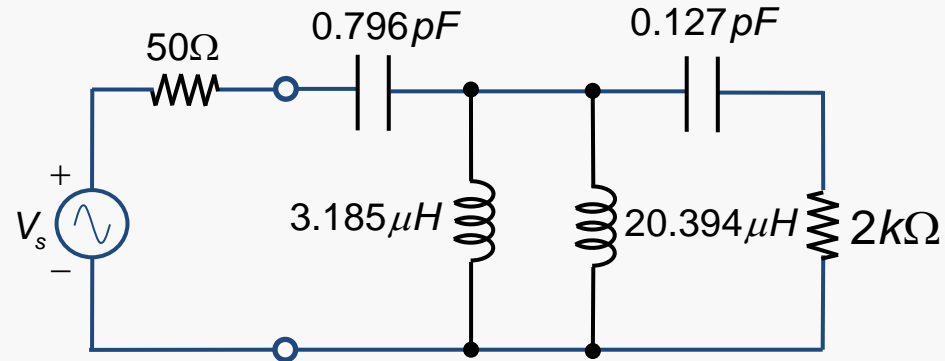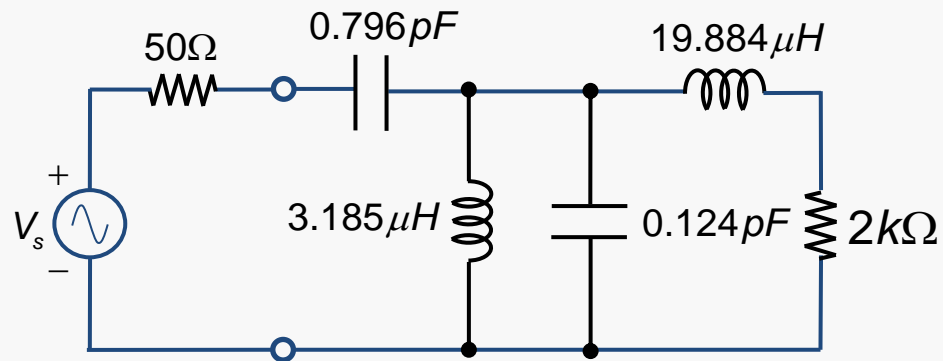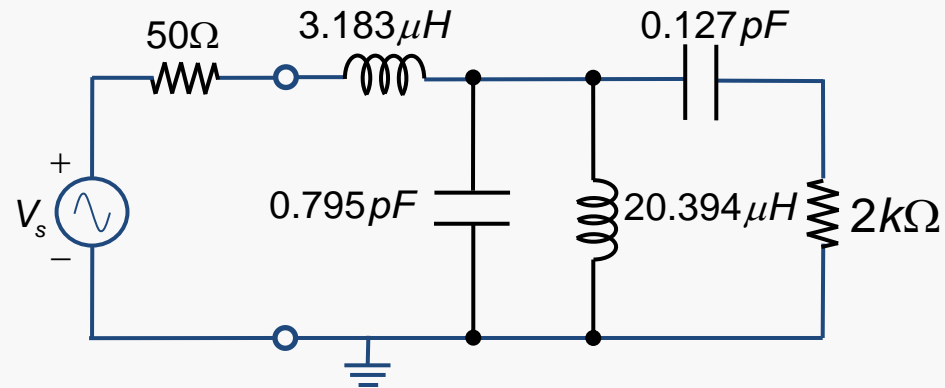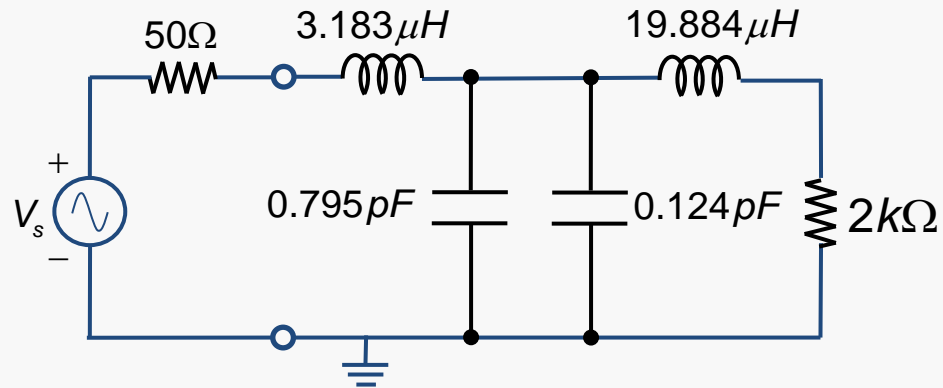


Example – T Matching Network (V)

T-SHAPE MATCHING (FOUR SOLUTIONS)

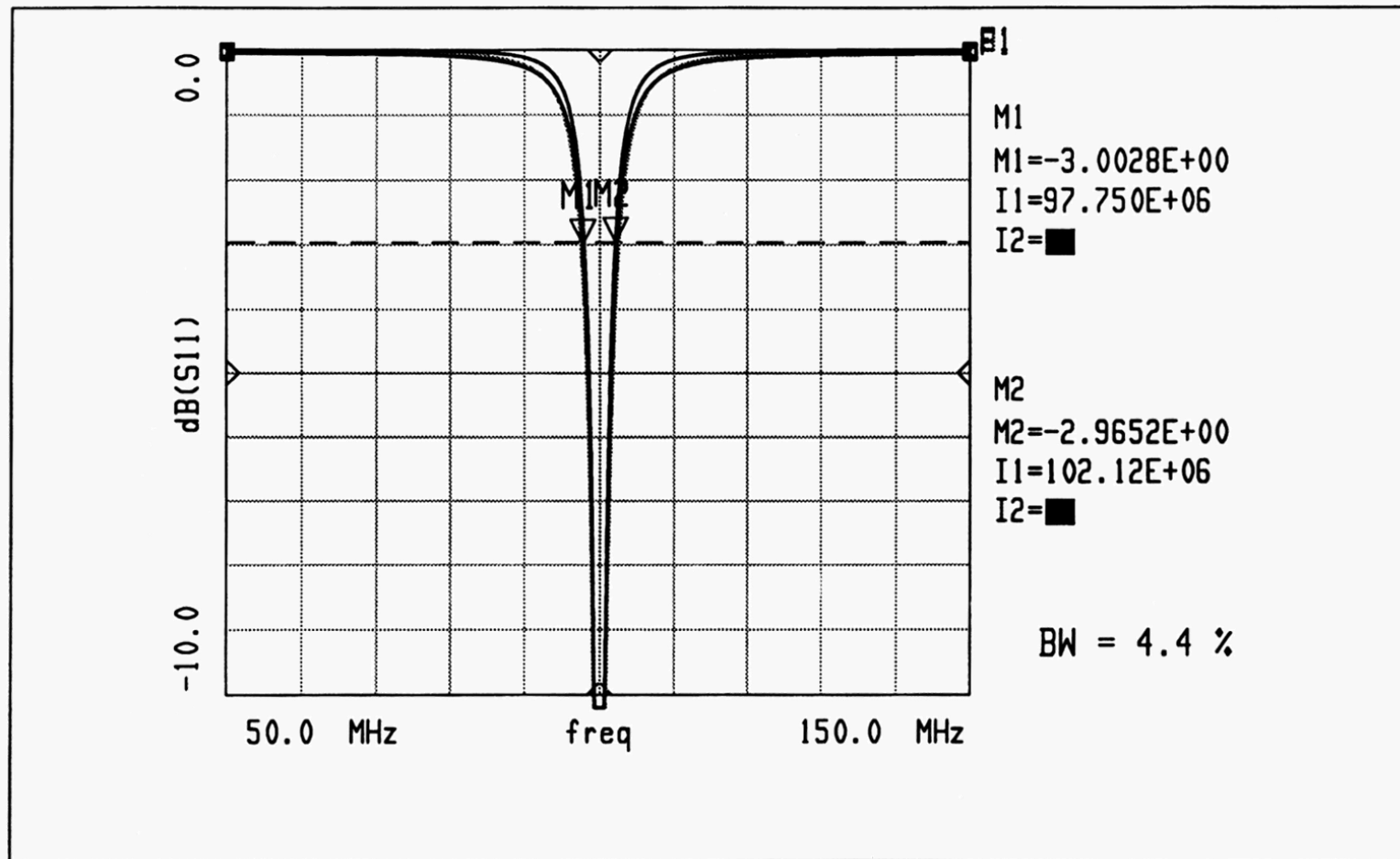


Cascaded L-Shape Matching (Low Q)


➤ Case (a) $R_s < R_V < \frac{1}{G_L}$

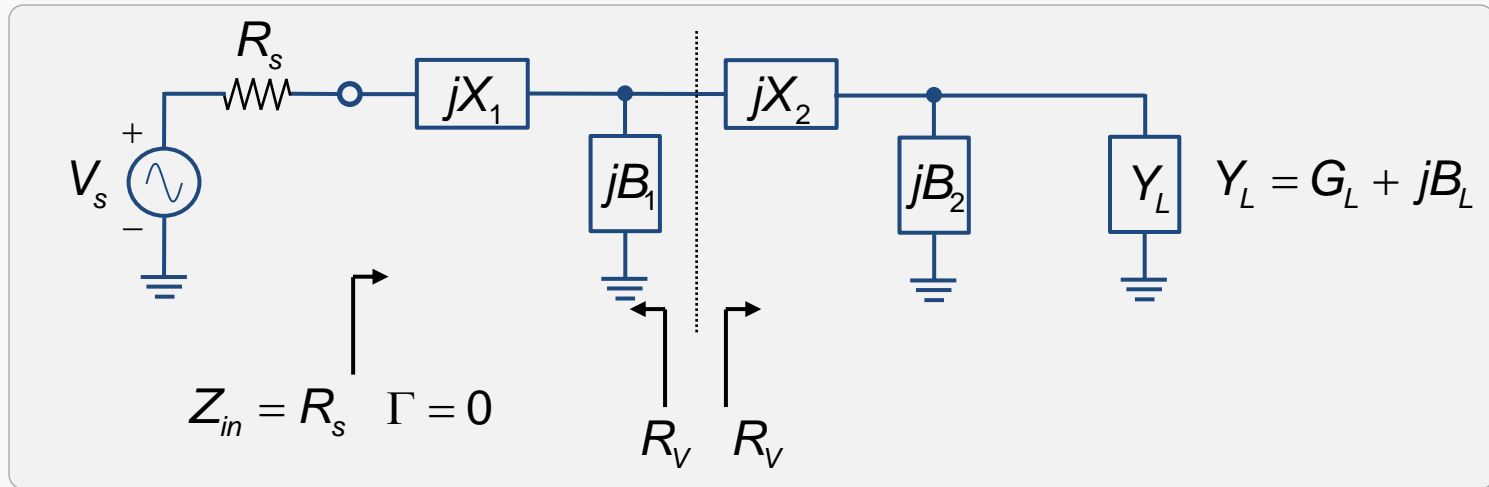

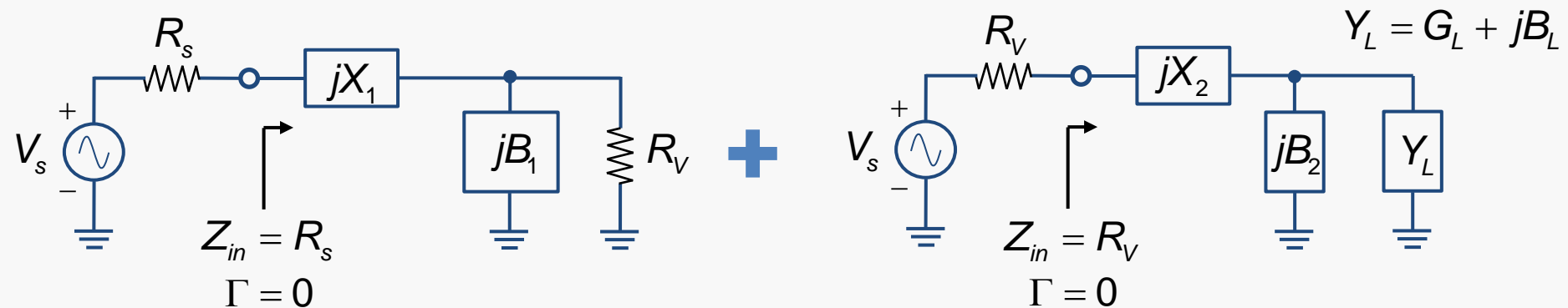Splitting into 2 “L-shape” matching networks




Cascaded L-Shape Matching (Low Q)

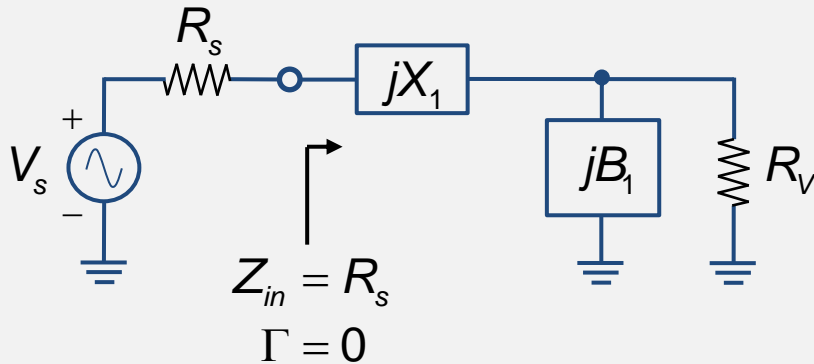

$$Q_1 = \pm \sqrt{\frac{R_V}{R_s} - 1}$$

+

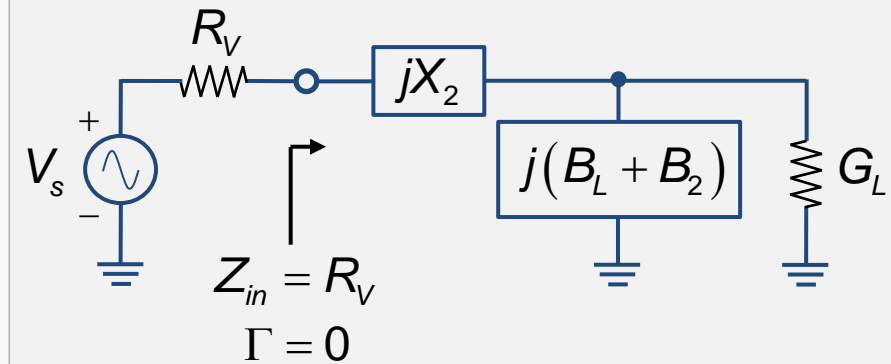

$$Q_2 = \pm \sqrt{\frac{1}{G_L R_V} - 1}$$


We want to have the maximum bandwidth (find minimum Q)

Let $|Q_1| = |Q_2| = Q \rightarrow R_V = \sqrt{\frac{R_s}{G_L}}$


$$BW \approx \frac{2}{Q\sqrt{2}} = \frac{\sqrt{2}}{Q} = \frac{\sqrt{2}}{\sqrt{\frac{1}{R_s G_L} - 1}}$$

Cascaded L-Shape Matching (Low Q)


➤ Case (b) $R_s > R_V > R_L$

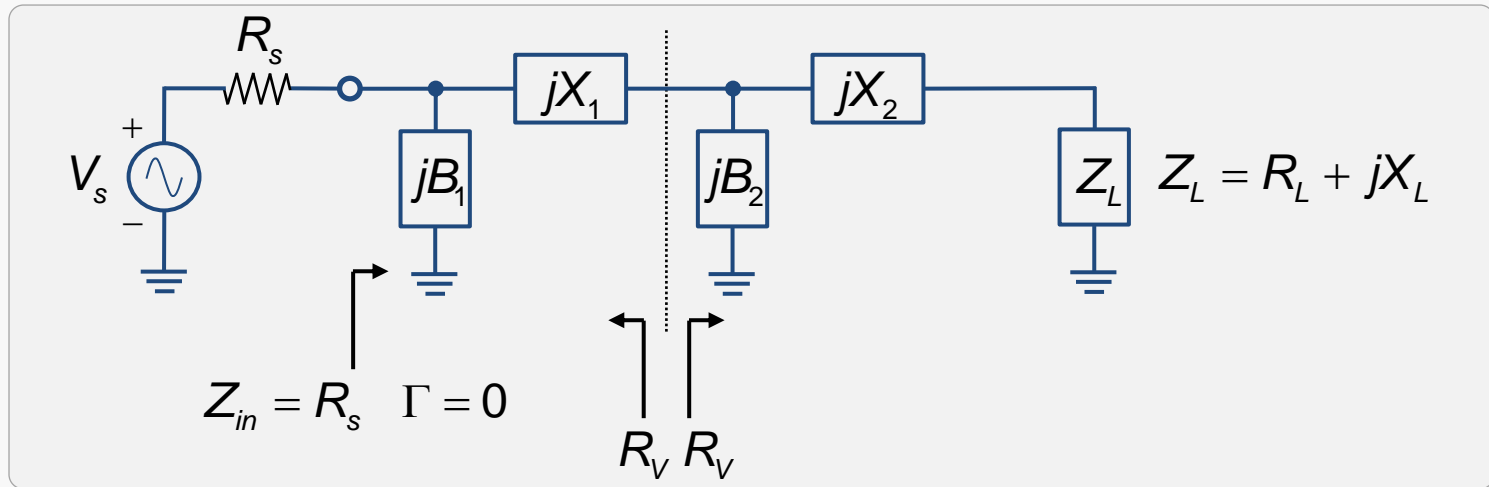

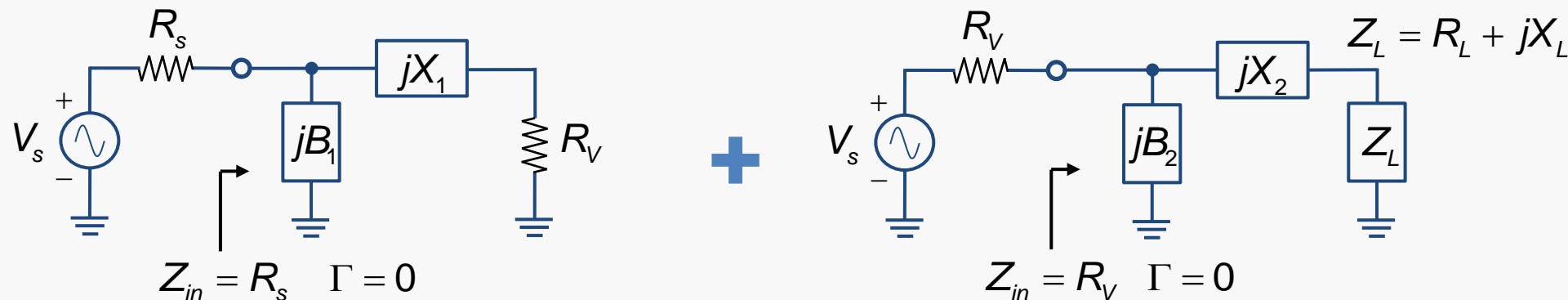Splitting into 2 "L-shape" matching networks




Cascaded L-Shape Matching (Low Q)

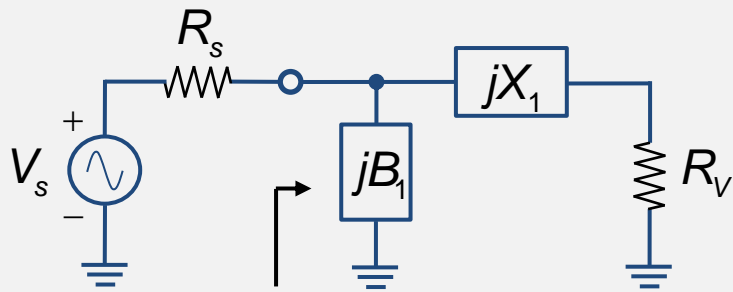

$$Z_{in} = R_s \quad \Gamma = 0$$

$$Q_1 = \pm \sqrt{\frac{R_s}{R_V} - 1}$$

+

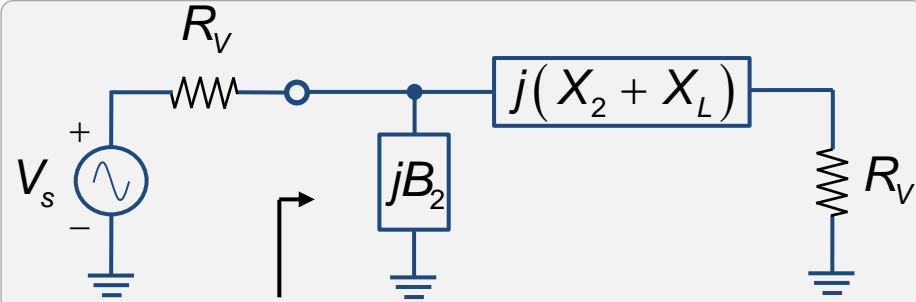

$$Z_{in} = R_V \quad \Gamma = 0$$

$$Q_2 = \pm \sqrt{\frac{R_V}{R_L} - 1}$$


We want to have the maximum bandwidth (find minimum Q)

Let $|Q_1| = |Q_2| = Q \rightarrow R_V = \sqrt{R_s R_L}$

$$BW \simeq \frac{2}{Q\sqrt{2}} = \frac{\sqrt{2}}{Q} = \frac{\sqrt{2}}{\sqrt{\frac{1}{\sqrt{R_s G_L}} - 1}}$$

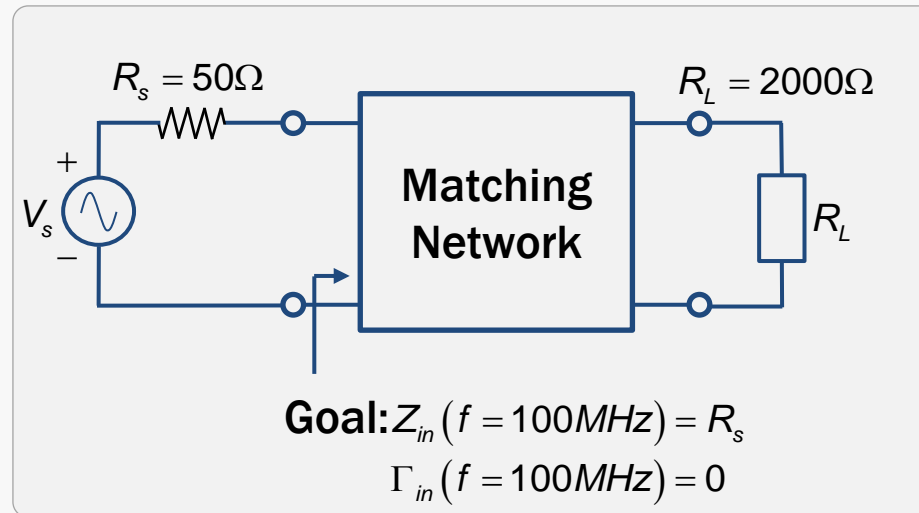Example – Cascaded L-Shape Matching (I)

- Use Cascaded L-shape matching networks to achieve $BW > 60\%$.




Choose R_V to let $R_s < R_V < R_L$


$$R_V = \sqrt{R_s R_L} = \sqrt{50 \cdot 2000} = 316.23$$

$$BW = \frac{\sqrt{2}}{\sqrt{\frac{1}{\sqrt{R_s G_L}} - 1}} = \frac{\sqrt{2}}{\sqrt{\sqrt{2000/50} - 1}} = 61.29\%$$

Example – Cascaded L-Shape Matching (II)

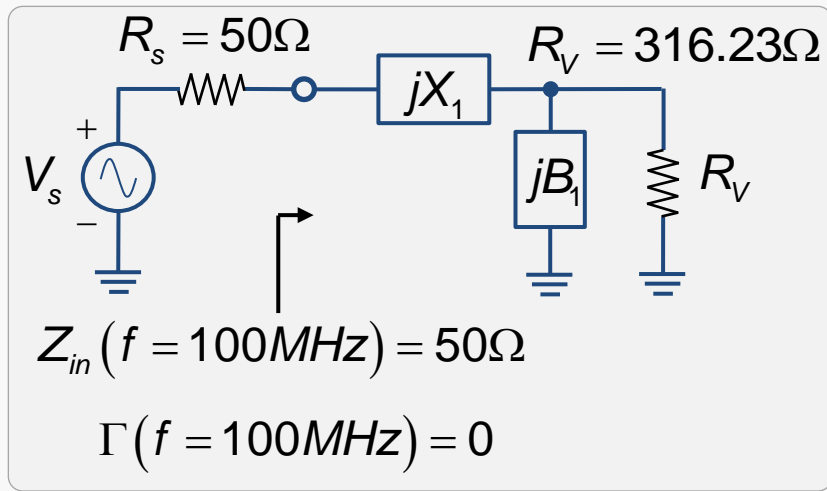

+

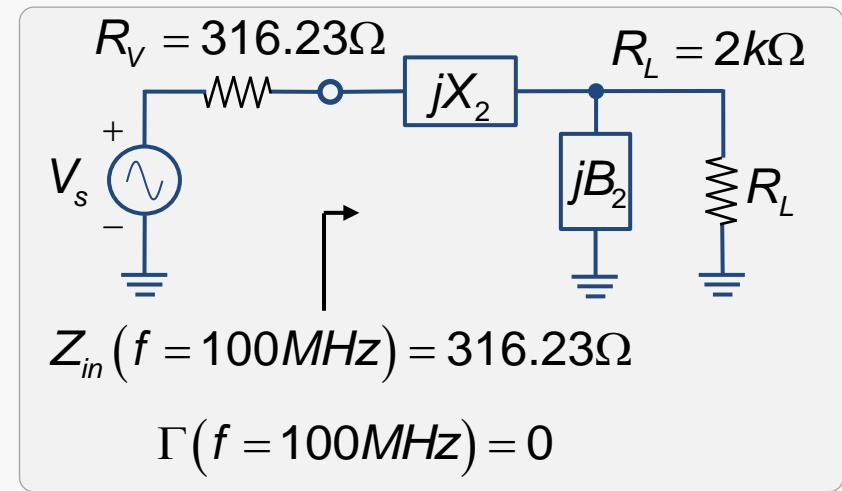

$$Q_1 = \pm \sqrt{\frac{R_V}{R_s} - 1} = \pm \sqrt{\frac{316.23}{50} - 1} = \pm 2.3075$$

$$Q_1 = +2.3075 \rightarrow \begin{cases} X_1 = R_s Q_1 = \omega_0 L & L = 183.63\text{nH} \\ B_1 = \frac{Q_1}{R_V} = \omega_0 C & C = 11.61\text{pF} \end{cases}$$





$$Q_1 = -2.3075 \rightarrow \begin{cases} X_1 = R_s Q_1 = \frac{-1}{\omega_0 C} & C = 13.79\text{pF} \\ B_1 = \frac{Q_1}{R_V} = \frac{-1}{\omega_0 L} & L = 218.11\text{nH} \end{cases}$$

$$Q_2 = \pm \sqrt{\frac{R_L}{R_V} - 1} = \pm \sqrt{\frac{2000}{316.23} - 1} = \pm 2.3075$$

$$Q_2 = +2.3075 \rightarrow \begin{cases} X_2 = R_V Q_2 = \omega_0 L & L = 1.161\mu\text{H} \\ B_2 = \frac{Q_2}{R_L} - B_L = \omega_0 C & C = 1.836\text{pF} \end{cases}$$


$$Q_2 = -2.3075 \rightarrow \begin{cases} X_2 = R_V Q_2 = \frac{-1}{\omega_0 C} & C = 2.181\text{pF} \\ B_2 = \frac{Q_2}{R_L} - B_L = \frac{-1}{\omega_0 L} & L = 1.379\mu\text{H} \end{cases}$$

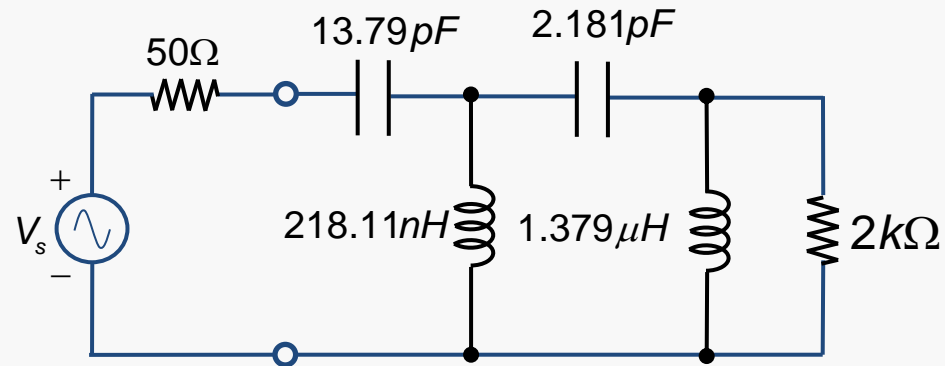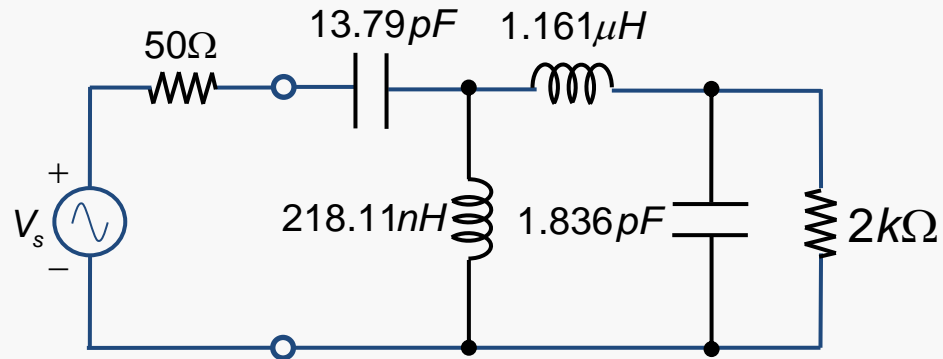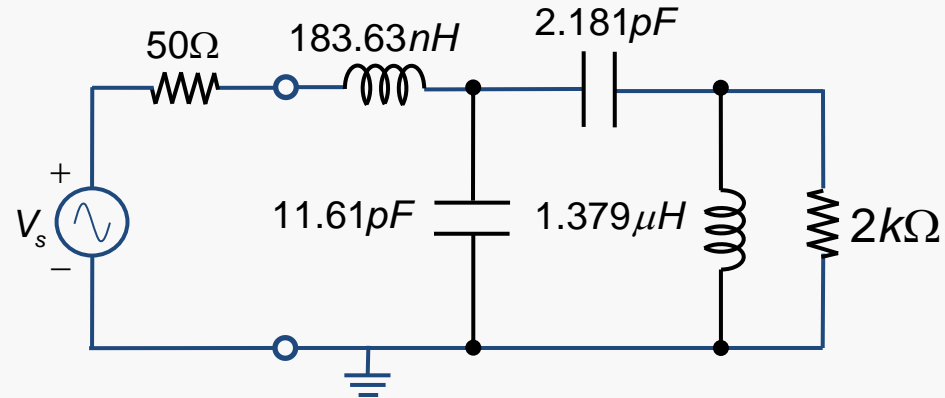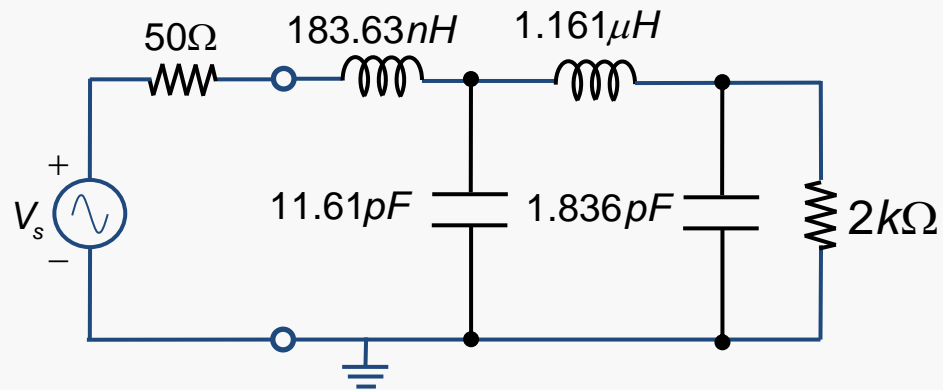Example – Cascaded L-Shape Matching (III)



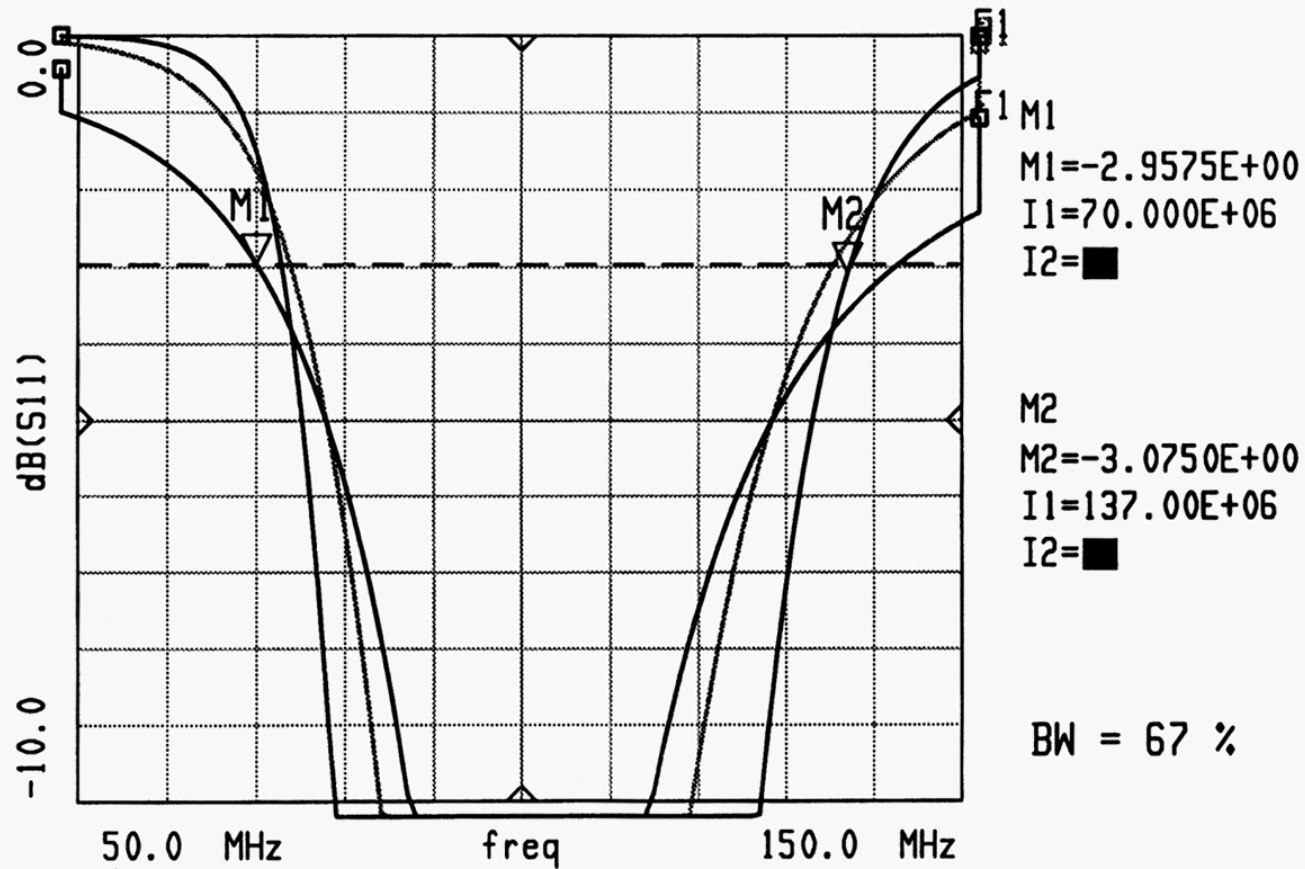
Example – Cascaded L-Shape Matching (IV)

CASCADED L-SHAPE MATCHING (FOUR SOLUTIONS)




Matching For Larger Bandwidth

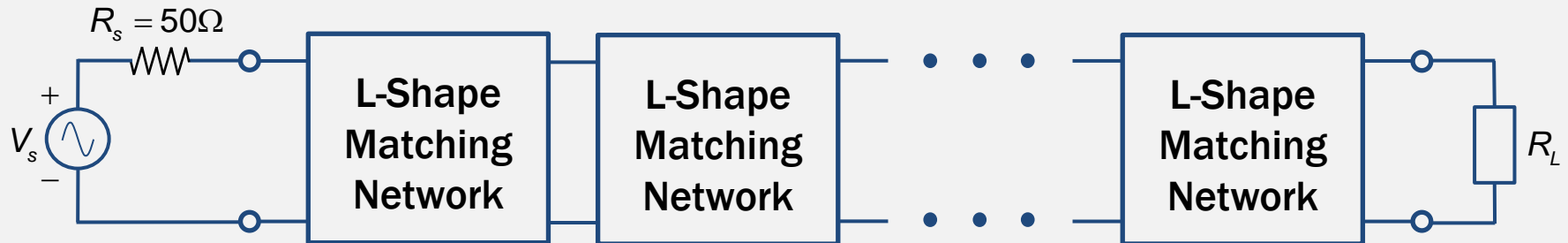- Use multi-section L-shape matching networks to extend BW.



CASCADED L-SHAPE MATCHING

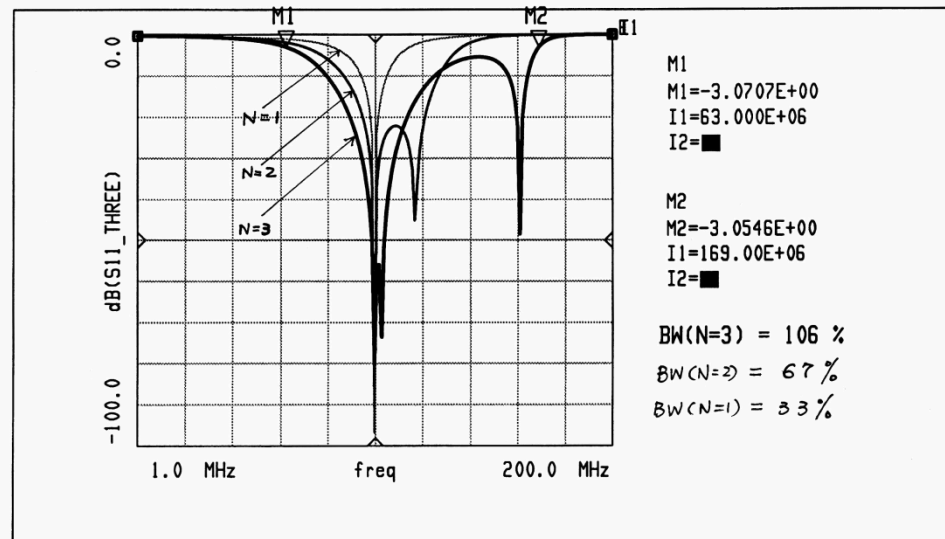

Summary

- Impedance matching is a procedure of transforming the complex load impedance Z_L to match with the source impedance Z_s or characteristics impedance Z_0 of the transmission line (Generally, $Z_s = R_s = Z_0$).
- The lossless lumped element matching networks that are commonly used include L-section, Pi-section, T-section, and cascaded L-section. L-section has medium but not adjustable matching bandwidth. Pi and T sections have rather small and adjustable matching bandwidth. Cascaded L-section can increase bandwidth as the number of stages increases.