

Fig 1. 4-Element lumped resonator. The L-C series elements determine the resonant frequency of the oscillator and hence the oscillating frequency.

The shunt capacitors are required to set the loaded Q of the resonator to at least 15 to ensure a compliant phase noise response.

Effective capacitance which resonates with the series inductor L_{series} is :-

$$C_e = \frac{1}{\frac{1}{C_{series}} + \frac{2C_{shunt}(\omega_0 R_o)^2}{(\omega_0 R_o C_{shunt})^2 + 1}}$$

R_o = input/output load resistance

Required inductance to resonate at f_o is given by :-

$$L_{series} = \frac{1}{\omega_0^2 C_e}$$

If we assume an unloaded Q of 120 for the inductor, therefore the effective Q, Q_e is given by : =

$$Q_e = \frac{1}{\frac{1}{Q_L} - \frac{1}{Q_U}} = \frac{1}{\frac{1}{15} - \frac{1}{120}} = 17$$

The required shunt reactance assuming an inductor value of 10nH gives $X_L = 2\pi f * 10^{-8} = 63\Omega$

$$X_{shunt} = R_o \left(\frac{2R_o Q_e}{X_L} - 1 \right)^{-1/2}$$
$$= 50 \left(\frac{2 * 50 * 17}{63} - 1 \right)^{-1/2} = 9.8\Omega$$

$$C_{shunt} = \frac{1}{2\pi f X_{shunt}} = \frac{1}{2\pi * 1E^9 * 9.8} = 16.2\text{pF}$$

Required inductance to resonate at f_o is given by :-

$$L_{series} = \frac{1}{\omega_o^2 C_e} \text{ therefore assuming}$$

$$L = 10\text{nH} \quad C_e = \frac{1}{\omega_o^2 L} = 2.53\text{pF}$$

$$C_e = \frac{1}{\frac{1}{C_{series}} + \frac{2C_{shunt}(\omega_o R_o)^2}{(\omega_o R_o C_{shunt})^2 + 1}} \quad \text{Re - arrange to get } C_{series} \text{ ie}$$

$$C_{series} = \frac{1}{\frac{1}{C_e} - \frac{2C_{shunt}(\omega_o R_o)^2}{(\omega_o R_o C_{shunt})^2 + 1}}$$

$$= \frac{1}{\frac{1}{2.53E^{-12}} - \frac{2 * 16.2E^{-12} (2\pi * 1E^9 * 50)^2}{(2\pi * 1E^9 * 50 * 16.2E^{-12})^2 + 1}} = 3.6\text{pF}$$

The calculated circuit element values for a 1GHz resonator $Q \sim 16$ are shown in the diagram Figure 4.

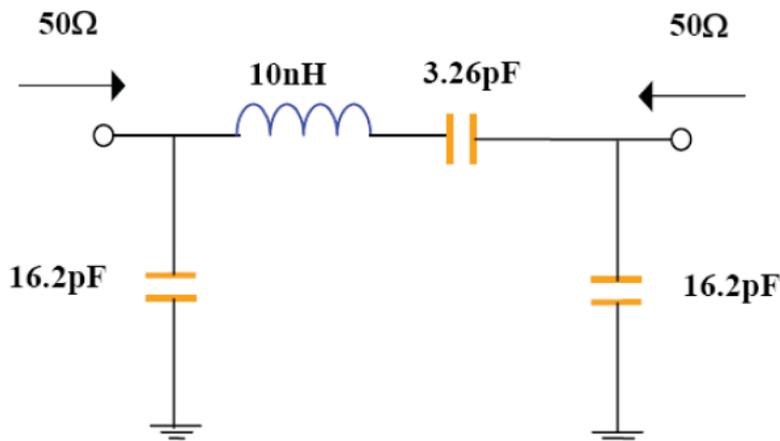


Fig 4. Final component values for the 4-element resonator designed to have a resonant frequency of 1GHz with a loaded Q of > 15 in a 50 ohm system.