 

SRAM Design

Increase Read Noise Margin





$$\beta_d \gg \beta_a$$

Increase cell Vdd




Increase Vth

Reduce wordline Vdd

  


Don't allow readcurrent through cell

SRAM Cell Design: Write Margin

   



How to Improve Write Margin

 

$$\beta_a \gg \beta_p$$

Decrease Cell Vdd

Increase WL Vdd

  

SRAM Cell Sizing

Tradeoffs


Read Noise Margin

$$\beta_d \sim 3 \times \beta_a$$

Cell Read Current


$$\beta_a \gg \beta_p$$

Write Noise Margin

 


Cell Size

Layout of SRAM Cell

 


7-T Cell


Read-SNM-free SRAM cell

 


Read/Write Circuitry

 


Read Waveforms

 


Write Waveforms

 


7-T Cell Layout

 


Hiding gaps

 

Area overheads

 

Same configuration

 

Same Speed

8-T Cell

