

Sequential Circuit Timing

Objectives

This section covers several timing considerations encountered in the design of synchronous sequential circuits. It has the following objectives:

- Define the following global timing parameters and show how they can be derived from the basic timing parameters of flip-flops and gates.
 - ◆ Maximum Clock Frequency
 - ◆ Maximum allowable clock skew
 - ◆ Global Setup and Hold Times
- Discuss ways to control the loading of data into registers and show why gating the clock signal to do this is a poor design practice.


Reading Assignment

- Sections 3.5 and 3.6. Please also see .ppt slides posted on the web - the animation helps a lot!

13.1. Maximum Clock Frequency

- The clock frequency for a synchronous sequential circuit is limited by the timing parameters of its flip-flops and gates. This limit is called *the maximum clock frequency* for the circuit. The *minimum clock period* is the reciprocal of this frequency.
- Relevant timing parameters
 - Gates:
 - ◆ Propagation delays: $\min t_{PLH}$, $\min t_{PHL}$, $\max t_{PLH}$, $\max t_{PHL}$
 - Flip-Flops:
 - ◆ Propagation delays: $\min t_{PLH}$, $\min t_{PHL}$, $\max t_{PLH}$, $\max t_{PHL}$
 - ◆ Setup time: t_{su}
 - ◆ Hold time: t_h

□ Example

 



$$T_W \geq \max t_{PFF} + t_{su}$$

- For the 7474, $\max t_{PLH} = 25\text{ns}$, $\max t_{PHL} = 40\text{ns}$, $t_{su} = 20\text{ns}$

$$T_W \geq \max (\max t_{PLH} + t_{su}, \max t_{PHL} + t_{su})$$



$$T_W \geq \max (25+20, 40+20) = 60$$

□ Example

  


$$T_W \geq \max t_{PFF} + \max t_{PINV} + t_{su}$$

□ Example

  

$$T_W \geq \max t_{PFF} + \max t_{PMUX} + t_{su}$$

□ Example

 

	t_p	t_{su}
D Flip-Flop:	20 ns	5 ns
JK Flip-Flop:	25 ns	10 ns
AND Gate:	12 ns	
OR Gate:	10 ns	

Paths from Q1 to Q1: None

Paths from Q1 to Q2: $T_w \geq \max t_{PDFF} + t_{JKsu} = 20 + 10 = 30 \text{ ns}$

$$T_w \geq \max t_{PDFF} + \max t_{AND} + t_{JKsu} = 20 + 12 + 10 = 42 \text{ ns}$$

Paths from Q2 to Q1: $T_w \geq \max t_{pJKFF} + t_{OR} + T_{Dsu} = 25 + 10 + 5 = 40 \text{ ns}$

Paths from Q2 to Q2: $T_w \geq \max t_{pJKFF} + \max t_{AND} + t_{JKsu} = 25 + 12 + 10 = 47 \text{ ns}$



$$TW \geq 47 \text{ ns}$$

□ Clock Skew

- If a clock edge does not arrive at different flip-flops at exactly the same time, then the clock is said to be *skewed* between these flip-flops. The difference between the times of arrival at the flip-flops is said to be the amount of *clock skew*.
- Clock skew is due to different delays on different paths from the clock generator to the various flip-flops.
 - ◆ Different length wires (wires have delay)
 - ◆ Gates (buffers) on the paths
 - ◆ Flip-Flops that clock on different edges (need to invert clock for some flip-flops)
 - ◆ Gating the clock to control loading of registers (a very bad idea)

□ Example (Effect of clock skew on clock rate)

■ Clock C2 skewed after C1

  



$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su}$$

(if clock not skewed, i.e., $t_{INV} = 0$)

$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su} - \min t_{INV}$$

(if clock skewed, i.e., $t_{INV} > 0$)

■ Clock C1 skewed after C2

  



$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su}$$

(if clock not skewed, i.e., $t_{INV} = 0$)

$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su} + \max t_{INV}$$

(if clock skewed, i.e., $t_{INV} > 0$)

  
□ Summary of maximum clock frequency calculations



C2 skewed after C1: $T_W \geq \max T_{PFF} + \max t_{NET} + t_{su} - \min t_{INV}$

C2 skewed before C1: $T_W \geq \max T_{PFF} + \max t_{NET} + t_{su} + \max t_{INV}$

□ Example

 


t_{XY} = Network delay from X to Y
 t_{XD} = Network delay from X to D
 t_{QY} = Network delay from Q to Y
 t_{QD} = Network delay from Q to D


■ For each of the following two connections find

- ◆ The minimum clock period
- ◆ The maximum and minimum delay from CLK to YOUT

■ Circuit 1:

 

 t_{XY} = Network delay from X to Y
 t_{XD} = Network delay from X to D
 t_{QY} = Network delay from Q to Y
 t_{QD} = Network delay from Q to D



Minimum Clock Period:

$$T_w \geq \max t_{pFF} + \max t_{QY} + (n-2) \max t_{XY} + \max t_{XD} + t_{su} \geq T_w$$

$$T_w \geq \max t_{pFF} + \max t_{QD} + t_{su}$$


Maximum Delay:

$$T_{CY} \leq \max t_{pFF} + \max t_{QY} + (n-1) \max t_{XY}$$


Minimum Delay:

$$T_{CY} \geq \min t_{pFF} + \min t_{QY}$$

■ Circuit 2:

 

 t_{XY} = Network delay from X to Y
 t_{XD} = Network delay from X to D
 t_{QY} = Network delay from Q to Y
 t_{QD} = Network delay from Q to D



Minimum Clock Period:

$$T_w \geq \max t_{pFF} + \max t_{XD} + t_{su}$$

$$T_w \geq \max t_{pFF} + \max t_{QD} + t_{su}$$

Maximum Delay:


$$T_{CY} \leq \max t_{pFF} + \max (\max t_{XY}, \max t_{QY})$$

Minimum Delay:


$$T_{CY} \geq \min t_{pFF} + \min (\min t_{XY}, \min t_{QY})$$

 2. Maximum Allowable Clock Skew



□ How much skew between C1 and C2 can be tolerated in the following circuit?





■ Case 1: C2 delayed after C1

 

■ Case 2: C1 delayed from C2

  

 
 
□ How does additional delay between the flip-flops affect the skew calculations?



$$t_{SK} \leq \min t_{PFF} - t_h$$

$$t_{sk} \leq \min t_{PFF} + \min t_{MUX} - t_h$$

 
 
□ Summary of allowable clock skew calculations



$$t_{SK} + t_h \leq t_{PFF} + t_{NET}$$

$$t_{SK} \leq \min t_{PFF} + \min t_{NET} - t_h$$

  - Example: What is the minimum clock period for the following circuit under the assumption that the clock C2 is skewed after C1 (i.e., C2 is delayed from C1)?



- First calculate the maximum allowable clock skew.

$$t_{SK} < \min t_{PFF} + \min t_{N1} - t_h$$
- Next calculate the minimum clock period due to the path from Q1 to D2.

$$T_W > \max t_{PFF} + \max t_{N1} + t_{su} - \min t_{SK}$$
- Finally calculate the minimum clock period due to the path from Q2 to D1


$$T_W > \max t_{PFF} + \max t_{N2} + t_{su} + \max t_{SK}$$

$$T_W > \max t_{PFF} + \max t_{N2} + t_{su} + (\min t_{PFF} + \min t_{N1} - t_h)$$


$$T_W > \max t_{PFF} + \min t_{PFF} + \max t_{N2} + \min t_{N1} + t_{su} - t_h$$

 3. Global Setup Time, Hold Time and Propagation Delay


□ Global setup and hold times (data delayed)



 □ Global setup & hold time (clock delayed)




 □ Global setup & hold time (data & clock delayed)




$$T_{SU} = t_{su} + \max t_{NET} - \min t_C \quad T_H = t_h - \min t_{NET} + \max t_C$$

□ Global propagation delay

 

$$T_P = t_C + t_{FF} + t_{NET}$$

□ Summary of global timing parameters

 


$$T_{SU} = t_{su} + \max t_{PN} - \min t_{PC} \leq t_{su} + \max t_{PN}$$

$$T_H = t_h + \max t_{PC} - \min t_{PN} \leq t_h + \max t_{PC}$$

$$T_P = t_{PFF} + t_{PN} + t_{PC}$$

□ Example

 


- Find T_{SU} and T_H for input signal LD relative to CLK.

$$\begin{aligned} T_{SU} &= t_{su} + \max t_{NET} - \min t_C \\ &= t_{su} + \max t_{INV} + \max t_{NAND} + \max t_{NAND} - \min t_{INV} \end{aligned}$$


$$\begin{aligned} T_H &= t_h - \min t_{NET} + \max t_C \\ &= t_h - \min t_{NAND} - \min t_{NAND} + \max t_{INV} \end{aligned}$$

 4. Register load control (gating the clock)

- ❑ A very bad way to add a load control signal LD to a register that does not have one is shown below




 - ❑ The reason this is such a bad idea is illustrated by the following timing diagram.




- ❑ The flip-flop sees two rising edges and will trigger twice. The only one we want is the second one.

 - ❑ If LD was constrained to only change when the clock was low, then the only problem would be the clock skew.




 - If gating the clock is the only way to control the loading of registers, then use the following approach:




- There is still clock skew, but at least we only have one triggering edge.

 - The best way to add a LD control signal is as follows:



5. Synchronous System Structure and Timing

 

Elec 326

31

Sequential Circuit Timing

6. Review

- How the flip-flop and gate timing parameters affect the maximum possible clock frequency.
 - How clock skew affect maximum possible clock frequency.
- How the delay of logic between flip-flops affects the maximum allowable clock skew.
- How flip-flop setup and hold times are translated by the combinational logic delays to get global setup and hold times.
- The detrimental effect of gating the clock signal.

Elec 326

32

Sequential Circuit Timing

