

11. Sequential Elements

J. A. Abraham


Department of Electrical and Computer Engineering
The University of Texas at Austin

EE 382M, VLSI I
Fall 2010

October 4, 2010

- How do you estimate block areas?
 - Begin with block diagram
 - Each block has
 - Inputs
 - Outputs
 - Function
 - Type: array, datapath, random logic
 - Estimation depends on type of logic


MIPS Floorplan

 

Area Estimation

- Arrays
 - Layout basic cell
 - Calculate core area from number of cells
 - Allow area for decoders, column circuitry
- Datapaths
 - Sketch slice plan
 - Count area of cells from cell library
 - Ensure wiring is possible
- Random Logic
 - Compare complexity do a design you have done
 - For design in a new technology, estimate from scaling design in the old technology

MIPS Slice Plan

 

Typical Layout Densities

- Typical number of high quality layout given below
- Derate by 2 for class projects to allow routing and some sloppy layout
- Allocate space for big wiring channels

Element	Area
Random logic (2 metal layers)	1000 – 1500 λ^2 /transistor
Datapath	250 – 750 λ^2 /transistor or, $6WL + 360\lambda^2$ /transistor
SRAM	1000 λ^2 /bit
DRAM	100 λ^2 /bit
ROM	100 λ^2 /bit


Sequencing

- **Combinational logic**

- Output depends on current inputs

- **Sequential logic**

 - Output depends on current and previous inputs
- Requires separating previous, current, future
- Called state or tokens
- Example, Finite-State Machine (FSM), pipeline



- If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- Example, fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But dispersion sets min time between pulses
- This is called wave pipelining in circuits
- In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones

Sequencing Overhead


- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
 - Called sequencing overhead
- Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence

Sequencing Elements

- **Latch**: Level sensitive
 - Also called transparent latch, D latch
- **Flip-Flop**: Edge triggered
 - Also called master-slave flip-flop, D flip-flop, D register, D Flop

- **Timing Diagrams**


- Transparent
- Opaque
- Edge-trigger

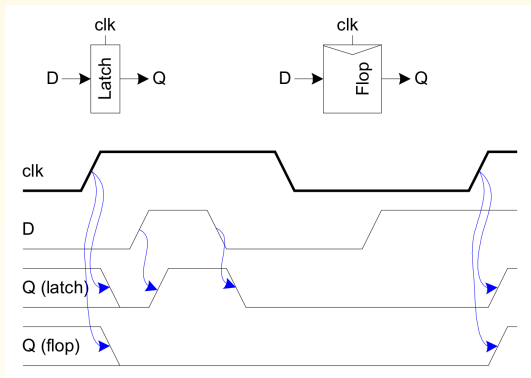

Pass Transistor Latch

- + Tiny
- + Low clock load
 - V_t drop
 - Non-restoring
 - Back driving
 - Output noise sensitivity
- Dynamic
- Diffusion input


Used in the 1970s

 

Latch Designs, Cont'd


Transmission Gate Latch

 - + No V_t drop
- Requires inverted clock



Inverting Buffer Latch

 
- + Restoring
- + No Backdriving
- + Fixes either
 - Output noise sensitivity
 - Or diffusion input
- Inverted output



Latch Designs, Cont'd


Latch with Tristate Feedback

 - + Static
- Backdriving risk
- Static latches are now essential



Latch with Buffered Input

 
- + Fixes diffusion input
- + Non-inverting



Latch Designs, Cont'd


Latch with Buffered Output

 - Widely used in standard cells
- + No backdriving
- + Very robust (most important)
 - Rather large
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading




Datapath Latch

- + Smaller, faster
- Unbuffered input

 


Flip-Flop Design

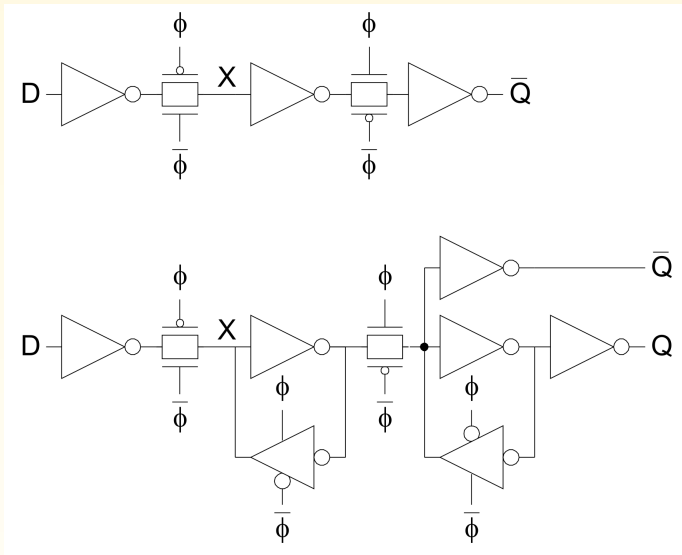Flip-flop is built as a pair of back-to-back latches




Enable

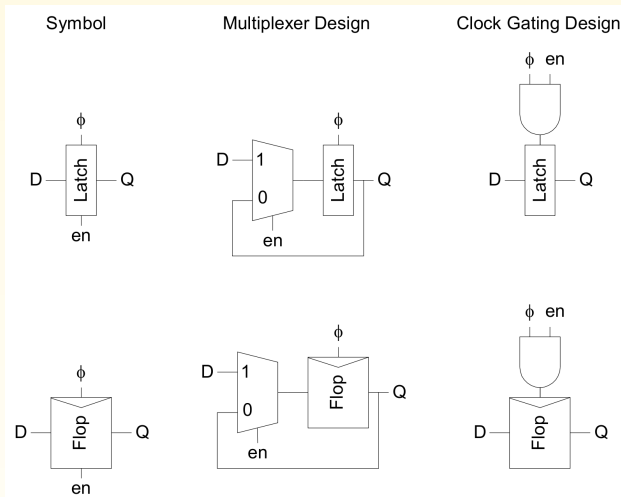- Enable: ignore clock when $en = 0$
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew




Reset

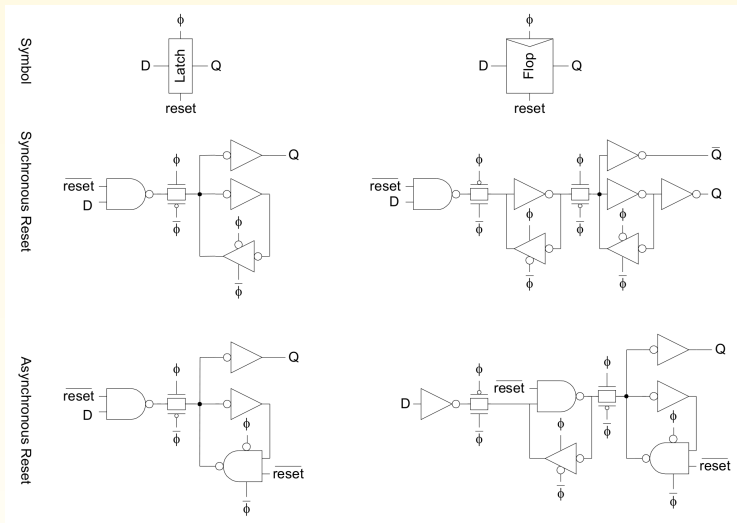- Force output low when reset asserted
- Synchronous vs. asynchronous



- Set forces output high when enabled

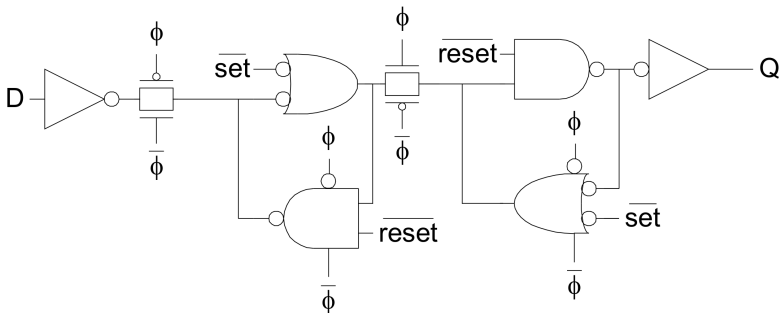Flip-flop with asynchronous set and reset




Sequencing Methods

Flip-Flops

2-Phase Transparent Latches


Pulsed Latches

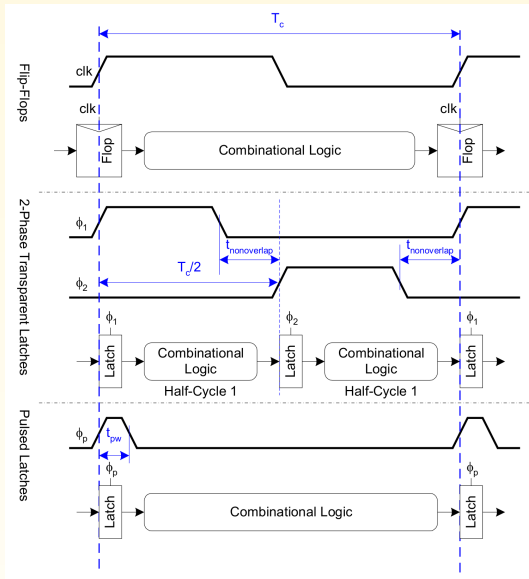


Timing Diagrams

Contamination and Propagation Delays

t_{pd}	Logic Propagation Delay
t_{cd}	Logic Contamination Delay
t_{pcq}	Latch/Flop Clk-Q Prop. Delay
t_{ccq}	Latch/Flop Clk-Q Cont. Delay
t_{pdq}	Latch D-Q Prop. Delay
t_{cdq}	Latch D-Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

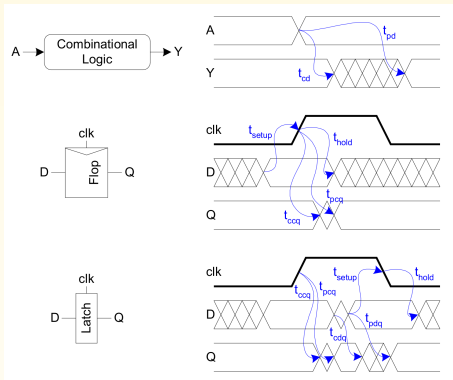

Example: Master-Slave Flip Flop

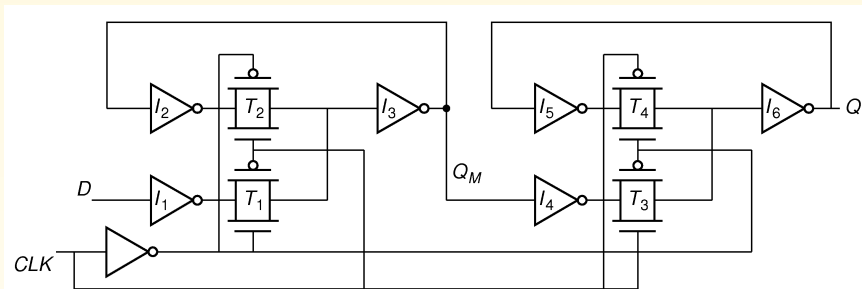


$$t_{setup} =$$

$$t_{pcq} =$$

$$t_{hold} =$$


Maximum Delay: Flip-Flops
 
$$t_{pd} \leq T_c - \underbrace{(t_{setup} + t_{pcq})}_{\text{sequencing overhead}}$$




Maximum Delay: 2-Phase Latches
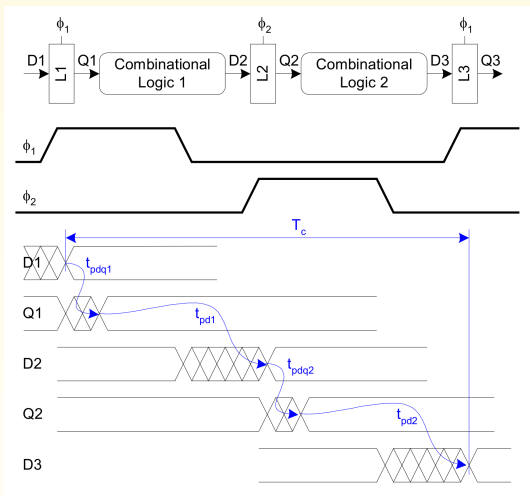
$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$




Maximum Delay: Pulsed Latches
 
$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}}$$



Minimum Delay: Flip-Flops


$$t_{cd} \geq t_{hold} - t_{ccq}$$

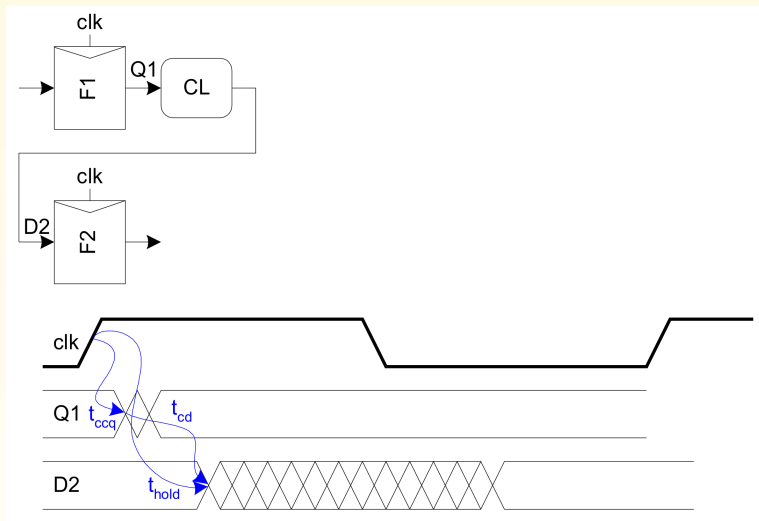

Minimum Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq t_{hold} - t_{ccq} - t_{nonoverlap}$$

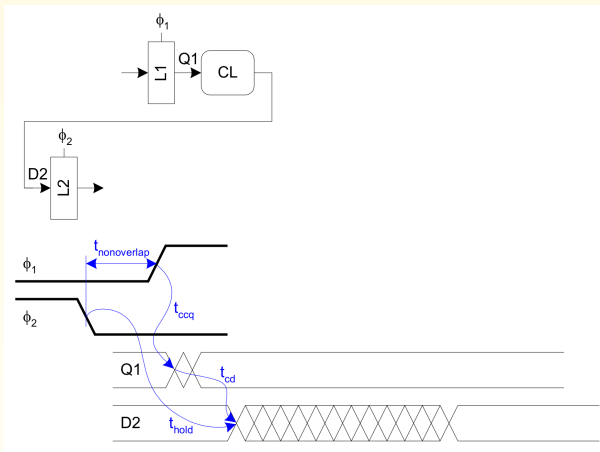
- Hole time reduced by nonoverlap
- Paradox: hold applies twice each cycle, versus only once for flops
 - But a flop is made of two latches!



Minimum Delay: Pulsed Latches


$$t_{cd} \geq t_{hold} - t_{ccq} + t_{pw}$$

Hold time increased by pulse width

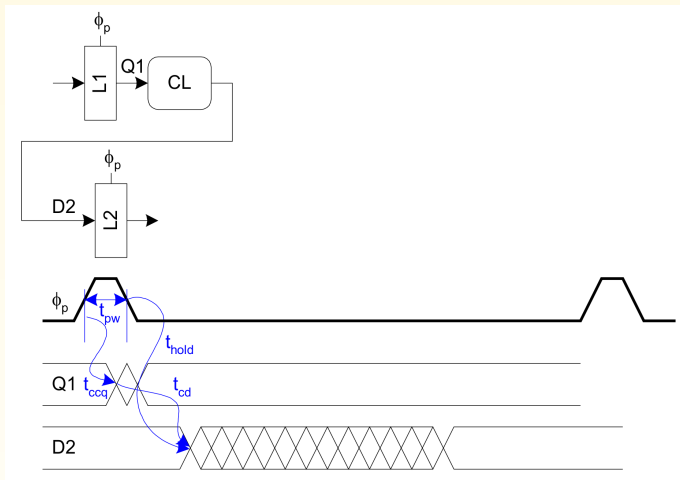

Clock Skew

 
- We have assumed zero clock skew
- Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing




Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
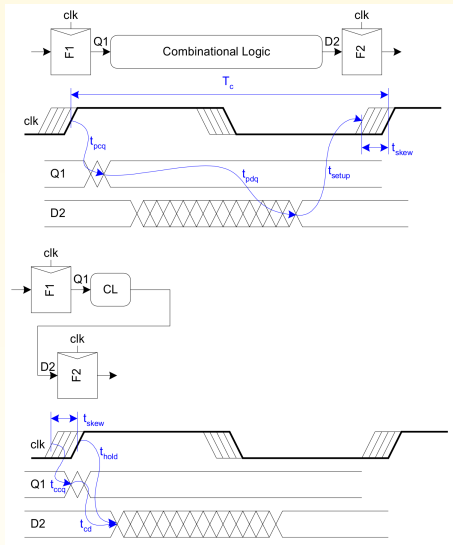
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$



Skew: Latches

 

• 2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$$

$$t_{borrow} \leq T_c/2 - (t_{setup} + t_{nonoverlap} + t_{skew})$$

• Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw} + t_{skew})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{hold} + t_{pw} - t_{ccq} + t_{skew}$$


$$t_{borrow} \leq t_{pw} - (t_{setup} + t_{skew})$$

Two-Phase Clocking

- If setup times are violated, reduce clock speed
- If hold times are violated, chip fails at any speed
- Use tools to analyze clock skew
- Easy way to guarantee hold times: use 2-phase latches with big non-overlap times (used in academic designs)
- Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop

 - Flip-Flop with non-overlapping clocks
- Very slow – nonoverlap adds to setup time, but no hold time problem
- Use timing analysis and add buffers to slow signals if hold time is at risk




Summary

- Flip-Flops
 - Very easy to use, supported by all tools
- 2-Phase Transparent Latches
 - Lost of skew tolerance and time borrowing
- Pulsed Latches
 - Fast, some skew tolerance and borrowing, hold time risk

	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay (t_{cd})	Time borrowing (t_{borrow})
Flip-flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-phase transparent latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw} + t_{skew})$	$t_{hold} - t_{ccq} + t_{pw} + t_{skew}$	$t_{pw} - (t_{setup} + t_{skew})$


High Performance Flops

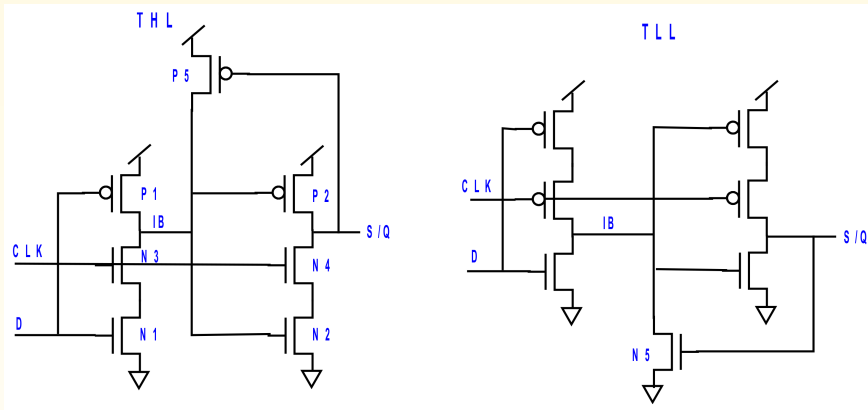The modified Svensson latch, DEC Alpha 21064




High Performance Flops, Cont'd

The amplifier-based flip-flop

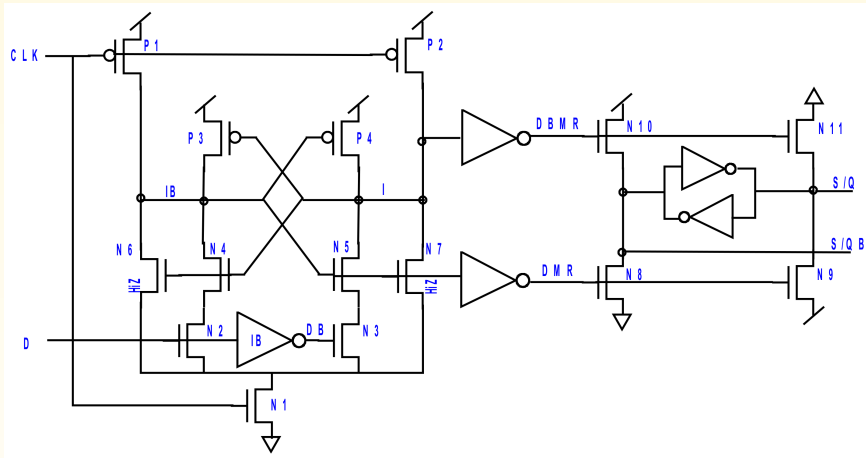


High Performance Flops, Cont'd

The hybrid latch flip-flop of AMD K6

 


Basic Flop in AMD Athlon Processor

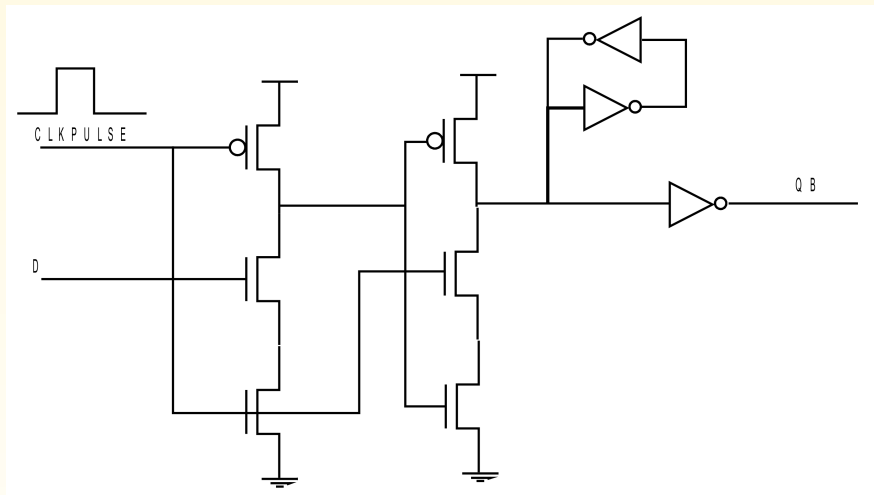Clock pulse is generated using monoshots at the rising edge





High Performance Flops, Cont'd

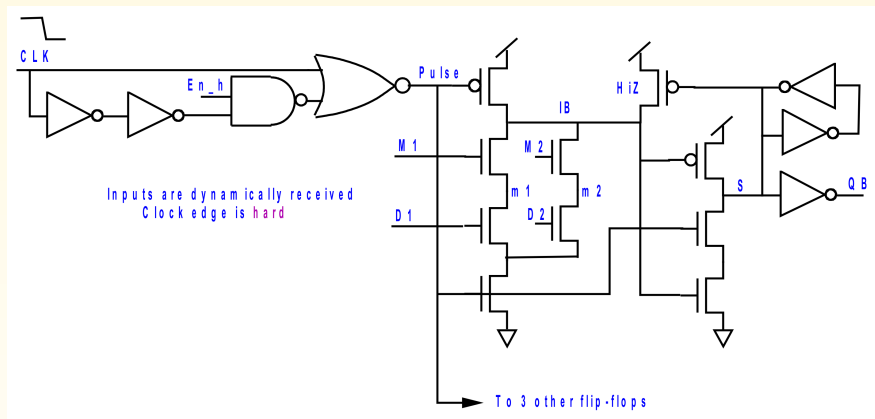The enabled two-way MUX pulsed flip-flop of K7



Cycle Stretching

  


Cycle time between A & B = 1200 ps

Cycle time between B & C = 700 ps

Fixing Hold-Time Violations

- Measure all hold times with respect to the main clock
- Adjust the hold time if the flop is receiving a delayed clock
- Compute the shortest path delay from the rising edge of the clock
- Check to see if there are any hold time failures

Example: Fixing Hold-Time Violations

 

CLK \rightarrow Q = 100 ps

Setup = 10 ps

Hold = 200 ps (A large hold time is used to illustrate the problem)

Shortest path delay from A \rightarrow E = 100 + 40 + 40 + 20 = 200 ps


Delay between CLK1 and CLK = 50 ps

Adjusted hold time = 200 + 50 = 250 ps

Hold Slack = (Path Delay) - (Adjusted Hold Time) = 200 - 250
= -50 ps

\Rightarrow **FAIL (Hold slack should be ≥ 0)**

 Example: Fixing Hold-Time Violations, Cont'd



CLK \rightarrow Q = 100 ps

Setup = 10 ps

Hold = 200 ps (A large hold time is used to illustrate the problem)

Insert 4 inverters after D, with each adding a 20 ps
(or can insert one AND gate)

Long path (4 invs.) = $100 + 50 + 50 + 20 + 80 + 10 = 310$ ps

Now the minimum cycle time at which the path can operate =
(Path Delay) - (CLK \rightarrow CLK1 Delay) = $310 - 50 = 260$ ps

If possible, add the additional delay to fix hold time violations in
the short path (without affecting the long paths)