

Example 9.14

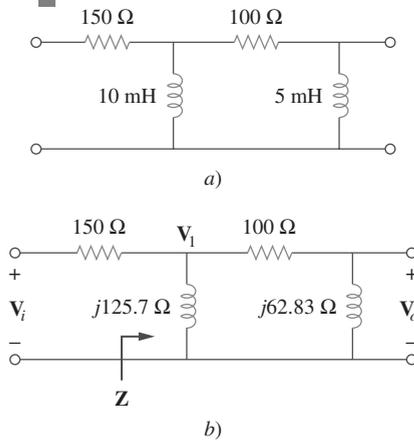


Figure 9.35
For example 9.14.

Referring to the circuit shown in Figure 9.35 a), calculate the Phase Shift produced at 2 kHz.

Answer:

At 2 kHz, the inductances of 10 mH and 5 mH are transformed in the impedance.

$$10 \text{ mH} \Rightarrow X_L = \omega L = 2\pi \times 2 \times 10^3 \times 10 \times 10^{-3} \\ = 40\pi = 125.7 \Omega$$

$$5 \text{ mH} \Rightarrow X_L = \omega L = 2\pi \times 2 \times 10^3 \times 5 \times 10^{-3} \\ = 20\pi = 62.83 \Omega$$

Consider the circuit of Figure 9.35 b). Z impedance is the combination parallel operation of $j125.7 \Omega$ y $100 + j62.83 \Omega$. so,

$$\mathbf{Z} = j125.7 \parallel (100 + j62.83) \\ = \frac{j125.7(100 + j62.83)}{100 + j188.5} = 69.56 / \underline{60.1^\circ} \Omega \quad (9.14.1)$$

When applying the voltage division,

$$\mathbf{V}_1 = \frac{\mathbf{Z}}{\mathbf{Z} + 150} \mathbf{V}_i = \frac{69.56 / \underline{60.1^\circ}}{184.7 + j60.3} \mathbf{V}_i \\ = 0.3582 / \underline{42.02^\circ} \mathbf{V}_i \quad (9.14.2)$$

and

$$\mathbf{V}_o = \frac{j62.832}{100 + j62.832} \mathbf{V}_1 = 0.532 / \underline{57.86^\circ} \mathbf{V}_1 \quad (9.14.3)$$

By combining equations (9.14.2) and (9.14.3),

$$\mathbf{V}_o = (0.532 / \underline{57.86^\circ})(0.3582 / \underline{42.02^\circ}) \mathbf{V}_i = 0.1906 / \underline{100^\circ} \mathbf{V}_i$$

Which indicates that the output is around 19% of the input in magnitude, but it advances to the entrance in 100° . If the circuit ends in a charge, this will affect the phase shift

Practice Problem 9.14

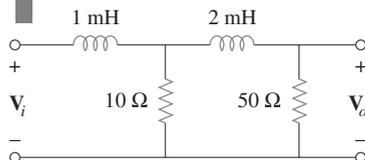


Figure 9.36
For the practice problem 9.14.

Refer to RL circuit of Figure 9.36. If 1 V is applied, find the magnitude and the phase shift produced at 5 kHz. Specify whether the displacement phase is advance or delayed.

Answer: 0.172, 120.4° , delayed