



Keywords: assembly, adc, a/d, a-d, 2-wire, serial interface, I2C, 16-bit, analog to digital converter, ADCs, pic Aug 29, 2003
microcontroller, PIC, microcontrollers, micros

APPLICATION NOTE 2394

Interfacing the MAX1169 ADC to a PIC Microcontroller

Abstract: This application note describes how to interface a MAX1169 analog-to-digital converter (ADC) to a PIC® microcontroller. It includes an example circuit and software for a PIC18F442. The software contains function calls to interface the ADC to the PIC microcontroller using the internal MSSP I²C port at 400kHz.

The MAX1169 is a 16-bit, low power ADC featuring a 2-Wire I²C compatible serial interface. The MAX1169's interface is capable of supporting both Fast Mode (400kHz) and High Speed Mode (up to 1.7MHz).

This application note consists of an example application circuit and software using the PIC18F442. The software contains function calls to interface the MAX1169 to the PIC using the internal MSSP I²C port at 400kHz. Since other microcontrollers have similar on-chip peripherals, the example I²C communication routines provided were purposely broken down into single I²C function calls so that the code can be quickly implemented with other microcontrollers. **Table 1** shows the single I²C compatible function calls used in the assembly program example.

The application circuit uses the MAX1169EVKIT, which consists of the MAX1169, an input buffer (MAX4430) and a proven PCB layout. The PIC and RS-232 transceiver IC (MAX3232) are not present on the MAX1169EVKIT. The SCL and SDA pads on the MAX1169EVKIT allow an easy connection for the I²C compatible serial interface. Install 1.5k Ω pull-up resistors on R3 and R4 for 400kHz I²C operation.

The pinout of the MAX1169 allows easy isolation of the analog section from the digital section. The analog section is grouped together on pins 8-13 on the right side of the IC and the digital section is located on pins 1-7 on the left side of the IC. Pin 14 is also part of the digital section but can be easily grouped with the left side of the IC. For optimum performance it is recommended to use separate analog and digital supplies as shown in the schematic in **Figure 1**.

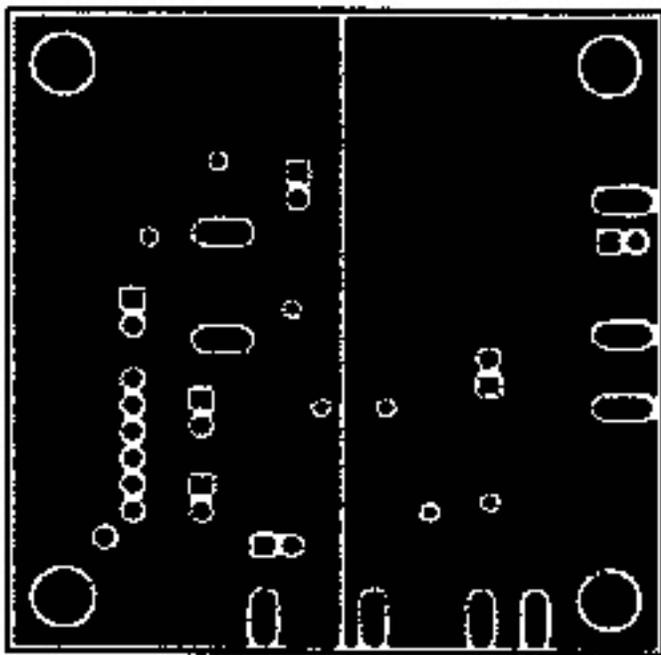
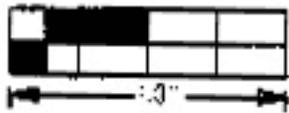
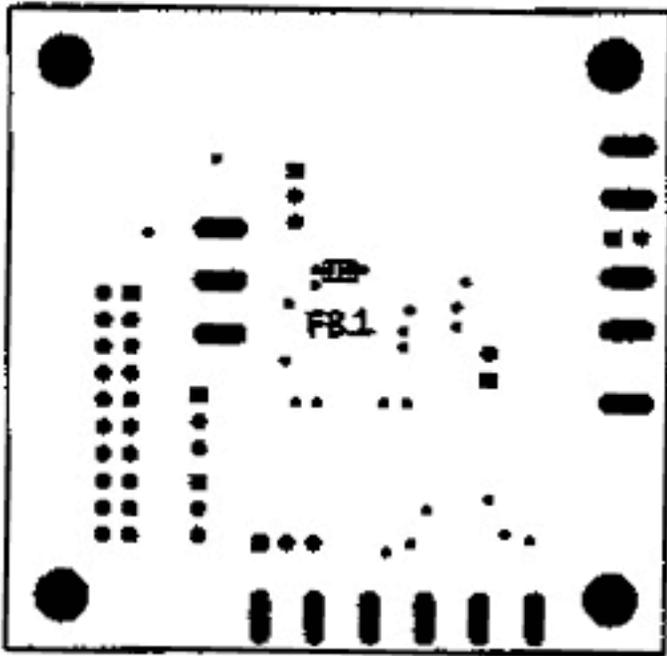
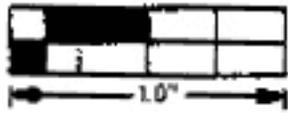




Figure 2. Separating the analog and digital grounds.

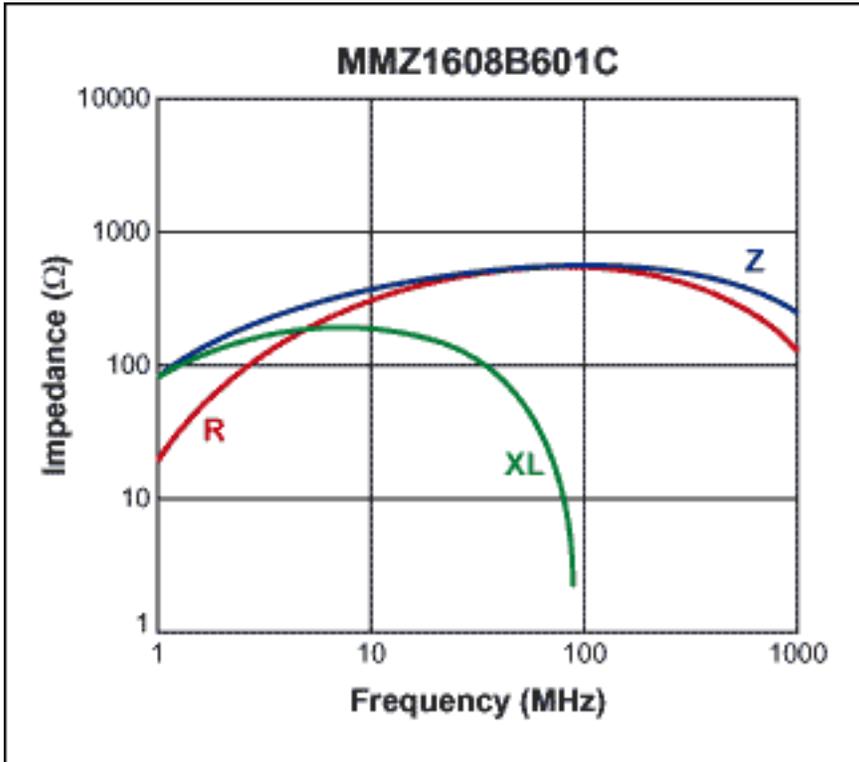


Figure 3. Impedance versus frequency curve for the TDK MMZ1608B601C ferrite bead.

The example assembly program reads continuous conversions from the MAX1169 16-bit ADC to the PIC at a 2-Wire interface frequency of 400kHz. Once the digitized analog voltage representation of the data is received by the PIC, it is immediately transmitted out by a software UART at 115kbps. The RS-232 transceiver allows the data to be captured by a personal computer with a standard serial port.

Table 1. Single I²C compatible function calls.

Single I ² C compatible function calls	Description
HWI ² C_start	Performs an I ² C compatible start condition.
HWI ² C_repeatedStart	Performs an I ² C compatible repeated start condition.
HWI ² C_W_slaveAddr	Performs all I ² C compatible write operations including the initial slave address write frame.
HWI ² C_readMore_W	Performs an I ² C compatible read operation with Master ACK.
HWI ² C_readLast_W	Performs an I ² C compatible read operation with Master NACK.
HWI ² C_stop	Performs an I ² C compatible stop condition.

[Download](#) an assembly example program that interfaces the MAX1169 to the PIC18F442's internal MSSP I²C peripheral.

PIC is a registered trademark of Microchip Technology, Inc.

Application Note 2394: <http://www.maxim-ic.com/an2394>

More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

Related Parts

MAX1169: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX3232: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX4430: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN2394, AN 2394, APP2394, Appnote2394, Appnote 2394

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>